

LM2623 Design Document

National Semiconductor
LM2623
May 2006



1.0 Design Specifications

Inputs	Outputs #1
VinMin=1.5	Vout1=2
VinMax=3.3	Iout1=0.5

2.0 Design Description

This design is a basic boost that is capable of providing constant current of 350mA and an open circuit maximum voltage of 5V at high efficiency. It is designed to power LUMILEDS 1W LED from single or two cells.

With an LED present, as the output voltage ramps to approximately 3.4V, the LED will turn on causing current to flow through R7. The voltage across R7 is amplified by a factor of 7X by the SOT-5 LM321MF and the gain resistors R5 and R6. This produces a voltage of 1.24 volts at the junction of R4 and R5 when 350mA flows through the LED. The 1.24 volts causes the LM2623 to stop switching which regulates the LED current at a constant value. This current loop controlled boost circuit requires 1 or 2 cells and will operate with full brightness down to 1.0V. It uses the LM2623MM, a mini-SO8 package

boost switcher with an internal 1.2amp switch, to boost the input voltage from 2-3V to the required LED voltage of 3.4V.

The LM2623A should be used for single cell operation since it guarantees a peak switch current greater than 2A.

The open circuit voltage with no LED present is set to 5V by the resistor ladder of R3-R6. If the LED is permanent, R3 can be omitted.


$$V_{outmax} = V_{fb} * (1 + R3 / (R4 + R5 + R6))$$

$$LED \text{ current} = V_{fb} / R7 * R6 / (R6 + R5)$$

The inductor is a Coilcraft DS1608 size, the capacitors are small ceramic, and the diode is a 0.5A rated Schottky in the SOD package.

Notes: Please note that A1 in the schematic is represented as U in the board layout.

3.0 Schematic

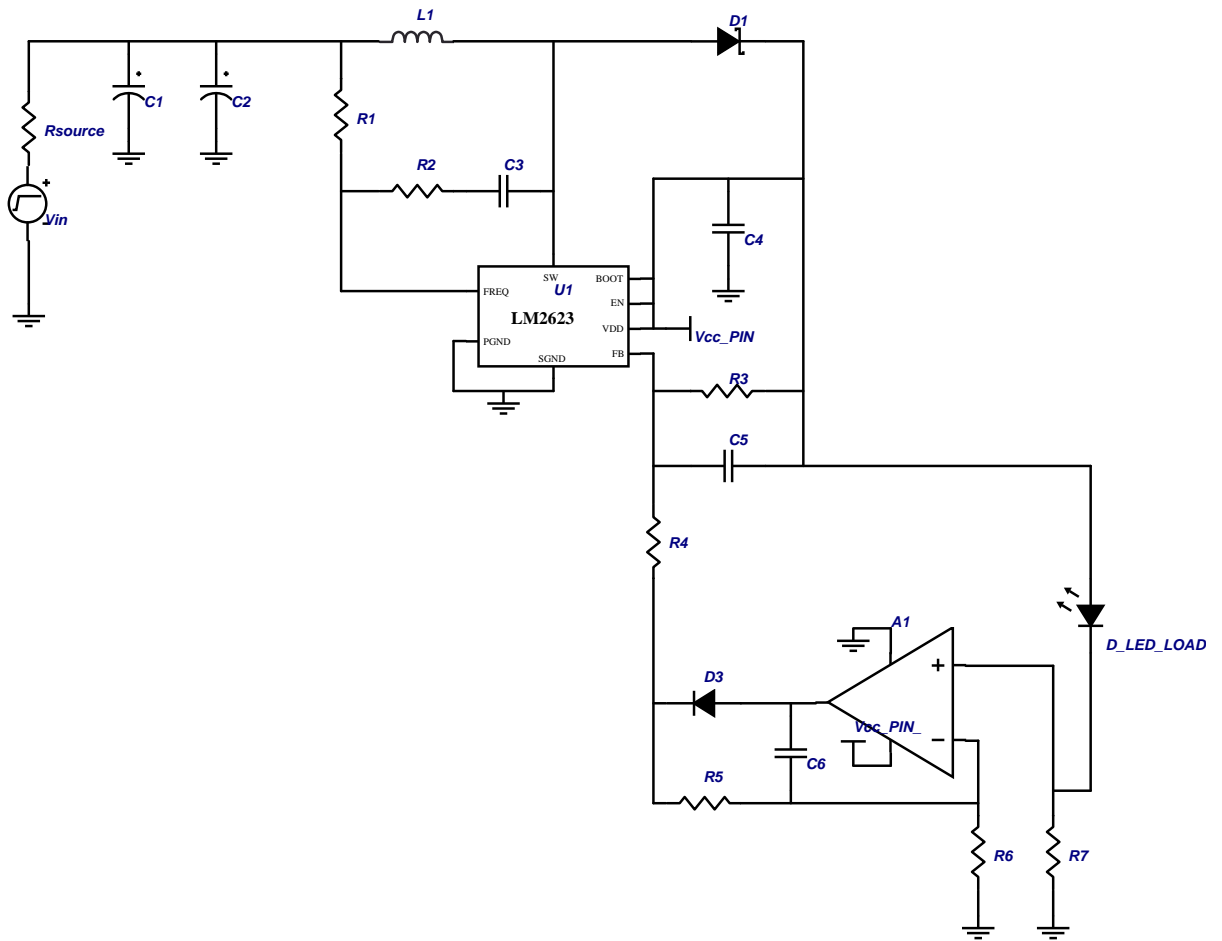

689758_578_0


FIGURE 1. Example Schematic Showing Connection for all Components.

4.0 Bill Of Materials

Part	Manufacturer	Part#	Attributes
A1	National Semiconductor	LM321	
C1	TDK	C3216X5R0J106M	10u F
C2	TDK	C3216X5R0J106M	10u F
C3	Vitramon	VJ0603A220KXAAB	22p F
C4	TDK	C3216X5R0J106M	10u F
C5	Vitramon	VJ0603A330KXAAB	33p F
C6	Vitramon	VJ0603Y103KXAAT	0.01u F
D1	ONSEMI	MBR0520LT1	0.385 V
D3	ONSEMI	MMSD4148T1	1 V
L1	Coilcraft	DO1608C-472	4.7u H, 0.09 Ohms
R1	Dale	CRCW08059092F	90.9k Ohms
R2	Dale	CRCW08053922F	39.2k Ohms
R3	Dale	CRCW06032103F	210k Ohms
R4	Dale	CRCW06031002F	10k Ohms
R5	Dale	CRCW06036812F	68.1k Ohms

Part	Manufacturer	Part#	Attributes
R6	Dale	CRCW06031002F	10k Ohms
R7	Dale	CRCW05081R0J(USE TWO 1 ohm IN PARALLEL)	0.5 Ohms
U1	National Semiconductor	LM2623	

5.0 Layout

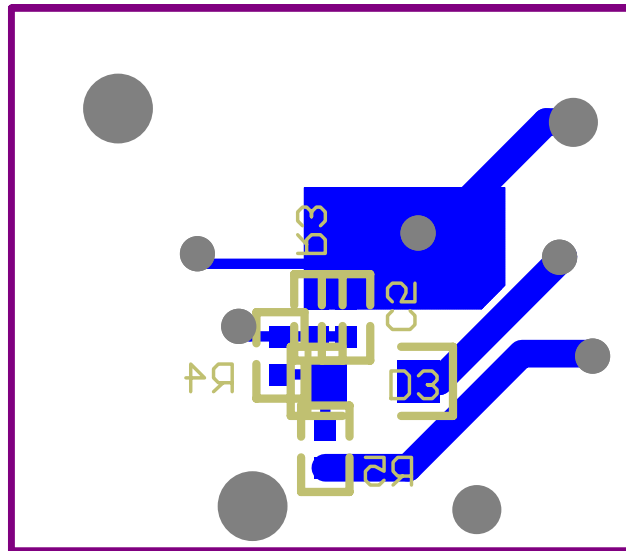

PADC_NSC0119_1o_1

FIGURE 2. Board's Bottom View


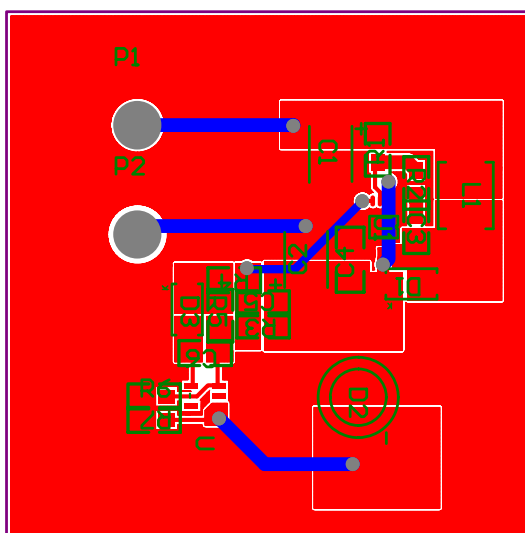


FIGURE 3. Board's Top View

PADC_NSC0119_1o_2


6.0 Waveforms

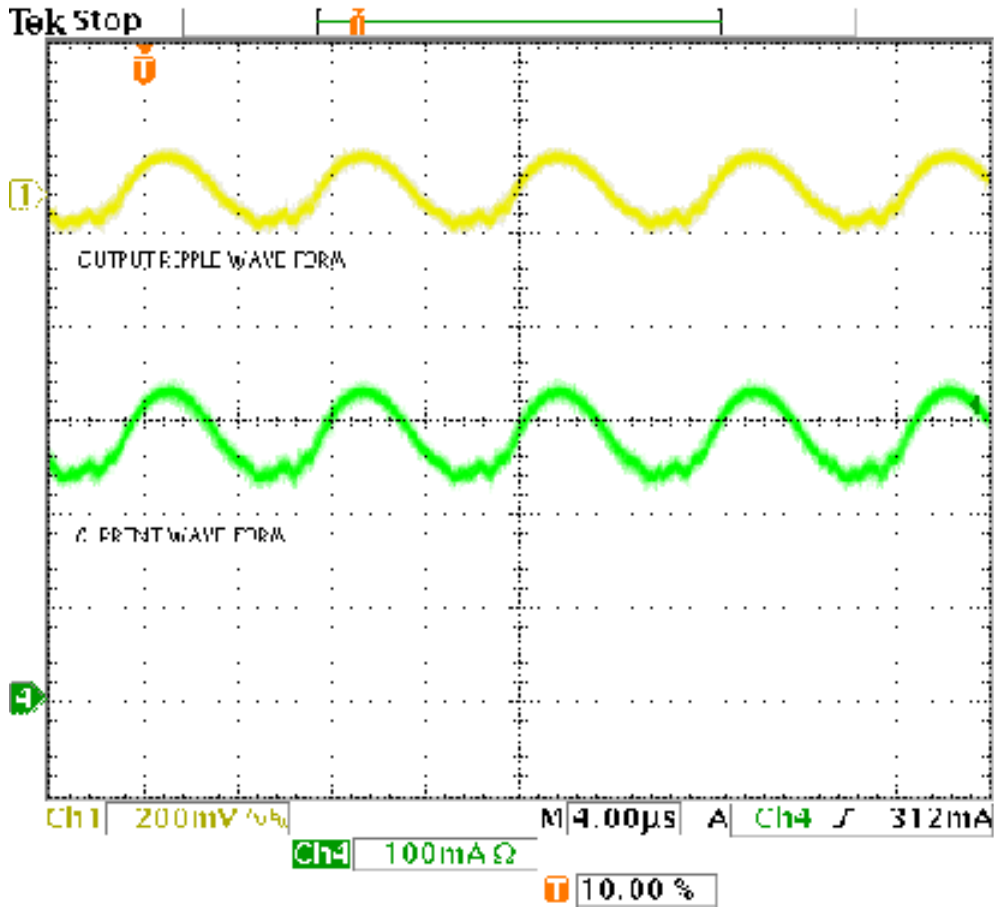

11 Nov 2002
11:06:59

PADC_NSC0119_wf_3

FIGURE 4. CURRENT AND RIPPLE

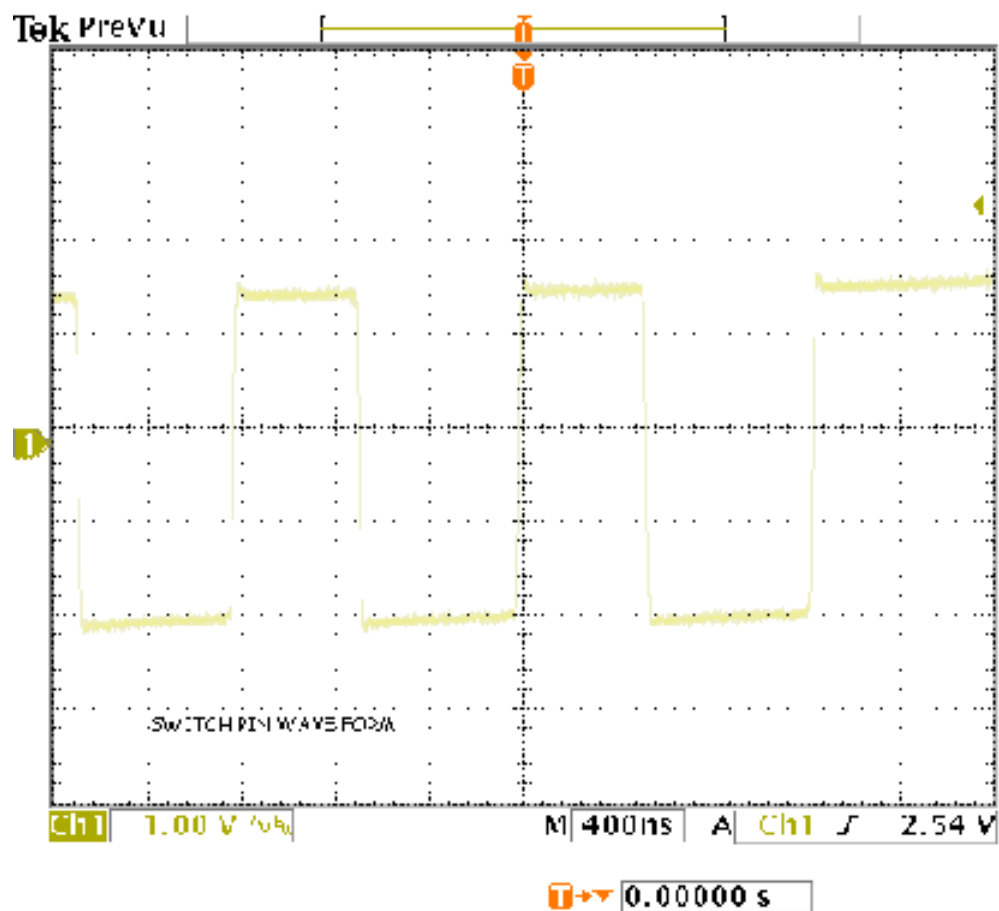

11 Nov 2002
10:42:32

PADC_NSC0119_wf_4

FIGURE 5. SWITCH PIN WAVE FORMS

Notes

National Semiconductor's design tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Reference designs are created using National's published specifications as well as the published specifications of other device manufacturers. While National does update this information periodically, this information may not be current at the time the reference design is built. National and/or its licensors do not warrant the accuracy or completeness of the specifications or any information contained therein. National and/or its licensors do not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. National and/or its licensors do not warrant that the designs are production worthy. You should completely validate and test your design implementation to confirm the system functionality for your application.

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which,
 - (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor certifies that the products and packing materials meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



National Semiconductor Americas Customer Support Center
 Email: new.feedback@nsc.com
 Tel: 1-800-272-9959

National Semiconductor Europe Customer Support Center
 Fax: +49 (0) 180-530-85-86
 Email: europe.support@nsc.com
 Deutsch Tel: +49 (0) 69 9508 6208
 English Tel: +49 (0) 870 24 0 2171
 Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Support Center
 Email: ap.support@nsc.com

National Semiconductor Japan Customer Support Center
 Fax: 81-3-5639-7507
 Email: jpn.feedback@nsc.com
 Tel: 81-3-5639-7560