

NCP1381/82 Demonstration Board 120 W Notebook Adapter with Power Factor Correction

Prepared by: Nicolas Cyr
ON Semiconductor

Overview

The NCP1381 and NCP1382 are quasiresonant controllers developed to ease the design of 80 to 200 W switching power supplies requiring a Power Factor Correction (PFC) stage. One of its typical applications is notebook adapter power supply, in which high-efficiency, low standby power and low EMI are the key requirements.

This demonstration board has been designed in order to demonstrate NCP1381/82 capabilities. It thus gives the choice to implement various options, while offering enough space to plug scope probes.

Features

To help designers quickly developing a notebook adapter, the NCP1381/82 has been introduced. This SOIC-14 package hosts a high performance controller with all necessary features to build a rugged and reliable switching power supply:

- **Current-mode operation with Quasi-Resonant operation:** implementing peak current mode control, the NCP1381/82 waits until the drain-source voltage crosses a minimum level. This is the quasi-resonance approach, minimizing both EMI radiations and capacitive losses.
- **Over Power Protection:** using a voltage image of the bulk level, via the Brown-Out divider, the designer can select a resistor which, placed in series with the current sense information, provides an efficient line compensation method.
- **Frequency clamp:** the controller monitors the sum of T_{ON} and T_{OFF} , providing a real frequency clamp. Also the T_{ON} maximum duration is safely limited to 50 μ s in case the peak current information is lost. If the maximum T_{ON} limit is reached, then the controller stops all pulses and enters a safe auto-recovery burst mode.
- **Go-to-standby signal for PFC front stage:** The NCP1381/82 includes an internal low impedance switch connected between pin 10 (V_{CC}) and pin 11 (GTS). The signal delivered by pin 11 being of low impedance, it becomes possible to connect PFC's V_{CC} directly to this pin and thus avoid any complicated



ON Semiconductor®

<http://onsemi.com>

APPLICATION NOTE

interface circuitry between the PWM controller and the PFC front-end section. In normal operation, pin 11 routes the PWM auxiliary V_{CC} to the PFC circuit which is directly supplied by the auxiliary winding. When the SMPS enters skip-cycle at low output power levels, the controller detects and confirms the presence of the skip activity by monitoring the signal applied on its pin ADJ_GTS (typically FB signal) and opens pin 11, shutting down the front-end PFC stage. When this signal level increases, e.g. when the SMPS goes back to a normal output power, pin 11 immediately (without delay) goes back to a low impedance state. Finally, in short-circuit conditions, the PFC is disabled to lower the stress applied to the PWM main switch.

- **Skip-cycle capability:** a continuous flow of pulses is not compatible with no-load standby power requirements. Slicing the switching pattern in bunch of pulses drastically reduces overall losses but can, in certain cases, bring acoustic noise in the transformer. Thanks to a skip operation taking place at low peak currents only, no mechanical noise appears in the transformer. This is further strengthened by ON Semiconductor soft skip technique, which forces the peak current in skip to gradually increase. In case the default skip value would be too large, connecting a resistor to the pin 6 will reduce or increase the skip cycle level. Adjusting the skip level also adjusts the maximum switching frequency before skip occurs.
- **Over Voltage Protection:** by sensing the plateau level after the power switch has opened, the controller can detect an over voltage condition through the auxiliary reflection of the output voltage. If an OVP is sensed, the controller stops all pulses and permanently stays latched until the V_{CC} is cycled down below 4 V.
- **External latch input:** by permanently monitoring pin 5, the controller detects when its level rises above 3.5 V, e.g. in presence of a fault condition like an OTP. This fault is permanently latched-off and needs the V_{CC} to go down below 4 V to reset, for instance when the user un-plugs the SMPS.

AND8260/D

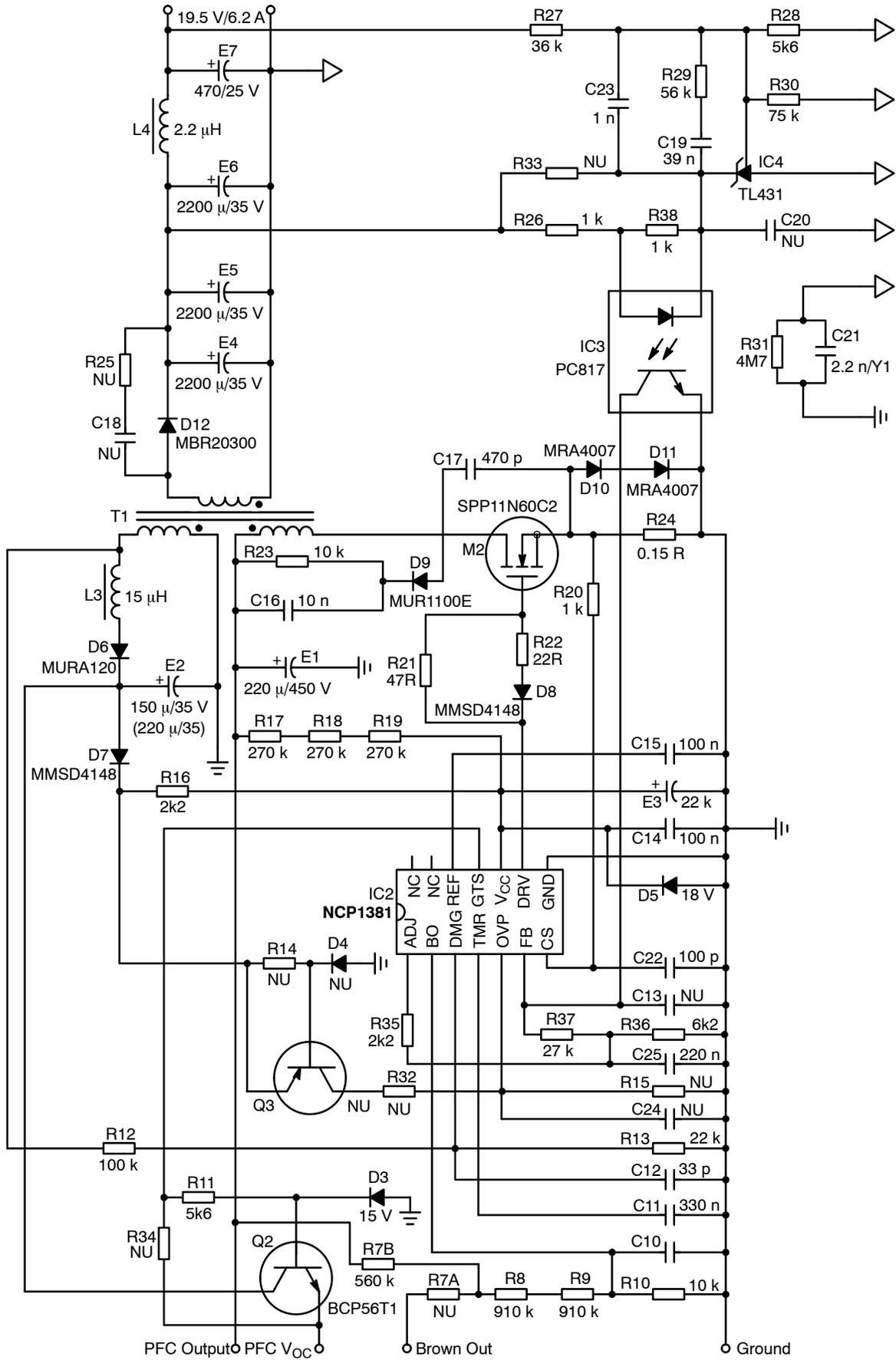


Figure 2. Valley Switching Converter

AND8260/D

DESIGN STEPS

PFC Stage

The PFC controller used is the MC33260, a controller for boost PFC stage featuring follower–boost capability. For the design of the PFC stage, please refer to the application notes AND8016 and AND8123.

Downstream Converter

Please refer to the application note AND8240 for the implementation of the NCP1381/82. Details of some design choices are described below.

Transformer

The primary inductance has been chosen in order to ensure a switching frequency lower than 130 kHz at high line when the output load is equal to 50% of the maximum load. An additional constraint is the turn ratio between primary and secondary inductors that must ensure that the voltage appearing across the switching MOSFET during OFF time is lower than 600 V with some margin.

Low line full load freq: 30 kHz

High line full load freq: 70 kHz

Valley jumping: < 50% load at high line

$L_p = 240 \mu\text{H}$

$I_{p\text{max}}$ at low line: 6 A

Turn ratio primary / secondary is equal to 4.4 (2.75 for the auxiliary winding), ensuring a reflected voltage from secondary to primary $V_{\text{REFLECT}} < 100 \text{ V}$ (exactly 90 V).

(See “Transformer construction” paragraph at the end of this document)

R_{SENSE}

The sense resistor is designed to allow the maximum peak current of 6 A. Knowing that the current sense comparator threshold is 800 mV, R_{SENSE} should then be smaller than 130 mW.

Brown–out

The voltage sensing for brown–out protection can either be taken in front of the PFC stage, for a true brown–out

protection, or after the PFC stage for a better overpower protection (see below). With the second solution, there is a minimum start–up voltage, but not any more minimum operating voltage, so it is not a true brown–out protection.

OPP

When OPP resistor is added, R_{SENSE} must be adjusted. In order to set the overpower protection for an output power of 130 W, R_{SENSE} is changed to 120 mW, and R_{OPP} is set to 2.7 kW.

PFC Control (GTS)

The board provides two ways of connecting the PFC controller to the GTS signal: directly, or through a buffer (made with a bipolar transistor).

The power levels at which PFC turn on and off are set by R35, R36, R37 and C25: these levels are currently 25 W (turn–off) and 40 W (turn–on), but can easily be adjusted depending on the needs.

Auxiliary Winding

In order to ensure a V_{CC} higher than 10 V in no–load conditions, auxiliary voltage is 30 V, and V_{CC} capacitor is split. A Zener diode is added to protect the controller. Splitting the tank capacitor allows to increase the stored energy (in capacitor E2), while keeping a small V_{CC} capacitor (capacitor E1) that ensures a fast start–up time.

Clamp

The MOSFET used cannot sustain voltages above 600 V, we thus need to add a clamping network to protect it. The RCD clamp made of D9, R23 and C16 give a sufficient protection without degrading too much the standby power. If a lower standby power is needed, R23 and C16 can be replaced by a 200 V TVS.

Secondary Side

For the simplicity of the demonstration board, a Schottky diode will be used as a rectifier, and not a synchronous rectifier as it would be in a real application.

The regulation is made around a TL431.

MEASUREMENTS: Power Factor and Efficiency

| Current Harmonic THD | Voltage Harmonic THD | Power Factor | I _{IN} (A _{dc}) | U _{IN} (V _{dc}) | I _{OUT} (A _{dc}) | U _{OUT} (V _{dc}) | P _{IN} (W) | P _{OUT} (W) | Eff. (%) |
|----------------------|----------------------|--------------|------------------------------------|------------------------------------|-------------------------------------|-------------------------------------|---------------------|----------------------|----------|
| 6.959 | 20.134 | 0.995 | 1.65 | 89.03 | 6.307 | 19.56 | 146.68 | 123.4 | 83.65 |
| 8.267 | 0.142 | 0.992 | 1.27 | 114.25 | 6.307 | 19.56 | 145.52 | 123.4 | 84.07 |
| 9.851 | 0.072 | 0.985 | 0.99 | 149.38 | 6.307 | 19.56 | 147.67 | 123.4 | 82.28 |
| 10.631 | 0.060 | 0.976 | 0.84 | 179.48 | 6.307 | 19.56 | 150.67 | 123.4 | 79.92 |
| 11.983 | 0.056 | 0.960 | 0.72 | 209.52 | 6.307 | 19.56 | 151.77 | 123.4 | 78.06 |
| 13.377 | 0.053 | 0.937 | 0.646 | 239.54 | 6.307 | 19.56 | 154.80 | 123.4 | 74.70 |
| 15.065 | 0.051 | 0.912 | 0.600 | 264.52 | 6.307 | 19.56 | 158.59 | 123.4 | 70.98 |

AND8260/D

No-load Power:

140 mW at 90 Vac
450 mW at 230 Vac.

Start-up



Figure 3. Start-up at 230 VAC



Figure 4. Start-up at 110 VAC

Load Transient

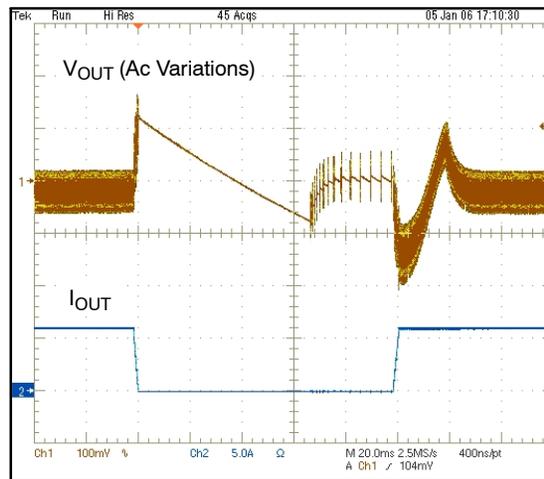


Figure 5. Load Dump from 100% to No-load

AND8260/D

Short-circuit

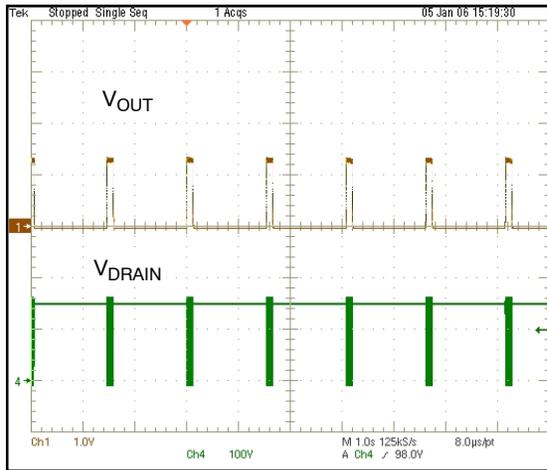


Figure 6. Short-circuit Burst Mode

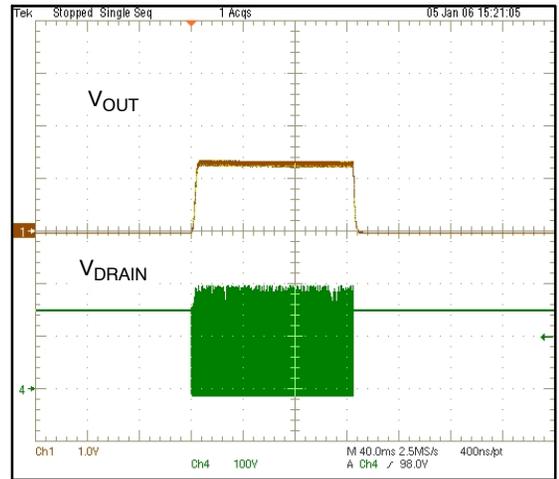


Figure 7. Detail of a Short-circuit Burst

Skip

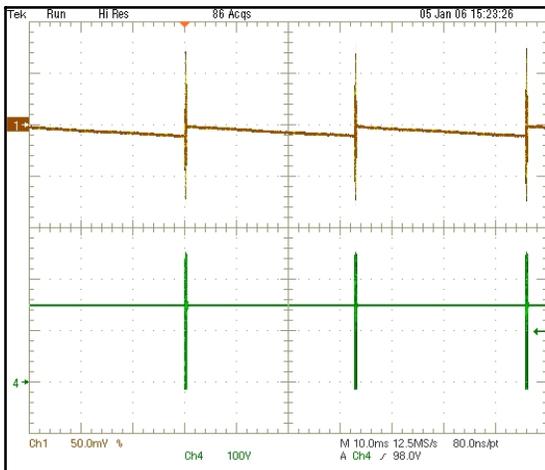


Figure 8. Skip Mode

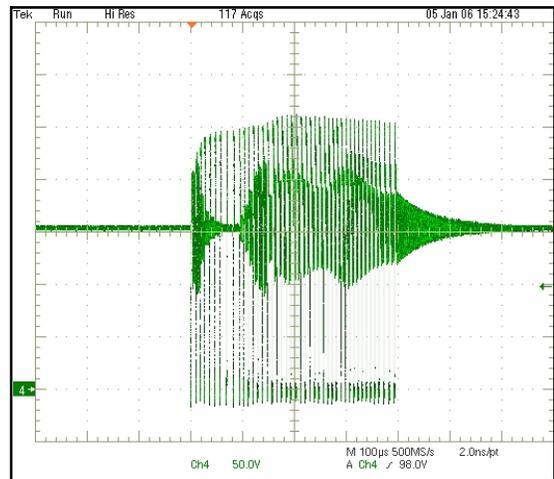


Figure 9. Detail of a Skip Burst

AND8260/D

PCB Layout

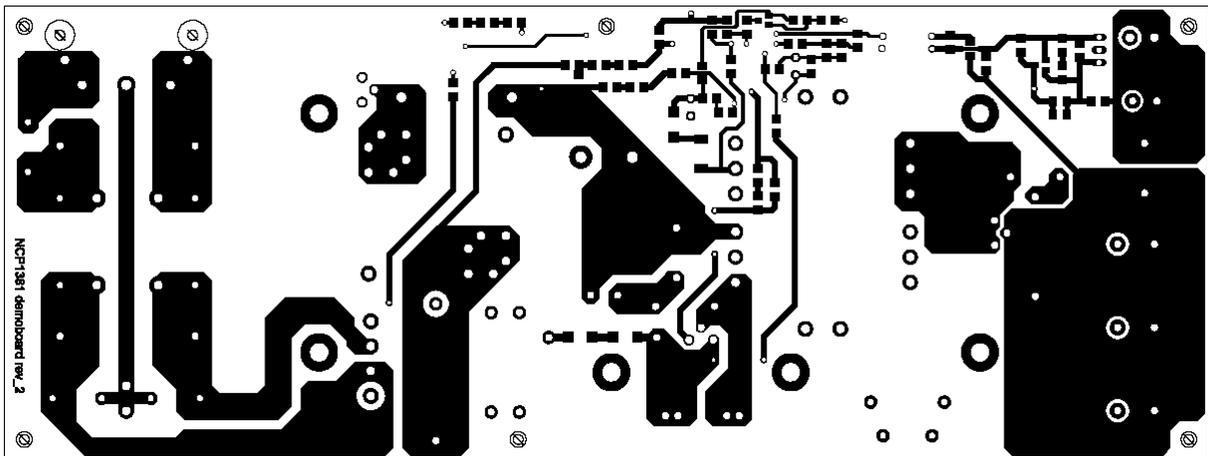


Figure 10. Solder Side (bottom view)

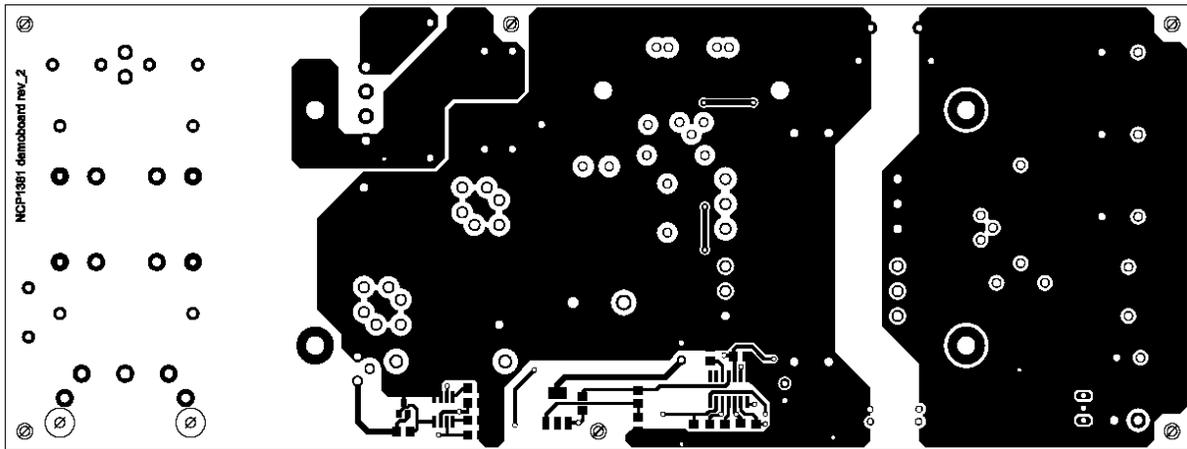


Figure 11. Top Side (top view)

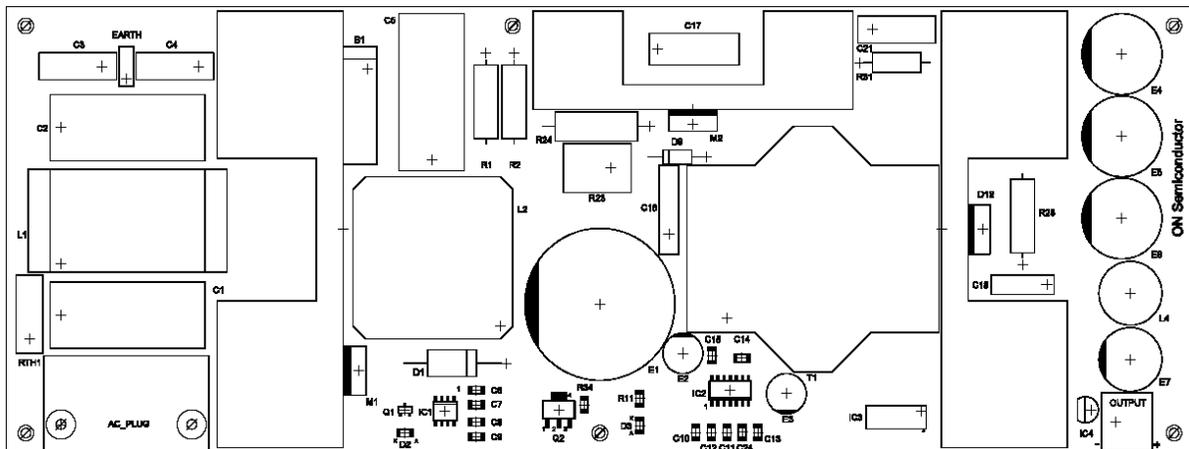


Figure 12. Top View of Component Side

AND8260/D

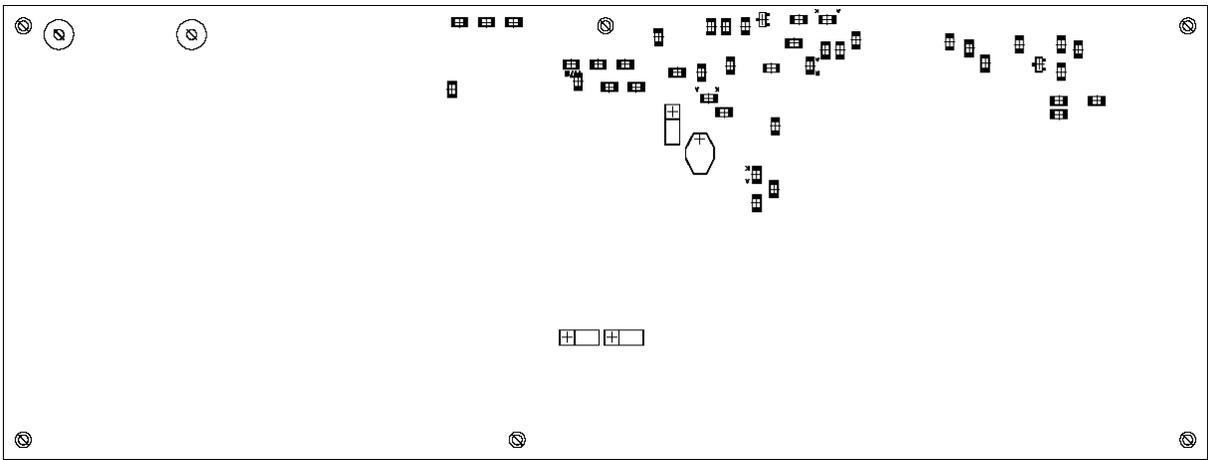


Figure 13. Bottom View of Solder Side (SMD Components)



Figure 14. Board Picture

AND8260/D


Table 1. BILL OF MATERIALS

| Part | Value | Package |
|------|------------------|---------|
| B1 | KBU810 | |
| C01 | 1 μ /X2 | |
| C02 | 1 μ /X2 | |
| C03 | 2n2/Y2/X1 | |
| C04 | 2n2/Y2/X1 | |
| C05 | 1 μ /X2 | |
| C06 | 470 p | C1206 |
| C07 | 100 n | C1206 |
| C08 | 220 n | C1206 |
| C09 | 2n2 | C1206 |
| C10 | 1 μ | C1206 |
| C11 | 330 n | C1206 |
| C12 | 33 p | C1206 |
| C13 | NU | C1206 |
| C14 | 100 n | C1206 |
| C15 | 100 n | C1206 |
| C16 | 10 n | |
| C17 | 470 p | |
| C18 | NU | |
| C19 | 39 n | C1206 |
| C20 | NU | |
| C21 | 2n2n/Y1/X1 | |
| C22 | 100 p | |
| C23 | 1 n | |
| C24 | NU | |
| C25 | 220 n | |
| D01 | MUR460 | |
| D02 | MMSD4148T1 | |
| D03 | 15 V | |
| D04 | NU | |
| D05 | 18 V | |
| D06 | MURA120 | |
| D07 | MMSD4148 | |
| D08 | MMSD4148 | |
| D09 | MUR1100E | |
| D10 | MRA4007 | |
| D11 | MRA4007 | |
| D12 | MBR20200 | |
| E1 | 220 μ /450 V | |
| E2 | 220 μ /35 V | |
| E3 | 33 μ /63 V | |
| E4 | 2200 μ /35 V | |
| E5 | 2200 μ /35 V | |
| E6 | 2200 μ /35 V | |
| E7 | 220/63 V | |
| F1 | T2A | |
| IC1 | MC33260 | |
| IC2 | NCP1381/82 | |
| IC3 | PC817 | |
| IC4 | TLV431 | |


| Part | Value | Package |
|------|-------------|---------|
| L1 | 6,3 mH | |
| L2 | 200 μ H | |
| L3 | 15 μ H | |
| L4 | 2,2 μ H | |
| M1 | SPP11N60C2 | |
| M2 | SPP11N60C2 | |
| Q1 | BC807 | |
| Q2 | BCP56T1 | |
| Q3 | NU | |
| R01 | 1R | 2W |
| R02 | 1R | 2W |
| R03 | 20 k | R1206 |
| R04 | 560 k | R1206 |
| R05 | 680 k | R1206 |
| R06 | 680 k | R1206 |
| R07A | NU | |
| R07B | 560 k | R1206 |
| R08 | 910 k | R1206 |
| R09 | 910 k | R1206 |
| R10 | 10 k | R1207 |
| R11 | 5k6 | R1206 |
| R12 | 100 k | R1206 |
| R13 | 22 k | R1207 |
| R14 | NU | |
| R15 | NU | |
| R16 | 2k2 | R1206 |
| R17 | 270 k | R1206 |
| R18 | 270 k | R1206 |
| R19 | 270 k | R1206 |
| R20 | 2k7 | R1206 |
| R21 | 47R | R1206 |
| R22 | 22R | R1206 |
| R23 | 10 k | R1206 |
| R24 | 0,12R | |
| R25 | NU | |
| R26 | 1 k | R1206 |
| R27 | 36 k | R1206 |
| R28 | 5k6 | R1206 |
| R29 | 56 k | R1206 |
| R30 | 75 k | R1206 |
| R31 | 4M7 | |
| R32 | NU | |
| R33 | NU | |
| R34 | NU | |
| R35 | 2k2 | R1206 |
| R36 | 6k2 | R1206 |
| R37 | 27 k | R1206 |
| R38 | 1 k | R1206 |
| RTH1 | strapped | |
| T1 | Transformer | |

AND8260/D

TRANSFORMER CONSTRUCTION

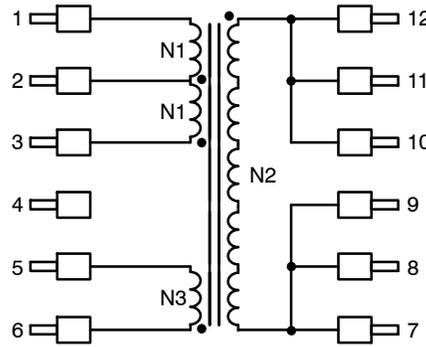

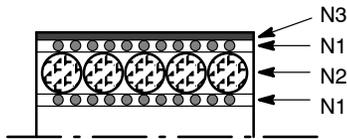Transformer Type: RM14
Material: N67
Marking: B65888-C1512-T1



N1 — 11 turns of multiwire 20 x $\phi 0,2$ mm 3 kV isolation
N2 — 5 turns of 5 paralleled multiwires 25 x $\phi 0,2$ mm 3 kV isolation
N1 — 11 turns of multiwire 20 x $\phi 0,2$ mm 1.5 kV isolation
N3 — 8 turns of wire $\phi 0,2$ mm

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:
Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5773-3850

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local Sales Representative