



Design Solution # 40

SP7655 Buck Converter for 12V to 1.2V conversion

Part Number: SP7655

Designed by: Tim Sullivan

Application Description: An SP7655 PowerBlox™ is used to create a 1.2volt output from a 12volt source.

Electrical Requirements:


Input Voltage: 12V +/-2volts
Output Voltage: 1.2 Volts
Output Current: up to 8A capable

Circuit Description:

This circuit has been designed to provide 1.2 volts from a 12volt nominal supply. It uses the PowerBlox™ solution SP7655 and 24 discrete parts (not including PCB and I/O pins) and uses approximately 2 square inches of board space. It is possible to maintain this small area usage by the incorporation of the high and low side FETs and the PWM controller into one package.

The solution uses an Inter-Technical 7mm X 7mm, low resistance inductor which is a good balance of size and performance for this solution. An inexpensive Sipex SPX5205 LDO was used to provide the 5V Vcc for the part. Ceramic capacitors were used on the converter input and output and a type 3 feedback configuration was implemented to provide excellent transient response.

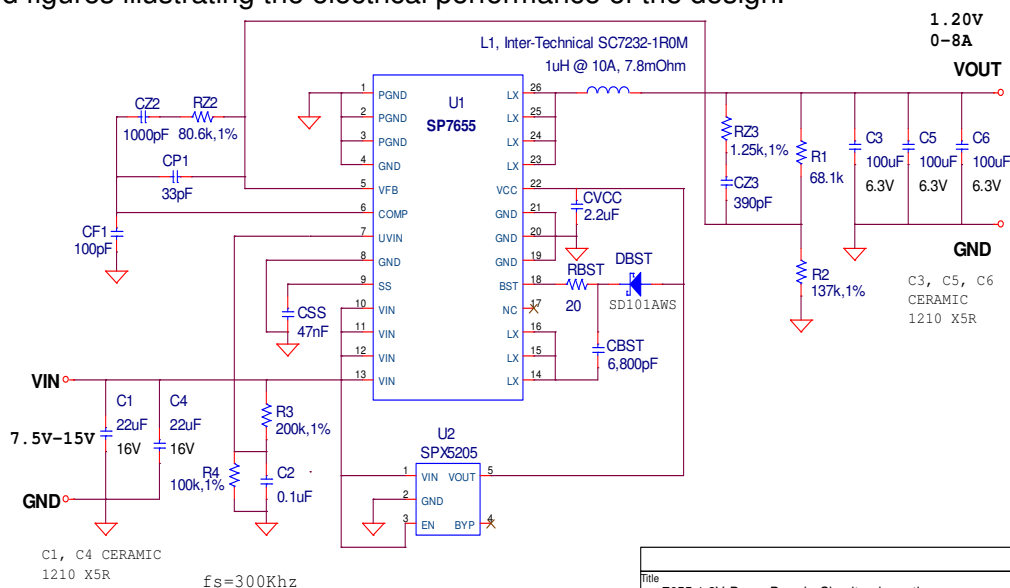This report includes an application schematic complete with component values, a complete Bill of Materials, and figures illustrating the electrical performance of the design.



All resistance values are in Ohms

Title		
7655 1.2V Demo Board - Circuit schematic		
Size	Document Number	Rev
A	<Doc>	
Date: Tuesday, May 16, 2006 Sheet 1 of 1		

Performance Measurements

7655 Efficiency
12Vin, 1.2Vout

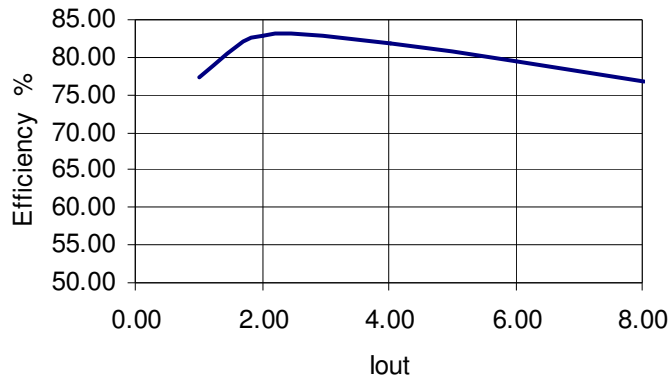


Figure 1 – Efficiency vs Load

7655 Load Regulation
12Vin, 0 to 8A Load

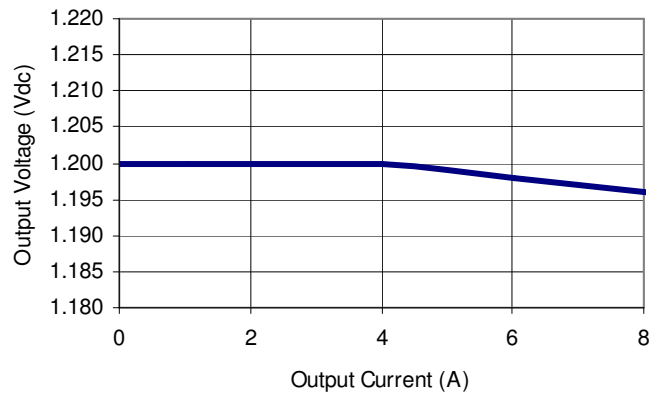


Figure 2 – Load Regulation

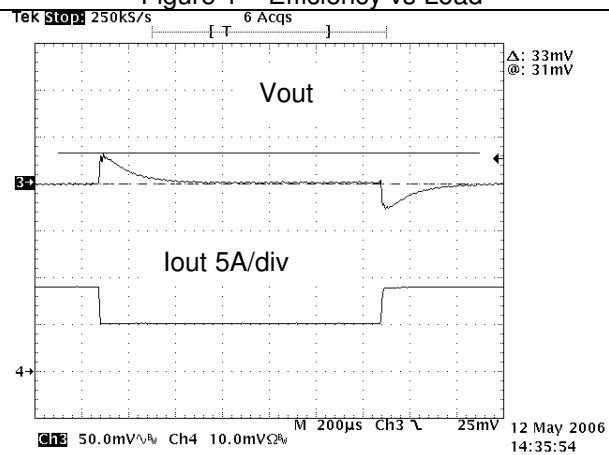


Figure 2 – Load Step Response 5->8 Amps

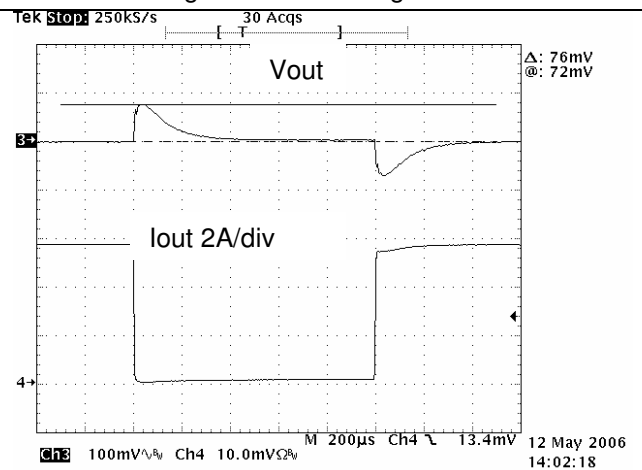


Figure 3 – Load Step Response 0->6 Amps

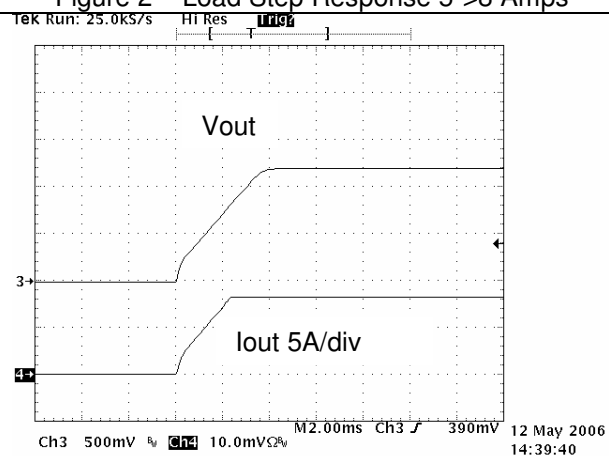


Figure 4 – Start-Up Response: Vin to 8 Amps


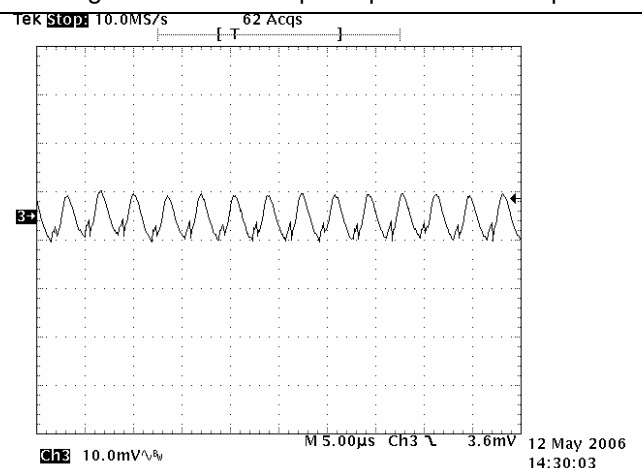


Figure 5 – Output Ripple, Output Current = 8Amps

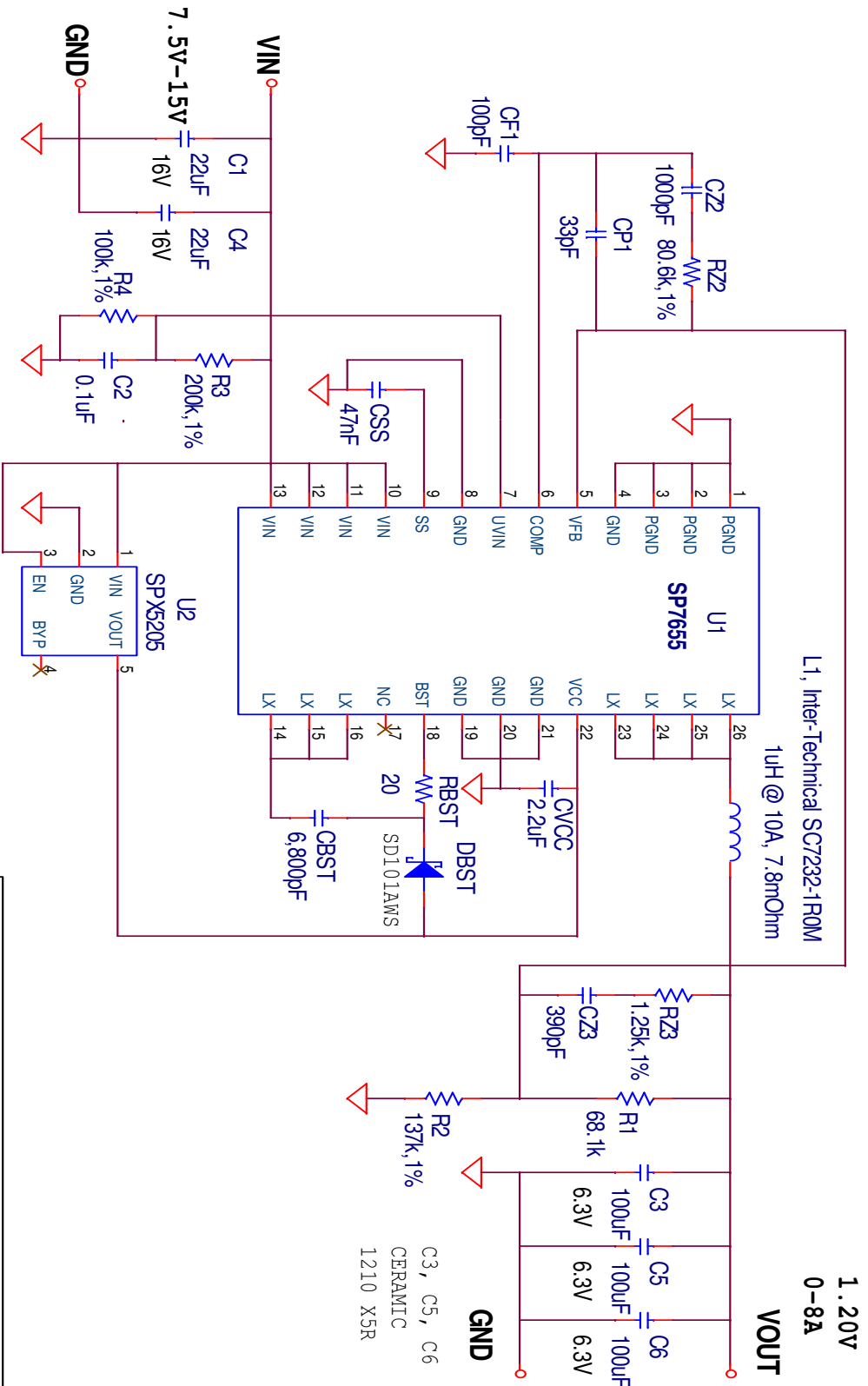

Circuit Schematic:

Note: All resistance values are in Ohms

Title			
7655 1.2V Demo Board - Circuit schematic			
Size	Document Number	Rev	
A	<Doc>		
Date:	Tuesday, May 16, 2006	Sheet	1 of 1

Converter Bill of Materials:

SP7655 Vin=12V Vout=1.2V Evaluation Board Rev. 00 List of Materials

Line No.	Ref. Des.	Qty.	Manuf.	Manuf. Part Number	Layout Size	Component
1	PCB	1	Sipex	146-6570-01	1.75"X2.75"	SP7655EB
2	U1	1	Sipex	SP7655EU	DFN-26	2-FETs Buck Ctrl
3	U2	1	Sipex	SPX5205M5-5.0	SOT-23-5	150mA LDO Voltage Reg
4	DBST	1	Vishay Semi	SD101AWS	SOD-323	15mA Schottky Diode
6	L1	1	Inter-Technical	SC7232-2R2M	6.8X6.8mm	2.2uH Coil 8A 10.4mohm
7	C3, C5, C6	3	TDK	C3225X5R0J107M	1210	100uF Ceramic X5R 6.3V
8	C1, C4	2	TDK	C3225X7R1H226M	1210	22uF Ceramic X7R 16V
9	CVCC	1	TDK	C1608X5R1A225K	0603	2.2uF Ceramic X5R 10V
10	CBST	1	TDK	C1608X5R1A682K	0603	6800pF Ceramic X5R 10V
11	C2	1	TDK	C1608X7R1H104K	0603	0.1uF Ceramic X7R 50V
12	CSS	1	TDK	C1608X7R1H473K	0603	47,000pF Ceramic X7R 50V
13	CP1	1	TDK	C1608COG1H330J	0603	33pF Ceramic COG 50V
14	CZ2	1	TDK	C1608COG1H102J	0603	1000pF Ceramic COG 50V
15	CF1	1	TDK	C1608COG1H101J	0603	100pF Ceramic COG 50V
16	CZ3	1	TDK	C1608COG1H391J	0603	390pF Ceramic COG 50V
17	RZ2	1	Panasonic	ERJ-3EKF78062V	0603	80.6K Ohm Thick Film Res 1%
18	R2	1	Panasonic	ERJ-3EKF1373V	0603	137K Ohm Thick Film Res 1%
19	RZ3	1	Panasonic	ERJ-3EKF1251V	0603	1.25K Ohm Thick Film Res 1%
20	R1	1	Panasonic	ERJ-3EKF6812V	0603	68.1K Ohm Thick Film Res 1%
21	R3	1	Panasonic	ERJ-3EKF2003V	0603	200K Ohm Thick Film Res 1%
22	R4	1	Panasonic	ERJ-3EKF1003R0V	0603	100K Ohm Thick Film Res 1%
23	RBST	1	Panasonic	ERJ-3EKF20R0V	0603	20.0 Ohm Thick Film Res 1%
24	VIN, VOUT, GND, GND2	4	Vector Electronic	K24C/M	.042 Dia	Input/Output Terminal Posts

Sept28-06

Design Solution 40

© Sipex Corporation