

TI Power Management Solution for Freescale™ i.MX31

*Gunjot Kaur**PMP - Portable Power*

ABSTRACT

This document details the voltage, current, and sequencing requirements for the i.MX31 and shows how to power it using the TPS650240.


1 Original Supply Power-Up/Power-Down Requirements and Restrictions

As noted in the i.MX31 data sheet, any i.MX31 board design must comply with the power-up and power-down sequence guidelines in the following discussion in order to ensure reliable operation of the device. Any deviation from the sequence in the following discussion may lead to excessive current during the power-up phase, prevent the device from booting, or may cause irreversible damage to the processor.

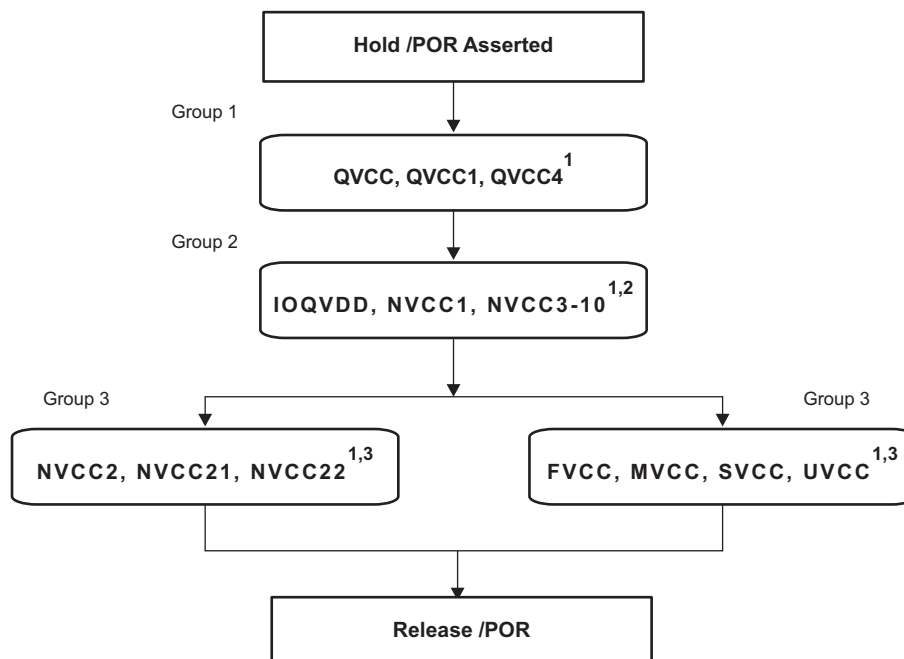1.1 Powering Up

The Power on Reset pin ($\overline{\text{POR}}$) must be kept asserted (low) throughout the power-up sequence. Power-up logic must ensure that all power sources reach their target values prior to the release of the $\overline{\text{POR}}$ pin. The [Figure 1](#) shows the power-up sequence for silicon Revision 2.0.

The stages need to be performed in the order shown. However, within each stage, supplies can be powered up in any order. Note the restrictions within each stage.



- (1) The board's design must ensure that supplies reach a 90% level before transition to the next state, using a power management IC or other means.
- (2) The NVCC1 supply must not precede IOQVDD by more than 0.2 V until IOQVDD has reached 1.5 V. If IOQVDD is powered up first, there are no restrictions.
- (3) The parallel paths in the flow indicate that supply group NVCC2, NVCC21, and NVCC22, and supply group FVCC, MVCC, SVCC, and UVCC ramp-ups are independent.

Figure 1. Power-Up Sequence

1.2 Powering Down

For silicon revisions beginning with Revision 2.0, the power-down sequence has no special requirements.

1.3 Measurements for Power Up of the i.MX31P

Measurements were made on the development board in order to analyze the power-up sequencing required for the i.MX31. The signals that needed to be measured were short listed.

GROUP 1		GROUP 2	
QVCC	QVCC	IOQVDD	1.8V_NVCC10
QVCC1	QVCC_ARM	NVCC1	1.8V_NVCC1
QVCC4	QVCC_L2	NVCC3 ²	NVCC3
GROUP 3		NVCC4 ²	NVCC4
NVCC2	1.4V_DDR	NVCC5 ²	2.7V_NVCC5/NVCC8
NVCC21	1.4V_DDR	NVCC6 ²	2.7V_NVCC6/NVCC9
NVCC22	1.4V_DDR	NVCC7 ²	1.8V_NVCC7
FVCC	VCC_VDIG	NVCC8 ²	2.7V_NVCC5/NVCC8
MVCC	VCC_VDIG	NVCC9 ²	2.7V_NVCC6/NVCC9
SVCC	VCC_VDIG	NVCC10 ²	1.8V_NVCC10
UVCC	VCC_VDIG		

The following results were obtained for the power up of the i.MX31 processor using the MC13783 Power Management and Audio Component.

Figure 2 shows the timing diagram for all the relevant power-up signals.

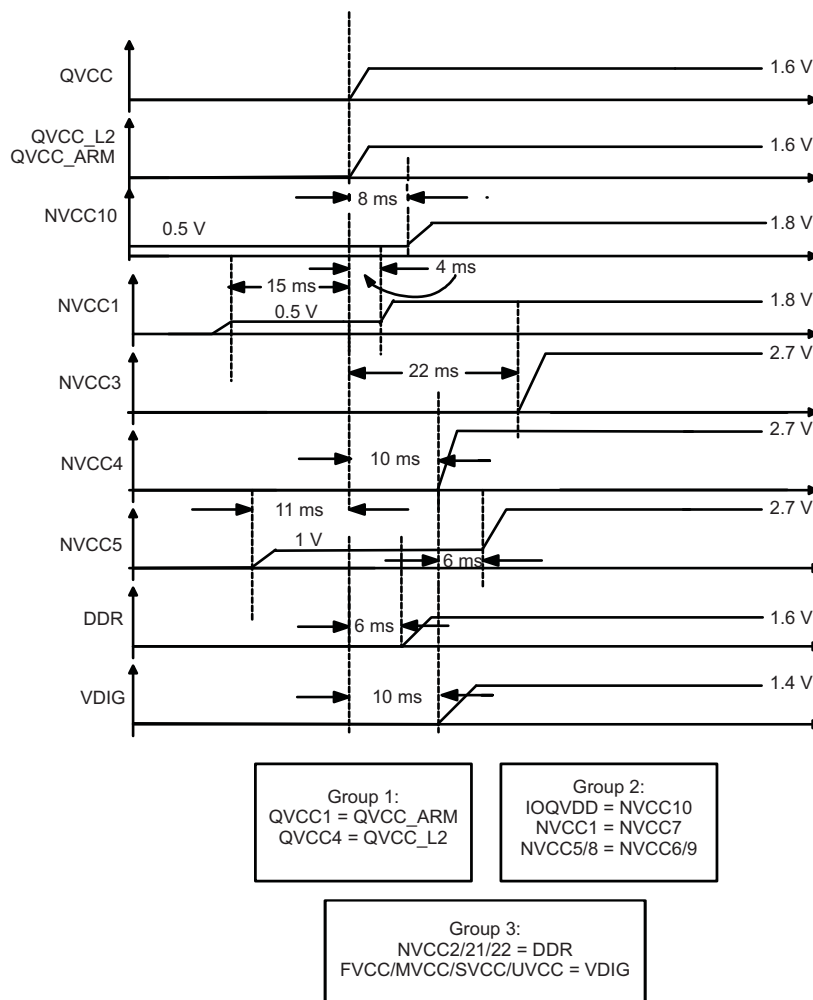


Figure 2. Power-Up of the i.MX31 Processor Timing Diagram

1.4 TI Solution for the i.MX31 Power-Up Sequence Using TPS650240

Figure 3 shows the proposed schematic for powering up the Freescale™ processor using TPS650240 power management integrated circuit (IC).



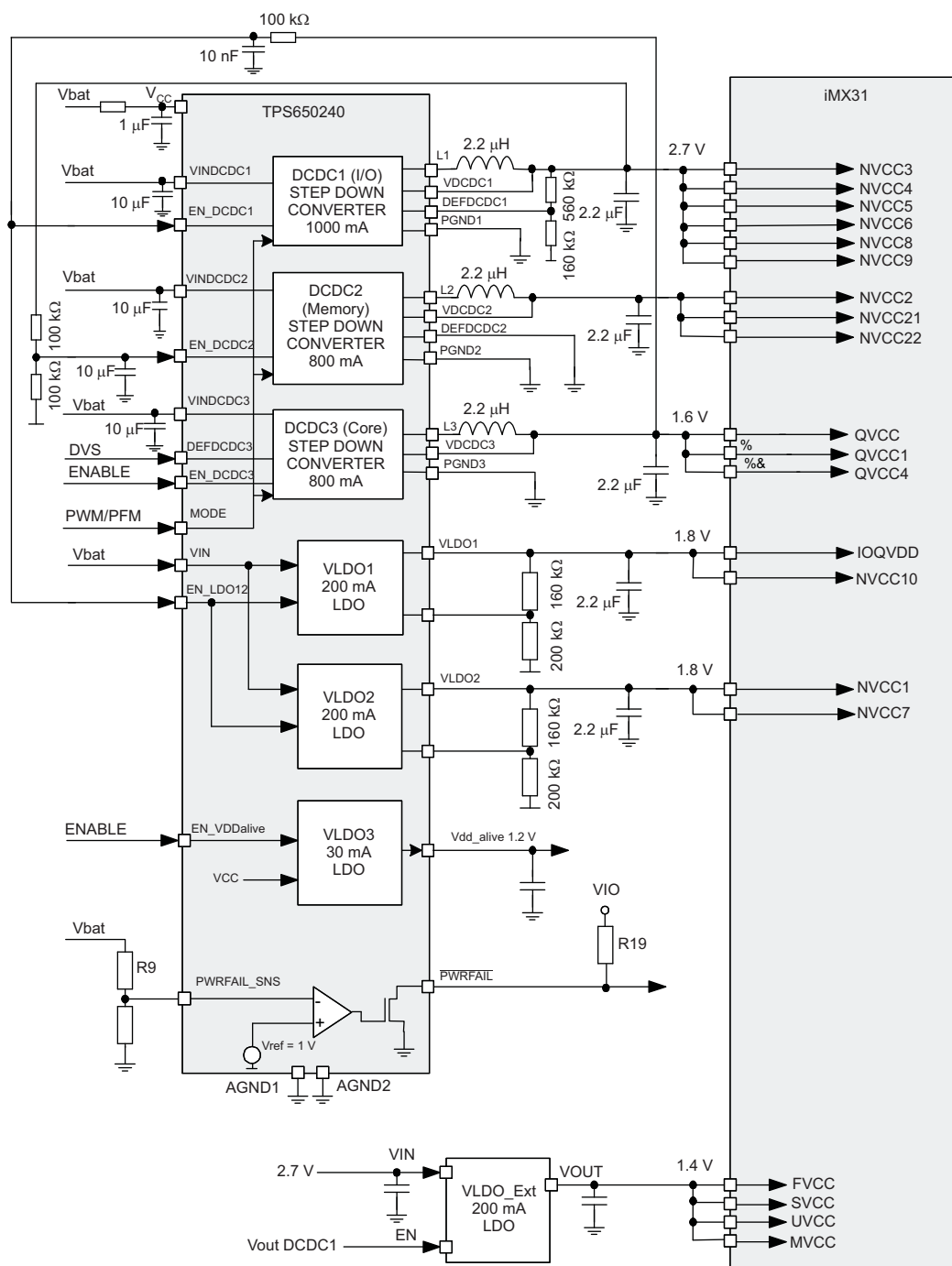


Figure 3. Proposed Schematic for i.MX31 Powering Using TPS650240

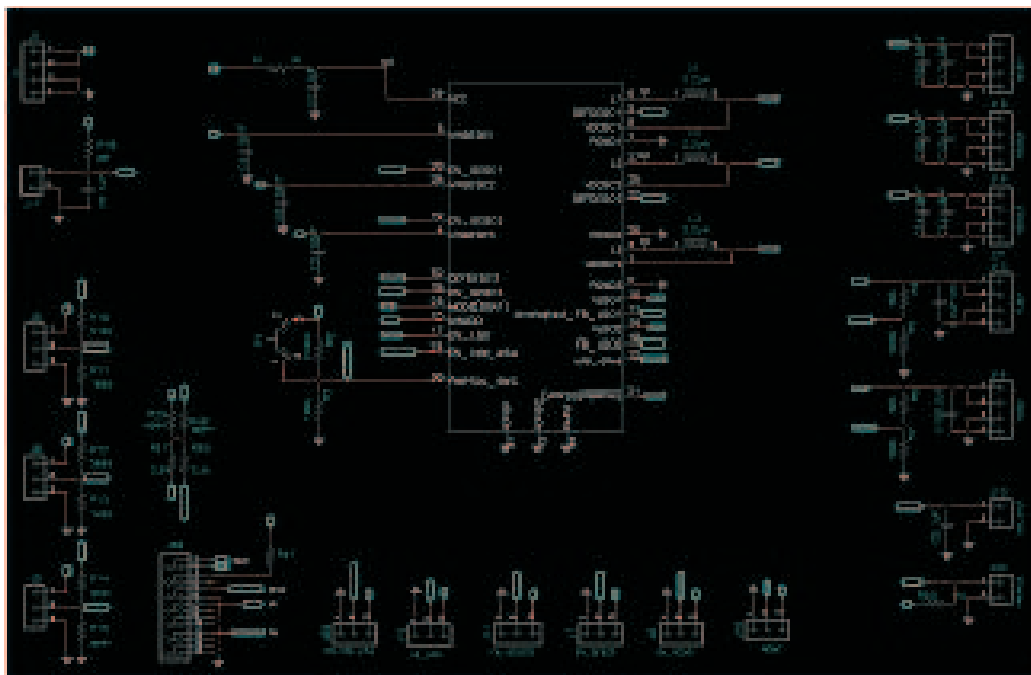The EVM was soldered according to the following schematic, and measurements were made in order to analyze the TPS650240 output voltages and sequencing.



 Signal analysis showed the following results for sequencing:



Orange → VDCDC3, Pink → VLDO1, Green → VDCDC1, Purple → VDCDC2

2 Summary

The TPS650240 devices provide voltages 1.5 V, 1.4 V, and 2.7 V for various signals in Groups 1, 2, and 3 of the sequencing scheme necessary for the powering up the i.MX31 multimedia application processor.

Step-down converter DCDC3 is enabled first to provide a 1.5-V signal for QVCC, QVCC1, and QVCC 4 as shown in [Figure 3](#).

The output of DCDC3 also enables the LDOs, VLDO1 and VLDO2. It also simultaneously enables the step-down converter DCDC1. IOQVDD, NVCC1-10 are then triggered. The necessary output levels are achieved using different resistor values.

The output of DCDC1 enables DCDC2 and the external LDO, simultaneously. Thus, as required, NVCC2, NVCC21, NVCC22, FVCC, SVCC, MVCC, and UVCC are all triggered in the end.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2008, Texas Instruments Incorporated