

MSP430 Stepper Motor Controller

Greg Morton

MSP430

ABSTRACT

This application report shows how to implement a controller for a stepper motor having bipolar windings using the MSP430F123 along with a pair of UC3717A Stepper Motor Drive ICs. Source code, schematic, bill of material, and board layout files are provided.

1 Stepper Motors

Stepper motors operate by sequentially energizing coils located in the stator. Depending upon the stepper motor's type; variable reluctance, permanent magnet, or hybrid, the rotor contains a toothed soft-iron core, permanent magnets, or both. What sets a stepper motor apart from other motor types is the ability to step (or turn) its rotor in small, precise increments and lock it in place.

Three configurations are typically found for wiring a stepper motor's windings; variable reluctance, unipolar, and bipolar. Each configuration requires different drive circuitry and its associated method of control. This application report focuses on controlling stepper motors with bipolar windings. Bipolar stepper motors are driven using an H-bridge circuit since current flow is bi-directional through the windings.

Based on its internal winding resistance, stepper motors are rated for maximum current at a particular voltage. Maximum torque is developed when maximum current is flowing through the windings. Operating at this voltage, however, is inefficient due to the ramp-up time it takes for current flow to overcome the winding's inherent inductance. Applying a voltage much higher than it's rated for to a stepper motor reduces this ramp-up time. To do this without overheating and destroying the motor, however, the winding current must still be limited to its maximum rated value. This is done by using a *chopper circuit* which controls the ratio of winding current *on* time to *off* time once the maximum current level is reached.

2 Implementation

2.1 Hardware

Figure 1 shows a block diagram of the MSP430 Stepper Motor Controller board. Although any MSP430 variant could have been used to implement a basic stepper motor controller using Timer A, the MSP430F123 was chosen since it contains a hardware UART for serial communications with a PC. Two UC3717A integrated circuits (ICs) provide the motor drive circuitry. Each UC3717A IC contains one H-bridge circuit for driving a single winding in a bipolar stepper motor. The UC3717A also contains a *chopper circuit* limiting the maximum current flowing through a motor's winding. To reduce external component count, the protection diodes required to clamp the inductive voltage spikes generated when switching current through a motor are also contained within the UC3717A.

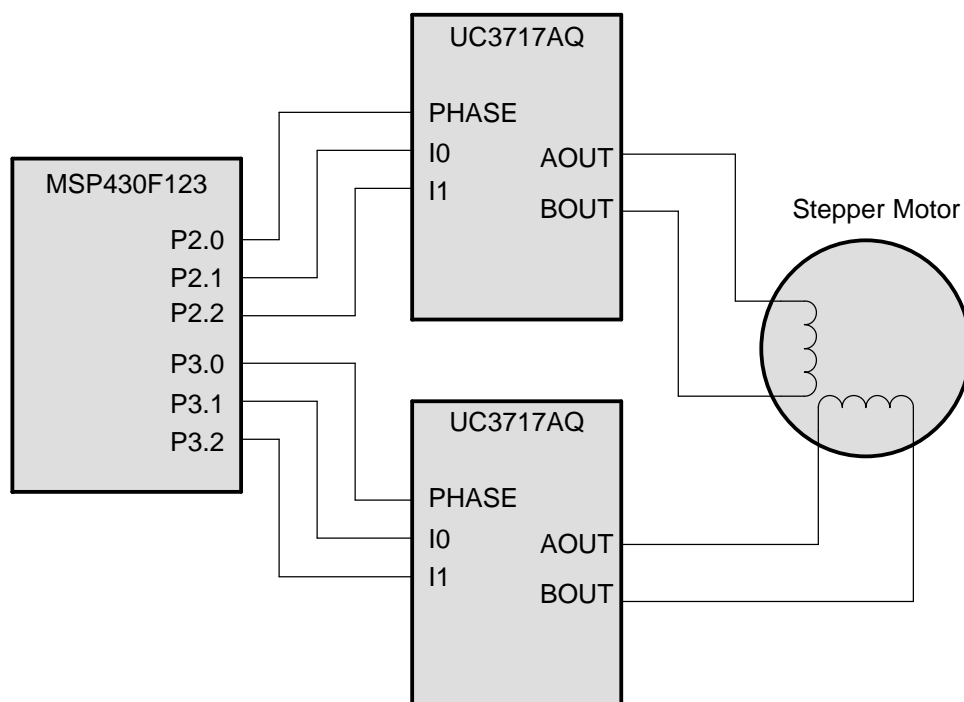


Figure 1. Block Diagram

Figure 2 shows a picture of the MSP430 Stepper Motor Controller board. Figure 4 shows the schematic. Port pins P2.0–P2.2 and P3.0–P3.2 on the MSP430 (U6) provide the control signals for the two UC3717A ICs (U1 and U5). Switches S1–S4 provide the inputs to the MSP430 to control the stepper motor. As an alternative, the stepper motor can also be controlled using a PC. A serial cable can be connected between connector J3 and a PC's serial port. U3 provides the RS-232 line driver/receiver required for level-shifting the RX and TX signals. The 32 kHz watch crystal, X1, provides the clock source for the MSP430's hardware UART. Connector J4 provides a convenient way to connect to a stepper motor. Connector J1 provides the JTAG connection for the MSP430 Flash Emulation Tool. DC power jack J2 enables the board to be powered by a +12V, 1.5A AD/DC adaptor. Battery holder B1 provides the option of powering the board with a +9V battery. Linear regulators U6 and U2 provide +5VDC and +3.3VDC respectively. Jumpers JP3 and JP4 provide an easy way to measure system current and motor current if desired. Jumper JP1 provides an easy way to monitor the UC3717A control signals with a scope. LEDs D1 and D2 are used to display operating modes.

A few external components are required by the UC3717A Stepper Motor Driver ICs. Components C10 and R4 for U1 and C9 and R8 for U5 set the *off* time for the UC3717A's chopper circuit. Components R3 and C8 for U1 and R7 and C12 for U5 form a low-pass filter to reduce switching transients appearing at the input to the UC3717A's *current* sensor section. Parallel resistors R1 and R2 for U1 and R5 and R6 for U5 provide a 1 ohm resistor for sensing current flowing through a stepper motor's windings. For a more detailed explanation, consult the UC3717A's data sheet ^[1].

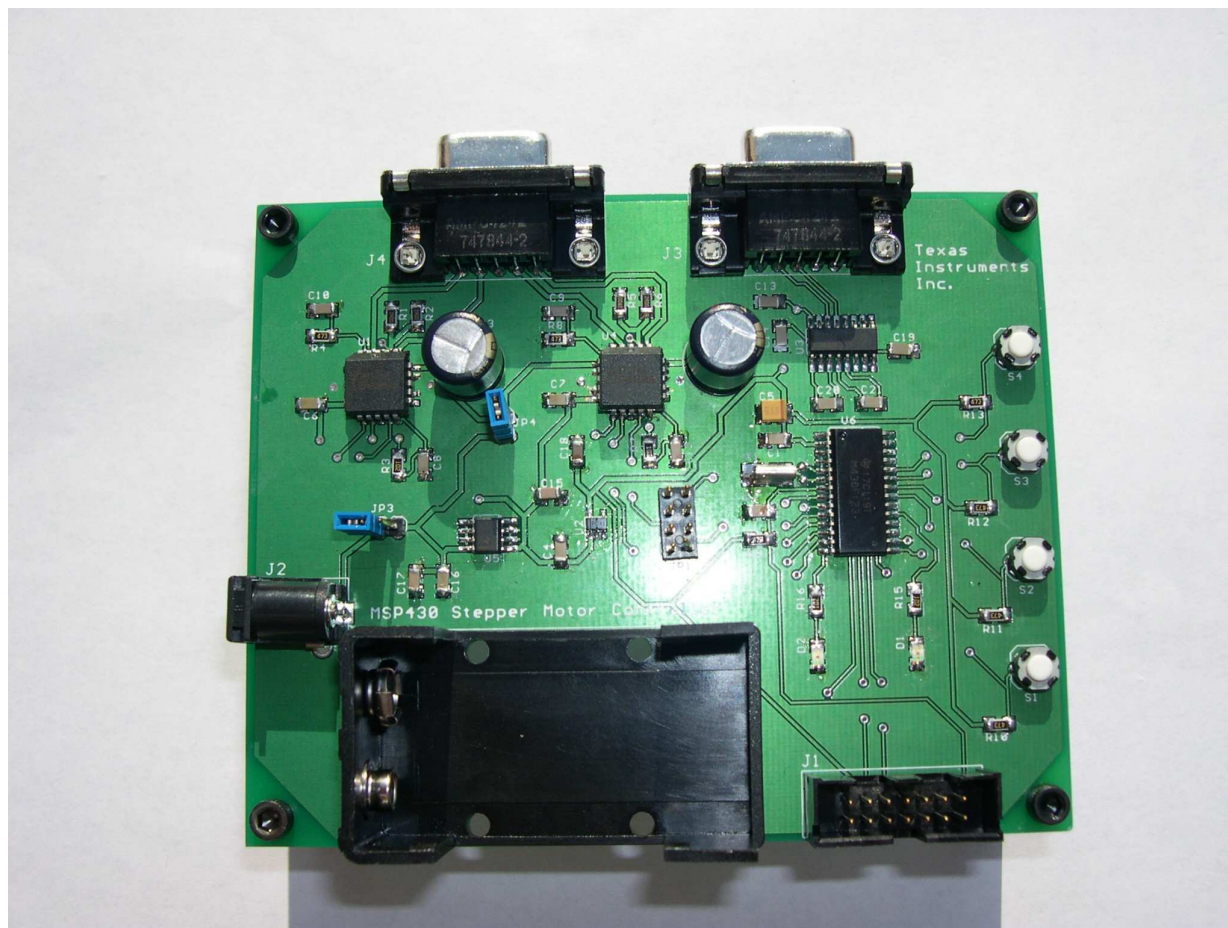


Figure 2. MSP430 Stepper Motor Controller Board

2.2 Software

Since most of the complexity with driving stepper motors involves limiting the winding current through the motor and the U3717A IC contains hardware to do this, the software implementation is relatively straight forward. For continuous mode operation, the MSP430's 16-bit Timer A is configured to generate an interrupt at the same rate as the motor is stepped. This is done by configuring Timer A for Up-mode and setting the maximum count in register TACCR0. Detailed information on Timer A operation can be found in [3]. Changing the value stored in TACCR0 changes the stepping rate. Stepping period equals $1/\text{SMCLK}$ frequency times the value stored in TACCR0. During the Timer A0 interrupt service routine (ISR) a state table lookup is performed to retrieve the next output state for the 6 port pins controlling the two UC3717A devices. The port pins are then updated and the state table index is incremented. Different state tables are used depending upon the direction the motor is stepped as well as the mode of operation; fullstepping or half-stepping. Figure 3 shows the stepping sequences for the various stepping modes and directions. During full-stepping I0 and I1 are held at a constant logic 0 state.

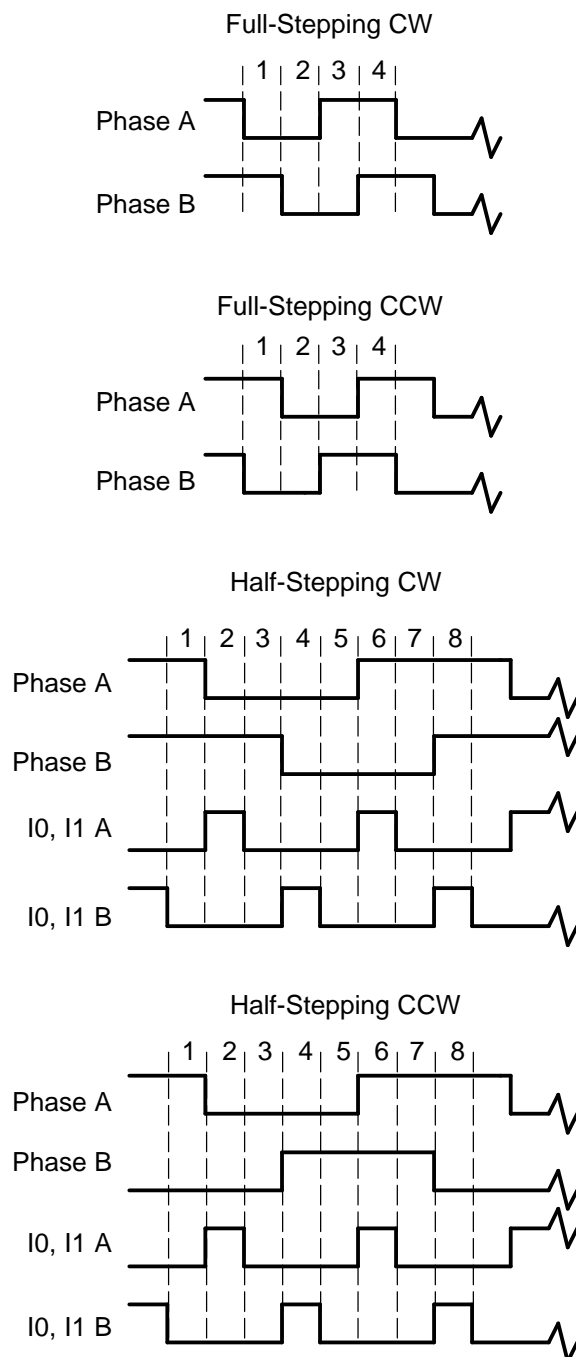


Figure 3. Stepping Sequences

Switches S1 through S4 are used to control stepper motor operation. Whenever any of the switches are pressed, the port 1 interrupt service routine (ISR) executes. The port 1 ISR disables port 1 interrupts and enables watchdog timer (WDT) interrupts. When enabled, the WDT ISR executes about once every 2 milliseconds. Each time the WDT ISR executes it checks the state of the switches. If switch S1, S3, or S4 is held in the *on* state for a *debounce count* of 5 consecutive interrupts or 10 milliseconds, then the operation associated with the particular switch is executed. Switch S2 works a little differently. If S2 is held

in the *on* state for more than 10 milliseconds and less than 1 second, then the stepper motor toggles between continuous mode and step mode. Holding S2 *on* for more than 1 second toggles between fullstepping and half-stepping modes. For as long as S2 is held in the *on* state it will continue to toggle between stepping modes every second. Once all the switches are in the off state, the WDT ISR disables itself and re-enables the port 1 ISR.

The serial port on a PC can also be used to operate the stepper motor controller board. Each time the MSP430 receives a character, the UART RX ISR executes. If a *matching* character is received, then the operation associated with the character is executed. At the end of the UART RX ISR, it transmits back to the PC the character it received. This provides feedback to the PC user that the MSP430 received the character sent to it by the PC.

2.3 Operation

Four switches, S1 through S4, control how the Stepper Motor Controller board operates. S1 controls direction. Each time S1 is pressed the motor changes its direction of rotation. S2 controls how the motor is stepped. Each time S2 is pressed for less than 1 second, the motor toggles between continuous mode and single step mode. Holding S2 down for more than 1 second toggles the stepping sequence between full-stepping and half-stepping. LED D2 is illuminated while operating in half-stepping mode. Otherwise, D2 is off. LED D1 is illuminated while in single step mode. Otherwise, D1 is off. While operating in continuous mode, pressing S3 increases the motor's stepping rate, S4 decreases it. For single step mode, the motor steps as long as S3 is pressed. S4 advances the motor one step each time it is pressed.

When using a serial cable to control the board, [Table 1](#) shows the operation performed when a character is received by the MSP430. LED operation does not change. D1 is illuminated while in single-step mode and D2 is illuminated while in half-stepping mode.

Table 1. Serial Port Operation

| CHARACTER | OPERATION |
|-----------|--|
| D or d | Toggles motor's direction |
| C or c | Toggles between continuous mode and step mode |
| M or m | Toggles between full-stepping and half-stepping mode |
| F or f | Increases motor's speed (continuous mode) / single steps motor (step mode) |
| S or s | Decreases motor's speed (continuous mode) / single steps motor (step mode) |

3 Schematics

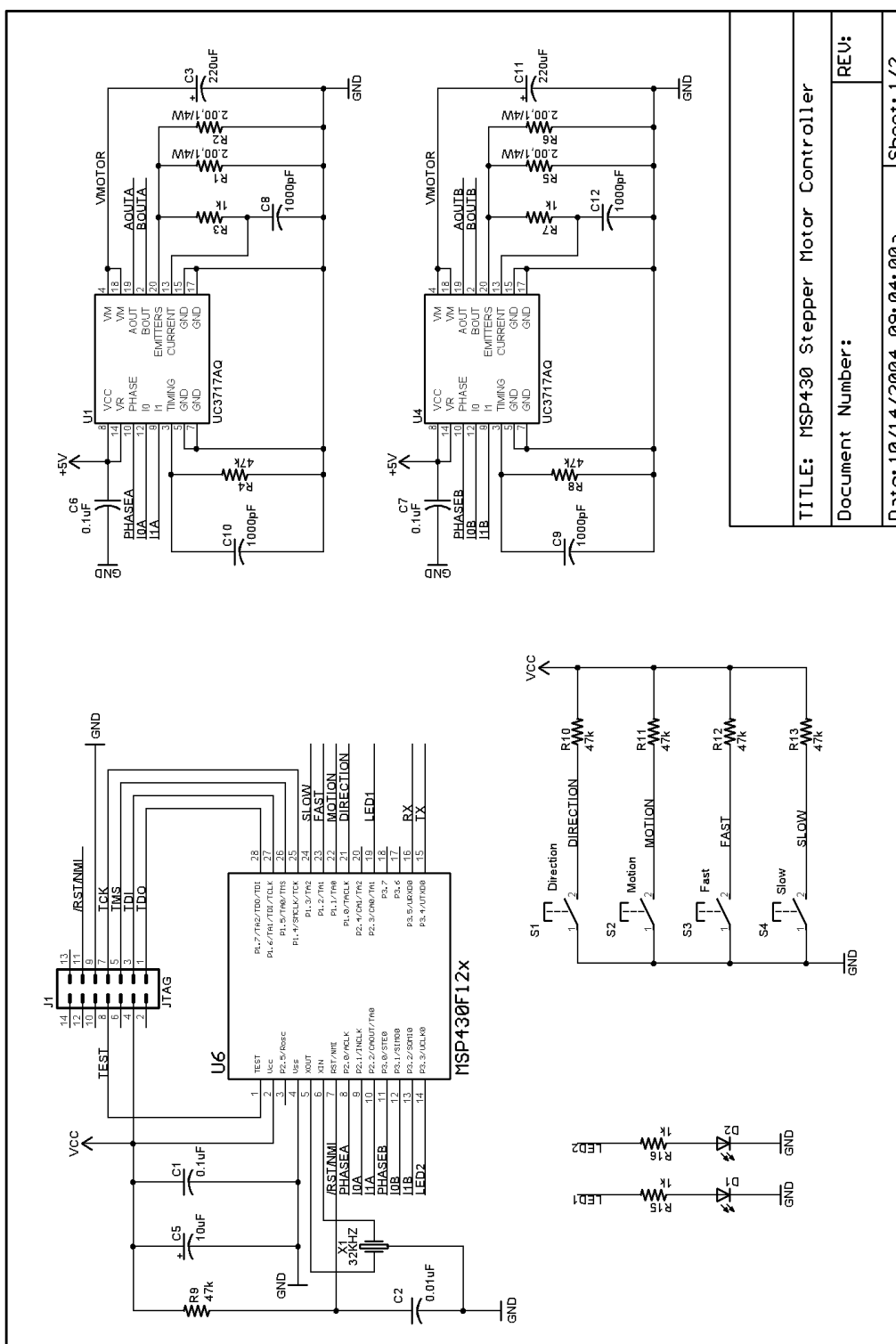


Figure 4. MSP430 Stepper Motor Schematic (1/2)

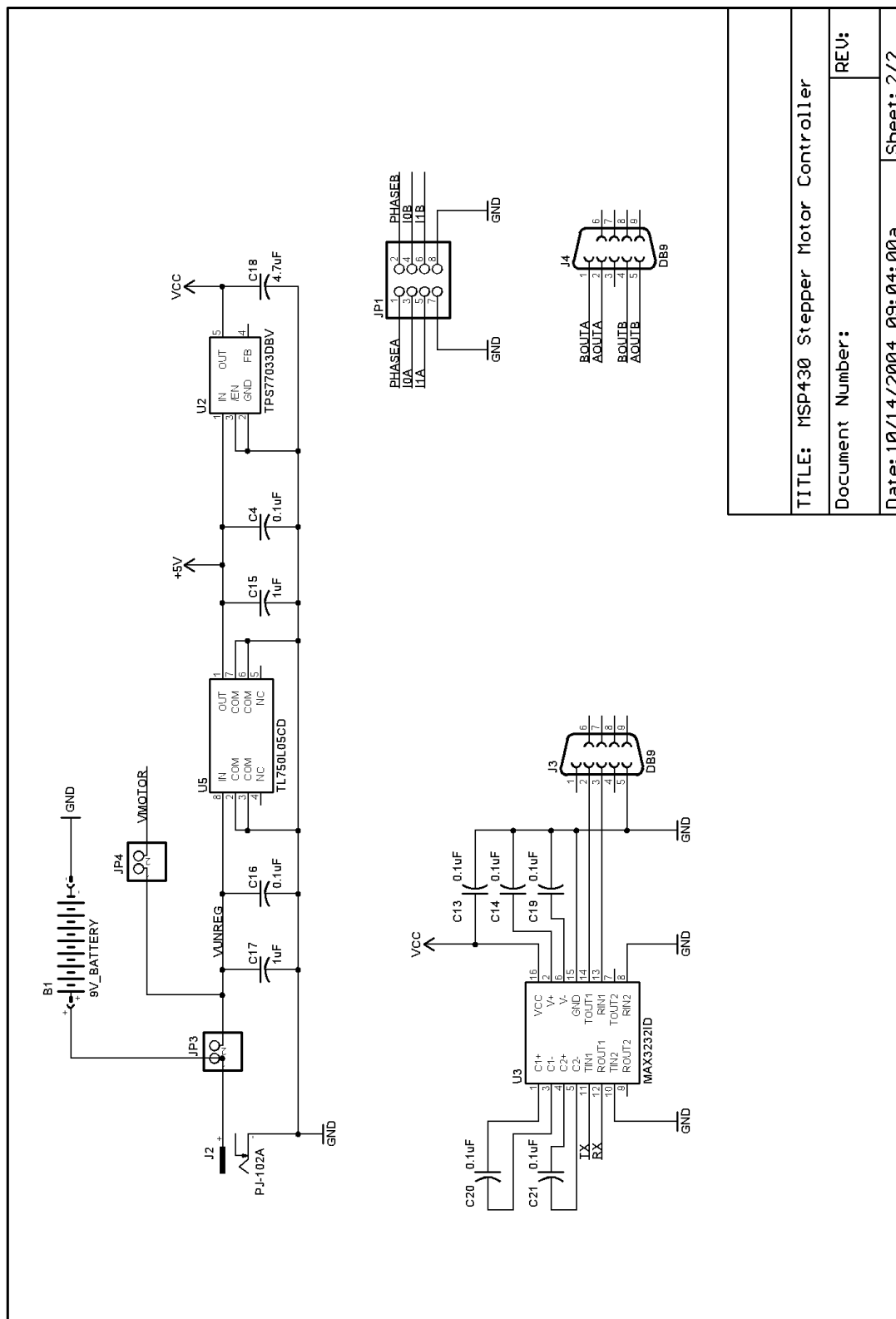


Figure 5. MSP430 Stepper Motor Schematic (2/2)

4 Bill of Materials

| REFERENCE DESIGNATOR | QTY | DESCRIPTION | MFG | MFG PART NUMBER |
|---|-----|---|---------------|-------------------|
| U1,U4 | 2 | Stepper Motor Drive Circuit | TI | UC3717AQ |
| U2 | 1 | 3.3 V, 50 mA low-dropout linear regulator | TI | TPS77033DBV |
| U3 | 1 | RS-232 Line Driver/Receiver | TI | MAX3232ID |
| U5 | 1 | 5.0 V, 150 mA low-dropout voltage regulator | TI | TL750L05CD |
| U6 | 1 | MSP430F123 | TI | MSP430F123IDW |
| S1,S2,S3,S4 | 4 | Momentary push button switch | Panasonic | EVQ11A04M |
| J1 | 1 | JTAG Connector | AMP | 103308-2 |
| J2 | 1 | DC Power Jack | CUI | PJ-102A |
| J3,J4 | 2 | Right-angle DB9 Connector | AMP | 747844-2 |
| B1 | 1 | 9 V Battery Holder | Keystone | 1294 |
| JP1 | 1 | 8-pin 0.100 Header | AMP | 87227-4 |
| JP3,JP4 | 2 | 2-pin 0.100 Header | AMP | 87227-1 |
| X1 | 1 | 32.768 kHz Crystal Oscillator | Epson | C-002RX32.7680K-A |
| R4,R8,R9,R10,R11, R12,R13 | 7 | 47K Ohm Resistor | Rohm | MCR18EZHJ473 |
| R3,R7,R15,R16 | 4 | 1.0 k Ω Resistor | Rohm | MCR18EZHJ102 |
| R1,R2,R5,R6 | 4 | 2.00 Ω Resistor 1/4W | Rohm | MCR18EZHFL2R00 |
| C3,C11 | 2 | 220 μ F, 35 V Capacitor | Panasonic | EEU-FC1V221 |
| C1,C4,C6,C7,C13, C14,C16,C19,C20,C21 | 10 | 0.1 μ F, 50 V Capacitor | Yageo America | 12062R104K9B20DF |
| C5 | 1 | 10 μ F, 16 V Capacitor | Kemet | T491B106K016AS |
| C15,C17 | 2 | 1 μ F, 25 V Capacitor | Panasonic | ECJ-3YB1E105K |
| C18 | 1 | 4.7 μ F, 25 V Capacitor | Panasonic | ECJ-3FF1E475Z |
| C2 | 1 | 0.01 μ F, 50 V Capacitor | Kemet | C1206C103K5RACTU |
| C8,C9,C10,C12 | 4 | 1000 pF, 50 V Capacitor | Yageo America | 1206CG102J9B200 |
| D1,D2 | 2 | LED, Red 1206 SMD | Lite-On | LTST-C150KRKT |

5 References

1. *Unitrode UC3717A Stepper Motor Drive Circuit Data Sheet* (uc3717a.pdf)
2. *MSP430x12x Mixed Signal Controller Data Sheet* ([SLAS312](#))
3. *MSP430x1xx Family User's Guide* ([SLAU049](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

| Products | | Applications | |
|------------------|--|---------------------|--|
| Amplifiers | amplifier.ti.com | Audio | www.ti.com/audio |
| Data Converters | dataconverter.ti.com | Automotive | www.ti.com/automotive |
| DSP | dsp.ti.com | Broadband | www.ti.com/broadband |
| Interface | interface.ti.com | Digital Control | www.ti.com/digitalcontrol |
| Logic | logic.ti.com | Military | www.ti.com/military |
| Power Mgmt | power.ti.com | Optical Networking | www.ti.com/opticalnetwork |
| Microcontrollers | microcontroller.ti.com | Security | www.ti.com/security |
| | | Telephony | www.ti.com/telephony |
| | | Video & Imaging | www.ti.com/video |
| | | Wireless | www.ti.com/wireless |

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2005, Texas Instruments Incorporated