

3.2 W LED power supply based on HVLED805


Introduction

This application note describes the demonstration board of the all-primary sensing switching regulator HVLED805 and presents the results of its bench evaluation. The board implements a 3.2 W (16 V / 0.2 A) wide range mains LED power supply with constant current.

HVLED805 combines a high-performance low-voltage PWM controller chip and an 800 V avalanche rugged power MOSFET in the same package. The PWM chip is a quasi-resonant (QR) current mode controller IC specifically designed for QR ZVS (zero voltage switching at switch turn-on) flyback converters. The device provides constant output current (CC) regulation using primary sensing feedback. This eliminates the need for the optocoupler, the secondary voltage reference, and also the current sensor, while still maintaining quite accurate regulation. The device can provide a constant output voltage regulation (CV). This makes the application able to work safely when the LED string opens due to a failure.

However, an auxiliary winding is required in the transformer to correctly perform CV/CC regulation, the chip is able to power itself directly from the rectified mains. This is useful during CC regulation, where the flyback voltage generated by the winding drops.

Figure 1. STEVAL-ILL037V1 demonstration board image

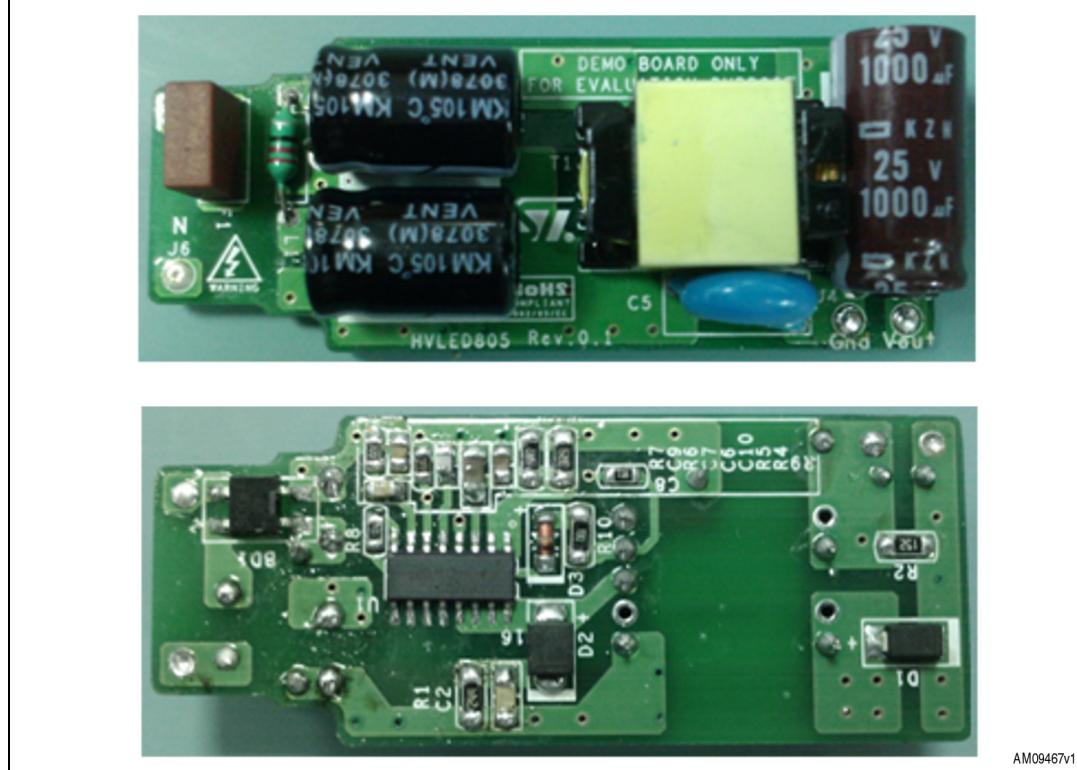

Contents

1	Test board design and evaluation	4
2	Transformer specification	8
3	Efficiency measurements	9
4	Typical board waveforms	10
5	Conclusion	13
6	References	14
7	Revision history	15

List of figures

Figure 1.	STEVAL-ILL037V1 demonstration board image	1
Figure 2.	For E26/E27 application	4
Figure 3.	Electrical schematic	5
Figure 4.	PCB top side and through hole components	7
Figure 5.	PCB bottom side and SMD components	7
Figure 6.	EEE13-11 vertical type for under 10 W	8
Figure 7.	Output characteristics	9
Figure 8.	Normal operation at full load - at 115 V _{AC}	10
Figure 9.	Normal operation at full load - at 230 V _{AC}	10
Figure 10.	Normal operation at no load - at 115 V _{AC}	11
Figure 11.	Normal operation at no load - at 230 V _{AC}	11
Figure 12.	Short-circuit at 115 V _{AC}	11
Figure 13.	Short-circuit at 230 V _{AC}	11
Figure 14.	Startup at full load at 115 V _{AC}	12
Figure 15.	Startup at full load at 230 V _{AC}	12

1 Test board design and evaluation

As a reference design, a 3.2 W LED power supply based on HVLED805 is presented.


- [Table 1](#) summarizes the electrical specifications of the application
- [Table 2](#) provides the bill of material
- [Table 4](#) lists transformer specifications

The electrical schematic is shown in [Figure 3](#) and the PCB layout in [Figure 4](#). and [5](#).

Table 1. STEVAL-ILL037V1 demonstration board: electrical specifications


Parameter	Value
Input voltage range (V_{IN})	90 - 265 V _{AC}
Mains frequency (f_L)	50 - 60 Hz
Output power consumption	3.2 W
Output voltage	16 V _{DC} (3~5 LEDs)
Output current	200 mA
Target average efficiency	>70%

Figure 2. For E26/E27 application

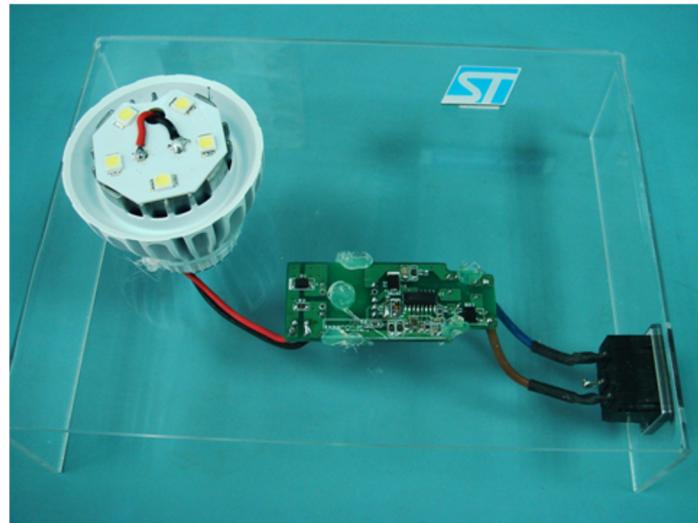

AM09468v1



Figure 3. Electrical schematic

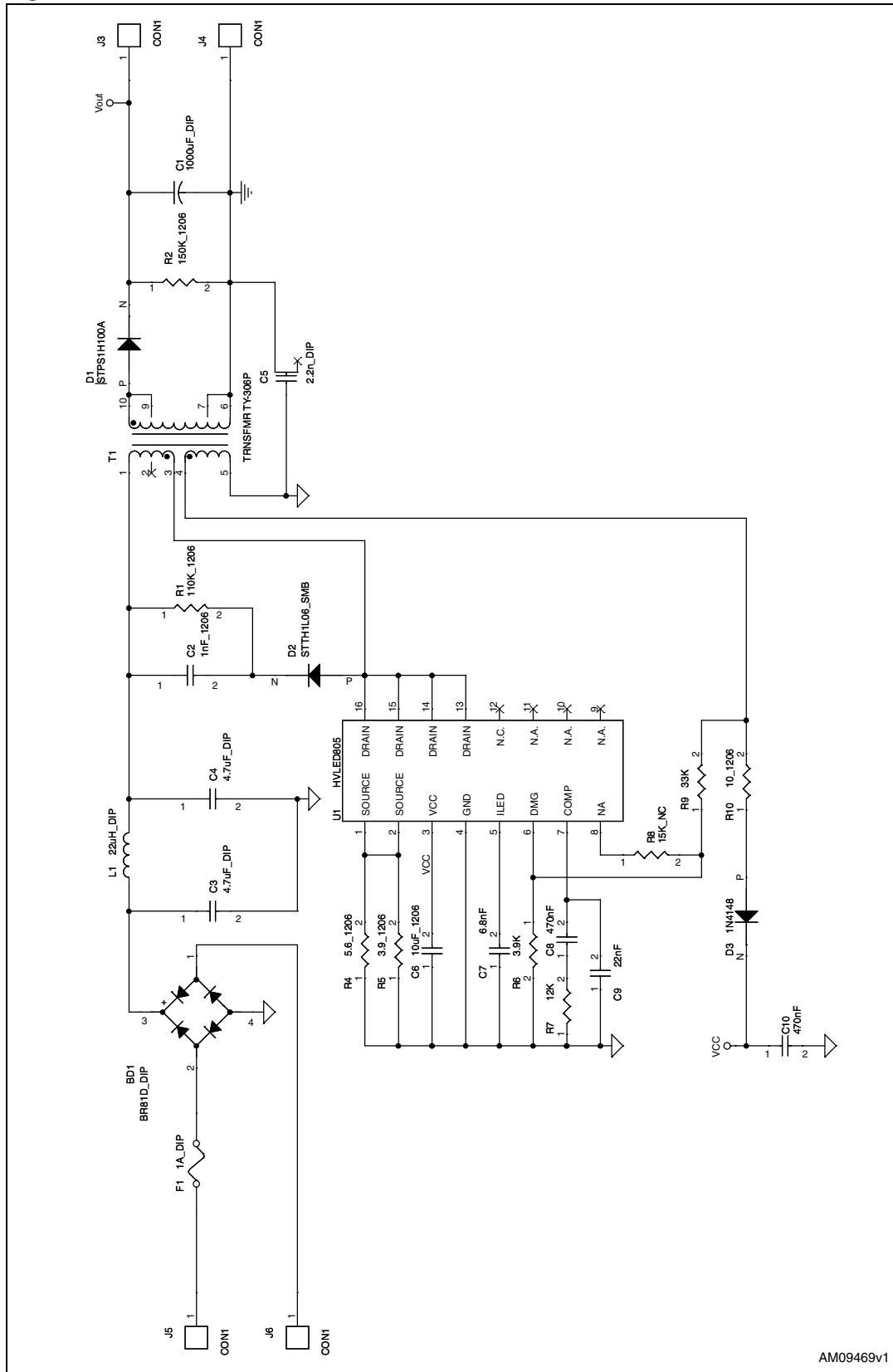

AM09469v1

Table 2. STEVAL-ILL037V1 demonstration board bill of material

Reference	Part	Note
BD1	BR81D	
C1	1000 μ F_DIP	
C2	1 nF_1206	
C3,C4	4.7 μ F_DIP	
C5	2.2 nF_DIP	
C6	22 μ F_1206	X5R
C7	6.8 nF	X7R
C8	470 nF	X7R
C9	22 nF	X7R
C10	470 nF	X7R
D1	STPS1H100U	STMicroelectronics
D2	STTH1L06_SMB	STMicroelectronics
D3	1N4148	CHENMKO
F1	1A_DIP	
L1	22 μ H_DIP	
R1	110 k Ω _1206	5%
R2	150 k Ω _1206	5%
R4	5.6 Ω _1206	1%
R5	3.9 Ω _1206	1%
R6	3.9 k Ω	1%
R7	12 k Ω	1%
R8	NC	
R9	33 k Ω	1%
R10	10 Ω _1206	5%
T1	QEE13	Yu-Jing
U1	HVLED805	STMicroelectronics

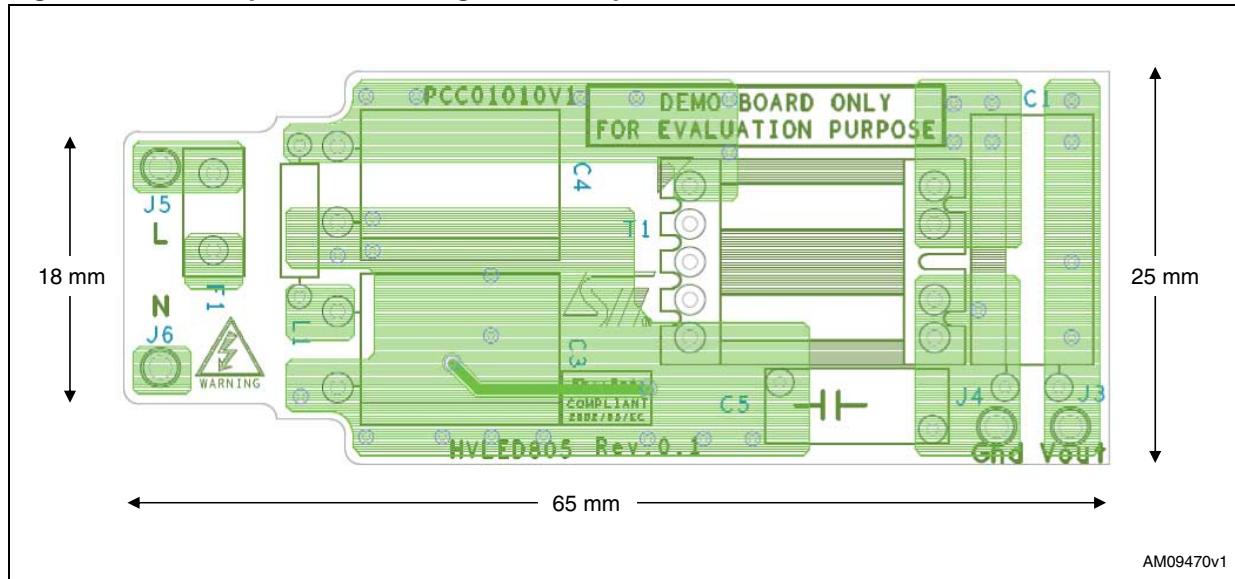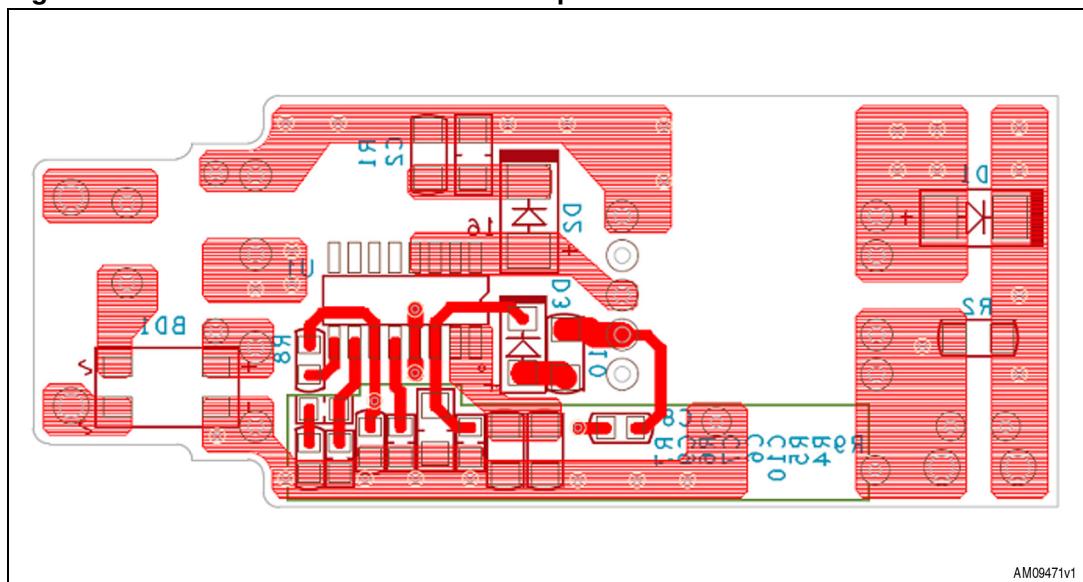Figure 4. PCB top side and through hole components**Figure 5.** PCB bottom side and SMD components

2 Transformer specification

Figure 6. EEE13-11 vertical type for under 10 W

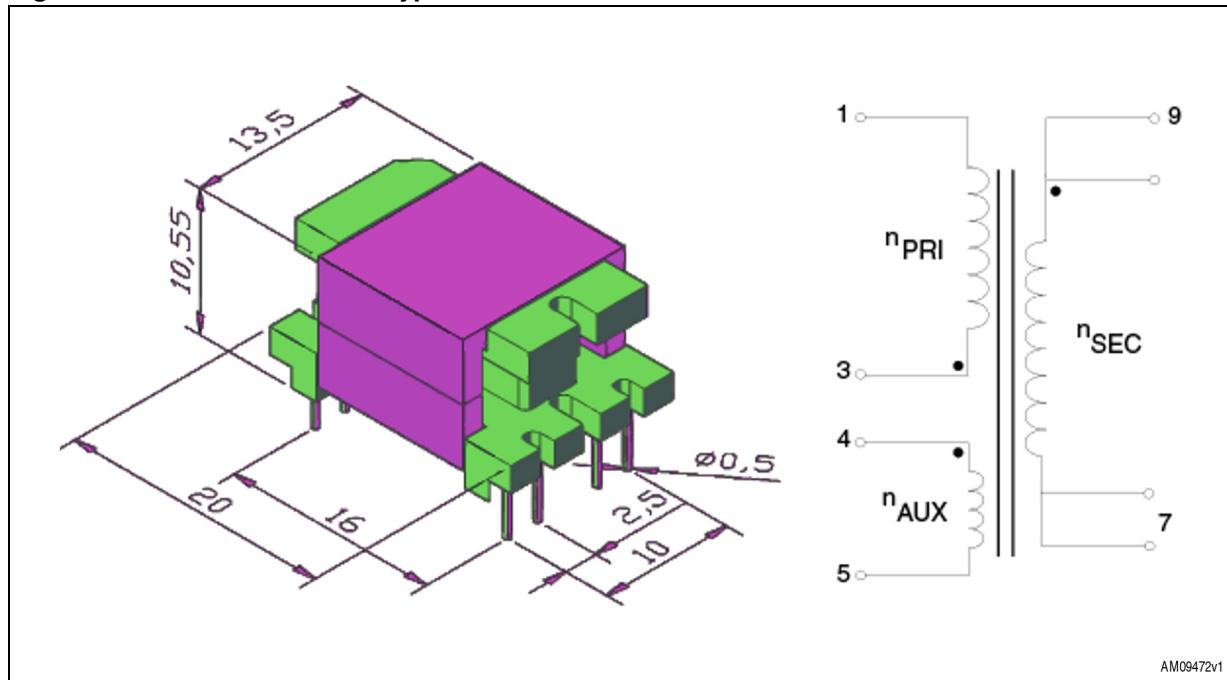


Table 3. Transformer specification

Core spec-EEE13							
Ae	36.7 mm ²		Le	27 mm	AW	2.5 mm*4.8 mm	
Wiring spec. for flyback 16 V output							
No.	Start	Finish	Wire	Winding	Turns	Inductance	LK inductance
L1	3	1	0.2 Φ*1C	Primary	72	1.9 mH±10%	31 µH ref.
L2	9	7	0.35 Φ*1C	Secondary	15	96 µH±10%	
L3	4	5	0.2 Φ*1C	AUX	20	85 µH ref.	

Note: Class B insulation system: SB14.2

- With standing voltage:
 - 1.0 kV/1 sec/AC/5 mA, primary to secondary
 - 0.5 kV/1 sec/AC/3 mA, primary to core
 - 1.0 kV/1 sec/AC/3 mA, secondary to core
- Manufacturer:
 - Yu-Jing Technology Co., LTD www.yujingtech.com.tw
 - Inductor P/N: 11999-310V600110 (EEE13-11V)

3 Efficiency measurements

The efficiency of the converter has been measured in different load and line voltage conditions.

The efficiency measurements have been done at 12 to 16 V_{DC} of the rated output power, at both 115 V_{AC} and 230 V_{AC}.

Table 4 and *5* show the results.


Table 4. Efficiency at 115 V_{AC}

V _{AC}	P _{in} (W)	V _{out} (V)	I _{out} (mA)	Eff (%)
115	2.972	12.016	196.00	79.24
	3.190	13.008	196.00	79.92
	3.420	14.016	196.00	80.33
	3.644	15.008	195.00	80.31
	3.877	16.016	195.00	80.56
Average eff. (%)				80.07

Table 5. Efficiency at 230 V_{AC}

V _{AC}	P _{in} (W)	V _{out} (V)	I _{out} (mA)	Eff (%)
230	3.238	12.016	195.00	72.36
	3.500	13.008	200.00	74.33
	3.792	14.016	204.00	75.40
	4.050	15.008	204.00	75.60
	4.262	16.016	204.00	76.66
Average eff. (%)				74.87

Figure 7. Output characteristics

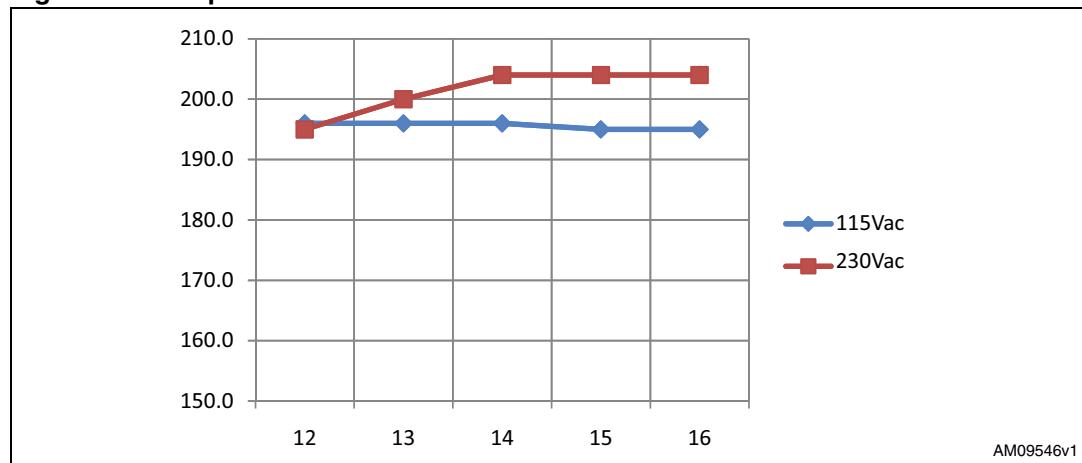

4 Typical board waveforms

Drain voltage and current waveforms were reported for the two nominal input voltages and for the minimum and the maximum voltage of the converter input operating range. [Figure 8](#) and [9](#) show the drain current and the drain voltage waveforms at the nominal input voltages and full load.

At low load OC enters into burst mode, reducing the switching frequency down to a minimum fixed value; [Figure 10](#) and [11](#) show the typical waveforms during no load conditions at both 115 V_{AC} and 230 V_{AC} circuits at nominal input voltage.

The CC mode technique eliminates the need for overload protection; in fact, the maximum output power is achieved on the corner point between CV mode and CC mode and coincides with the full load condition. [Figure 12](#) and [13](#) show the typical waveforms during short-circuit at nominal input voltage.

[Figure 14](#) and [15](#) show the startup in full load conditions and nominal input voltage; the maximum drain-source voltage is well below the BVDSS of the IC.

Figure 8. Normal operation at full load - at 115 V_{AC}

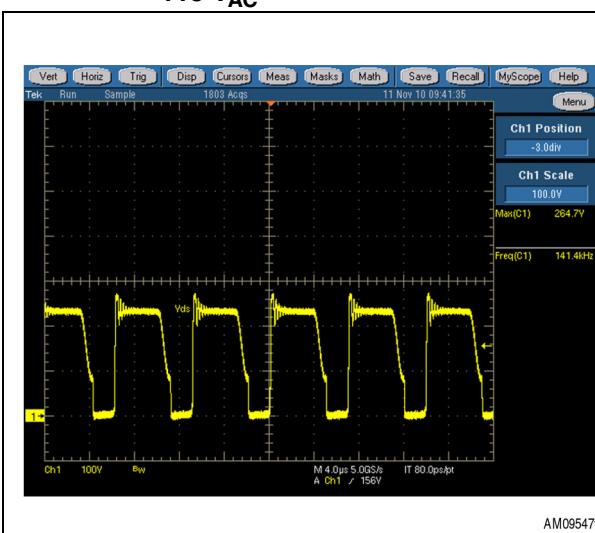


Figure 9. Normal operation at full load - at 230 V_{AC}

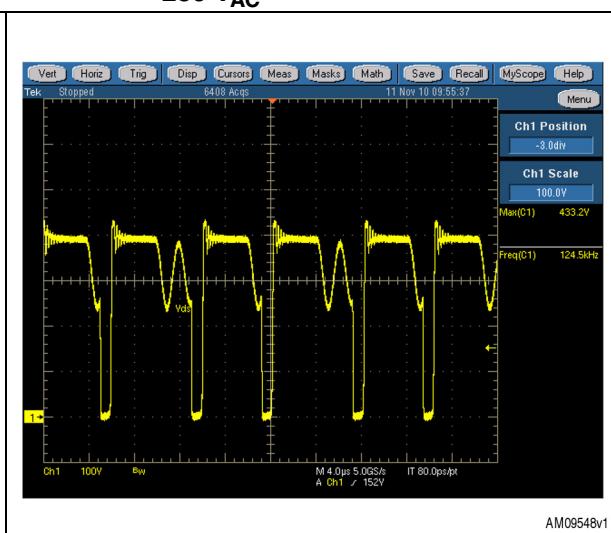


Figure 10. Normal operation at no load - at 115 V_{AC}

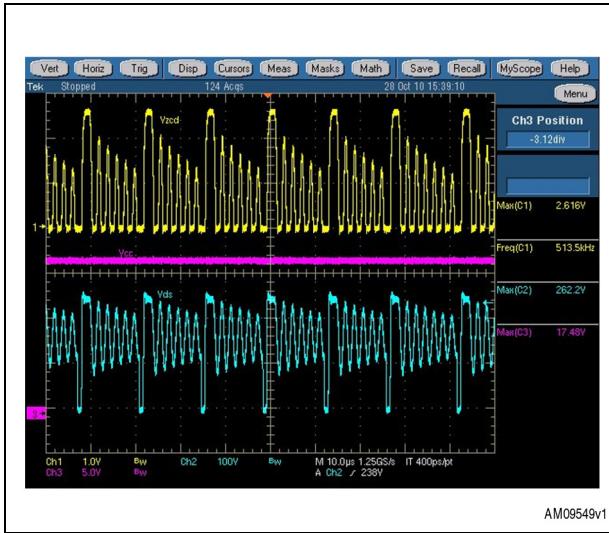


Figure 11. Normal operation at no load - at 230 V_{AC}

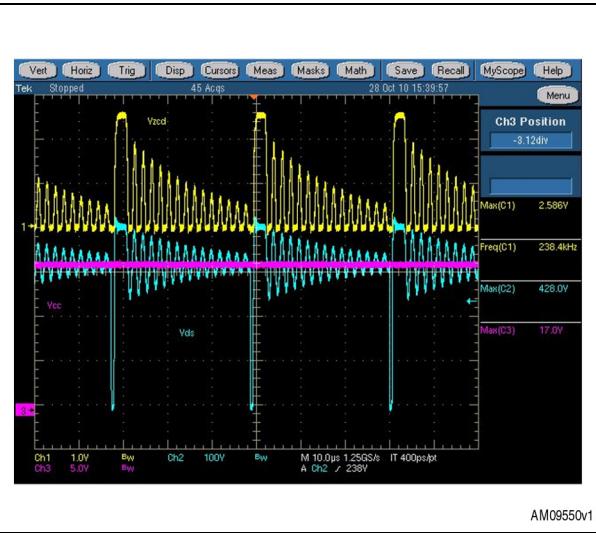


Figure 12. Short-circuit at 115 V_{AC}

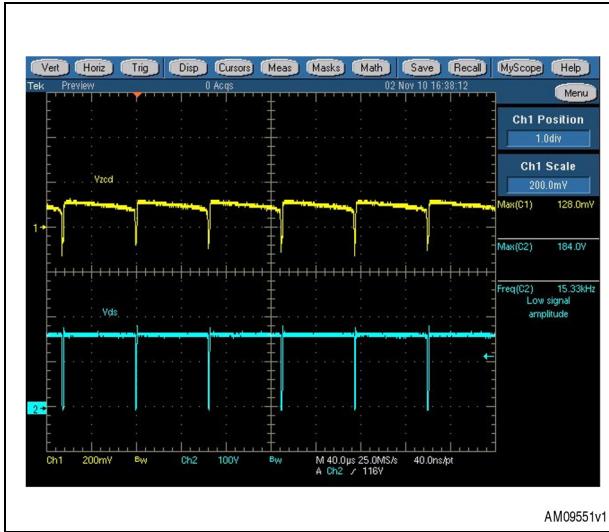


Figure 13. Short-circuit at 230 V_{AC}

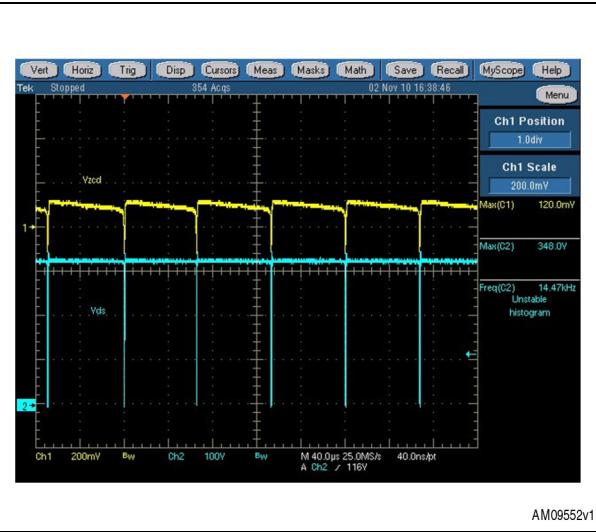
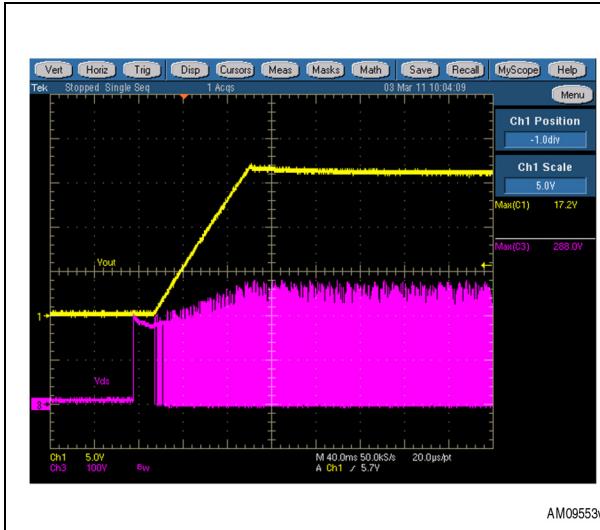


Figure 14. Startup at full load at 115 V_{AC}Figure 15. Startup at full load at 230 V_{AC}

5 Conclusion

The LED power supply demonstration board using the HVLED805 device was presented and the results show that good performances can be obtained using this new device.

Auxiliary winding is required in the transformer to correctly perform CV/CC regulation, and the chip is able to power itself directly from the rectified mains. This is particularly useful during CC regulation, where the flyback voltage generated by the winding drops.

The HVLED805 is able to meet the most restrictive worldwide standards regarding efficiency. The embedded onboard protections and the 800 V power section considerably increase the end-product safety and reliability.

6 References

1. HVLED805 datasheet
2. AN3093 application note

7 Revision history

Table 6. Document revision history

Date	Revision	Changes
30-Mar-2011	1	Initial release.
21-Jul-2011	2	<ul style="list-style-type: none">– Updated Figure 3.– Updated component D1 in Table 2.

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY TWO AUTHORIZED ST REPRESENTATIVES, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2011 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com