

# EVAL-2HS01G-300W

300W LLC Evaluation Board with LLC  
controller ICE2HS01G

Power Management & Supply



N e v e r   s t o p   t h i n k i n g .

**Edition 2012-05-07**

**Published by Infineon Technologies Asia Pacific,  
168 Kallang Way,  
349253 Singapore, Singapore**

**© Infineon Technologies AP 2010.  
All Rights Reserved.**

**Attention please!**

The information herein is given to describe certain components and shall not be considered as a guarantee of characteristics.

Terms of delivery and rights to technical change reserved.

We hereby disclaim any and all warranties, including but not limited to warranties of non-infringement, regarding circuits, descriptions and charts stated herein.

**Information**

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office ([www.infineon.com](http://www.infineon.com)).

**Warnings**

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

---

**EVAL2HS01G300W****Revision History:**                      **2012-05****V2.0****Previous Version:**                      **NA**

|  |  |
|--|--|
|  |  |
|  |  |
|  |  |
|  |  |
|  |  |
|  |  |
|  |  |
|  |  |
|  |  |

300W LLC Evaluation Board with LLC controller ICE2HS01G

License to Infineon Technologies Asia Pacific Pte Ltd

**A N - P S 0 0 6 0****Li Dong****Ke Chunshan**

---

## Table of Content

|           |                                              |           |
|-----------|----------------------------------------------|-----------|
| <b>1</b>  | <b>Introduction.....</b>                     | <b>5</b>  |
| <b>2</b>  | <b>Evaluation Board .....</b>                | <b>5</b>  |
|           | <b>Technical Specifications.....</b>         | <b>5</b>  |
| <b>3</b>  | <b>Control Circuit Diagram .....</b>         | <b>6</b>  |
| <b>4</b>  | <b>Power Circuit Diagram .....</b>           | <b>7</b>  |
| <b>5</b>  | <b>PCB Layout – Top.....</b>                 | <b>8</b>  |
| <b>6</b>  | <b>PCB Layout – Bottom.....</b>              | <b>8</b>  |
| <b>7</b>  | <b>Component List .....</b>                  | <b>9</b>  |
| <b>8</b>  | <b>Magnetic components.....</b>              | <b>11</b> |
| 8.1       | Main transformer .....                       | 11        |
| 8.2       | Resonant choke .....                         | 12        |
| 8.3       | Pulse transformer .....                      | 13        |
| <b>9</b>  | <b>Efficiency Test .....</b>                 | <b>14</b> |
| <b>10</b> | <b>Test Waveforms .....</b>                  | <b>14</b> |
| 10.1      | Soft start at full load and light load ..... | 14        |
| 10.2      | Burst mode operation at no load.....         | 16        |
| 10.3      | SR soft start at full load.....              | 16        |
| 10.4      | Zero Voltage Switching .....                 | 17        |
| 10.5      | Main under voltage protection.....           | 18        |
| 10.6      | Dynamic load response.....                   | 19        |
| 10.7      | Hold up time test .....                      | 20        |




## 1 Introduction

The evaluation board presented is a 300W LLC Converter with 400VDC input and 12V output. It is controlled by Infineon's 2nd generation half-bridge LLC controller ICE2HS01G. The ICE2HS01G is designed especially for high efficiency application with its synchronous rectification (SR) control for the secondary side. With its new driving techniques, SR can be realized for half-bridge LLC converter operated with secondary switching current in both CCM and DCM conditions.

In this application note, the schematic circuit, PCB layout and BOM for the evaluation board are shared, followed by the performance of the board, such as the efficiency and operation waveforms. For the detailed step-by-step design procedure of this converter, please refer to our design guide.


## 2 Evaluation Board

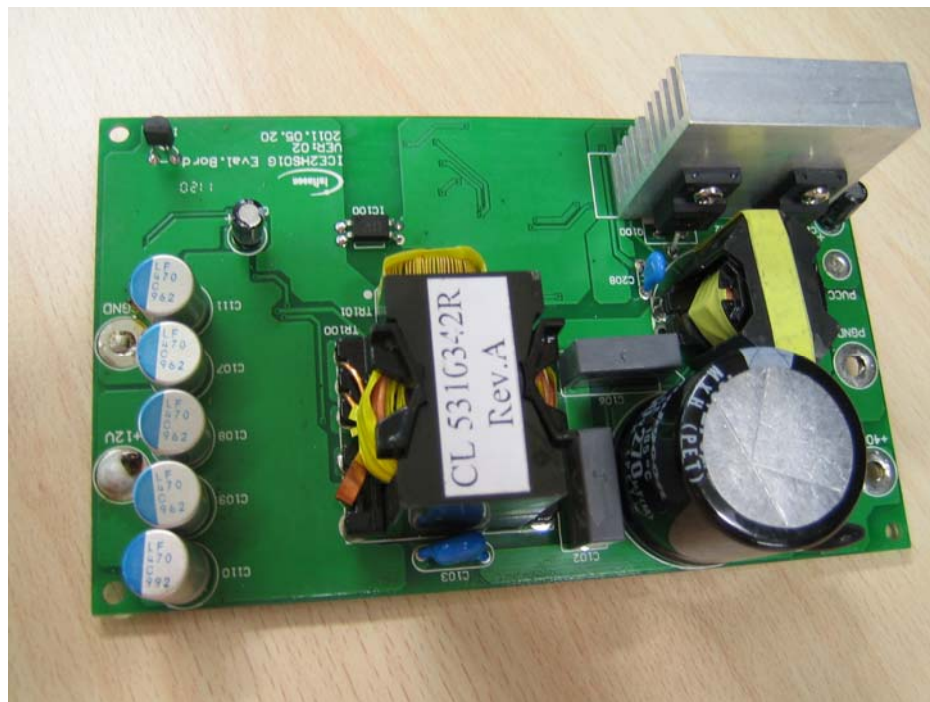


### Technical Specifications

|                                       |                                                           |
|---------------------------------------|-----------------------------------------------------------|
| Input voltage $V_{in}$                | 400VDC                                                    |
| Output voltage and current $V_o, I_o$ | 12VDC, 25A                                                |
| Output power $P_{in}$                 | ~ 300W                                                    |
| Efficiency $\eta$                     | >97% at 100% load<br>>97% at 50% load<br>~96% at 20% load |
| Resonant frequency $f_r$              | 85kHz                                                     |

### 3 Control Circuit Diagram

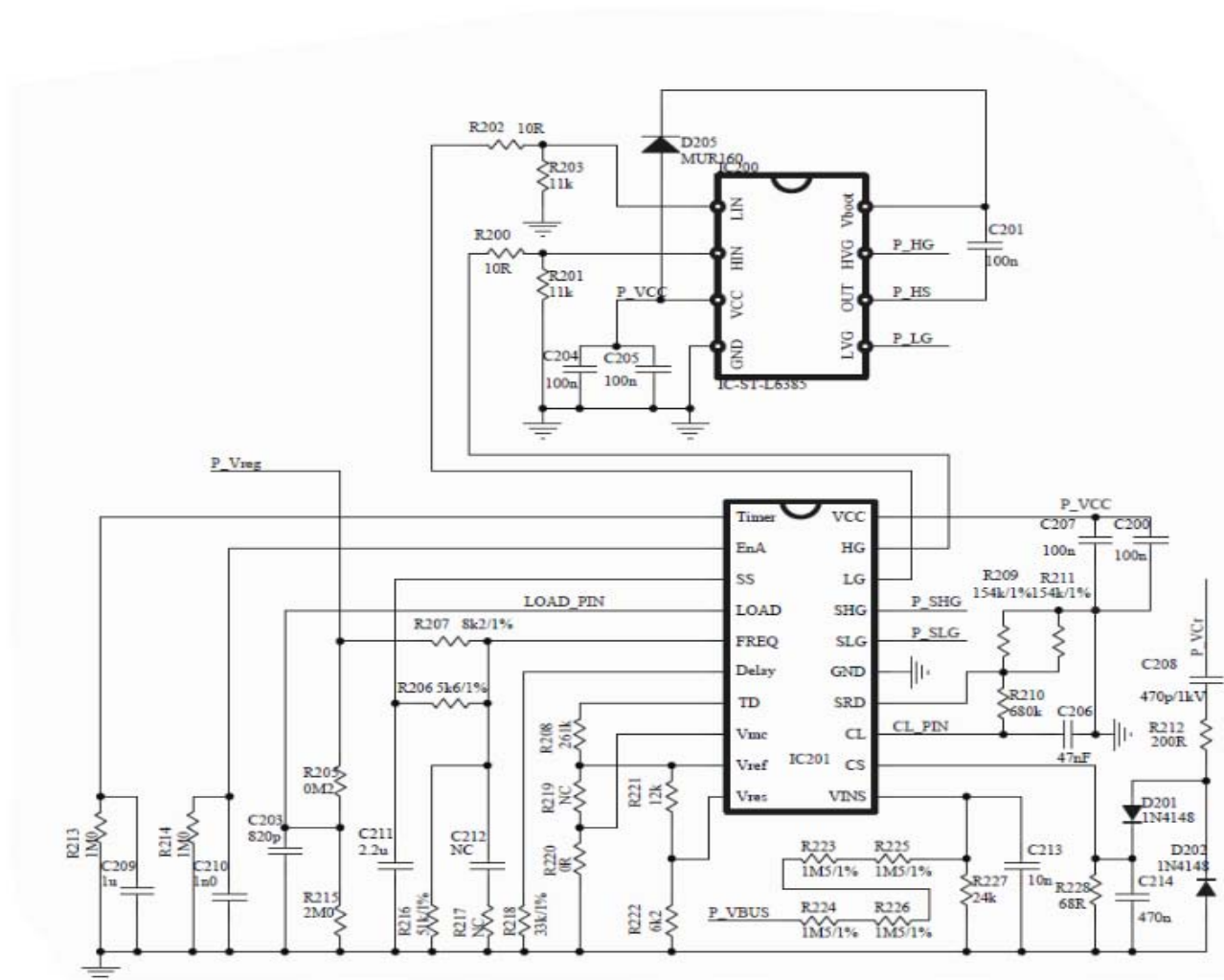

## 4 Power Circuit Diagram

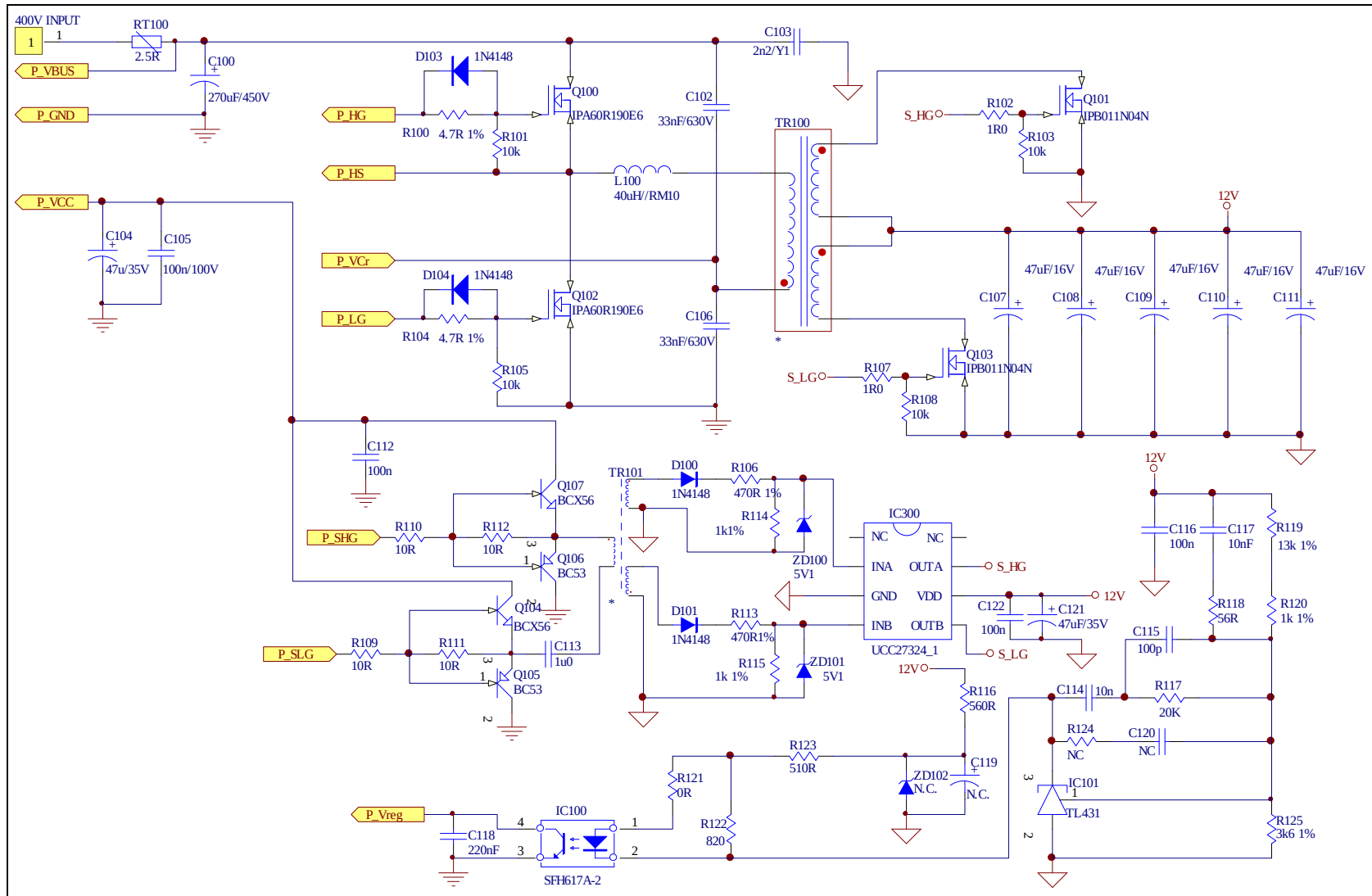





## 7 Component List

| Designator                               | Description  | Footprint    | Description          | Quantity |
|------------------------------------------|--------------|--------------|----------------------|----------|
| PCB                                      | Double Layer |              | 2 ounce copper       | 1        |
| C100                                     | 270uF/450V   | RB30         | Aluminum Electrolyte | 1        |
| C102,<br>C106                            | 33nF/630V    | MKT6/13/10   | CERAMIC              | 2        |
| C103                                     | 2n2/Y1       | CY10         | CERAMIC              | 1        |
| C104                                     | 47u/35V      | RB6.5        | Aluminum Electrolyte | 1        |
| C105                                     | 100n/100V    | 1206C        | CERAMIC              | 1        |
| C107,<br>C108,<br>C109,<br>C110,<br>C111 | 47uF/16V     | RB10         | Aluminum Electrolyte | 5        |
| C112,<br>C116                            | 100n         | 1206C        | CERAMIC              | 2        |
| C113                                     | 1u0          | 1206C        | CERAMIC              | 1        |
| C114                                     | 47n          | 1206C        | CERAMIC              | 1        |
| C115                                     | 100p         | 1206C        | CERAMIC              | 1        |
| C117,<br>C118                            | 10nF         | 1206C        | CERAMIC              | 2        |
| C119                                     | 1u           | 1206C        | Aluminum Electrolyte | 1        |
| C120                                     | NC           | 1206C        |                      | 0        |
| C121                                     | 47uF/35V     | RB6.5        | Aluminum Electrolyte | 1        |
| C122,<br>C200,<br>C205                   | 100n         | MKT2/7/5     | CERAMIC              | 3        |
| C201,<br>C204,<br>C207                   | 100n         | MKT2/7/5_0M8 | CERAMIC              | 3        |
| C203                                     | 820p         | MKT2/7/5     | CERAMIC              | 1        |
| C206                                     | 47nF         | 0805C        | CERAMIC              | 1        |
| C208                                     | 220p/1kv     | MKT2/7/5     | CERAMIC              | 1        |
| C209                                     | 1u           | 0805C        | CERAMIC              | 1        |
| C210                                     | 1n0          | 0805C        | CERAMIC              | 1        |
| C211                                     | 2.2u         | 0805C        | CERAMIC              | 1        |
| C212                                     | NC           | 0805C        | CERAMIC              | 1        |
| C213                                     | 10n          | 0805C        | CERAMIC              | 1        |
| C214                                     | 220n         | 0805C        | CERAMIC              | 1        |
| D100,<br>D101,<br>D201,<br>D202          | 1N4148       | 1206D        | DIODE                | 4        |
| IC100                                    | SFH617A-2    | DIP4/10      | OPTO COUPLER         | 1        |
| IC101                                    | TL431        | TO92-CBE     |                      | 1        |
| IC200                                    | IC-ST-L6385  | SO-8         | Half-bridge driver   | 1        |

|                                          |             |        |                             |   |
|------------------------------------------|-------------|--------|-----------------------------|---|
| IC201                                    | ICE2HS01G   | SOL-20 |                             | 1 |
| IC300                                    | UCC27324_1  | SO-8   | Resonant-Mode<br>Controller | 1 |
| L100                                     | 40uH//RM10  | RM10   | CHOKE                       | 1 |
| Q100,<br>Q102                            | IPA60R199C6 | T0-220 | MOSFET                      | 2 |
| Q101,<br>Q103                            | IPB011N04N  | TO-263 | MOSFET                      | 2 |
| Q104,<br>Q107                            | BCX56       | SOT-89 | NPN Transistor              | 2 |
| Q105,<br>Q106                            | BC53        | SOT-89 | PNP Transistor              | 2 |
| R100,<br>R104,<br>R109,<br>R111,<br>R112 | 10R         | 1206R  | RESISTOR                    | 5 |
| R101,<br>R103,<br>R105,<br>R108          | 10k         | 1206R  | RESISTOR                    | 4 |
| R102,<br>R107                            | 1R0         | 1206R  | RESISTOR                    | 2 |
| R106,<br>R113                            | 2k0         | 1206R  | RESISTOR                    | 2 |
| R110                                     | 10R         | 1206   | RESISTOR                    | 1 |
| R114,<br>R115                            | 4k7         | 1206R  | RESISTOR                    | 2 |
| R116                                     | 560         | 1206R  | RESISTOR                    | 1 |
| R117                                     | 3k9         | 1206R  | RESISTOR                    | 1 |
| R118                                     | 56R         | 1206R  | RESISTOR                    | 1 |
| R119                                     | 11k         | 1206R  | RESISTOR                    | 1 |
| R120                                     | 2k7         | 1206R  | RESISTOR                    | 1 |
| R121                                     | 0R          | 1206R  | RESISTOR                    | 1 |
| R122                                     | 820         | 1206R  | RESISTOR                    | 1 |
| R123                                     | 2k2         | 1206R  | RESISTOR                    | 1 |
| R124                                     | NC          | 1206R  | RESISTOR                    | 1 |
| R125                                     | 3k6         | 1206R  | RESISTOR                    | 1 |
| R200,<br>R202                            | 10R         | 0805r  | RESISTOR                    | 2 |
| R201,<br>R203                            | 11k         | 0805r  | RESISTOR                    | 2 |
| R205                                     | 0M2         | 0805r  | RESISTOR                    | 1 |
| R206                                     | 5k6/1%      | 0805r  | RESISTOR                    | 1 |
| R207                                     | 12k/0.1%    | 0805r  | RESISTOR                    | 1 |
| R208                                     | 240k        | 0805r  | RESISTOR                    | 1 |
| R209                                     | 150k/1%     | 0805r  | RESISTOR                    | 1 |
| R210                                     | 470k        | 0805r  | RESISTOR                    | 1 |

|                                 |         |             |                             |   |
|---------------------------------|---------|-------------|-----------------------------|---|
| R211                            | 110k/1% | 0805r       | RESISTOR                    | 1 |
| R212                            | 200R    | 1206R       | RESISTOR                    | 1 |
| R213,<br>R214                   | 1M0     | 0805r       | RESISTOR                    | 2 |
| R215                            | 2M0     | 0805r       | RESISTOR                    | 1 |
| R216                            | 24k/1%  | 0805r       | RESISTOR                    | 1 |
| R217                            | NC      | 0805r       | RESISTOR                    | 1 |
| R218                            | 51k/1%  | 0805r       | RESISTOR                    | 1 |
| R219                            | 100k    | 0805r       | RESISTOR                    | 1 |
| R220                            | 820R    | 0805r       | RESISTOR                    | 1 |
| R221                            | N.C.    | 0805r       | RESISTOR                    | 1 |
| R222                            | 0R      | 0805r       | RESISTOR                    | 1 |
| R223,<br>R224,<br>R225,<br>R226 | 1M5/1%  | 1206R       | RESISTOR                    | 4 |
| R227                            | 24k     | 0805R       | RESISTOR                    | 1 |
| R228                            | 62R     | 0805R       | RESISTOR                    | 1 |
| RT100                           | 2.5R    | NTC7.5      | NTC THERMISTOR              | 1 |
| TR100                           |         | PQ3230      | LLC Resonant<br>Transformer | 1 |
| TR101                           |         | WNP12048LM4 | Pulse Transformer           | 1 |
| ZD100,<br>ZD101                 | 5V1     | 1206D       | Zener Diode                 | 2 |
| ZD102                           | 9v1     | 1206D       | Zener Diode                 | 1 |

## 8 Specifications for Magnetic components



### 8.1 Main transformer

Core: PC95 PQ3230 (TDK)

Primary inductance  $L_p$ : 690uH $\pm$ 3% , between Pin 3 and Pin 4 (Gapped)

Leakage inductance: <2% of  $L_p$  with either Pin 7&11 shorted or Pin9&11 shorted

Teflon tube used for the pinout.

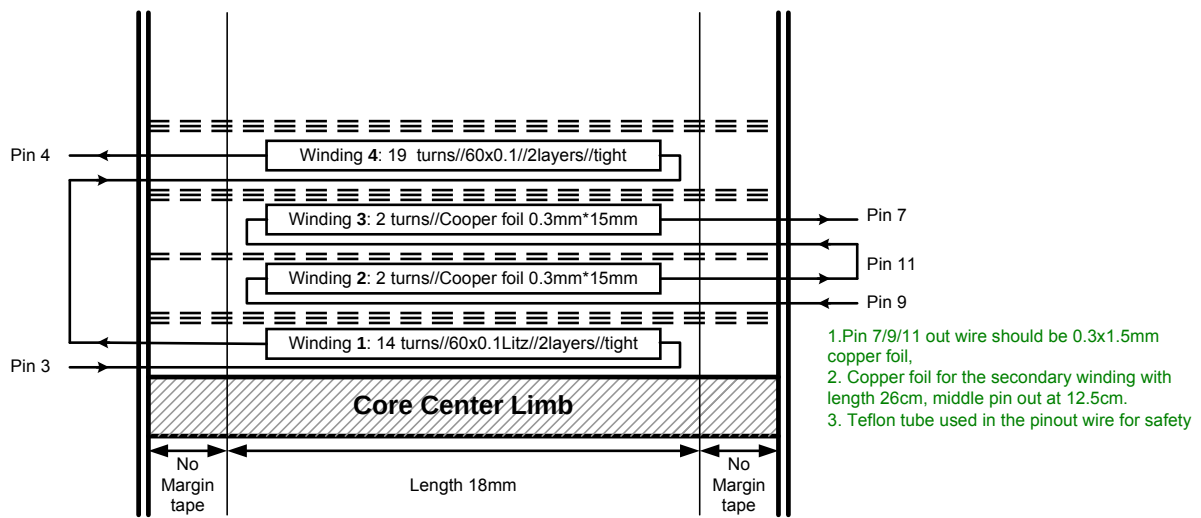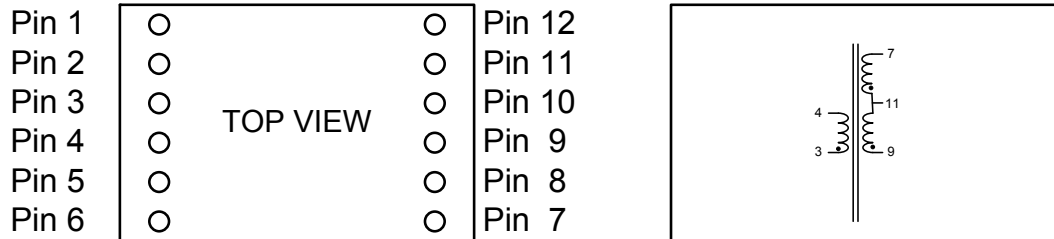


| Windings | Start | End   | Wire          | Turns | Layers | Method |
|----------|-------|-------|---------------|-------|--------|--------|
| 1        | 3     | float | 60x0.1mm Litz | 14    | 2      | Tight  |
| 2        | 9     | 11    | 0.3mm*15mm    | 2     | NA     | Tight  |
| 3        | 11    | 7     | 0.3mm*15mm    | 2     | NA     | Tight  |
| 4        | float | 4     | 60x0.1mm Litz | 19    | 2      | Tight  |

## 8.2 Resonant choke

Core: RM10

Material: N87

Inductance: L=40uH

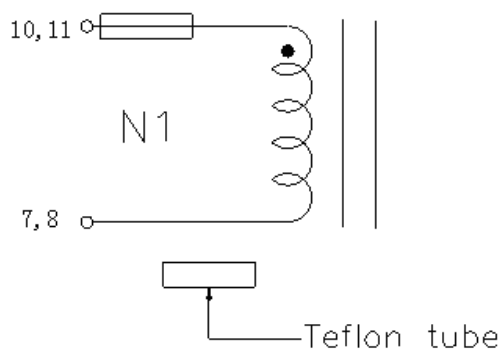


| Windings | Start-End   | Wire                            | Turns | Method |
|----------|-------------|---------------------------------|-------|--------|
| N1       | 10,11 — 7,8 | 2UEW, $\phi 0.10\text{mm}$ *50p | 44    | tight  |

### 8.3 Pulse transformer

Core: T14\*8\*7

Material: Ferrite


Inductance: 2.0mH Min ( no gap)

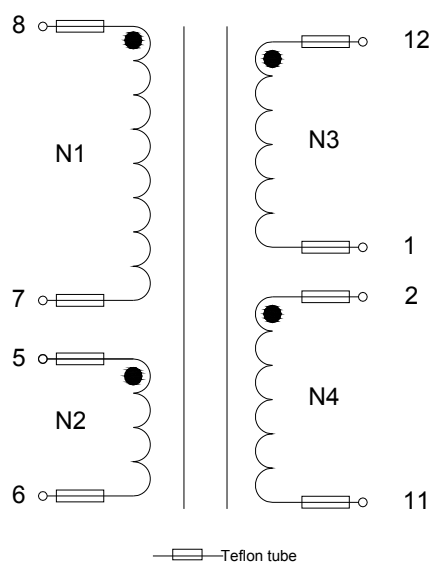

| Winding | Start | Finish | Wire                            | Turns(Ts) | Winding             |
|---------|-------|--------|---------------------------------|-----------|---------------------|
| N1      | 8     | 7      | TLW-B, $\phi 0.20\text{mm}$ *1P | 22TS      | 2 wires in parallel |
| N2      | 5     | 6      | TLW-B, $\phi 0.20\text{mm}$ *1P | 18TS      |                     |
| N3      | 12    | 1      | TLW-B, $\phi 0.20\text{mm}$ *1P | 15TS      |                     |
| N4      | 2     | 11     | TLW-B, $\phi 0.20\text{mm}$ *1P | 15TS      |                     |

## 9 Efficiency Test

| V <sub>out</sub> (V) | I <sub>out</sub> (A) | P <sub>out</sub> (W) | Load(%) | V <sub>in</sub> (V) | I <sub>in</sub> (A) | P <sub>in</sub> (W) | V <sub>cc</sub> (V) | I <sub>vcc</sub> (A) | P <sub>vcc</sub> (W) | Eff.(%) |
|----------------------|----------------------|----------------------|---------|---------------------|---------------------|---------------------|---------------------|----------------------|----------------------|---------|
| 12.17                | 1.25                 | 15.21                | 5%      | 399.99              | 0.04                | 17.06               | 15.00               | 0.03                 | 0.375                | 87.2    |
| 12.17                | 2.49                 | 30.31                | 10%     | 399.89              | 0.08                | 32.17               | 15.00               | 0.03                 | 0.375                | 93.1    |
| 12.17                | 4.98                 | 60.59                | 20%     | 399.77              | 0.16                | 62.70               | 15.00               | 0.03                 | 0.375                | 96.1    |
| 12.16                | 12.41                | 150.95               | 50%     | 399.34              | 0.39                | 154.46              | 15.00               | 0.03                 | 0.375                | 97.5    |
| 12.16                | 24.87                | 302.42               | 101%    | 399.22              | 0.78                | 310.84              | 15.00               | 0.03                 | 0.375                | 97.2    |

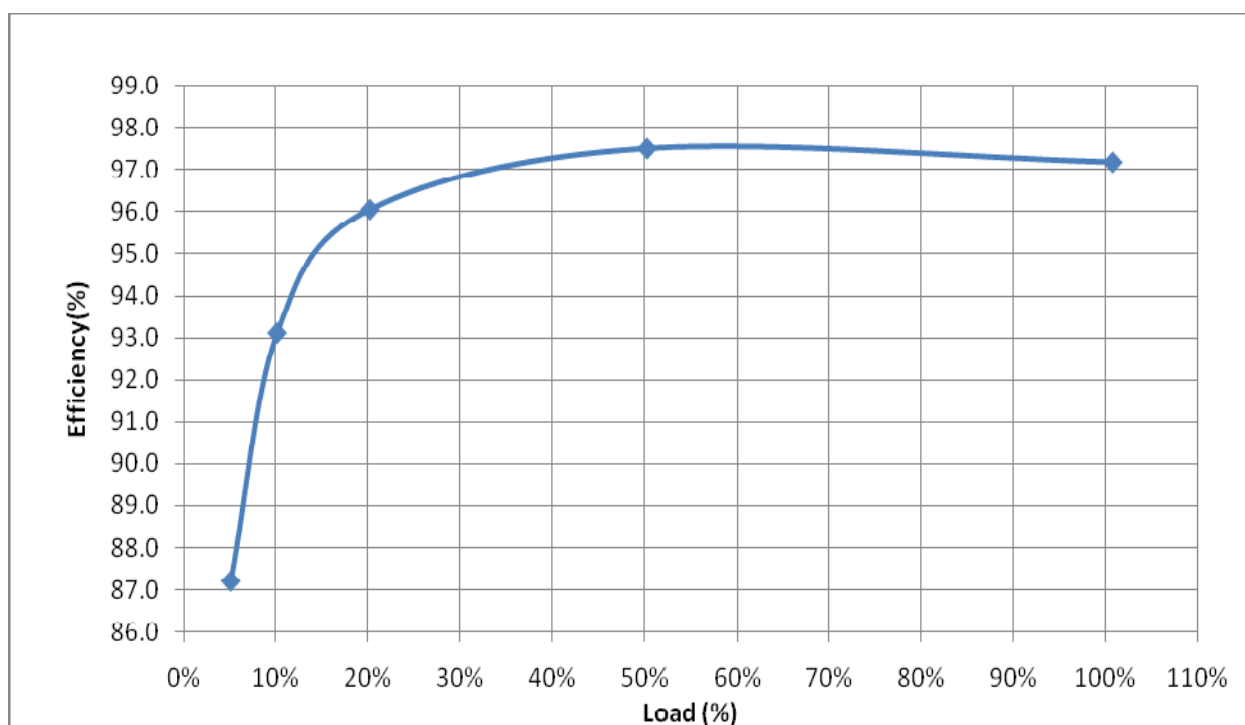


## 10 Test Waveforms

### 10.1 Soft start at full load and light load

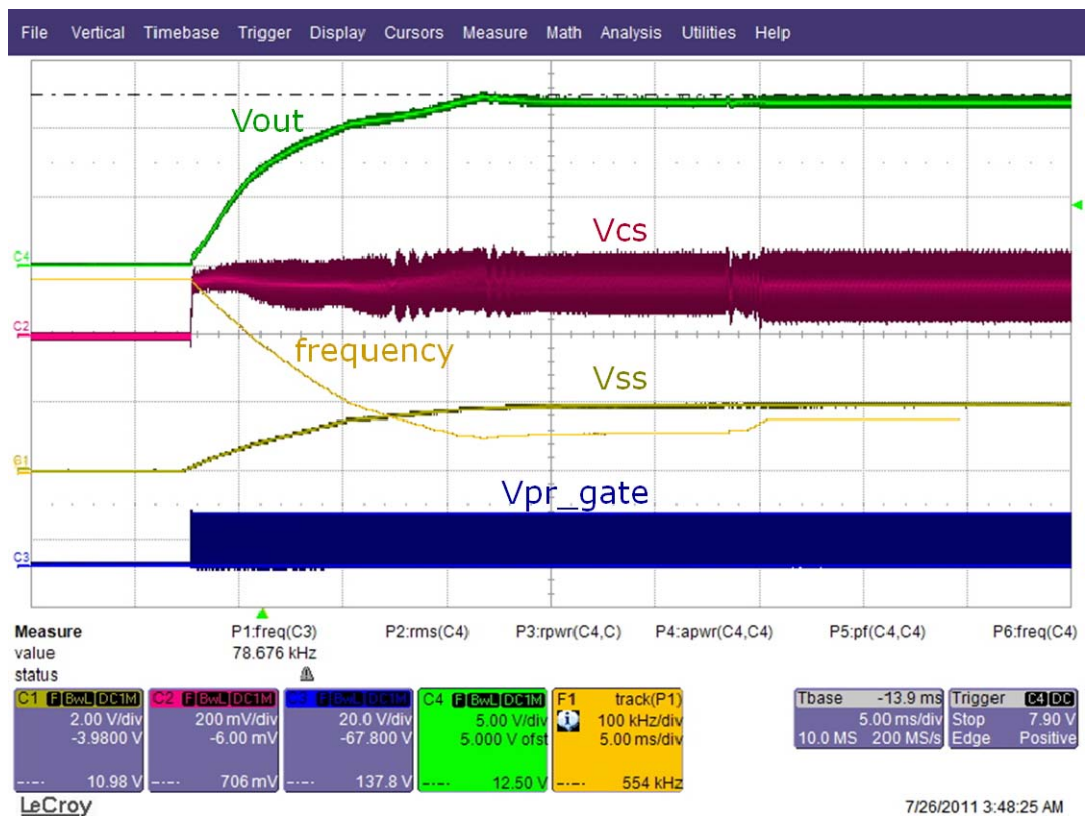
#### A. Full load

The output voltage rises up to nominal value in around 15ms. The overshoot is less than 5%. The soft start is achieved by decreasing the switching frequency gradually from 280 KHz to 80kHz until stable operation is reached.



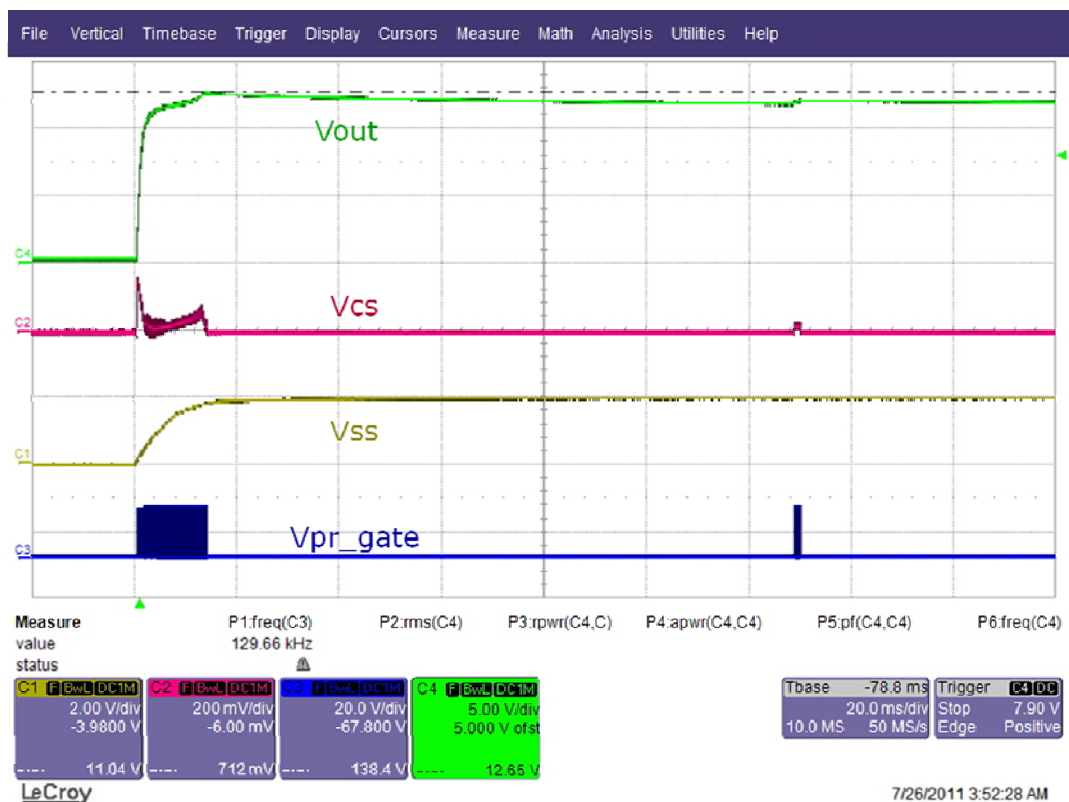
## B. No load

The output voltage rises up to nominal value in around 15ms. The overshoot is less than 5%. IC operates in burst mode after softstart.



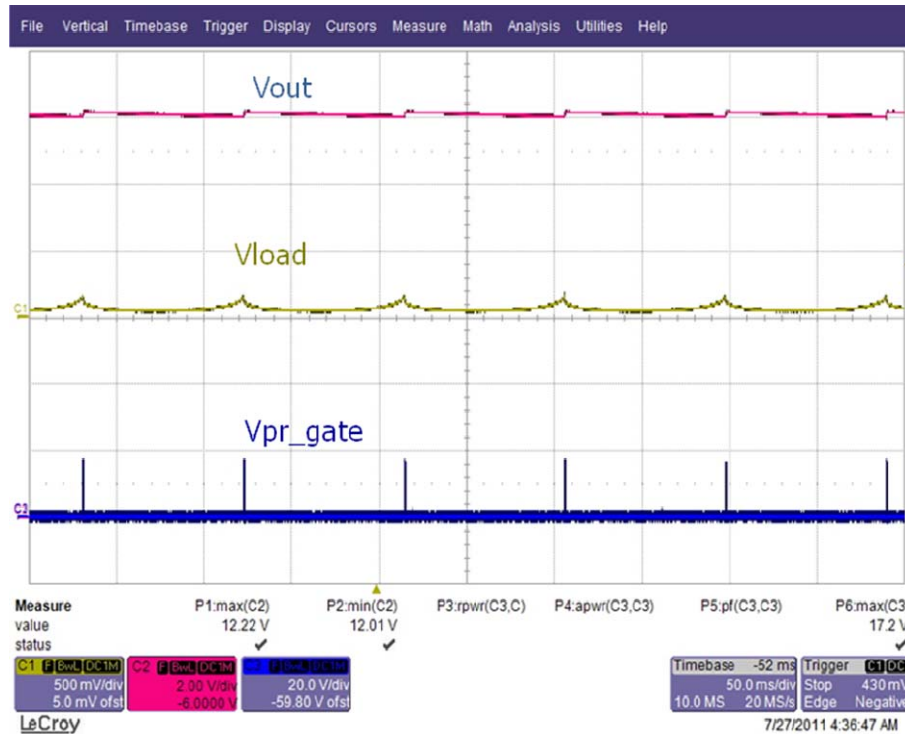
## 10.2 Burst mode operation at no load

When IC is operating in burst mode, the ripple of out voltage is less than 250mV.


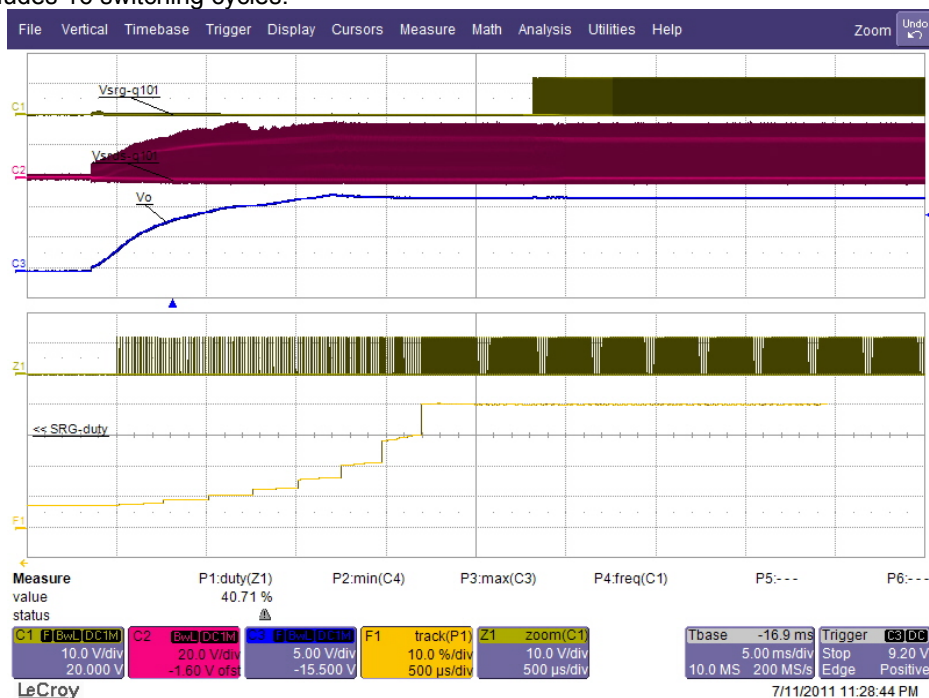
## 10.3 SR soft start at full load

The SR operation is enabled after the output voltage has been built up. In ICE2HS01G, SR operation will start with small duty, around one-tenth of its normal duty, which will be kept same for 16 consecutive switching cycles. Then, the duty is increased gradually step by step to the full duty. Total 7 steps are built for the softstart and each step includes 16 switching cycles.







## 10.4 Zero Voltage Switching

With proper design of LLC converter, ZVS can be realized over all load range. Channel 1 shows the resonant current flowing through the resonant capacitor. Channel 2 and 4 represent the gate-source voltage and drain source voltage of Q102.

### A. Full load

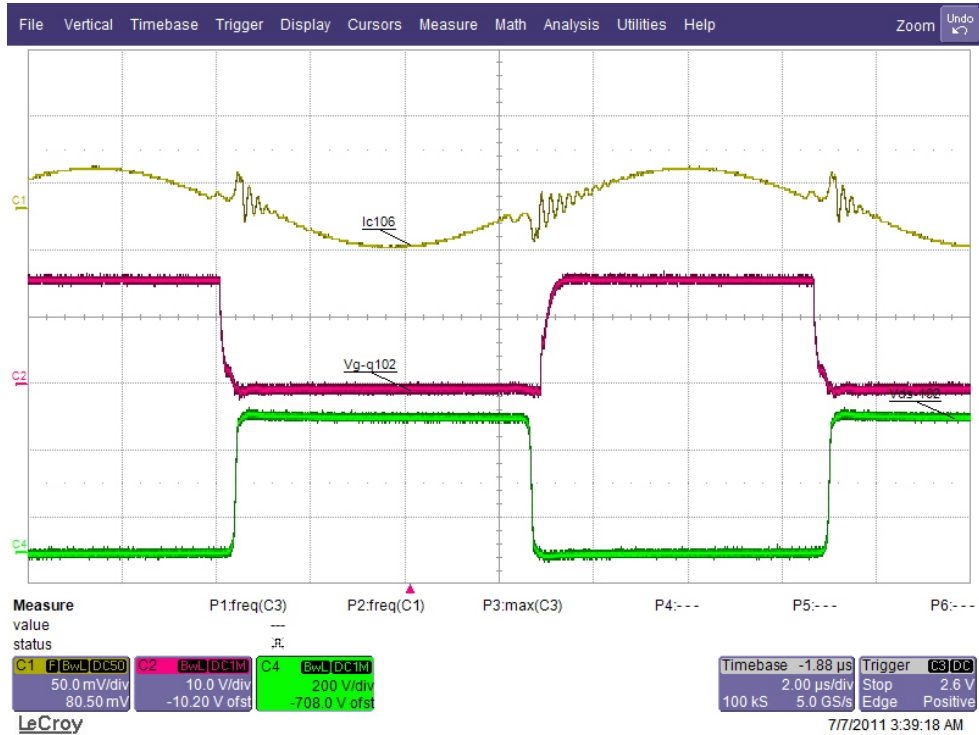


### B. Light load( $I_{out}=1A$ )

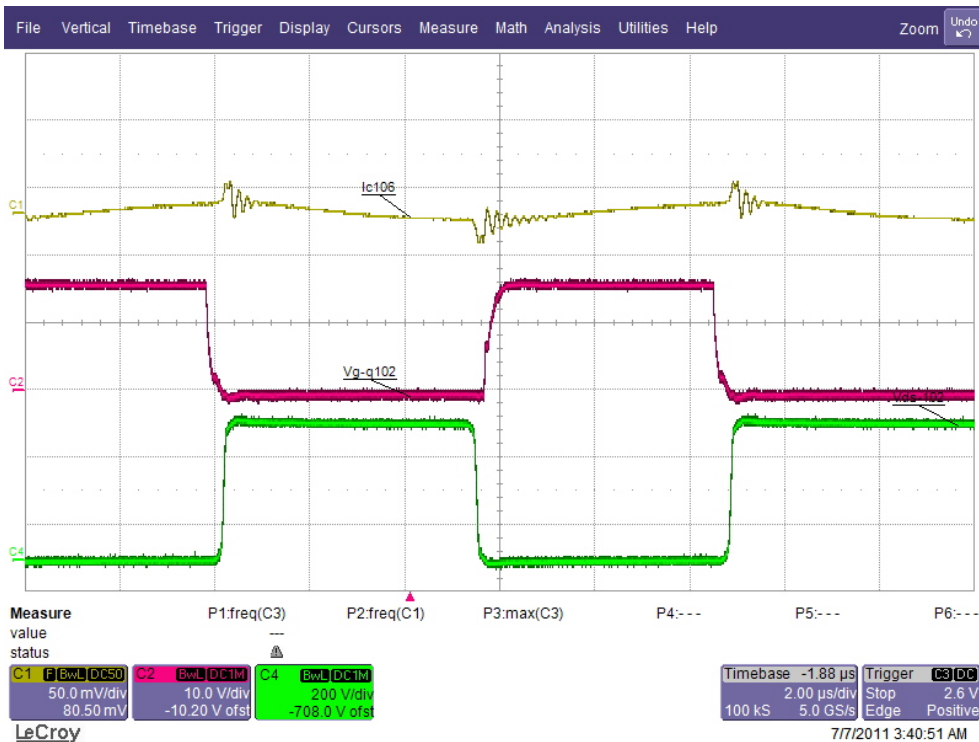


## 10.5 Main under voltage protection
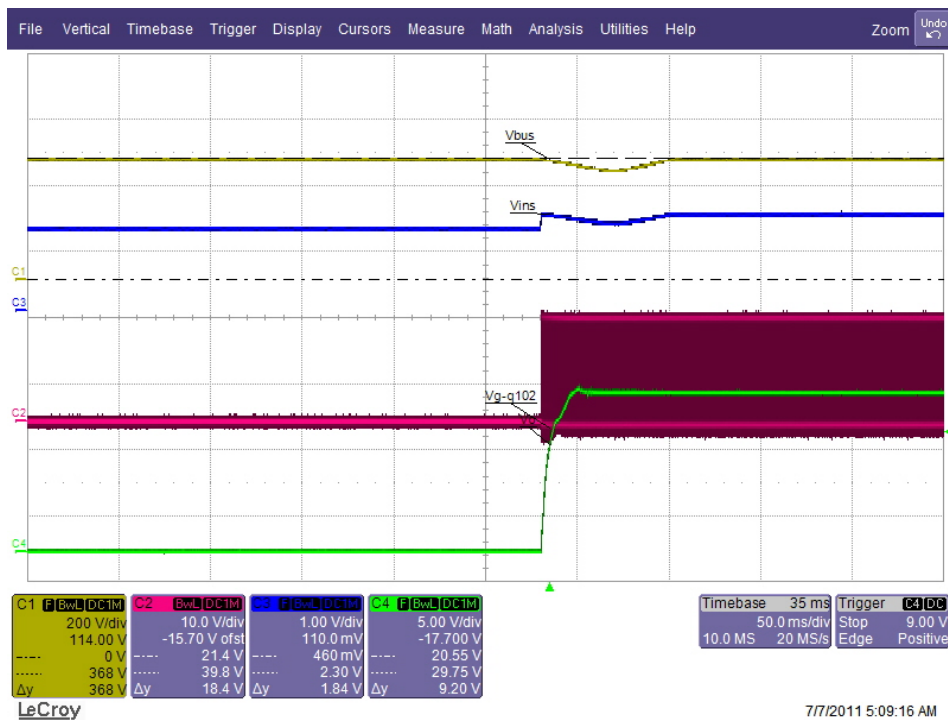
### A. IC starts operation when Vbus resumes to normal value Vbus-on=368Vdc.



7/7/2011 5:09:16 AM
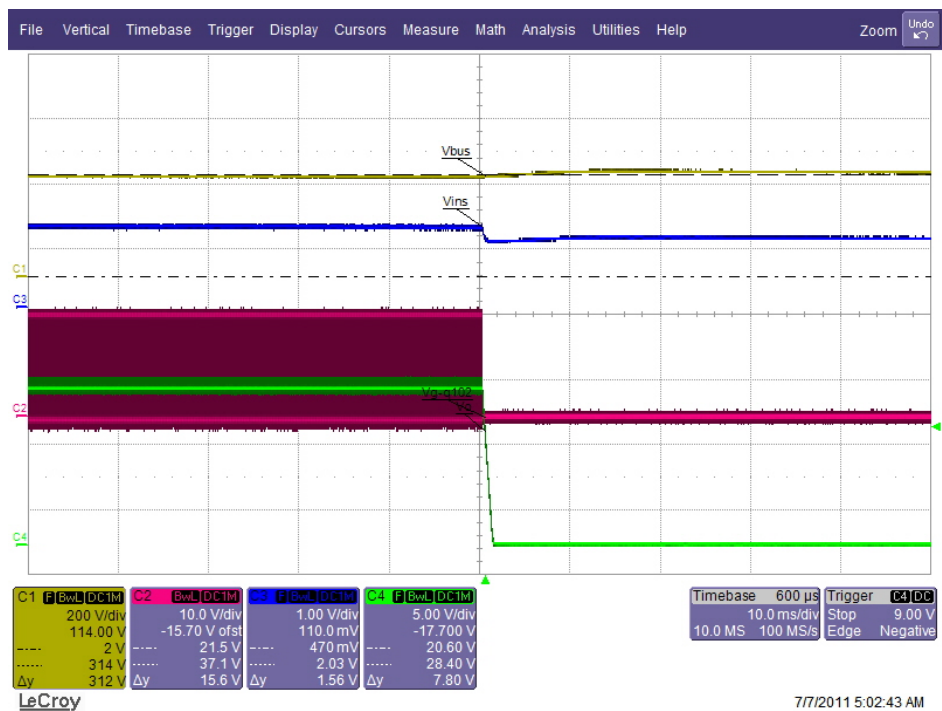
### B. IC stop switching when Vbus drops to designed value Vbus-off=312V




7/7/2011 5:02:43 AM

## 10.6 Dynamic load response

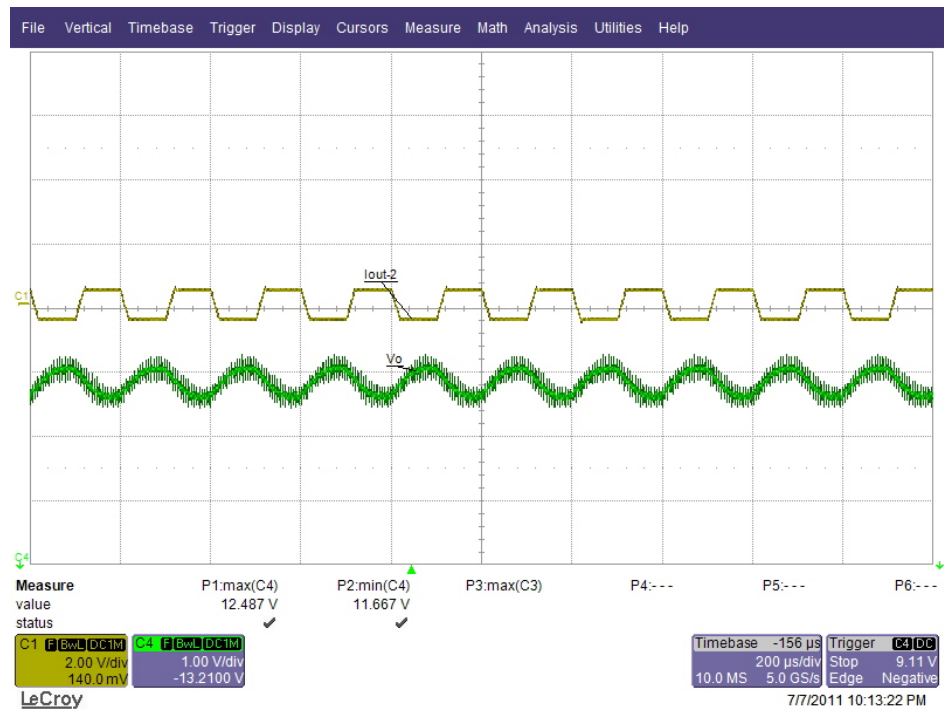
### A. 12V@2.5A~20A, 5KHz, 800m A/u S

The ripple of output voltage is around 0.8V.


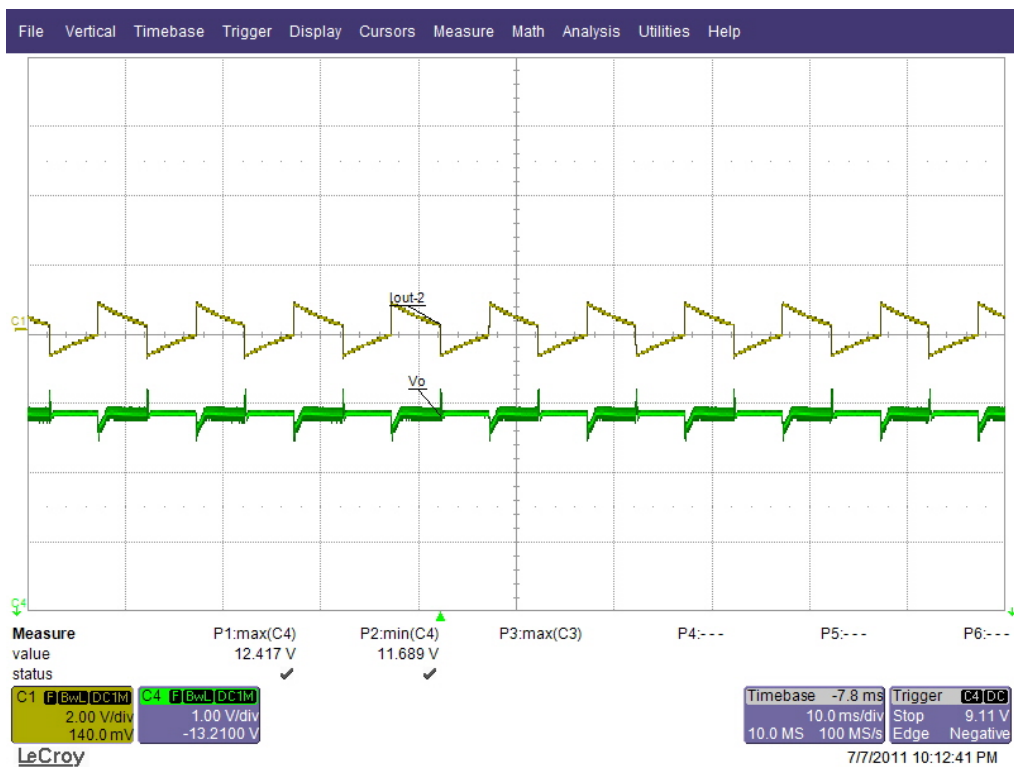
### B. 12V@ 2.5A~20A, 100Hz, 800m A/u S

The ripple of output voltage is around 0.8V.



## 10.7 Hold up time test

The hold up time is about 22mS at full load after the input is disconnected from the board.

