PMP6010

PMP6010 Test Results



Literature Number:SLUU925



Lighting Power Products Longmont Design Center

Montu Doshi & Matt Reynolds December 15, 2011 Rev 1.0

UCC28810 & LM3466 Isolated 120VAC 60W LED Three String LED Driver Reference Design

Table of Contents

60W Rev-001 Design Photograph	
Duty Cycle	
Peak Input Current	
Primary Inductance	
Calculating Primary Turns	
Scope Shots	
AC Line Voltage and Current	10
Primary Waveforms	1
Secondary Waveforms	1
Output Current Sense waveforms	1
Fault Condition Waveforms	1
ENAL	4



1 60W REV-001 DESIGN PCB






2 TARGET ELECTRICAL SPECIFICATION

- $V_{IN} \rightarrow 90VAC 132VAC$
- $V_0 \rightarrow 40V 50V$
- $-P_0 \rightarrow 60W$
- − I_0 → 1.25A
- Efficiency → 85%

3 PROPOSED SOLUTION/SCHEMATIC

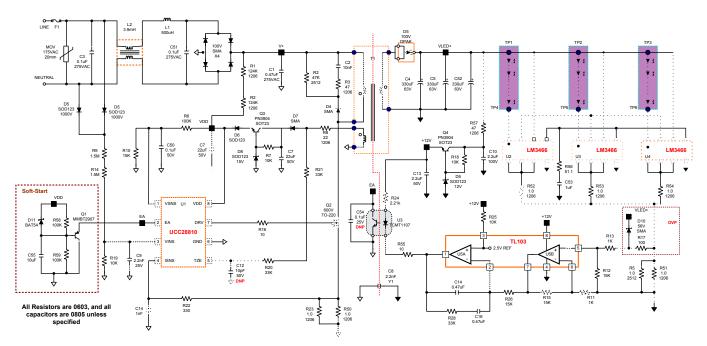



4 TRANSFORMER DESIGN

4.1 **Design Parameters**

$$\bullet \quad V_{AC\text{-MIN}} = 90 \ V_{AC}$$

•
$$V_{AC-MAX} = 132 V_{AC}$$

$$\begin{array}{lll} \bullet & V_{\text{AC-MAX}} & = & & 132 \ V_{\text{AC}} \\ \bullet & P_{\text{OUT}} & = & 60 \ W \\ \bullet & V_{\text{OUT}} & \approx & 47 V \end{array}$$

•
$$V_{DC-MIN} = \sqrt{2} \times 90 V_{AC}$$
 = 127V

•
$$V_{DC-MAX} = \sqrt{2} \times 132 V_{AC}$$
 = 186V

•
$$V_{O-MAX}$$
 $\approx 50V$

•
$$P_{IN} = \frac{P_{OUT}}{\eta}$$
 (85%) = 70W

•
$$I_{\text{IN-AVE}}$$
 = $\frac{P_{\text{OUT}}}{\eta}$ (85%) = 70W
• $I_{\text{IN-AVE}}$ = $\frac{P_{\text{OUT}}}{\eta \times V_{\text{DC-MIN}}}$ = 550mA

•
$$f_{SW-MIN} = 120kHz$$

Assume we want a 600V MOSFET

Therefore N_P/N_S maximum would be 5:1. I will choose ~ 3:1

Duty Cycle

$$D = \frac{\left(V_{O} \times \frac{N_{P}}{N_{S}}\right)}{\left(V_{O} \times \frac{N_{P}}{N_{S}}\right) + \left(V_{IN}\right)}$$


Typical Duty Cycle 0.46

$$D = \frac{\left(V_{O} \times \frac{N_{P}}{N_{S}}\right)}{\left(V_{O} \times \frac{N_{P}}{N_{S}}\right) + \left(V_{IN-MIN}\right)}$$

 $D_{MAX} = 0.54$



Peak Input Current

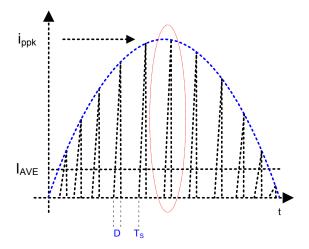

$$I_{\text{IN-AVE}} = \frac{P_{\text{OUT}}}{\eta \times V_{\text{DC-MIN}}} = 550 \text{mA}$$

Energy =
$$\frac{1}{2} \times L \times i_{ppk}^2$$

Or, area of the triangle = 1/2 base x height

$$i_{PPK} = \frac{2 \times I_{AVE}}{D} \approx 2.0A$$

Therefore
$$\rightarrow i_{\rm PPK} = \sqrt{\frac{P_{\rm IN} \times 2}{f_{\rm SW} \times L}}$$

Primary Inductance

$$V = L \frac{di}{dt}$$

$$L = \frac{V_{\text{IN-MIN}} \times D_{\text{MAX}}}{f_{\text{SW-MIN}} \times i_{\text{PPK}}} \text{ = 300uH}$$

Choose 200uH - 225uH

Calculating Primary Turns



Maximum operating flux density for most cores is 0.20T

$$B_{\text{MAX}} = \frac{L_{\text{PRI}} \times i_{\text{PPK}}}{N_{\text{PRI}} \times A_{\text{e}}}$$

Where A_e equals the specific cores effective area.

PQ26/20 (guess) effective core parameters.

 $Ae = 119mm^2$

$$N_{P} = \frac{L_{PRI} \times i_{PPK}}{B_{MAX} \times A_{e}}$$

B = Tesla

L = Henrys

 $A_e = m^2$

$$N_{\rm P} = \frac{200 \times 10^{-6} (2.0 A)}{(0.20 T) \times 51.8 \times 10^{-6} m^2} \approx 39 \text{ turns}$$

Alternatively:

 $N_{P}^{2} = \frac{L_{PRI}}{A_{L}} \ \, \text{Choose an AL, and calculate primary turns.} \ \, \text{Graphs similar to the one on the right are quick and}$


simple to use. Define AL (160nH/T 2), and then determine gap. Look for standard A_L numbers when designing your transformer.

$$N_{_{P}} = \sqrt{\frac{L_{_{PRI}}}{A_{_{L}}}} \; \text{= 35turns} \rightarrow \text{Al = 160nH/T}^2$$

$$N_{_{P}} = \sqrt{\frac{L_{_{PRI}}}{A_{_{L}}}} \text{ = 45turns} \rightarrow \text{Al = 100nH/T}^2$$



4.2 Core/Bobbin Selection

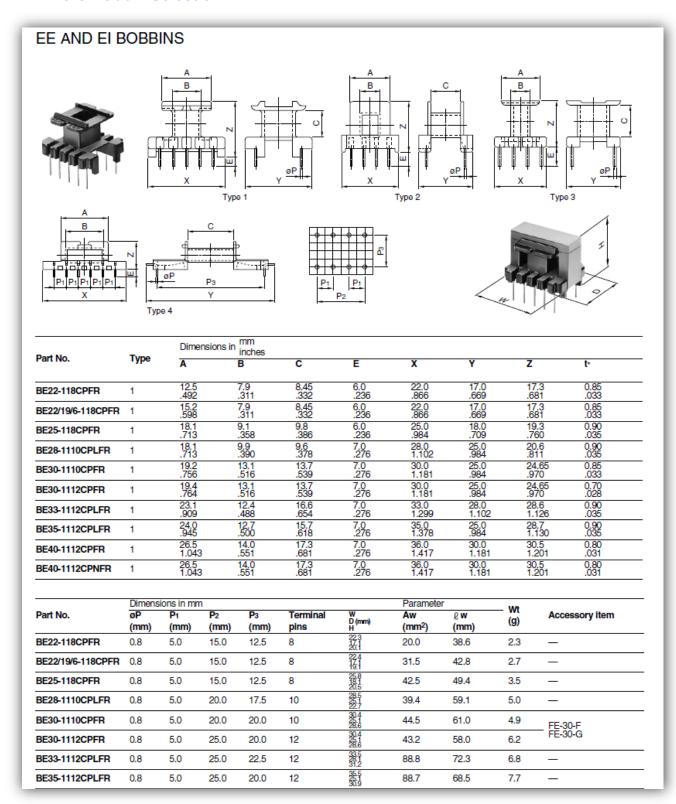



	Effective	paramete	er		Electrical characteristics				
Part No.	C ₁	Ae	ρe	Ve	AL-value (nH/N²)*		Core loss (W) max.	Wt	Bobbin item
	(mm ⁻¹)	(mm²)	(mm)	(mm³)	Without air gap	With air gap	100kHz, 200mT, 100°C	(g)	DODDIII Itelii
PC40EE20/20/5-Z	1.38	31.0	43.0	1340	1400±25%	100±7% 160±10%	0.51	7.5	_
PC40EF20-Z	1.34	33.5	44.9	1500	1570±25%	100±7% 160±10%	0.69	7.4	_
PC40EE22-Z	0.970	41.0	39.6	1620	2180±25%	125±7% 250±10%	0.61	8.8	BE22-1110CPFR BE22-118CPFR BE-22-5116
PC40EE25/19-Z	1.22	40.0	48.7	1950	2000±25%	100±7% 200±10%	0.86	9.1	_
PC40EF25-Z	1.11	51.8	57.8	2990	2000±25%	100±7% 160±10%	1.40	15	_
PC40EE25.4-Z	1.21	40.3	48.7	1963	2000±25%	125±7% 250±10%	0.90	10	_
PC40EE30-Z	0.529	109.0	57.7	6290	4690±25%	200±5% 400±7%	2.90	32	BE30-1110CPFR BE30-1112CPFR BE-30-5112
PC40EE30/30/7-Z	1.12	59.7	66.9	4000	2100±25%	160±5% 250±7%	1.51	22	_

4.3 Wire selection and transformer build

W_B - Bobbin width is equal to dimension 12mm from the above illustration.

W_M - Equals the margin tape required width.

O_D – Outside diameter of the wire used.

As an example, if we have 18mm of bobbin width, and we want to add 4mm of tape on each side, then we have 10mm of width.

I want to split the primary into two windings (series connected), 52T total (13 X 2 X 2) across bobbin.

$$O_{\text{D-MAX}} = \frac{W_{\text{B}} - 2W_{\text{M}}}{Turns}$$

- 22-gauge wire has an O_D of 0.6438mm diameter
- 24-gauge wire has an O_D of 0.511mm diameter
- 28-gauge wire has an O_D of 0.321mm diameter

One could use triple insulated wire on the secondary; therefore no margin tape is required.

- Primary wire gauge= 20Ga
- Secondary (triple insulated) wire gauge= 20Ga
- Auxiliary wire gauge= 24Ga

Gauge to diameter and vice versa conversion

http://www.66pacific.com/calculators/wire_calc.aspx

Triple insulated wire

http://www.furukawa.co.jp/makisen/eng/product/texe series.htm

We need to guarantee that the primary inductance keeps us in DCM.



4.4 Transfomer Design #1

$$V_{IN} = 90V_{AC} - 132V_{AC}$$

$$V_0 = 40V \sim 50V$$

$$I_{PRI-PK} = 2.0A$$

$$P_{OUT} = 60W \text{ (max)}$$


Core/bobbin = EF25 vertical type


- Mag Inc R material
- Ferroxcube 3F3 material
- Epcos N87 material

 $A_1 = 160 \text{nH/turns}^2$

$$-$$
 N_{PRI} = 40T - N_{SEC} = 12T - N_{AUX} = 5T

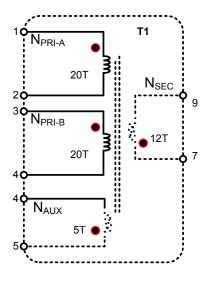Primary (Aux Winding):
$$V_{AUX} = \left(\frac{V_{OUT}}{N_{SFC}}\right) \times P_2$$



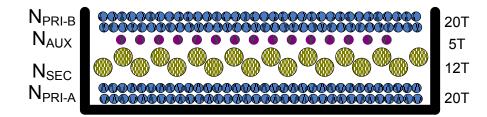




4.5 60W Driver Performance

Input Voltage	Input Power	Power Factor	Output Voltage	Output Current	Output Power	Efficiency
115VAC	67W	0.980	47V	1.25A	58W	86.5%

Scope Shots

AC Line Voltage and Current


 $P_{OUT} = 45W$

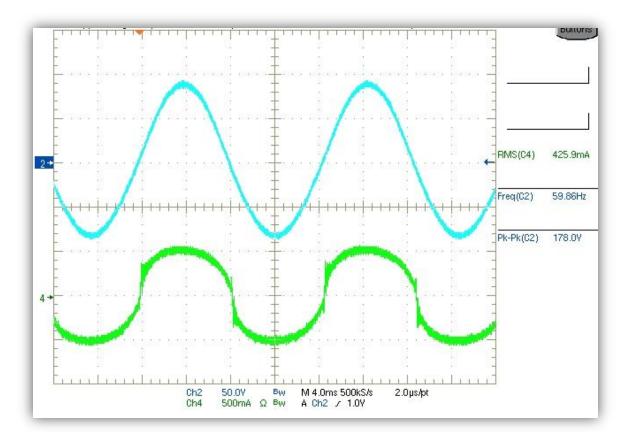




Primary Waveforms

V_{DS} (blue), Primary V_{CC} (pink)

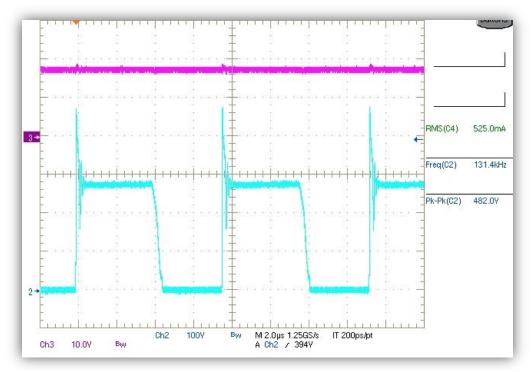


V_{DS} (pink), I_{DS} (blue)

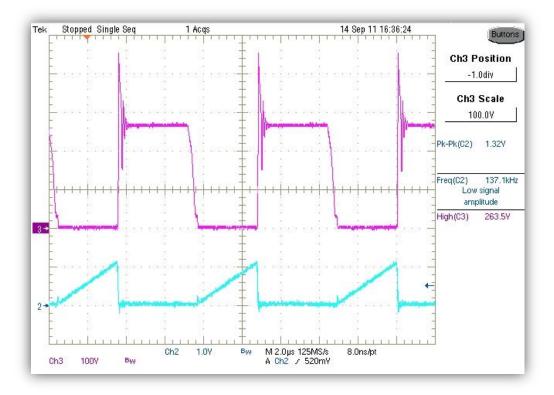




Secondary Waveforms

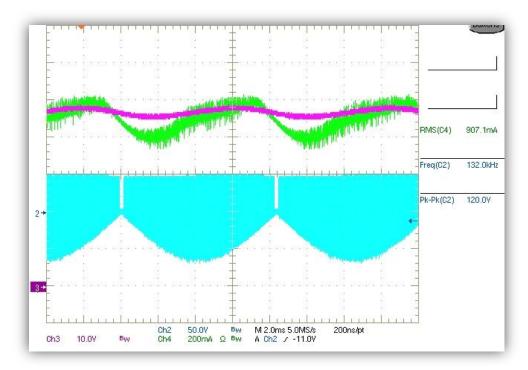Diode voltage anode (blue), Total output current (green), Output voltage (pink) - Pout = 45W



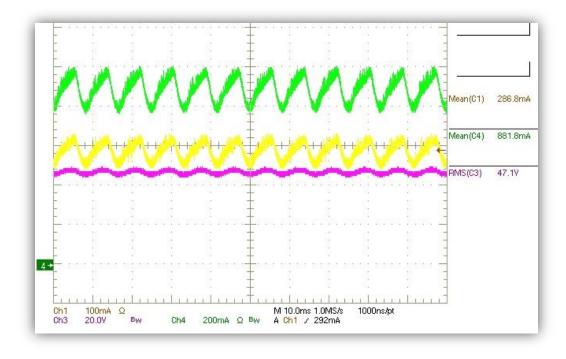
Output voltage (pink), Total output current (green), Single LM3446 current output (yellow) - $P_{OUT} = 45W$






Output Current Sense waveforms

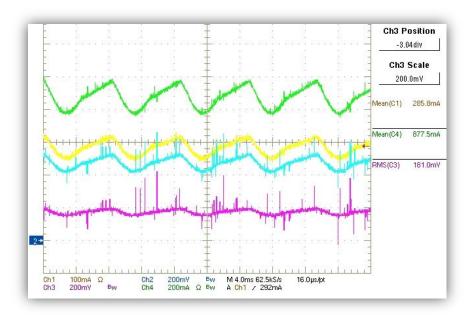CH1 (yellow) output current of single LM3466, CH4 (green) total current, CH2 (blue) single channel sense voltage, CH3 (pink) total output current sense - P_{OUT} = 45W



Fault Condition Waveforms

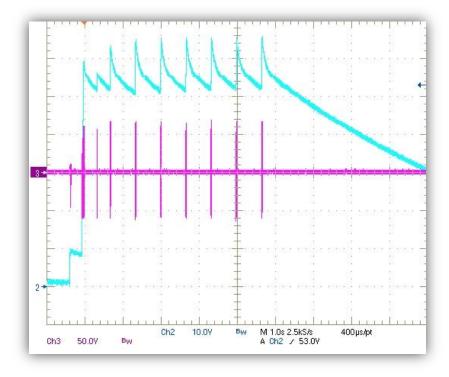
Start up into open load, and shutdown - Blue Trace (CH@) is output voltage, Pink trace (CH3) anode of secondary diode (no damage to LED driver)





EMI

Rev-001

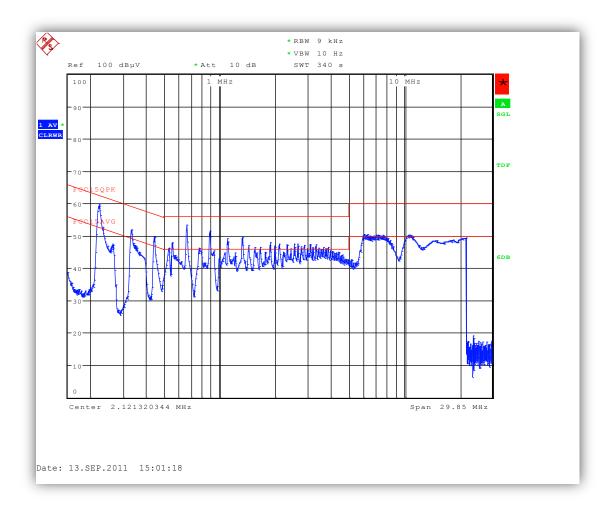



5 REVISION HISTORY

Date	Author	Revision	Description
Dec 18, 2011	Matt Reynolds	1.0	- Initial report.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

Applications

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Wireless Connectivity

Audio www.ti.com/audio Automotive and Transportation www.ti.com/automotive **Amplifiers** amplifier.ti.com Communications and Telecom www.ti.com/communications dataconverter.ti.com Computers and Peripherals www.ti.com/computers **Data Converters DLP® Products** www.dlp.com Consumer Electronics www.ti.com/consumer-apps DSP dsp.ti.com **Energy and Lighting** www.ti.com/energy Clocks and Timers www.ti.com/clocks Industrial www.ti.com/industrial Interface interface.ti.com Medical www.ti.com/medical Logic logic.ti.com Security www.ti.com/security Power Mgmt www.ti.com/space-avionics-defense power.ti.com Space, Avionics and Defense Microcontrollers Video and Imaging microcontroller.ti.com www.ti.com/video www.ti-rfid.com **OMAP Mobile Processors** www.ti.com/omap

TI E2E Community Home Page

www.ti.com/wirelessconnectivity

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2012, Texas Instruments Incorporated

e2e.ti.com