
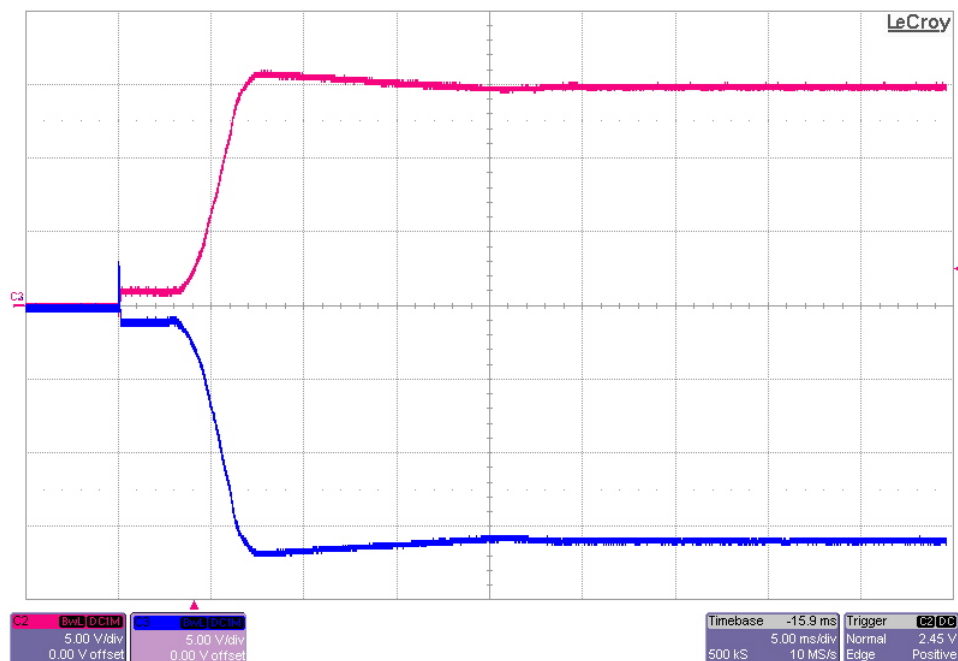


1 Startup

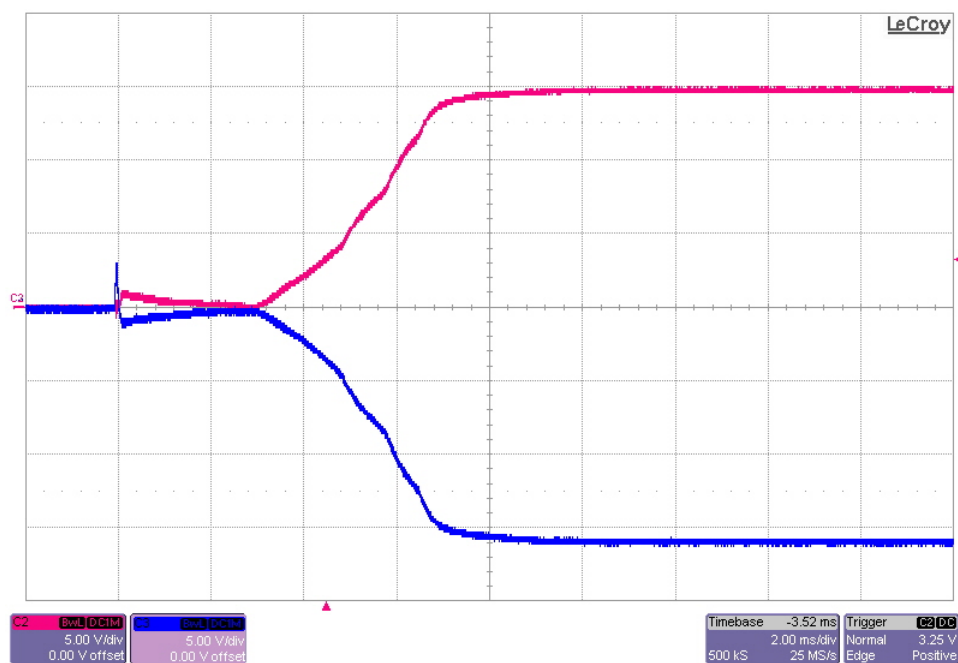
The photo below shows the +/-15V output voltage startup waveform after the application of 30Vdc. The outputs were loaded to 0A. (5V/DIV, 5mS/DIV)




The photo below shows the +/-15V output voltage startup waveform after the application of 30Vdc. The outputs were loaded to 200A each. (5V/DIV, 2mS/DIV)



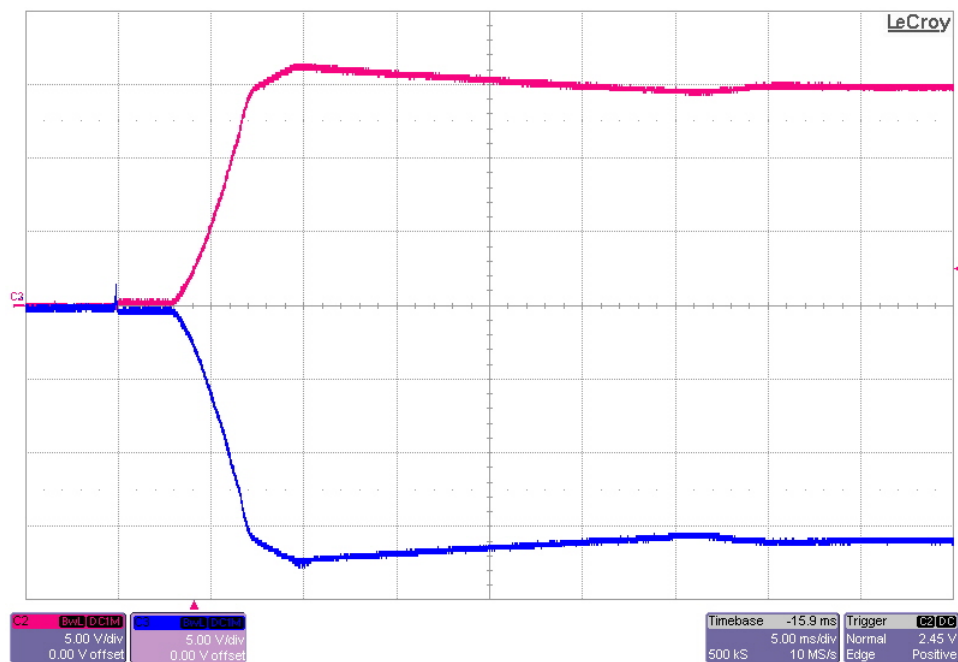The photo below shows the +/-15V output voltage startup waveform after the application of 12Vdc. The outputs were loaded to 0A. (5V/DIV, 5mS/DIV)




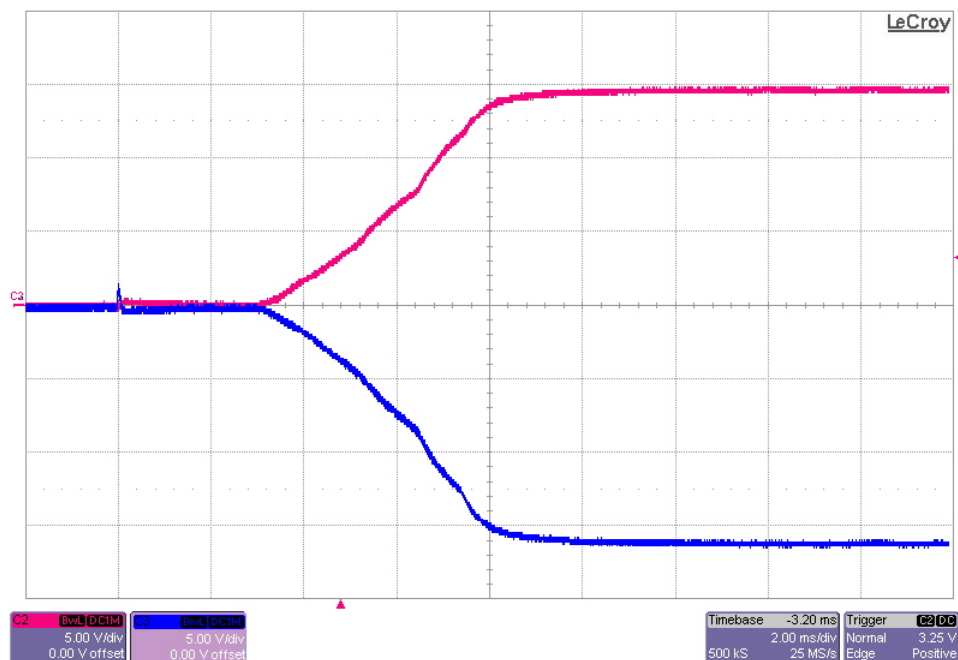The photo below shows the +/-15V output voltage startup waveform after the application of 12Vdc. The outputs were loaded to 200A each. (5V/DIV, 2mS/DIV)




2 Output Ripple Voltage

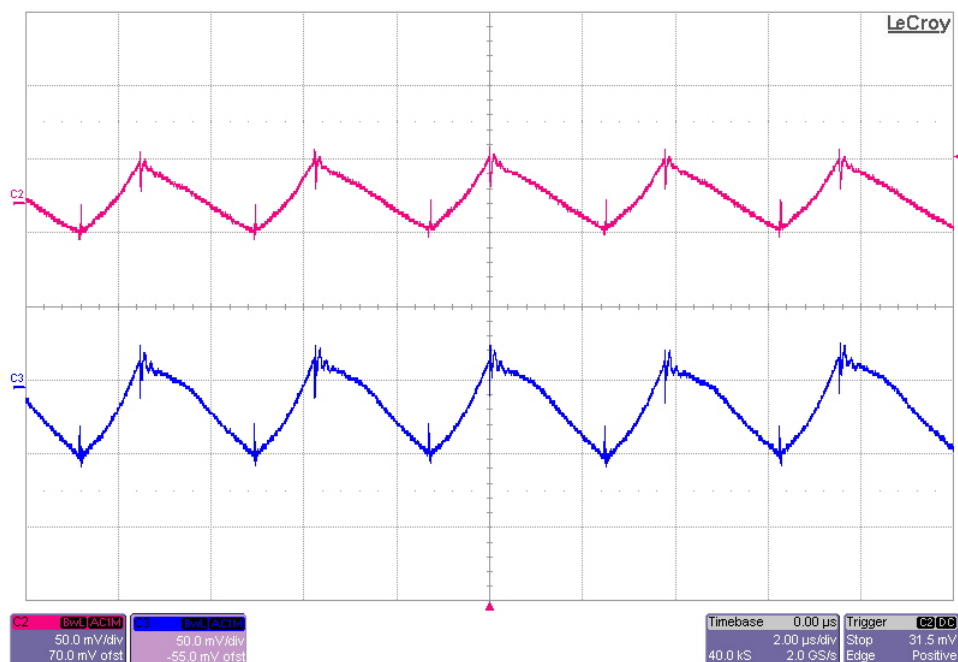
The +/-15V output ripple voltage is shown in the figure below (+15V on top, -15V on bottom). The image was taken with the output loaded to 200mA each and the input voltage set to 9Vdc. (50mV/DIV, 2uS/DIV)



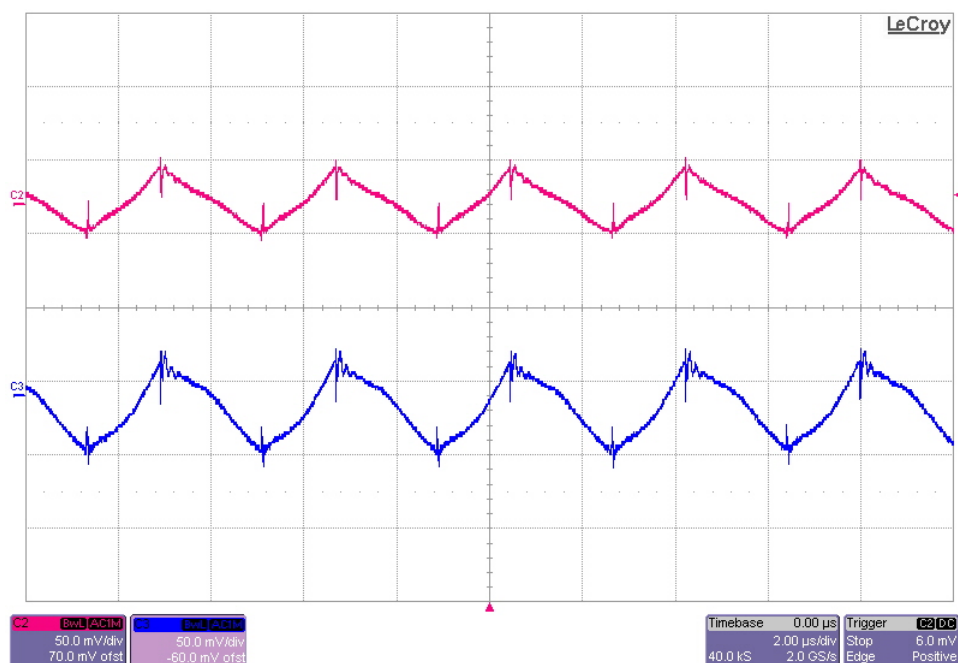The +/-15V output ripple voltage is shown in the figure below (+15V on top, -15V on bottom). The image was taken with the output loaded to 200mA each and the input voltage set to 12Vdc. (50mV/DIV, 2uS/DIV)





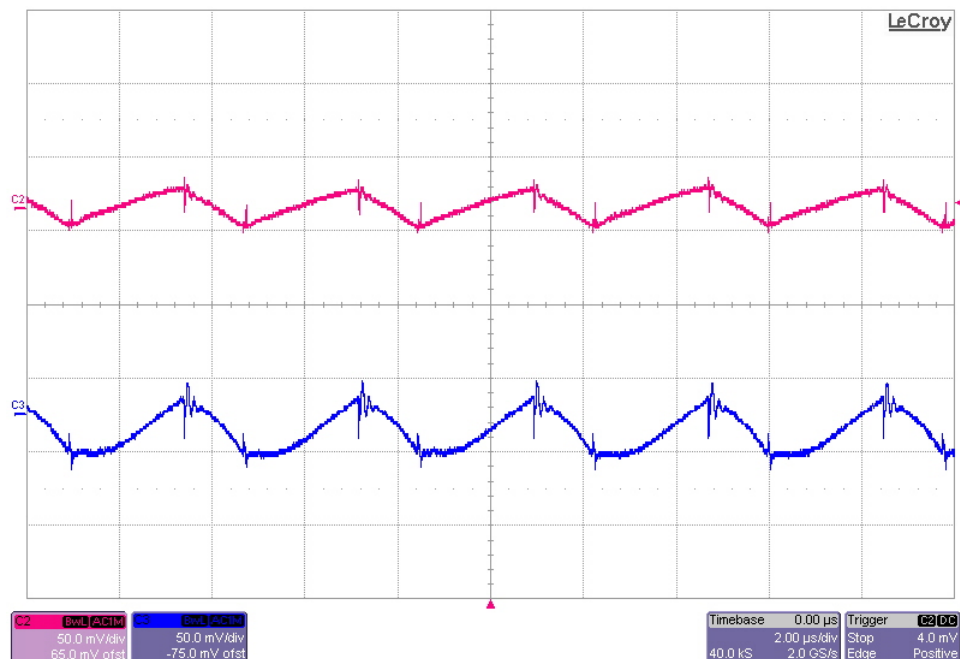The +/-15V output ripple voltage is shown in the figure below (+15V on top, -15V on bottom). The image was taken with the output loaded to 200mA each and the input voltage set to 30Vdc. (50mV/DIV, 2uS/DIV)



3 Efficiency

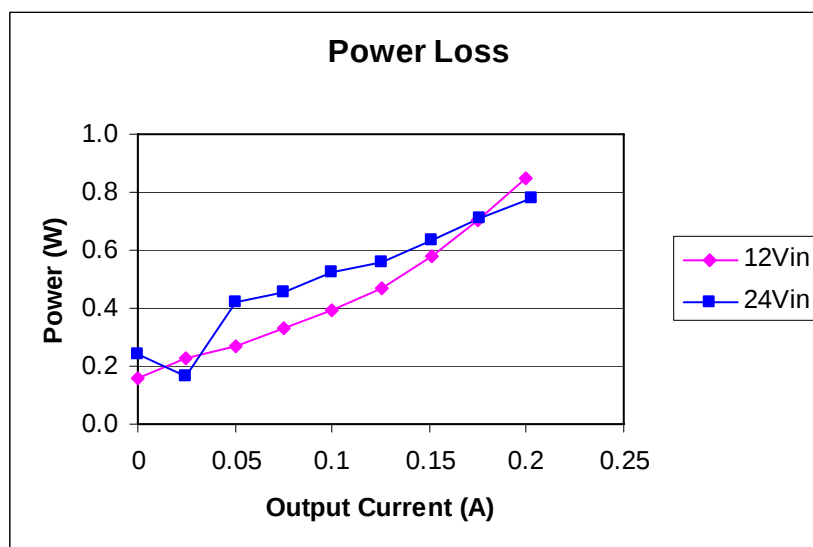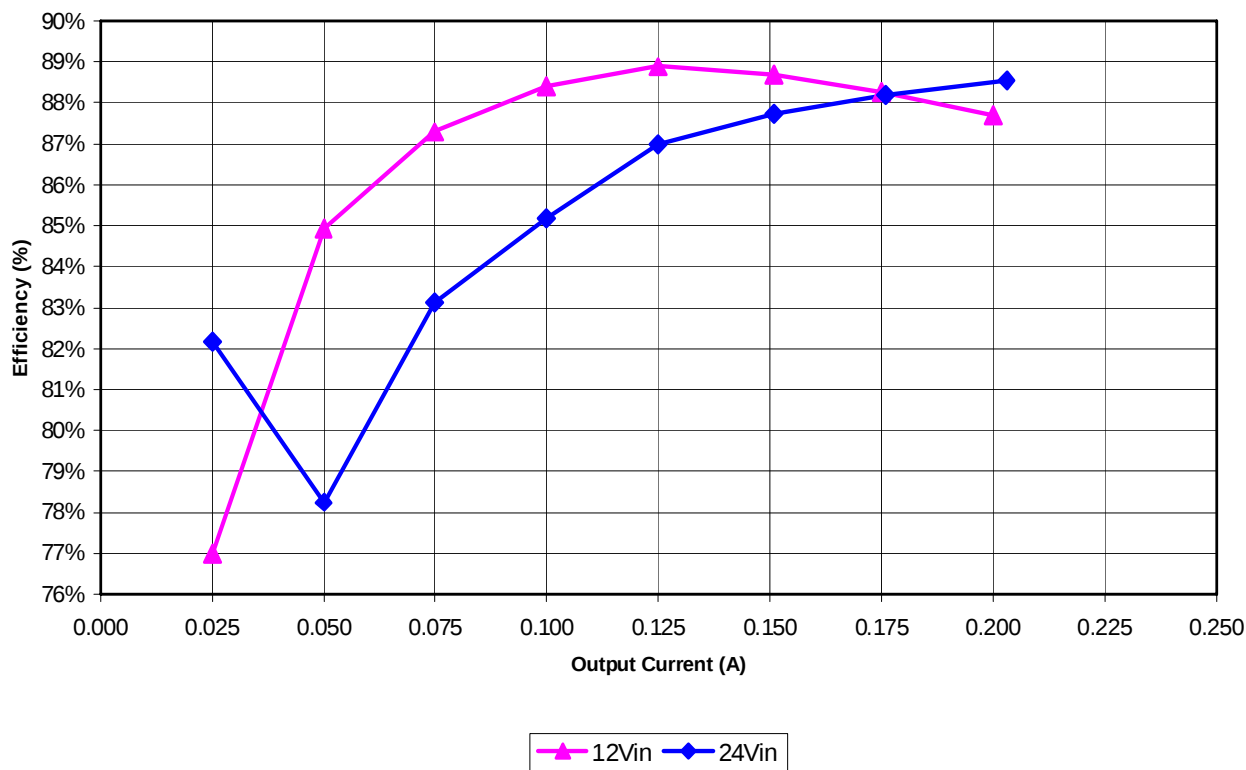The converter efficiency is shown in the figure below. The outputs were loaded equally. The converter is operating in DCM for $V_{in} = 24V$ and 25mA out.



4 Cross Regulation

The output voltage regulation is shown in the table below for balanced load.

Vin	Iin	Vout1	Iout1	Vout2	Iout2	Po
12.1185	0.013	15.03	0.000	-15.04	0.000	0.000
12.0540	0.081	15.01	0.025	-15.06	0.025	0.752
12.0404	0.147	14.95	0.050	-15.12	0.050	1.504
12.0764	0.214	14.97	0.075	-15.11	0.075	2.256
12.0606	0.282	14.97	0.100	-15.10	0.100	3.007
12.0477	0.351	14.95	0.125	-15.12	0.125	3.759
12.0325	0.424	14.90	0.151	-15.17	0.150	4.525
12.0657	0.497	14.85	0.175	-15.22	0.177	5.293
12.0509	0.572	14.79	0.200	-15.28	0.202	6.045

Vin	Iin	Vout1	Iout1	Vout2	Iout2	Po
24.0890	0.010	15.04	0.000	-15.04	0.000	0.000
24.0829	0.038	15.00	0.025	-15.08	0.025	0.752
24.0261	0.080	15.01	0.050	-15.07	0.050	1.504
24.0191	0.113	14.98	0.075	-15.10	0.075	2.256
24.0116	0.147	14.95	0.100	-15.12	0.100	3.007
24.0044	0.180	14.95	0.125	-15.12	0.125	3.759
24.0963	0.214	14.96	0.151	-15.10	0.150	4.524
24.0889	0.249	14.97	0.176	-15.09	0.176	5.291
24.0822	0.284	14.97	0.203	-15.09	0.200	6.057


Cross Reg Data

Vin	Iin	Vout1	Iout1	Vout2	Iout2	Po	12Vin Eff	Pin	12Vin Ploss
12.0953	0.351	14.67	0.202	-15.40	0.050	3.733	0.879	4.245	0.512
12.1034	0.311	14.54	0.200	-15.53	0.025	3.296	0.876	3.764	0.468
12.1082	0.288	14.27	0.202	-15.80	0.010	3.041	0.872	3.487	0.447
12.1147	0.257	13.27	0.202	-16.80	0.000	2.681	0.861	3.113	0.433


Vin	Iin	Vout1	Iout1	Vout2	Iout2	Po	24Vin Eff	Pin	24Vin Ploss
24.1027	0.178	14.74	0.200	-15.33	0.050	3.715	0.866	4.290	0.576
24.1068	0.160	14.53	0.200	-15.54	0.025	3.295	0.854	3.857	0.563
24.1096	0.146	14.13	0.200	-15.94	0.010	2.985	0.848	3.520	0.535
24.1147	0.121	12.15	0.200	-17.92	0.000	2.430	0.833	2.918	0.488

5 Load Transients

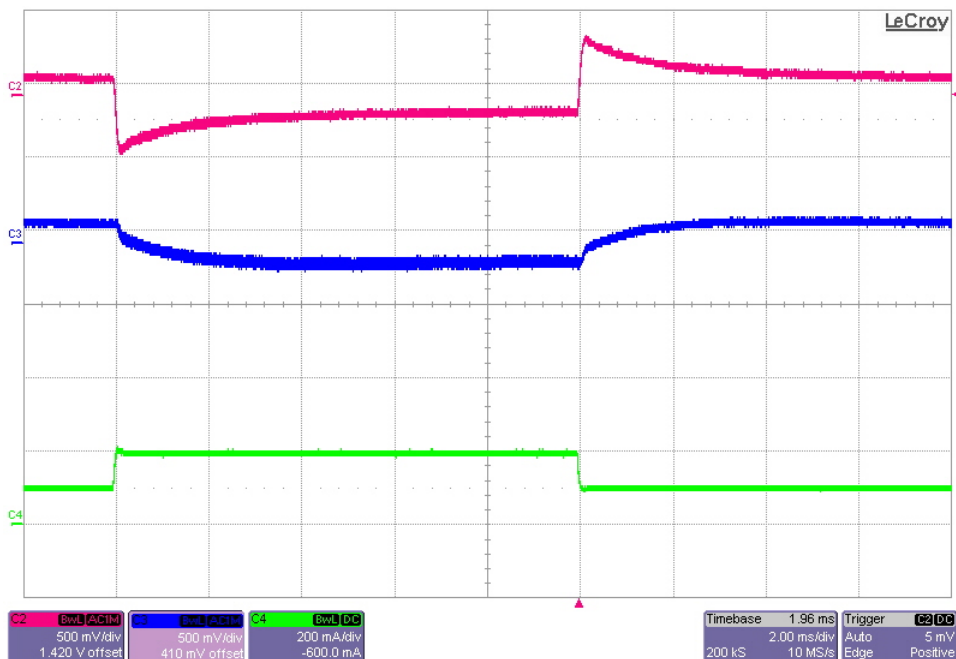The photo below shows the +/-15V output voltage (AC coupled) when the +15V load current is pulsed between 100mA and 200mA each. (+15V on top, -15V in middle) $V_{in} = 12V_{dc}$. (500mV/DIV, 200mA/DIV, 2mS/DIV)




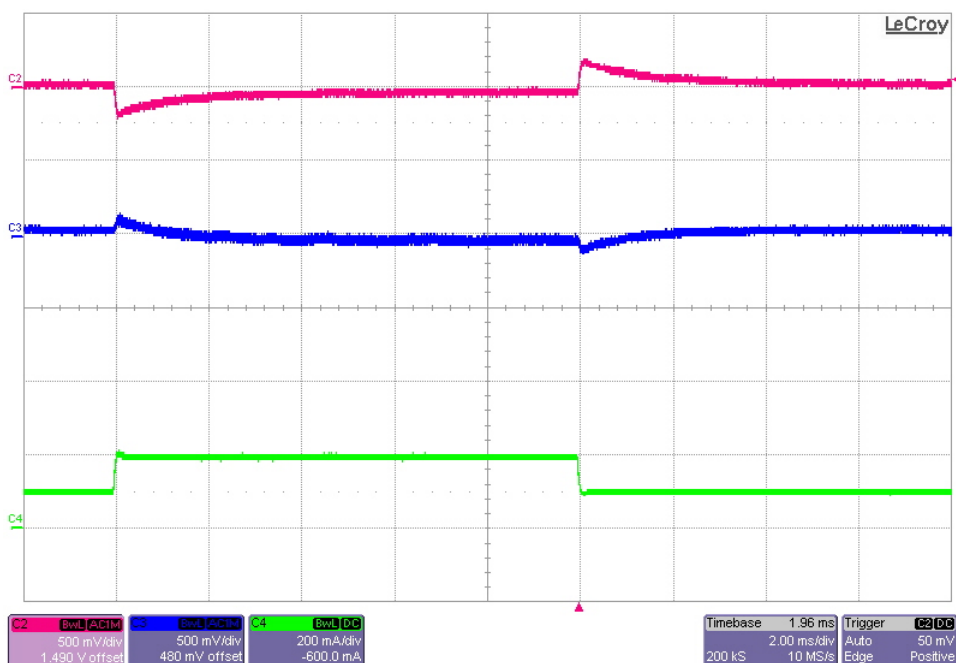The photo below shows the +/-15V output voltage (AC coupled) when the +15V load current is pulsed between 100mA and 200mA each. (+15V on top, -15V in middle) $V_{in} = 30V_{dc}$. (500mV/DIV, 200mA/DIV, 2mS/DIV)




6 Waveforms

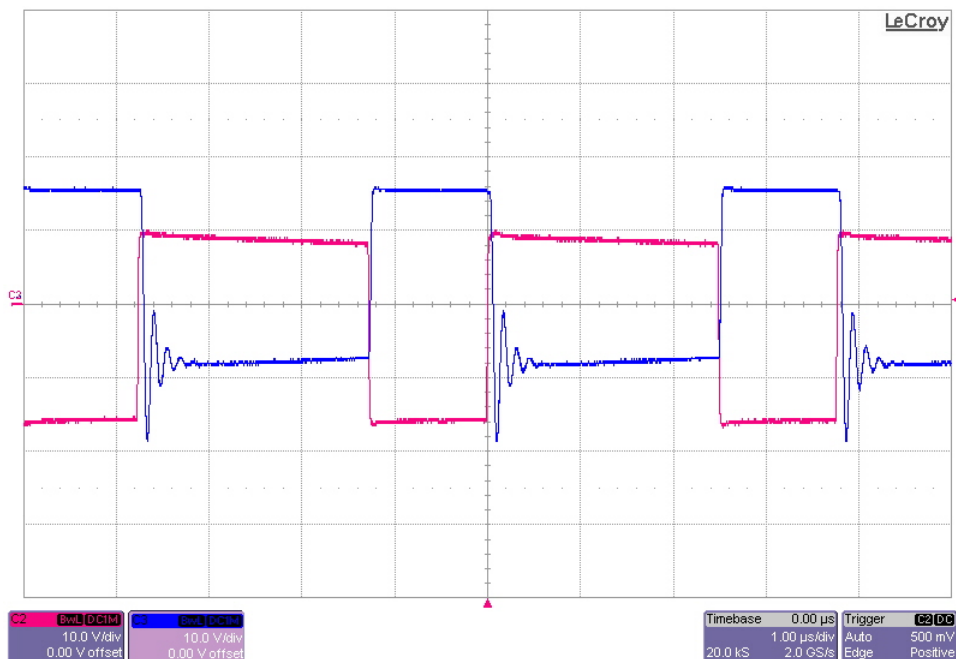
The photo below shows the switching waveform on each output rectifier diode. The input voltage is 9V and the output is loaded to 200mA each. (10V/DIV, 1uS/DIV)



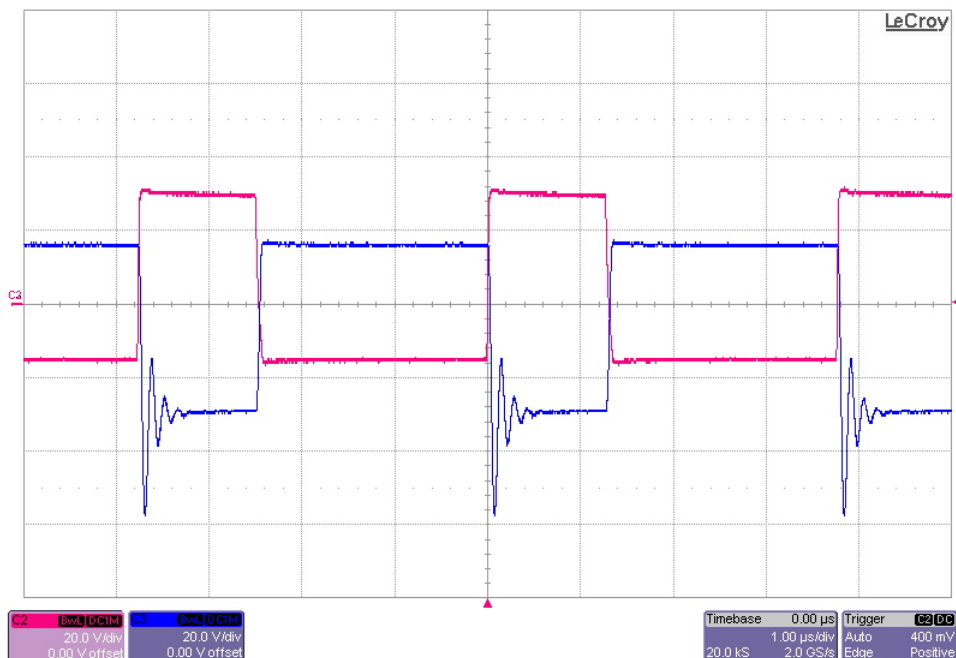
The photo below shows the switching waveform on each output rectifier diode. The input voltage is 30V and the output is loaded to 200mA each. (20V/DIV, 1uS/DIV)



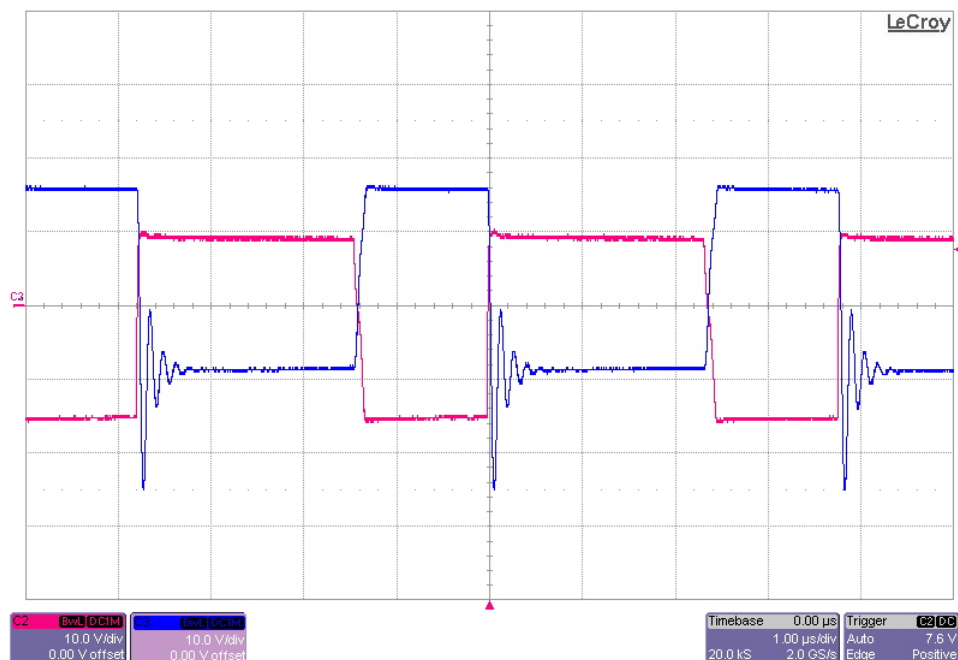The photo below shows the switching waveform on each output rectifier diode. The input voltage is 9V and the output is loaded to 25mA each. (10V/DIV, 1uS/DIV)



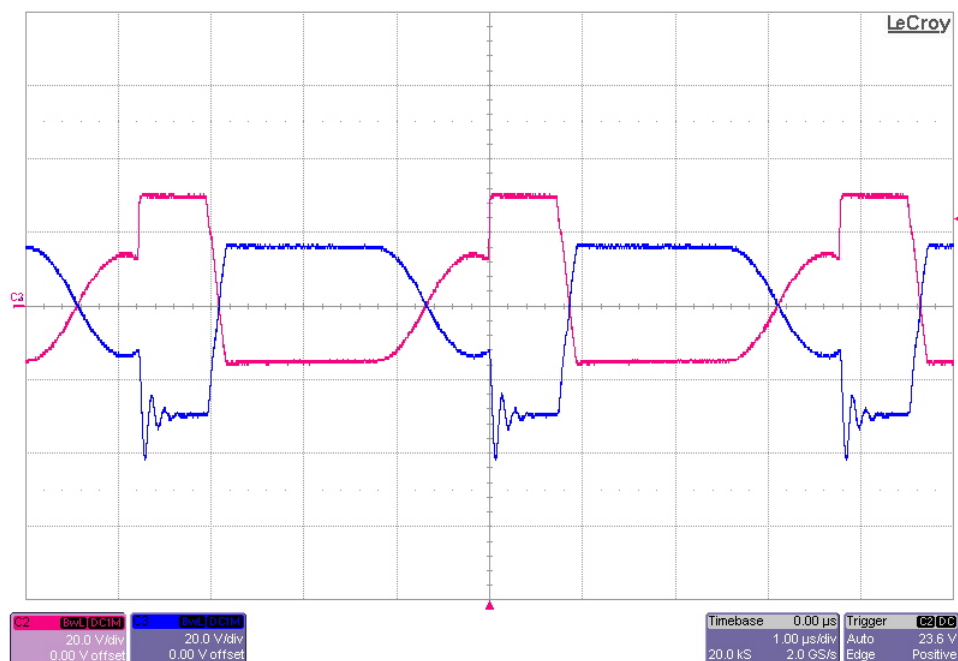
The photo below shows the switching waveform on each output rectifier diode. The input voltage is 30V and the output is loaded to 25mA each. (20V/DIV, 1uS/DIV)



7 Loop Gain


The plot below shows the loop gain with 9V and 30V input voltages. The outputs are loaded to 200mA each.

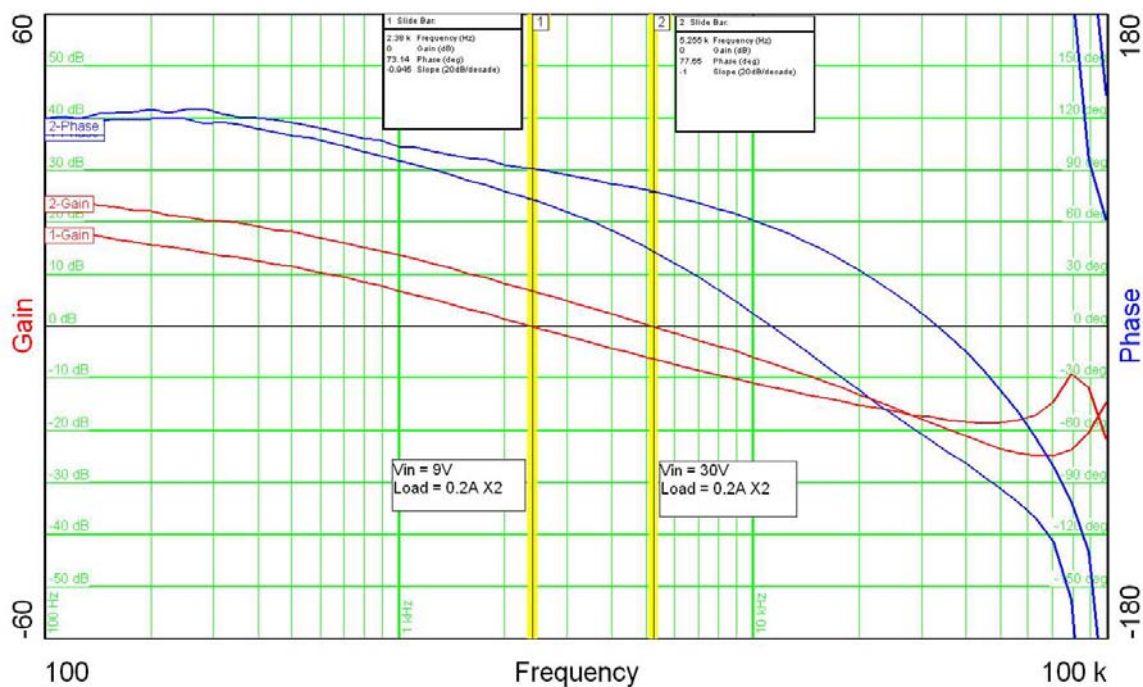Loop Gain (9Vin) BW: 2.4KHz PM: 73 degrees
 Loop Gain (30Vin) BW: 5.3KHz PM: 78 degrees



The plot below shows the loop gain with 9V and 30V input voltages. The outputs are loaded to 50mA each.

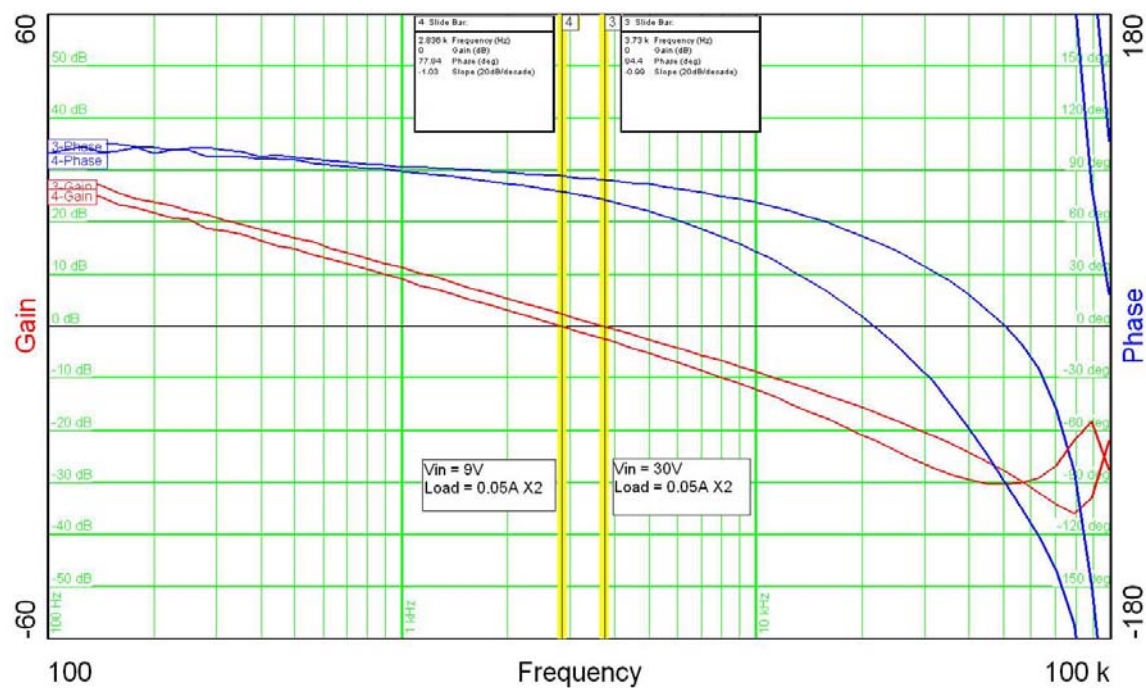Loop Gain (9Vin) BW: 2.8KHz PM: 78 degrees
 Loop Gain (30Vin) BW: 3.7KHz PM: 84 degrees



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics & Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video
Wireless	www.ti.com/wireless-apps