

Using a portable-power boost converter in an isolated flyback application

By Jeff Falin, Senior Applications Engineer,
and Brian King, Member, Group Technical Staff

Some electronic applications require an isolated auxiliary power supply that must be generated from a low-voltage AC adapter. Examples of such applications include isolated MOSFET drive circuits and relay controls. Finding an isolated power-supply controller that will operate at such low voltages can prove difficult. Fortunately, it is possible to configure some low-power boost converters, such as the Texas Instruments (TI) TPS61175, to operate and control a flyback power stage. This article explains how to use the TPS61175 in an isolated flyback application.

Consider, for example, an application that is supplied from a 5-V wall wart and requires an isolated 5-V, 500-mA auxiliary supply. In this application, the input voltage can range from 3 to 6 V, and small size is a higher priority than efficiency. The low output-power and isolation requirements make the flyback an obvious choice for the power-supply topology. Taking into account the size limitations, a boost controller with an integrated FET is ideal for this type of application. With its 2.9-V minimum input voltage, the TPS61175 is one of the few boost converters that can meet these input-voltage specifications. In addition, the switching frequency of up to 2.2 MHz allows for a smaller transformer and reduced component sizes for the input and output filters.

The TPS61175 is a highly integrated current-mode controller. This controller internally limits the peak FET current to 3 A, which makes continuous conduction mode (CCM) a good choice. Selecting an operating frequency of 1 MHz keeps the switching losses manageable and reduces the transformer inductance and physical size. Although the TPS61175 includes a fixed amount of internal slope compensation, limiting the maximum duty cycle to less than 50% eliminates the possibility of bimodal operation and also reduces the rms current in the output capacitors.

Equation 1 computes the required primary-to-secondary turns ratio, N_{p2s} , of the transformer:

$$N_{p2s} = \frac{V_{IN(min)} \times D_{max}}{(V_{OUT} + V_d) \times (1 - D_{max})} \quad (1)$$

In order to limit the duty cycle to 45%, a ratio of 1:2.5 was selected. The internal MOSFET of the TPS61175 is rated for 40 V, so the voltage stress is not an issue for this design.

In CCM converters, using too large an inductance can cause the right-half-plane zero (RHPZ) to limit the bandwidth of the feedback loop. The location of the RHPZ is determined by Equation 2:

$$RHPZ = R_{Load} \times \frac{(1 - D)^2}{2\pi \times L_{Sec} \times D} \quad (2)$$

If this frequency is not significantly higher than the unity-gain frequency of the feedback loop, stability is jeopardized. Fortunately, with a 1-MHz switching frequency, a relatively large inductance can be used and still allow for an adequate loop bandwidth. Selecting a primary inductance of 1.2 μ H keeps the converter in CCM operation down to a load current of 150 mA and puts the RHPZ in the neighborhood of 200 kHz.

The amount of output capacitance required for a given peak-to-peak output ripple voltage is determined by Equation 3:

$$C_{min} = \frac{I_{OUT} \times \{1 - D \times [V_{IN(max)}]\}}{f_{SW} \times V_{PP}} \quad (3)$$

In this design, using a single 22- μ F ceramic capacitor limits the ripple voltage to 17 mV_{PP} with a 6-V input. Using another 22- μ F ceramic capacitor on the input limits the input ripple voltage to similar levels.

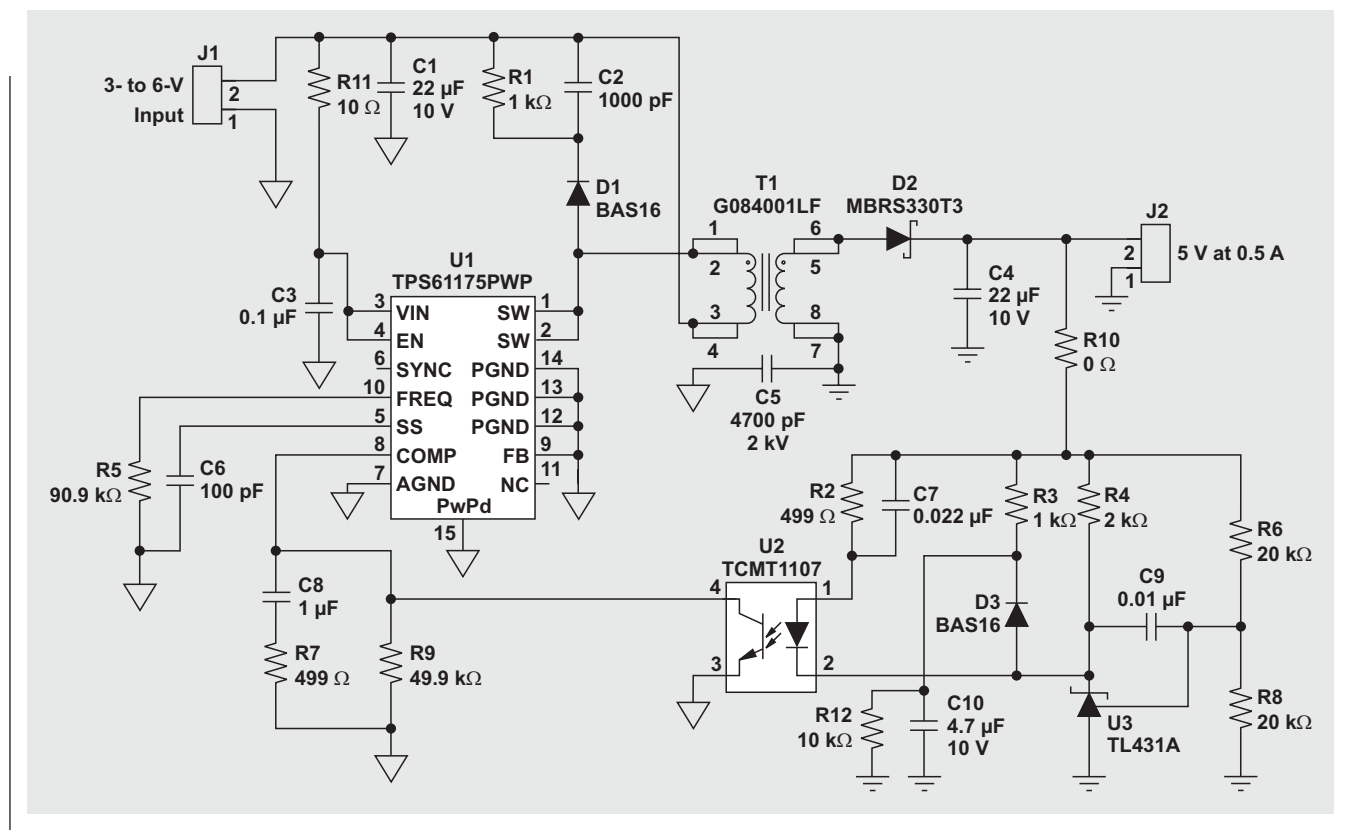
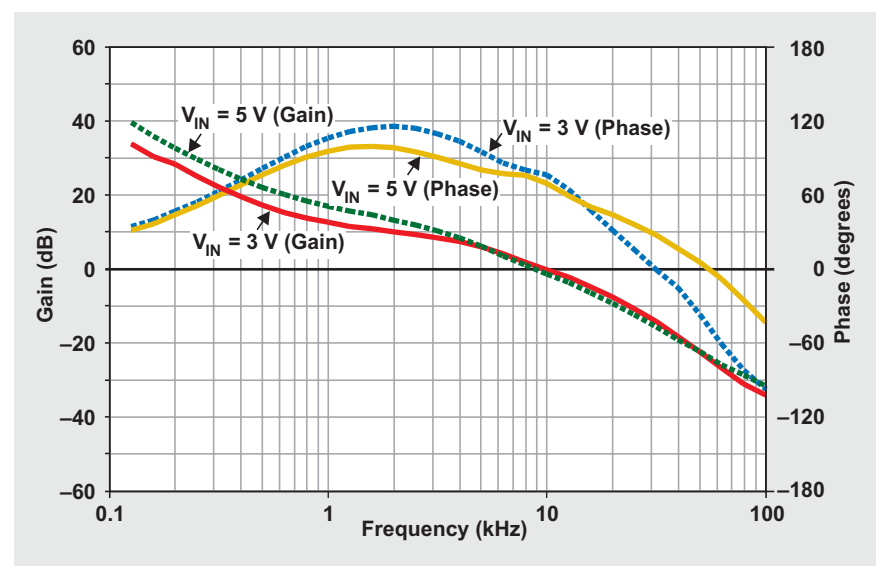
Figure 1. TPS61175 boost controller used in simple isolated flyback


Figure 1 shows a schematic for this power-supply design. The TPS61175 contains a transconductance error amplifier. Normally, in nonisolated applications, the output voltage is fed back through a resistor divider to the feedback pin (FB, or pin 9). For an isolated feedback, the feedback pin must be grounded. This turns the output of the transconductance amplifier, located at the COMP pin, into a 130- μ A current source. Connecting a 49.9-k Ω resistor (R9) from the COMP pin to ground allows the optocoupler to control the voltage of the COMP pin over its entire dynamic range (0.75 to 3 V).

The value of R2 must be small enough to allow the TI TL431 to sufficiently drive the optocoupler. The DC gain of the optocoupler circuit is determined by the current-transfer ratio (CTR), R2, and R9. Because the optocoupler needs to drive only 130 μ A, the CTR is relatively low (approximately 10%), but the 100:1 ratio of R9 to R2 gives the optocoupler circuit a total DC gain of 20 dB. C8 and R7 were added to attenuate the gain and allow the loop to

Figure 2. The optocoupler limits the bandwidth to around 10 kHz

cross near 10 kHz. C8 and R9 form a pole at 30 Hz, while C8 and R7 form a zero at 3 kHz. This lowers the gain by 40 dB at frequencies above 3 kHz.

Figure 2 shows Bode plots of the feedback loop at full rated load for input voltages of 3 and 5 V. The response

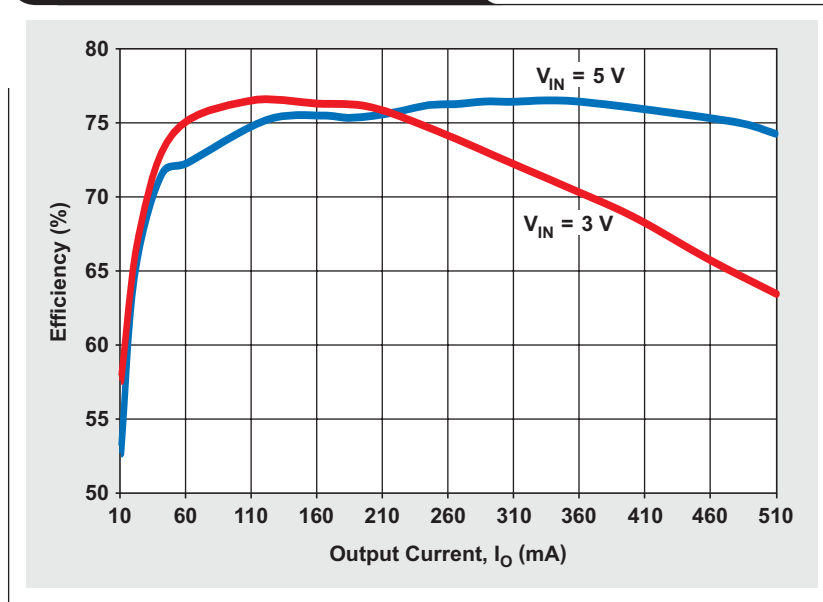
Figure 3. Efficiency with a 5-V input

was measured by breaking the loop and injecting a disturbance at R10. In the power stage, the load resistance and output capacitance form a pole at 700 Hz. This pole is compensated for by the zero of the TL431 circuit, formed by the values of C9 and R6. An additional zero was added at 30 kHz by placing C7 in parallel with R2. This zero helps negate the limited bandwidth of the optocoupler and increases the phase margin.

The efficiency of this design is shown in Figure 3. With a typical ON resistance of 130 m Ω , the internal MOSFET contributes around 850 mW of conduction losses with a 5-V input. The output diode dissipates approximately 200 mW. The remaining loss can be attributed to switching losses, bias loss in the TPS61175 and TL431, and losses in the snubber.

This simple design can be placed in a small amount of board space. Figure 4 shows the parts placement for this design on a single-sided PWB. The design consumes a total of 1.5 in² on one side of the board.

This simple and compact design demonstrates how integrated boost converters, usually relegated to portable applications, can be leveraged in isolated auxiliary supplies. This example showed how to use the TPS61175 with a low input voltage. With a 40-V rating on the drain of the internal FET, and a maximum input-voltage rating of 18 V, this design could be adjusted to work with a 12-V input, with an internally set peak-current limit of 3 A.

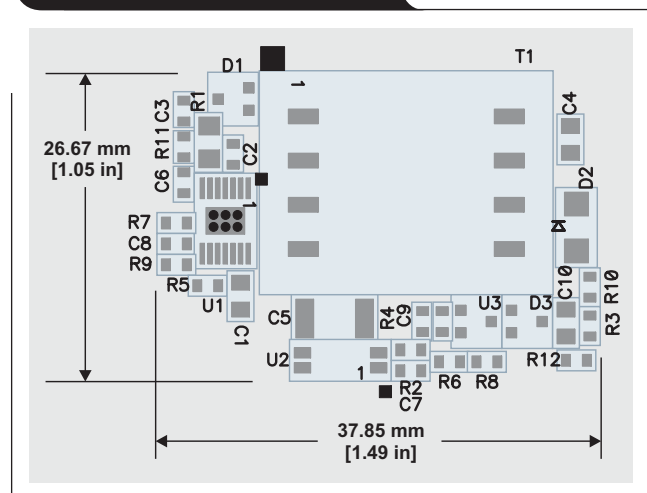Figure 4. Typical PWB layout

Related Web sites

power.ti.com

www.ti.com/sc/device/TPS61175

www.ti.com/sc/device/TL431

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI Semiconductor KnowledgeBase Home Page

support.ti.com/sc/knowledgebase

Product Information Centers

Americas Phone +1(972) 644-5580

Brazil Phone 0800-891-2616

Mexico Phone 0800-670-7544

Fax +1(972) 927-6377
Internet/Email support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone

European Free Call 00800-ASK-TEXAS
(00800 275 83927)
International +49 (0) 8161 80 2121
Russian Support +7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax +(49) (0) 8161 80 2045
Internet support.ti.com/sc/pic/euro.htm

Japan

Fax International +81-3-3344-5317
Domestic 0120-81-0036

Internet/Email International support.ti.com/sc/pic/japan.htm
Domestic www.tij.co.jp/pic

Asia

Phone

International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010

Fax +886-2-2378-6808
Email tiasia@ti.com or ti-china@ti.com
Internet support.ti.com/sc/pic/asia.htm

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as TI or its management "believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

E093008

All trademarks are the property of their respective owners.