

PMP6014
TPS92074
120Vac Non Dimmable 8W LED Driver Reference
Design



December, 2013

120Vac Non Dimmable 8W LED Driver Reference Design

1 Introduction

This TPS92074 reference design presents the TPS92074 controller driving a 30V string of LEDs at 250mA in a buck configuration. It is a non dimmable reference design.

2 Description

This reference design provides a high-brightness LED driver based on the TPS92074. It is designed to operate with an input voltage in the range of 90VAC to 132VAC with a 120 VAC nominal input voltage. This design is set up for a 250mA output current with an output voltage range of 25 V to 35 V.

2.1 *Typical Applications*

This converter design describes an application of the TPS92074 as an LED driver with the specifications listed below. For applications with a different output voltage or current range refer to the TPS92074 datasheet.

2.2 *Features*

2.2.1 Connector Description

This section describes the connectors of the reference design board.

2.2.1.1 J1

This connector is for the AC input to the board. Use the screw down terminal to connect Line and Neutral to the circuit.

2.2.1.2 J2, J3

This connector is for the LED load. J2 is connected to LED+ and J3 is connected to LED-

3 Electrical Performance Specifications

Table 1: TPS92074 120Vac Non Dimmable Buck Electrical Performance Specifications

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNITS
Input Characteristics					
Voltage range	Normal operation	90	120	132	VAC
Maximum input current	At 120VAC 60Hz input voltage		0.11		A
Output Characteristics					
Output voltage, VOUT		25	30	35	V
Output load current, IOUT	Input voltage = 120V 60Hz, Load = 30V LED	240	250	260	mA
Output current accuracy	Input voltage = 120V 60Hz, Load = 30V LED		< ±5		%
Output current ripple	Input voltage = 120V 60Hz, Load = 30V LED		<150		mApp
Output current line regulation	Input voltage 90V to 132V 60Hz, Load = 30V LED		< ±5		%
Systems Characteristics					
Switching frequency	Input voltage = 120V 60Hz, Load = 30V LED		55		kHz
Power Factor	Input voltage = 120V 60Hz, Load = 30V LED		0.97		
Efficiency	Input voltage = 120V 60Hz, Load = 30V LED		88		%

4 Schematic

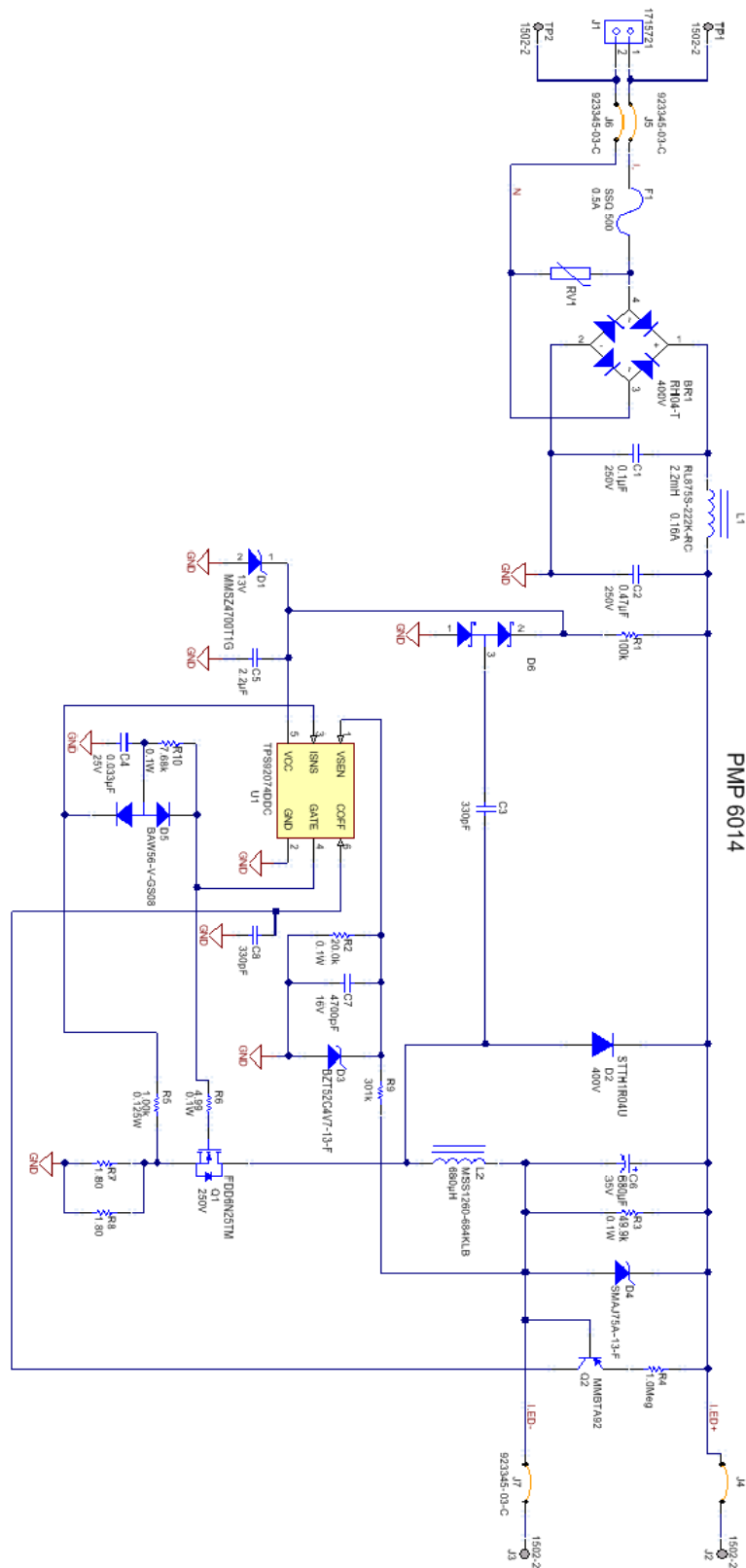


Figure 1: TPS92074 120Vac Non Dimmable 8W LED Driver Schematic

5 Performance Data and Typical Characteristic Curves

Figures 2 through 11 present typical performance curves for TPS92074 120Vac Non Dimmable 8W LED Driver

5.1 Efficiency

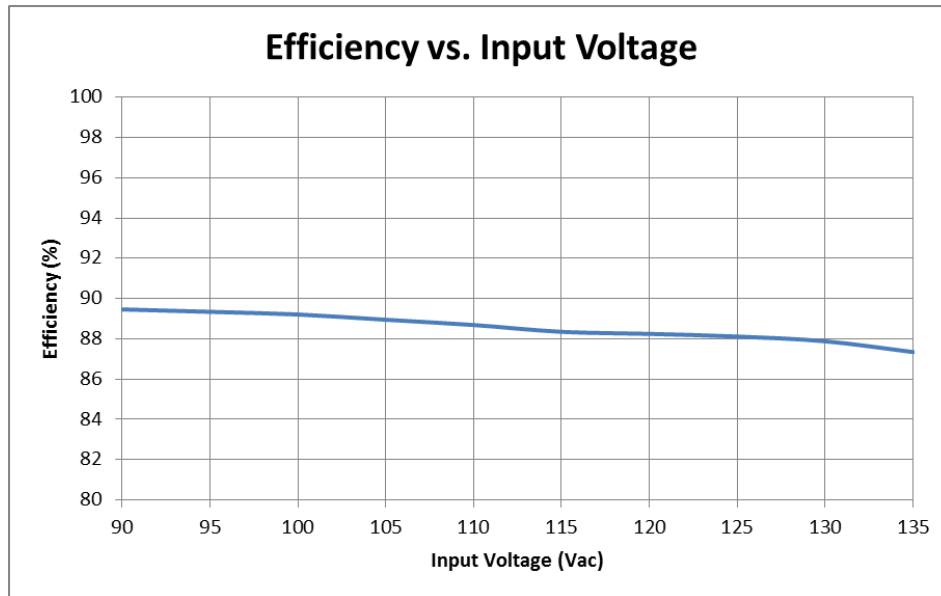


Figure 2: Efficiency with 30V LED stack

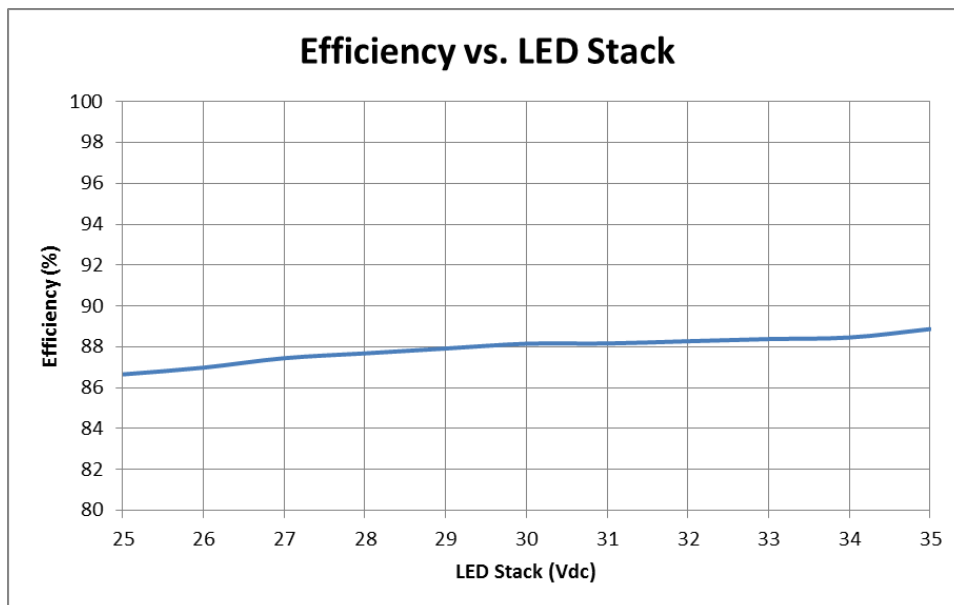


Figure 3: Efficiency at 120Vac 60Hz input

5.2 Current Regulation

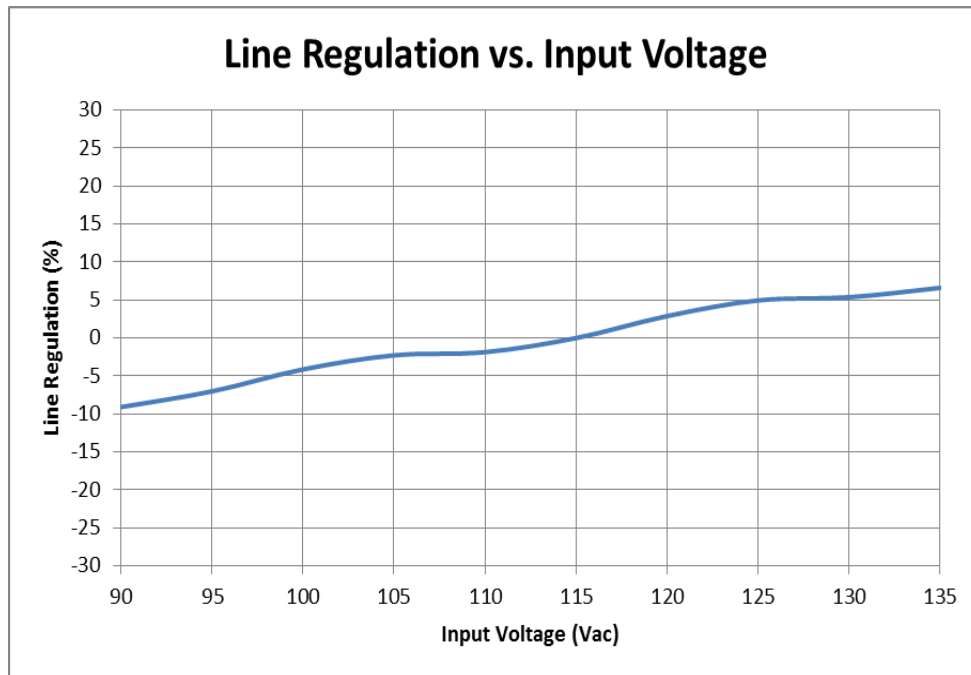


Figure 4: Line Regulation 30V LED stack

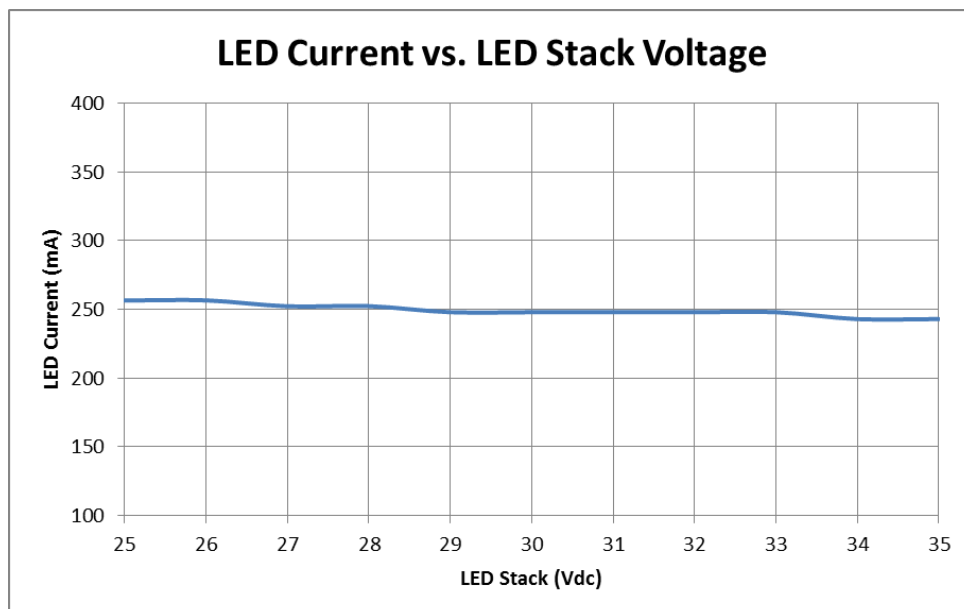


Figure 5: LED Current vs. LED stack voltage 120Vac 60Hz input

5.3 Power Factor

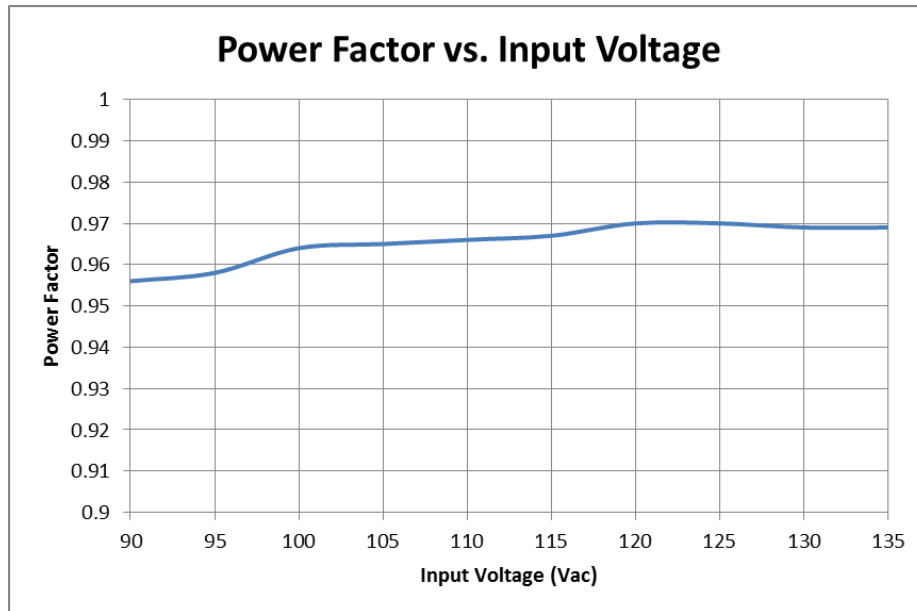


Figure 6: Power Factor 120Vac 60Hz input 30V LED stack

5.4 Waveforms

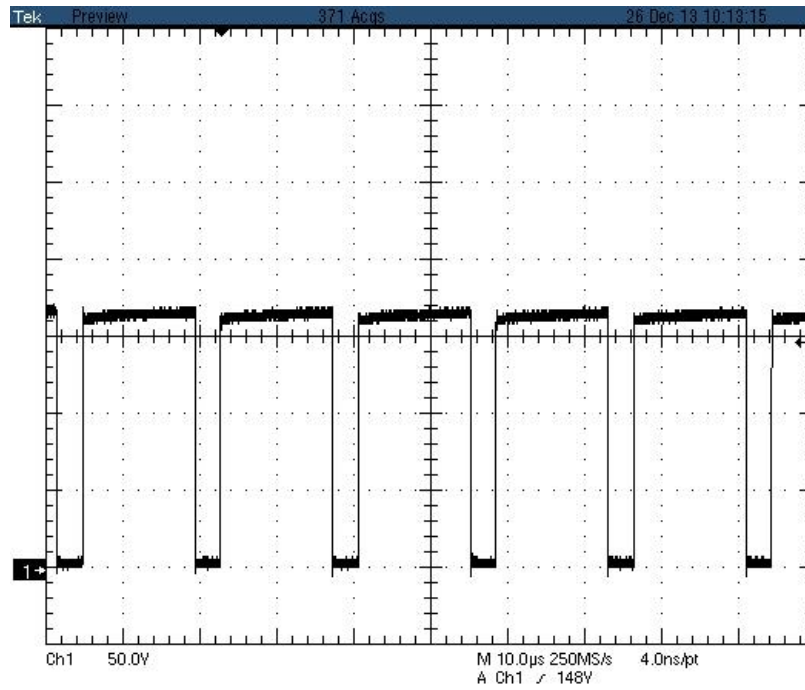


Figure 7: Q1 Drain Waveform at 120Vac 60Hz input

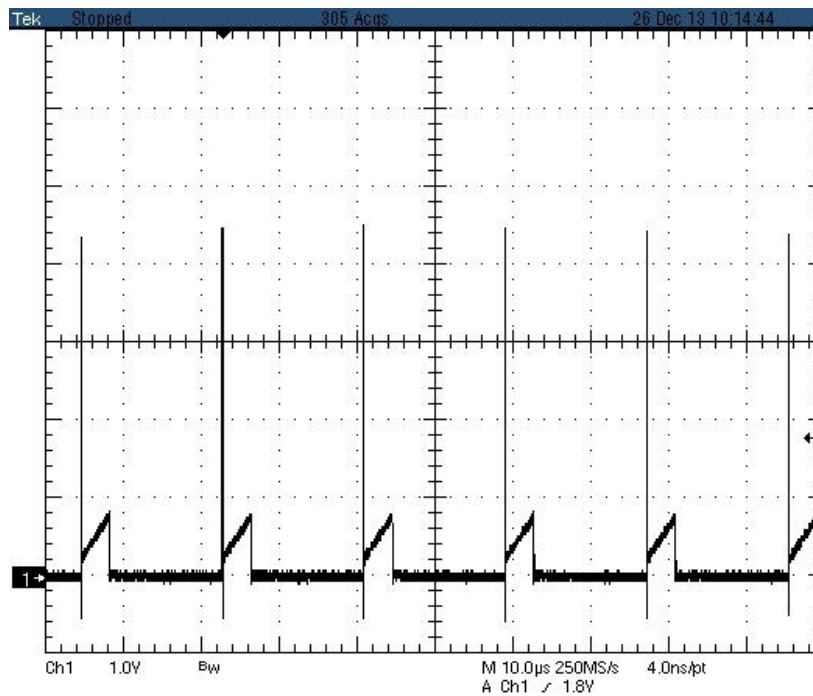


Figure 8: Current sense voltage at 120Vac 60Hz input


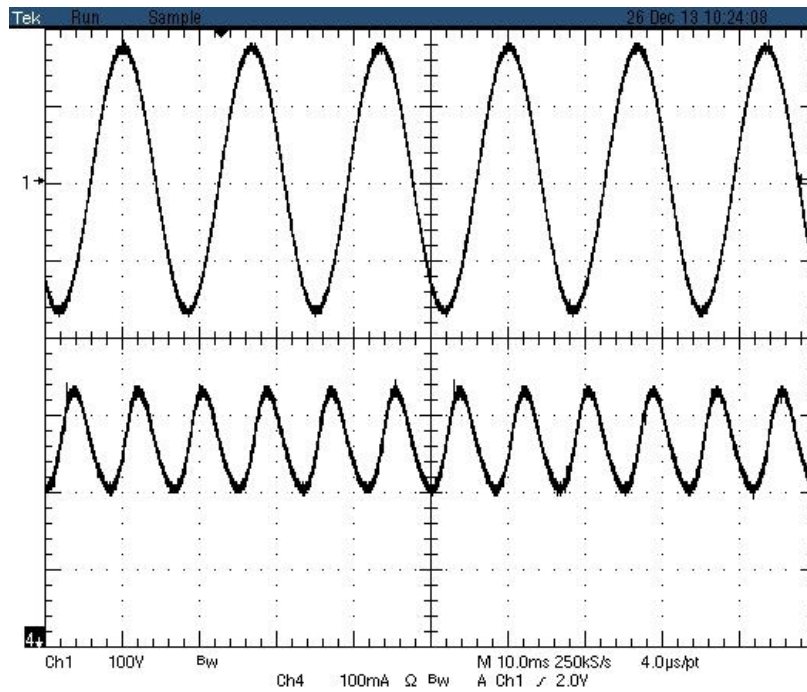



Figure 9: Ch1 Input AC Voltage Ch4 Output LED Current
120Vac 60Hz input 30V LED stack

5.5 EMI Performance

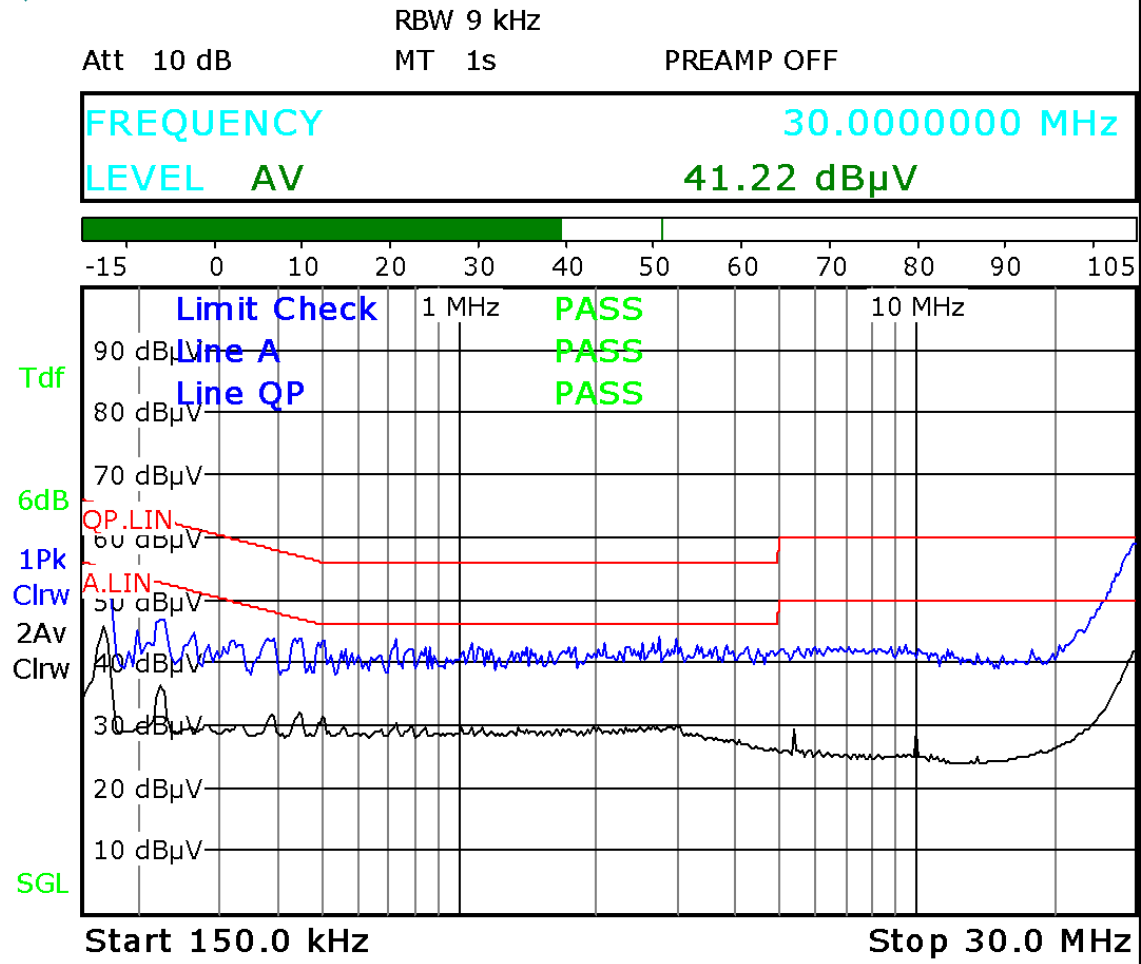

Date: 19.DEC.2013 06:05:45

Figure 10: 120VAC Line-Conducted Average EMI Scan

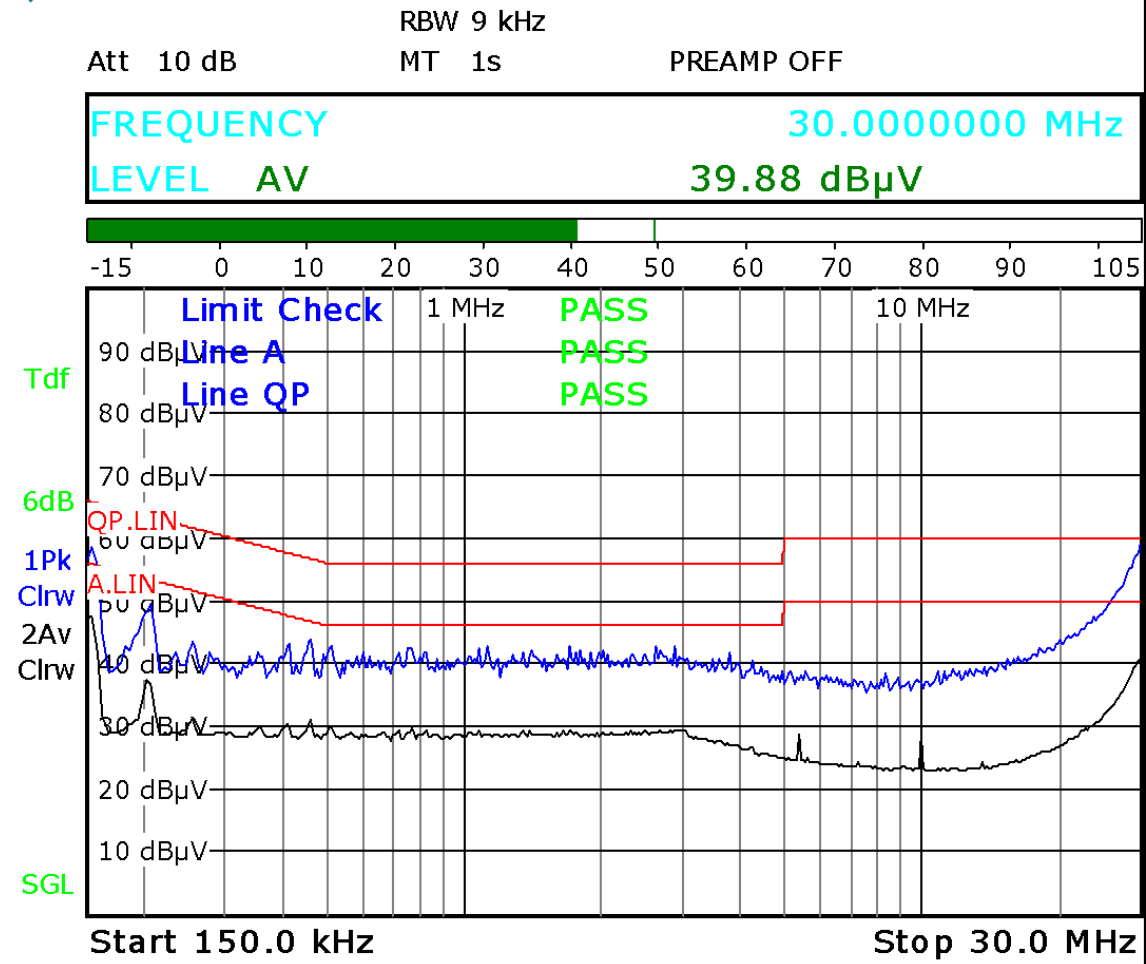

Date: 19.DEC.2013 23:48:01

Figure 11: 120VAC Neutral-Conducted Average EMI Scan

6 TPS92074 120Vac Non Dimmable 8W LED Driver Reference Design PCB layout

The following figures (Figure 12 through Figure 13) show the design of the printed circuit board.

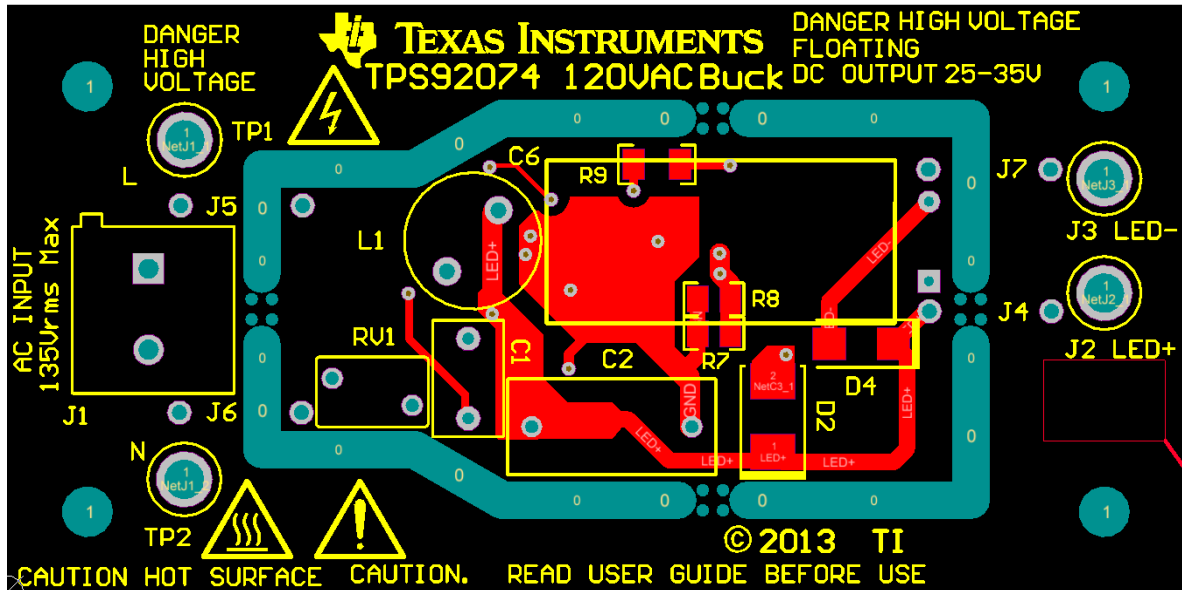


Figure 12: Top Layer and Top Overlay (Top view)

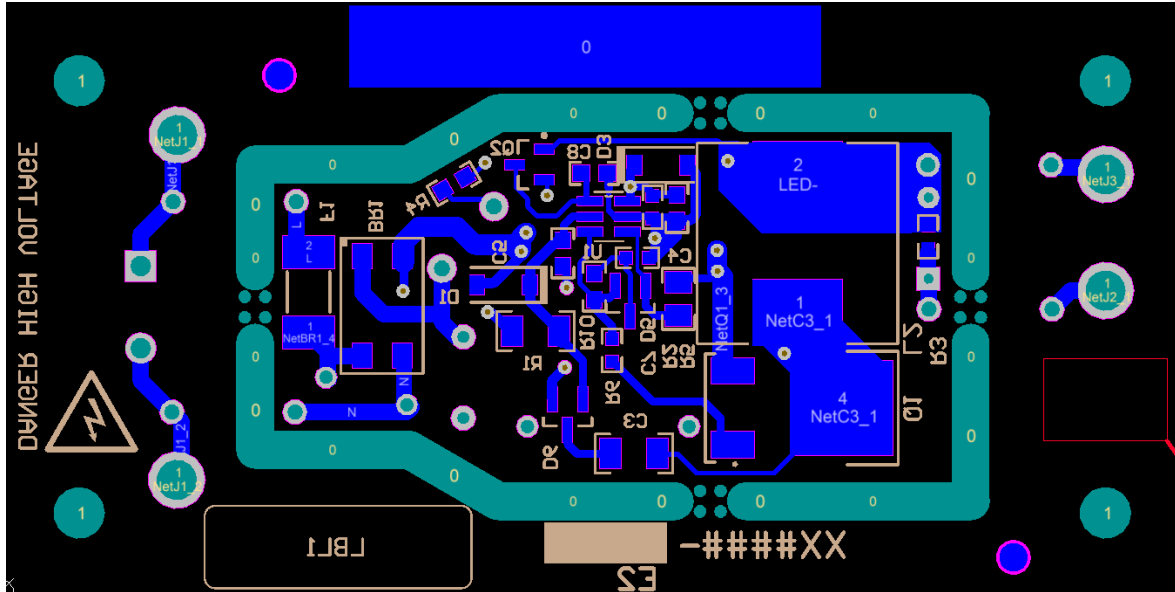


Figure 13: Bottom Layer and Bottom Overlay (Bottom view)

Bill of Materials

Designator	Quantity	Value	Description	Package	PartNumber	Manufacturer
BR1	1	400V	Diode, Switching-Bridge, 400V, 0.5A, MiniDip	4-SMD	RH04-T	Diodes Inc
C1	1	0.1uF	CAP, Film, 0.1uF, 250V, +/-5%, TH	7.3x9.5x4.5mm	B32529C3104K	EPCOS Inc
C2	1	0.47uF	CAP, Film, 0.47uF, 250V, +/-10%, TH	13x12x6mm	B32521C3474K	EPCOS Inc
C3	1	330pF	CAP, CERM, 330pF, 630V, +/-5%, C0G/NP0, 1206	1206	C3216C0G2J331J	TDK
C4	1	0.033uF	CAP, CERM, 0.033uF, 25V, X7R, 20%, 0603	0603 (1608 Metric)	C1608X7R1E333M	TDK Corporation
C5	1	2.2uF	CAP, CERM, 2.2uF, 16V, +10/-%, X5R, 0603	0603	GRM188R61C225KE15	MuRata
C6	1	680uF	CAP, Alum, 680uF, 35V, +/-20%, Radial	Radial, Can	EEU-FR1V681	Panasonic
C7	1	4700pF	CAP, CERM, 4700pF, 16V, X7R, 10%, 0603	0603	C0603C472K4RACTU	Kemet
C8	1	330pF	CAP, CERM, 330pF, 50V, +1/-%, C0G/NP0, 0603	0603	06035A221FAT2A	AVX
D1	1	13V	Diode, Zener, 13V, 500mW, SOD-123	SOD-123	MMSZ4700T1G	ON Semiconductor
D2	1	400V	Diode, Ultra Fast, 400V, 1A, SMB	DO-214AA, SMB	STTH1R04U	STMicroelectronics
D3	1	4.7V	Diode, Zener, 4.7V, 500mW, SOD-123	SOD-123	BZT52C4V7-13-F	Diodes Inc
D4	1	75V	Diode, TVS, 75V, 400W, SMA	DO-214AC, SMA	SMAJ75A-13-F	Diodes Inc
D5	1	75V	Diode, Sw Dual, Common Anode, 75V, 350mW, SOT23	SOT-23-3	BAW56-V-GS08	Vishay
D6	1	30V	Diode, Schottky, 30V, 0.2A, SOT-23	SOT-23	BAT54S-7-F	Diodes Inc.
F1	1	0.5A	Fuse, 0.5A, 125V, SMD	6.10x2.54x2.54mm	SSQ 500	Bel Fuse
L1	1	2.2mH	Inductor, Shielded, Ferrite, 2.2mH, 0.16A, 7.56 ohm, TH	Dia 7.8 x 7.5mm	RL875S-222K-RC	Bourns
L2	1	680uH	Inductor, Shielded Drum Core, Ferrite, 680uH, 0.8A, 0.87 ohm, SMD	12x6x12mm	MSS1260T-474KLB	Coilcraft
Q1	1	250V	MOSFET, N-CH, 250V, 4.4A, DPAK	TO-252-3, DPak	FDD6N25TM	Fairchild
Q2	1	300V	Transistor, PNP, 300V, 0.2A, SOT-23	SOT-23	MMBTA92	Fairchild
R1	1	100k	RES, 100k ohm, 1%, 0.25W, 1206	1206	STD	STD
R2	1	20.0k	RES, 20.0k ohm, 1%, 0.1W, 0603	0603	STD	STD
R3	1	49.9k	RES, 49.9k ohm, 1%, 0.1W, 0603	0603	STD	STD
R4	1	1.00M	RES, 1.00meg ohm, 1%, 0.1W, 0603	0603	STD	STD
R11	1	1.00k	RES, 1.00k ohm, 1%, 0.125W, 0805	0805	STD	STD
R6	1	4.99	RES, 4.99 ohm, 1%, 0.1W, 0603	0603	STD	STD
R7	1	1.80	RES, 1.80 ohm, 1%, 0.125W, 0805	0805	STD	STD
R8	1	1.80	RES, 1.80 ohm, 1%, 0.125W, 0805	0805	STD	STD
R9	1	301k	RES, 301k ohm, 1%, 0.25W, 1206	1206	STD	STD
R10	1	7.68k	RES, 7.68k ohm, 1%, 0.1W, 0603	0603	STD	STD
RV1	1	200V	Varistor, 200V, 600A, 5MM Radial, TH	7x4.4x10mm Radial	ERZ-V05D201	Panasonic
U1	1		Non-Isolated, Buck PFC LED Driver with Digital Reference Control	DDC0006A	TPS92074DDC	Texas Instruments

EVALUATION BOARD/KIT/MODULE (REF DESIGN) WARNINGS, RESTRICTIONS AND DISCLAIMER

For Feasibility Evaluation Only, in Laboratory/Development Environments. The REF DESIGN is not a complete product. It is intended solely for use for preliminary feasibility evaluation in laboratory / development environments by technically qualified electronics experts who are familiar with the dangers and application risks associated with handling electrical / mechanical components, systems and subsystems. It should not be used as all or part of a production unit.

Your Sole Responsibility and Risk. You acknowledge, represent and agree that:

1. You have unique knowledge concerning Federal, State and local regulatory requirements (including but not limited to Food and Drug Administration regulations, if applicable) which relate to your products and which relate to your use (and/or that of your employees, affiliates, contractors or designees) of the REF DESIGN for evaluation, testing and other purposes.
2. You have full and exclusive responsibility to assure the safety and compliance of your products with all such laws and other applicable regulatory requirements, and also to assure the safety of any activities to be conducted by you and/or your employees, affiliates, contractors or designees, using the REF DESIGN. Further, you are responsible to assure that any interfaces (electronic and/or mechanical) between the REF DESIGN and any human body are designed with suitable isolation and means to safely limit accessible leakage currents to minimize the risk of electrical shock hazard.
3. Since the REF DESIGN is not a completed product, it may not meet all applicable regulatory and safety compliance standards (such as UL, CSA, VDE, CE, RoHS and WEEE) which may normally be associated with similar items. You assume full responsibility to determine and/or assure compliance with any such standards and related certifications as may be applicable. You will employ reasonable safeguards to ensure that your use of the REF DESIGN will not result in any property damage, injury or death, even if the REF DESIGN should fail to perform as described or expected.

Certain Instructions. Exceeding the specified REF DESIGN ratings (including but not limited to input and output voltage, current, power, and environmental ranges) may cause property damage, personal injury or death. If there are questions concerning these ratings please contact a TI field representative prior to connecting interface electronics including input power and intended loads. Any loads applied outside of the specified output range may result in unintended and/or inaccurate operation and/or possible permanent damage to the REF DESIGN and/or interface electronics. Please consult the REF DESIGN User's Guide prior to connecting any load to the REF DESIGN output. If there is uncertainty as to the load specification, please contact a TI field representative. During normal operation, some circuit components may have case temperatures greater than 60°C as long as the input and output ranges are maintained at nominal ambient operating temperature. These components include but are not limited to linear regulators, switching transistors, pass transistors, and current sense resistors which can be identified using the REF DESIGN schematic located in the REF DESIGN User's Guide. When placing measurement probes near these devices during normal operation, please be aware that these devices may be very warm to the touch.

Agreement to Defend, Indemnify and Hold Harmless. You agree to defend, indemnify and hold TI, its licensors and their representatives harmless from and against any and all claims, damages, losses, expenses, costs and liabilities (collectively, "Claims") arising out of or in connection with any use of the REF DESIGN that is not in accordance with the terms of this agreement. This obligation shall apply whether Claims arise under the law of tort or contract or any other legal theory, and even if the REF DESIGN fails to perform as described or expected.

Safety-Critical or Life-Critical Applications. If you intend to evaluate TI components for possible use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, such as devices which are classified as FDA Class III or similar classification, then you must specifically notify TI of such intent and enter into a separate Assurance and Indemnity Agreement.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.