

## *Advanced Low Power Reference Design*

Florian Feckl

Low Power DC/DC, ALPS

# Battery Runtime Extension for GSM High Power Applications

## User's Guide & Test Report

### CIRCUIT DESCRIPTION

In this Reference Design, the TPS61280 Boost Converter with integrated Bypass Switch powers a Radio Frequency Power Amplifier (RFPA) in GSM Mode.


The TPS61280 RFPA Combo Board enables longer battery runtime by applying a user defined minimum supply voltage for a Radio Frequency system. The whole board features a pre-developed and tested RF compliant power application.

### BENEFITS

- Pre-Developed RF Power Application
- Longer Battery runtime
- Avoiding system load dump
- Extended Voltage Range for 2G High Power operation
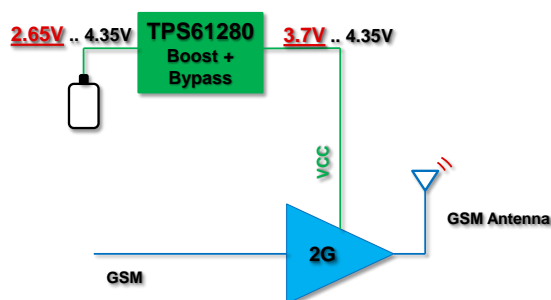
### LINKS

[TPS61280 Product Page](#)  
[TPS61280 Evaluation Module](#)  
[E2E Support Forum](#)



## TABLE OF CONTENTS

|          |   |           |
|----------|---|-----------|
| <b>1</b> | <b>Introduction .....</b>                   | <b>4</b>  |
| <b>2</b> | <b>Board Description .....</b>              | <b>5</b>  |
| 2.1      | Power Block Diagram .....                   | 6         |
| 2.2      | Interface Block Diagram .....               | 7         |
| 2.3      | User Interface Connection .....             | 8         |
| 2.4      | Assembly drawing .....                      | 9         |
| 2.5      | Interface Connectors .....                  | 10        |
| <b>3</b> | <b>Schematics .....</b>                     | <b>11</b> |
| <b>4</b> | <b>Layout .....</b>                         | <b>14</b> |
| 4.1      | Layer Stack-up .....                        | 14        |
| 4.2      | Layer routing .....                         | 15        |
| <b>5</b> | <b>Measurement Setup .....</b>              | <b>19</b> |
| 5.1      | Block Diagrams .....                        | 19        |
| <b>6</b> | <b>GSM Measurements .....</b>               | <b>20</b> |
| 6.1      | Power vs. Time, PvT .....                   | 20        |
| 6.2      | Output Radio Frequency Spectrum, ORFS ..... | 21        |
| 6.3      | Receive Band Noise, RXBN .....              | 22        |
| <b>7</b> | <b>Appendix .....</b>                       | <b>24</b> |
| 7.1      | References .....                            | 24        |
| 7.2      | Related Links and Web sites .....           | 24        |
| 7.3      | Acronyms .....                              | 24        |

## LIST OF FIGURES

|  |    |
|--|----|
| Figure 1: Picture of the board including connections.....                    | 5  |
| Figure 3: Board Power Block Diagram .....                                    | 6  |
| Figure 2: Reference Design Interface Block Diagram.....                      | 7  |
| Figure 11: Assembly Drawing .....  | 9  |
| Figure 4: SKY77629 Schematic .....   | 11 |
| Figure 5: TPS61280 Schematic .....   | 12 |
| Figure 6: Decoupling Circuits Schematic.....                                 | 12 |
| Figure 7: 20-Pin-Connector Interface Schematic.....                          | 13 |
| Figure 8: TPS61280 I/O Connectors .....                                      | 13 |
| Figure 9: CAD Board RF Stack-up .....  | 14 |
| Figure 10: RF Stack-up.....  | 14 |
| Figure 12: Corresponding Layer set.....                                      | 15 |
| Figure 13: Layer 1, Top.....   | 15 |
| Figure 14: Layer 2.....  | 16 |
| Figure 15: Layer 3.....  | 16 |
| Figure 16: Layer 4.....  | 17 |
| Figure 17: Layer 5.....  | 17 |
| Figure 18: Layer 6, Bottom.....  | 18 |
| Figure 19: RXBN Test Setup.....  | 19 |
| Figure 20: PvT & ORFS Test Setup .....                                       | 19 |
| Figure 22: PvT, 34dBm $P_{OUT}$ .....  | 20 |
| Figure 23: ORFS, 34dBm $P_{OUT}$ .....                                       | 21 |
| Figure 24: Receive Band Noise 34dBm $P_{OUT}$ , several input voltages ..... | 22 |
| Figure 25: Receive Band Noise 34dBm $P_{OUT}$ , Spread Spectrum effect ..... | 23 |

## **1 Introduction**

More and more application uses batteries with a low cut off voltage. Such battery types can be Li-Ion (Nickel-Rich as well as Silicon Anode) or LiFePO4 chemistry types. This can be a great benefit for the runtime of a handset systems' charge cycle. For some subsystems, however, this means that the supply voltage can go beyond their necessary optimum supply range.

One example is a GSM transmitter in a battery powered system. This kind of RFPA (Radio Frequency Power Amplifier) requires a certain window for an optimized slot transmission on the one hand. On the other hand, a GSM pulse can cause a line dump due to the high pulse load.


The TPS61280 is a Boost Converter with adjustable input current limit. Its input voltage range goes from 2.3V to 4.8V, which covers typical battery voltage ranges. This device has an additional bypass switch integrated and features a seamless transition between bypass and boost mode.

The device is designed as a pre-regulator to guarantee a minimum supply voltage, especially for noise sensitive applications.

The TPS61280 RFPA Combo Reference Design gives a pre developed example how to supply the power rail of a GSM RFPA. The Design shows the "care-about's" in terms of analog circuitry as well as layout and board design.

## 2 **Board Description**

This Evaluation Board contains a fully functional TPS61280 Boost + Bypass and a SKY77629 Multimode Power Amplifier (MMPA) solution. The TPS61280 can supply all applicable power rails of the SKY77629. This Reference Design focuses on GSM communication. This means the main care was taken on the GSM Amplifier supply rail. Figure 1 is a picture of the whole reference design in a test setup.

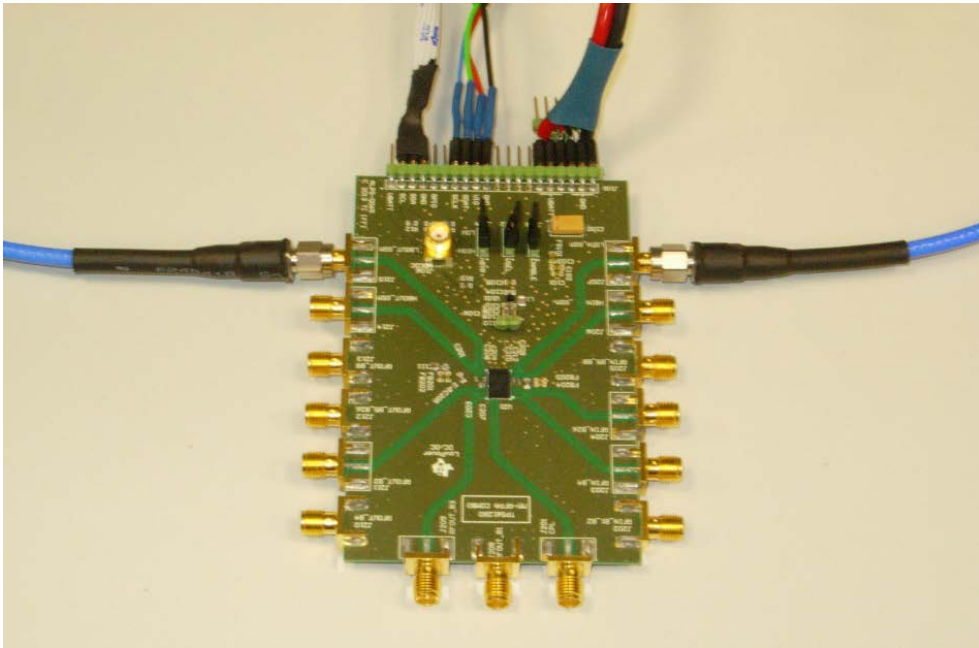

**Figure 1: Picture of the board including connections**

## 2.1 Power Block Diagram

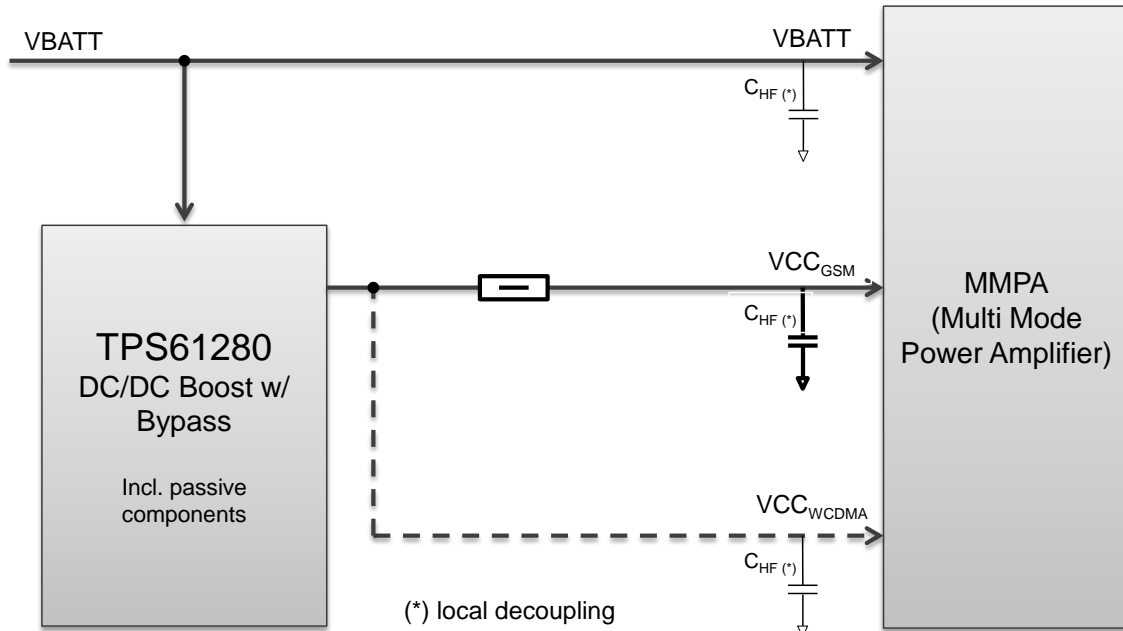


Figure 2: Board Power Block Diagram

Figure 2 shows the board's power block diagram. The TPS61280 supplies the  $V_{CC}$  rails for GSM and WCDMA bands. Due to the focus on GSM, the WCDMA rail is dotted. All rails are locally decoupled close to the PA.

As LC-Filter a ferrite bead in combination with the local coupling caps is used. The ferrite bead used is a BLM18PG121SN1 from Murata with a DC resistance of 50mΩ.

## 2.2 Interface Block Diagram

Figure 3 shows the Block Diagram of the whole Reference Design.

The power parts are illustrated in blue. The input rail  $V_{BATT}$  supplies the Boost + Bypass Converter as well as the control rail of the MMPA.

The RF path is figured in green; with the focus is on the 2G Low Band. The communication interfaces are drawn in red.

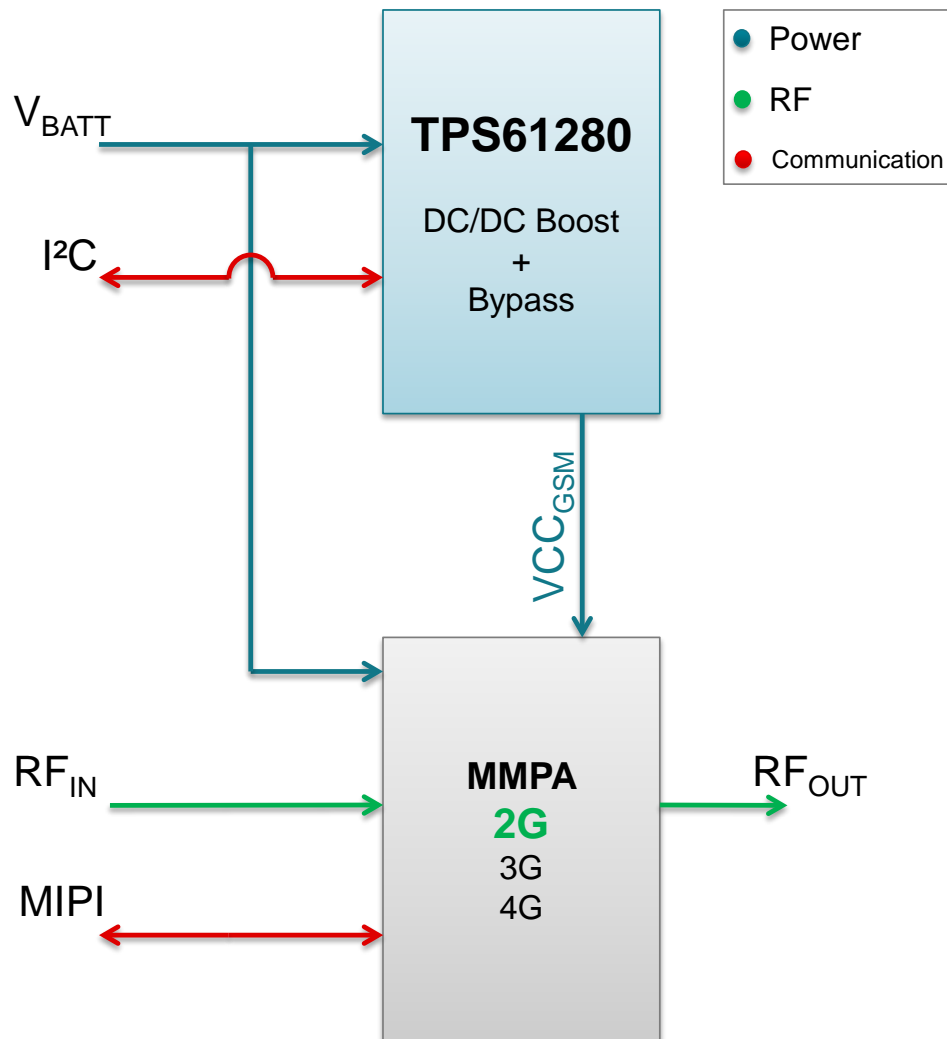


Figure 3: Reference Design Interface Block Diagram

## 2.3 User Interface Connection

The TPS61280 can be controlled via an I<sup>2</sup>C Interface. Therefore a USB connection interface is needed. This Interface is available on the Texas Instruments' [tools web page](#).

TPS61280 Evaluation Board User's Guide gives a guideline how to connect and interact with the device. This Users Guide can be seen through the following link: <http://www.ti.com/lit/ug/slvu955/slvu955.pdf>

The Combo Board enables the user to access all available interfaces, from an RF, control signal and power perspective.

The TPS61280 is accessible via the standardized I<sup>2</sup>C Bus. For further information, please see the [TPS61280 Datasheet](#).

The SKY77629 MMPA is able to communicate via the MIPI Interface. For further Information's, please refer to the Skyworks webpage.



## 2.4 Assembly drawing

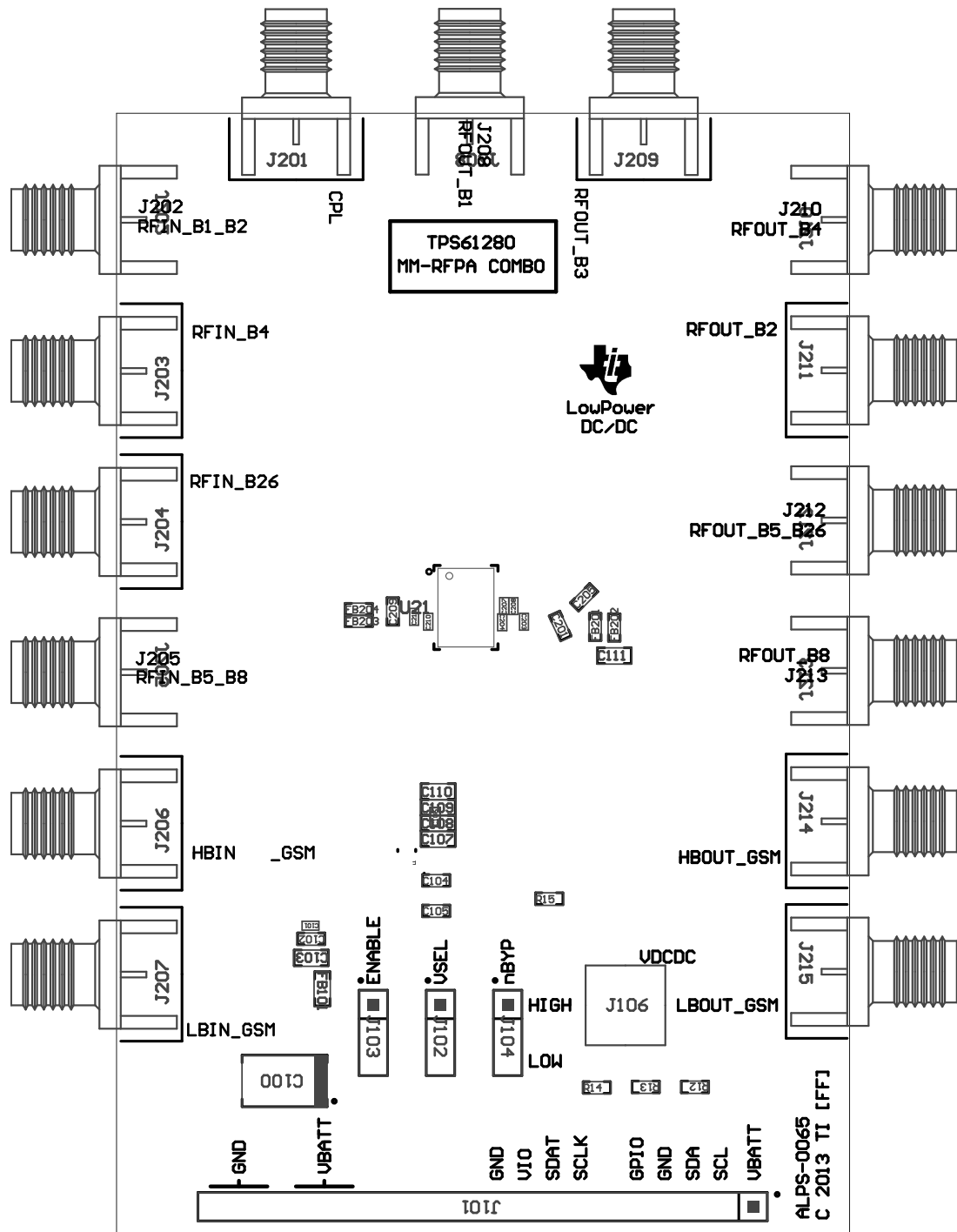


Figure 4: Assembly Drawing

## 2.5 Interface Connectors

| PIN | Name  | Description  | Port direction |
|-----|-------|--|----------------|
| 1   | VBATT | Input (Battery) Voltage, 2.3V to 4.8V                                | Input          |
| 2   |       |  |                |
| 3   | VBATT | Input Voltage Sense Line, Pin is routed close to TPS61280 Input      | Observation    |
| 4   | GND   | GND Voltage Sense Line, Pin is routed close to TPS61280 local ground | Observation    |
| 5   | GND   | GND connection   | Input          |
| 6   |       |  |                |
| 7   |       | n/c  |                |
| ..  |       |  |                |
| 10  |       |  |                |
| 11  | GND   | GND, SKY77629 MIPI Interface   | n/a            |
| 12  | VIO   | Logic Input, SKY77629 MIPI Interface                                 | Input          |
| 13  | SDAT  | Logic Input, SKY77629 MIPI Interface                                 | Input          |
| 14  | SCLK  | Logic Input, SKY77629 MIPI Interface                                 | Input          |
| 15  |       | n/c  |                |
| 16  | GPIO  | TPS61280 GPIO Pin  | Input/Output   |
| 17  | GND   | Ground connection, TPS61280 I <sup>2</sup> C Interface               | n/a            |
| 18  | SDA   | Data Line, TPS61280 I <sup>2</sup> C Interface                       | Input          |
| 19  | SCL   | Clock Line, TPS61280 I <sup>2</sup> C Interface                      | Input          |
| 20  | VBATT | Input Voltage, TPS61280 I <sup>2</sup> C Interface                   | n/a            |

**Table 1: J101 Connector Pin assignment**

| PIN  | Name         | Description                            | Port direction    |
|------|--------------|--|-------------------|
| J106 | VDCDC        | TPS61280 Output Voltage, 50Ohm matched | Observation Point |
| J201 | CPL          |  | n/c               |
| J202 | RFIN_B1_B1   | WCDMA band 1 & 2                       | Input             |
| J203 | RFIN_B4      | WCDMA band 3 & 4                       | Input             |
| J204 | RFIN_B26     | LTE band 26                            | Input             |
| J205 | RFIN_B5_B8   | WCDMA band 5 & 8                       | Input             |
| J206 | HBIN_GSM     | GSM high band                          | Input             |
| J207 | LBIN_GSM     | GSM low band                           | Input             |
| J208 | RFOUT_B1     | WCDMA band 1                           | Output            |
| J209 | RFOUT_B3     | WCDMA band 3                           | Output            |
| J210 | RFOUT_B4     | WCDMA band 4                           | Output            |
| J211 | RFOUT_B2     | WCDMA band 2                           | Output            |
| J212 | RFOUT_B5_B26 | WCDMA band 5 & 26                      | Output            |
| J213 | RFOUT_B8     | WCDMA band 8                           | Output            |
| J214 | HBOUT_GSM    | GSM high band                          | Output            |
| J215 | LBOUT_GSM    | GSM low band                           | Output            |


**Table 2: RF Connector description**

| PIN  | Name | Description              | Port direction |
|------|------|--------------------------|----------------|
| J102 | VSEL | Target voltage selection | Input          |
| J103 | EN   | Device enable/disable    | Input          |
| J104 | /BYP | Forced Bypass operation  | Input          |

**Table 3: TPS61280 Control Connectors**

### 3 Schematics

Figure 5 through Figure 9 illustrate simplified parts of the Reference Design's schematic. For the entire schematic drawing, please refer to the document in the Reference Design web folder.

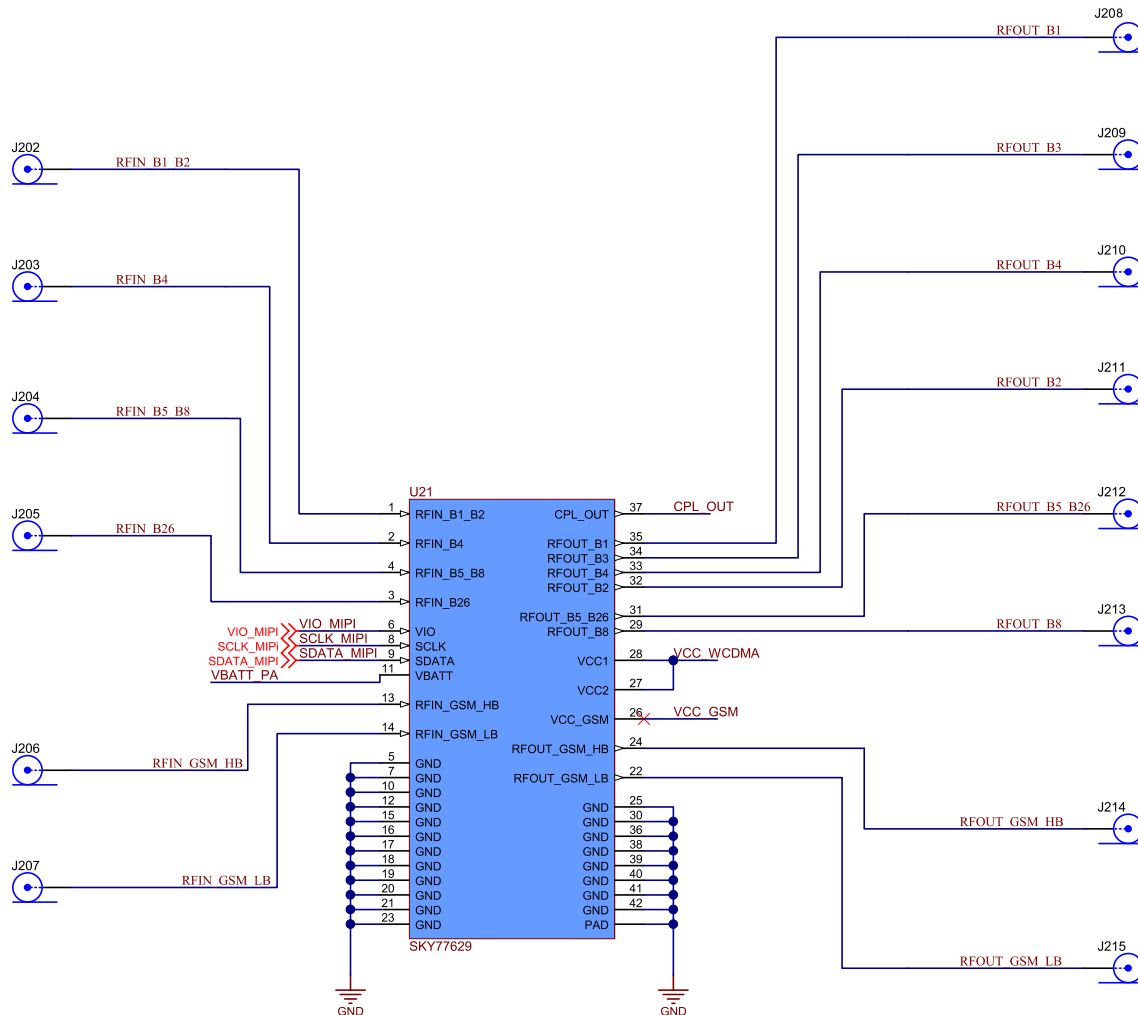

**Figure 5: SKY77629 Schematic**

Figure 5 shows the MMPA's schematic drawing. All RF terminals are lead trough to SMA connectors.

Figure 6 is the illustration of the power stage solution with TPS61280. The output voltage can be monitored via an impedance matched RF connector. The output rail applies several additional capacitor footprints to enable high flexibility.

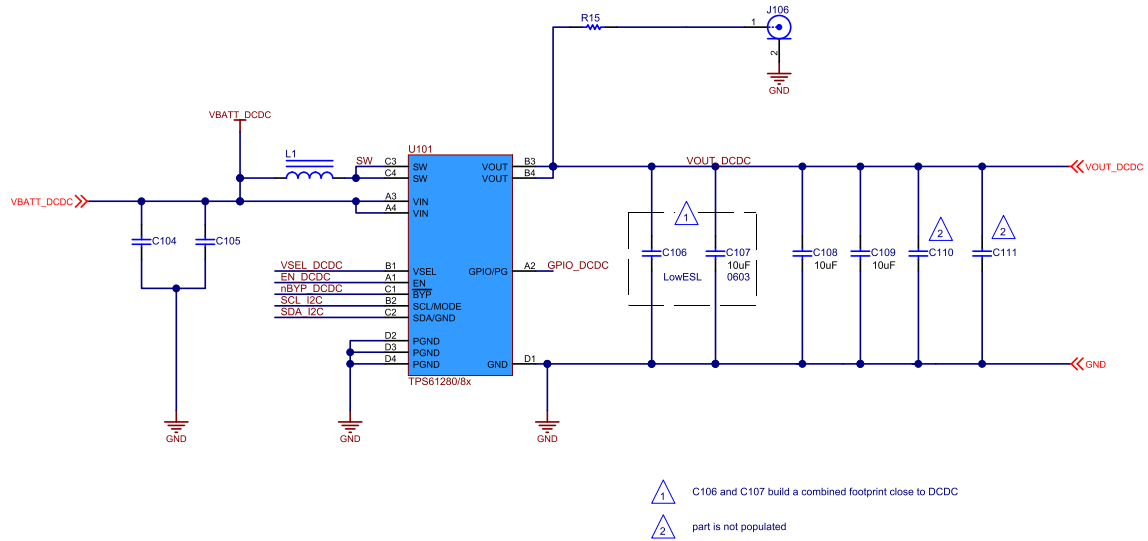
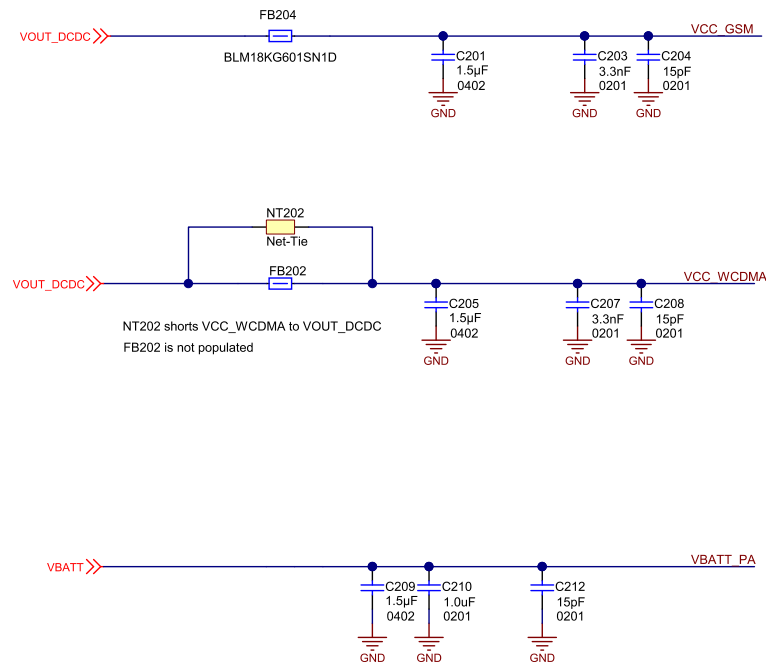
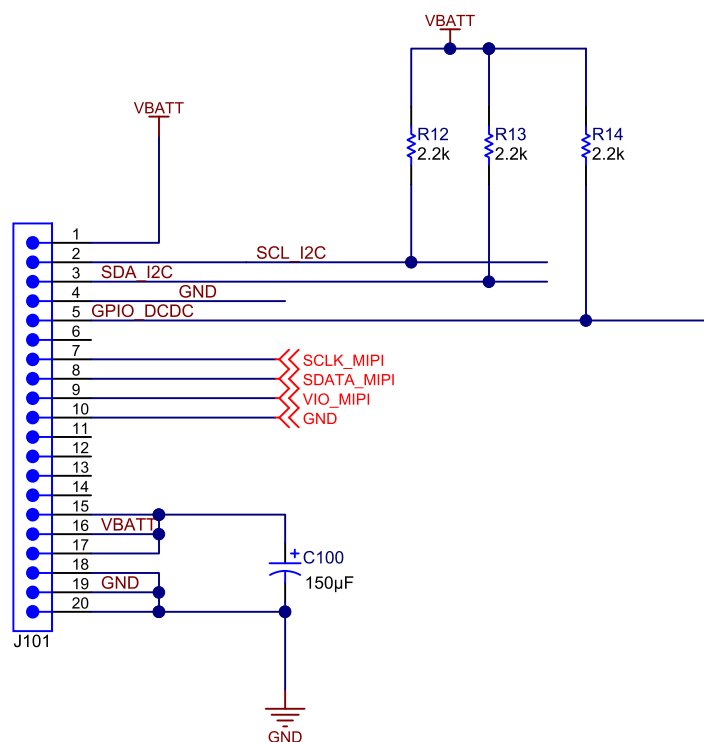
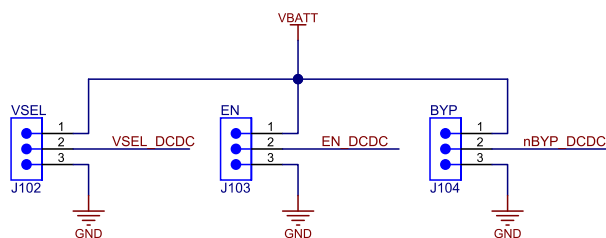

**Figure 6: TPS61280 Schematic**

Figure 7 shows the decoupling circuits applied to all supply rails of the Radio Frequency Power Amplifier. These circuits enable high flexibility in RF compliant power design. Both rails,  $V_{CC;GSM}$  and  $V_{CC;WCDMA}$  do have the ability to add a ferrite bead.


**Figure 7: Decoupling Circuits Schematic**



**Figure 8: 20-Pin-Connector Interface Schematic**



**Figure 9: TPS61280 I/O Connectors**


Figure 8 and Figure 9 show the circuit for the I/O and Power Interface connections. The Pin assignment and a detailed terminal description can be found in section 2.5.

## 4 Layout

This board is designed to apply an optimized RF performance. The 6-layer board stack-up reflects this by a 50Ω matching on the one hand. On the other hand it reflects an industrial practicable state of the art stack-up.


### 4.1 Layer Stack-up

Figure 10 shows the way the board is fabricated with the whole 6 layer stack-up.

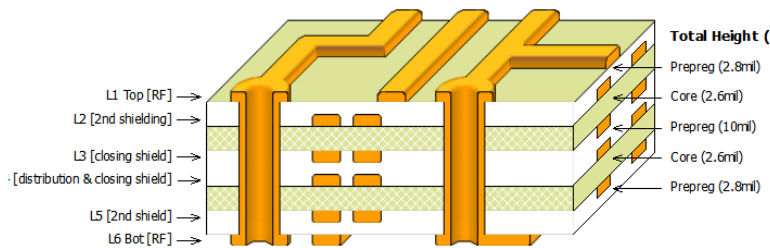

**Figure 10: CAD Board RF Stack-up**

Figure 11 shows a profile sketch of the routing basics. The red rectangle represents the RF traces. These traces are basically routed with a defined distance to the ground planes (shown in gray) on the same layer and the next inner layer. Only the next but one layer is fully flooded. This achieves a highly matched coupling for this micro-strip line.

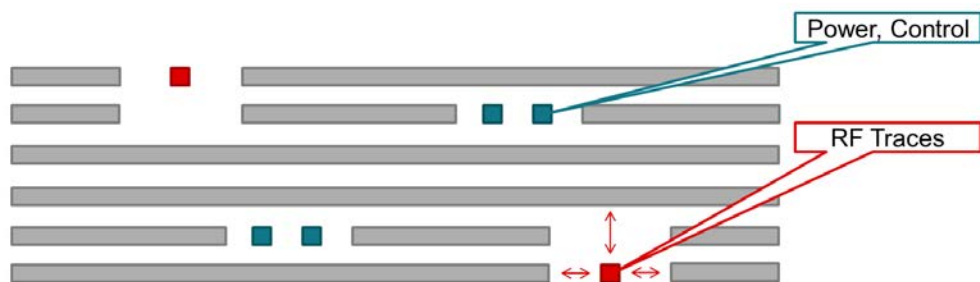

**Figure 11: RF Stack-up**

## 4.2 Layer routing

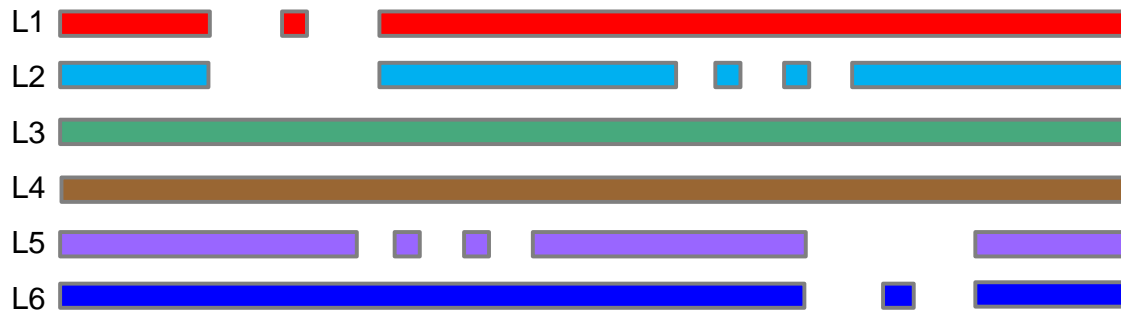


Figure 12: Corresponding Layer set

Figure 12 shows a profile sketch of the entire layers. The color is corresponding to the colors of the board layer, shown in Figure 13 to Figure 18.

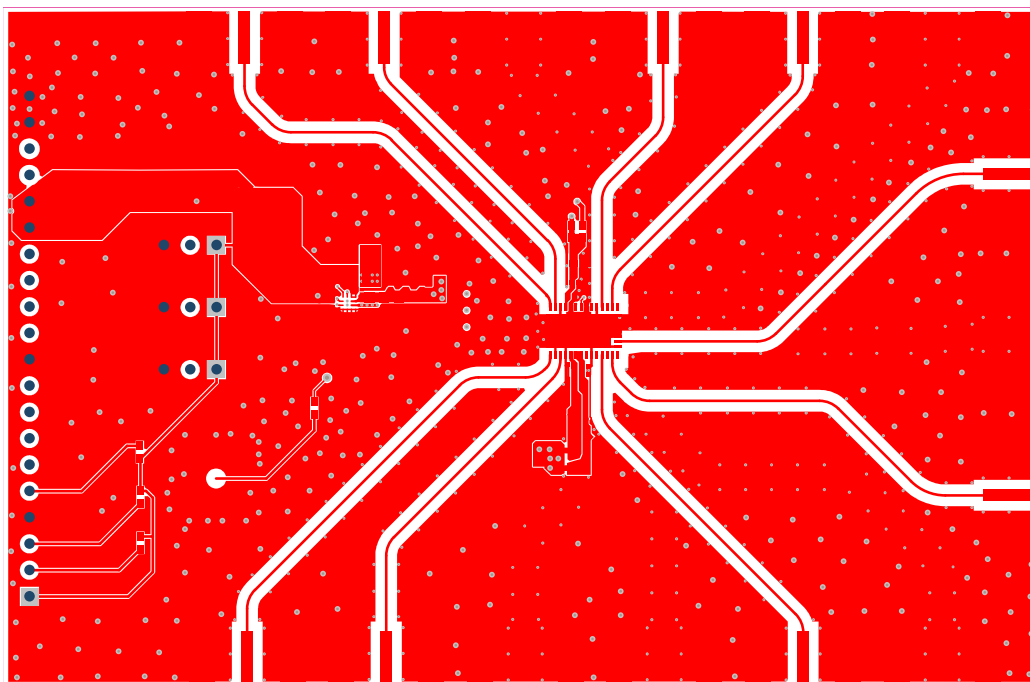
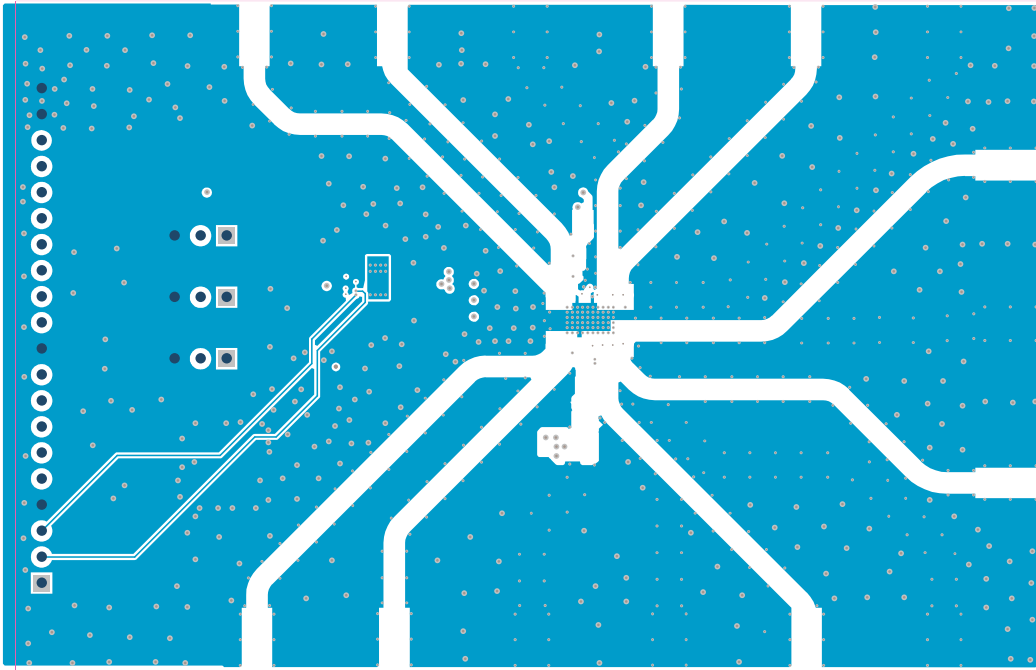
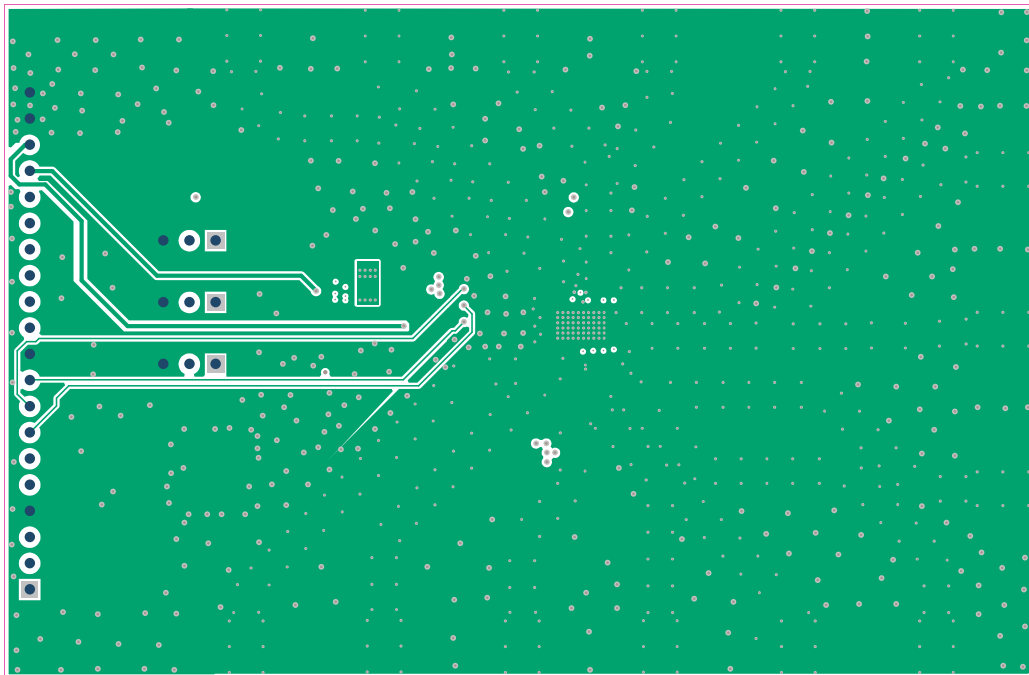


Figure 13: Layer 1, Top

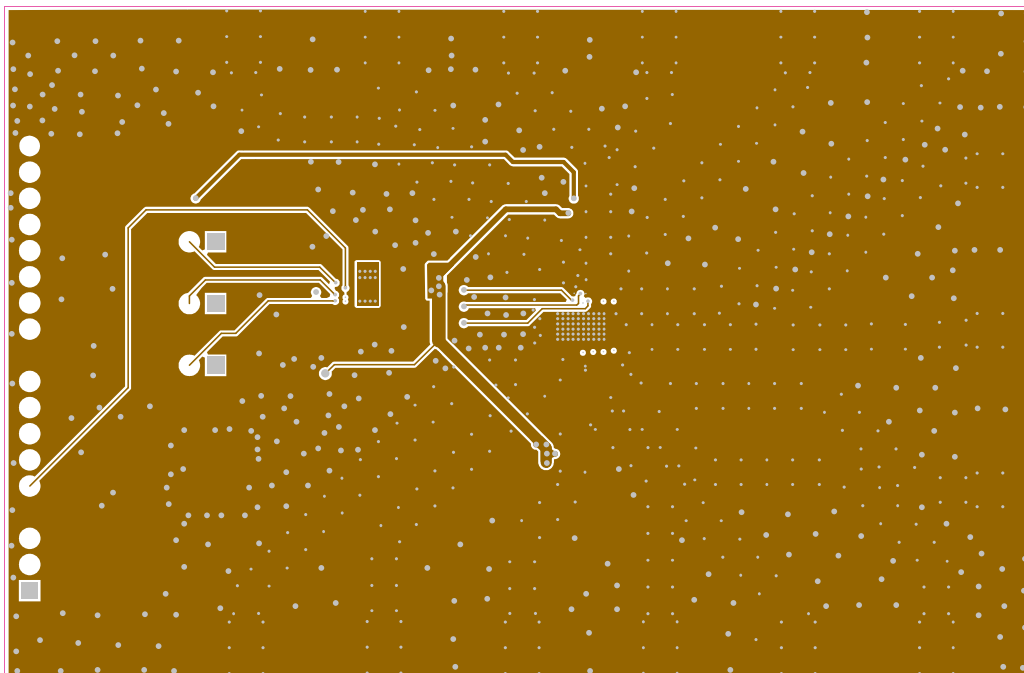


**Figure 14: Layer 2**

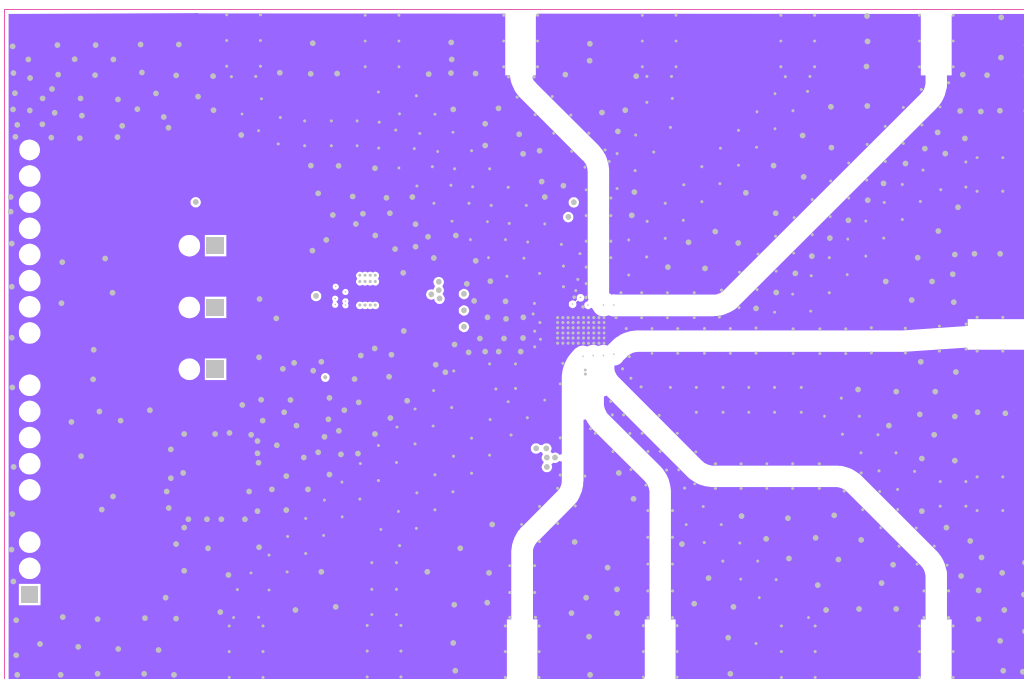


**Figure 15: Layer 3**





**Figure 16: Layer 4**



**Figure 17: Layer 5**

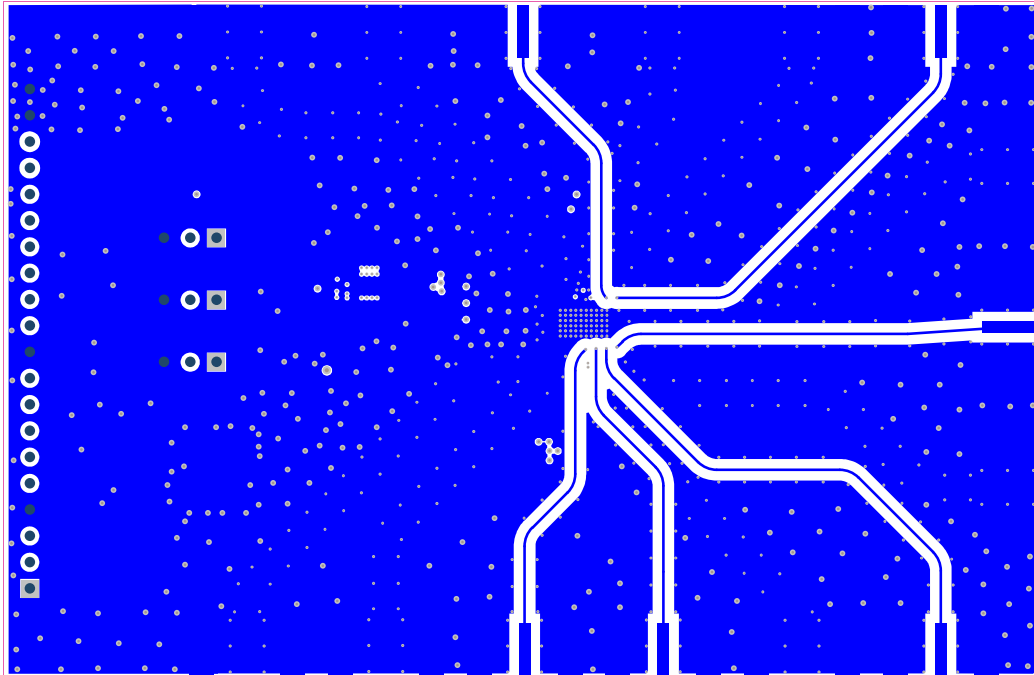


Figure 18: Layer 6, Bottom

## 5 Measurement Setup

This section shows the setup used for each measurement. Two block diagrams show the way the device and the measurement equipment is connected.

### 5.1 Block Diagrams

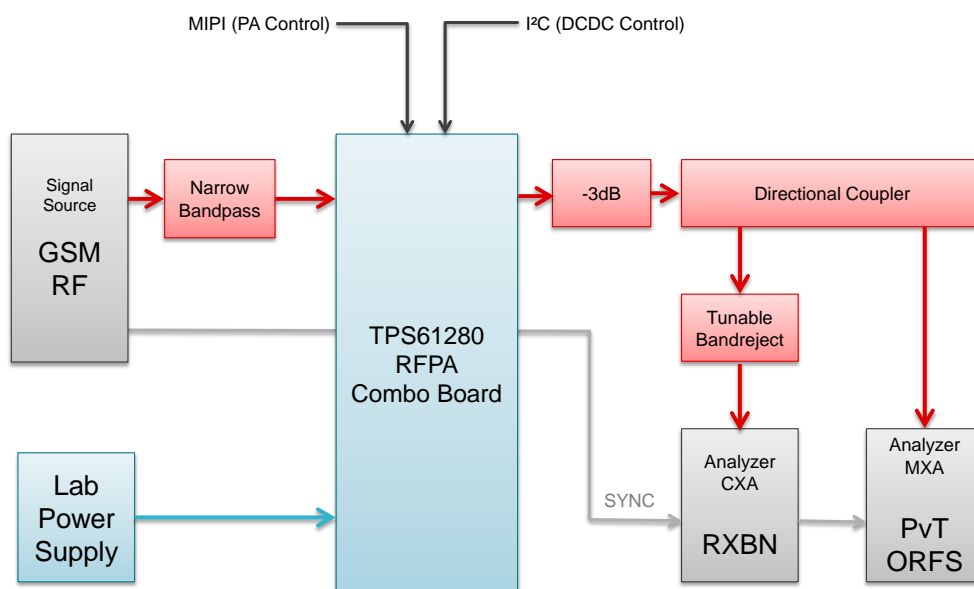


Figure 19: RXBN Test Setup

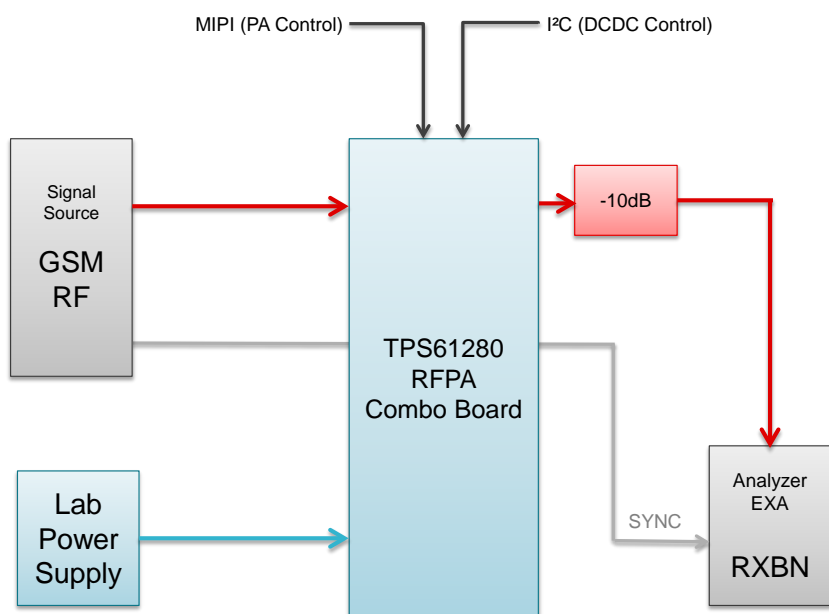


Figure 20: PvT & ORFS Test Setup

## 6 GSM Measurements

### 6.1 Power vs. Time, PvT

The GSM measurement Power vs. Time (PvT) shows the behavior of the RFPA's output when applying a single slot. The Power ramp up- and down-curve has to be in certain time-domain window. The measurement reflects this by the green borders in the figure below.

For this measurement a Input Voltage of 2.7V is applied. The Boost Converter is supposed to boost up the voltage to 3.7V.

This is a Single-Slot GSM 900 PvT Measurement.  $F_{TX} = 890.2\text{MHz}$ , which is the first frequency slot within the GSM 900 Band.

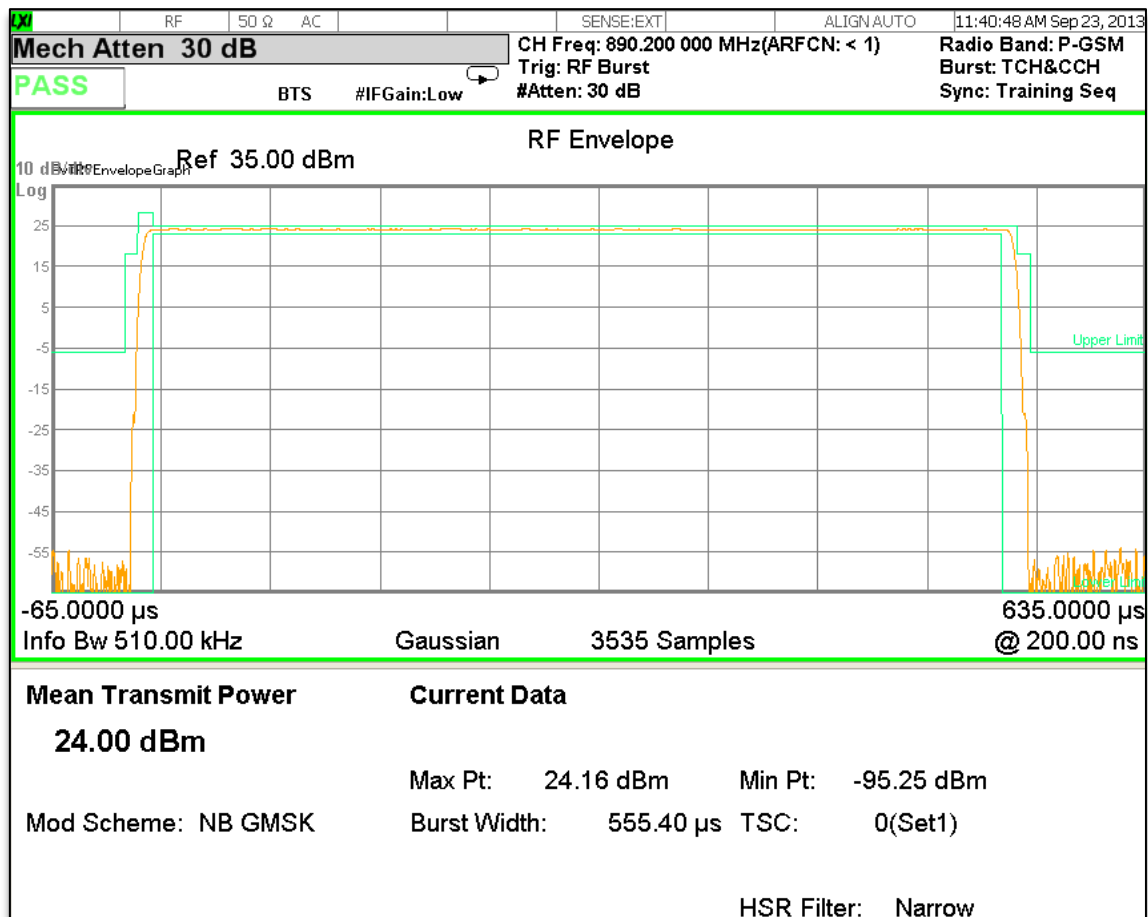


Figure 21: PvT, 34dBm  $P_{OUT}$

## 6.2 Output Radio Frequency Spectrum, ORFS

The following Figure 22 shows the measurement table of the GSM Output Radio Frequency Spectrum for transmission. Every row reflects the specification corner with its measured values and the necessary attenuation.

|                   |         |                |          |            |        |             |        |                                      |        |                    |         |                          |  |
|-------------------|---------|----------------|----------|------------|--------|-------------|--------|--------------------------------------|--------|--------------------|---------|--------------------------|--|
| RF                |         | 50 Ω           |          | AC         |        |             |        | SENSE:EXT                            |        | ALIGN:AUTO         |         | 11:44:46 AM Sep 23, 2013 |  |
| CH Freq           |         | 890.200000 MHz |          |            |        |             |        | CH Freq: 890.200 000 MHz(ARFCN: < 1) |        |                    |         | Radio Band: P-GSM        |  |
| PASS              |         | BTS            |          | IFGain:Low |        |             |        | Trig: RF Burst                       |        | Avg: 100.0 % of 20 |         | Burst: TCH&CCH           |  |
|                   |         |                |          |            |        |             |        | #Atten: 30 dB                        |        |                    |         | Sync: RF Amptd           |  |
| Modulation        |         |                |          |            |        |             |        |                                      |        |                    |         |                          |  |
| Offset Freq List: |         |                |          |            |        | Short       |        | VBW/RBW Ratio: 1                     |        |                    |         |                          |  |
| Ref Power:        |         |                |          |            |        | 17.05 dBm / |        | 30 kHz                               |        |                    |         |                          |  |
| ----- Lower ----- |         |                |          |            |        |             |        | ----- Upper -----                    |        |                    |         |                          |  |
| ----- Limit ----- |         |                |          |            |        |             |        | ----- Limit -----                    |        |                    |         |                          |  |
| Offset Freq       | Res BW  | dB             | ΔLim(dB) | dBm        | Rel dB | Abs dBm     | dB     | ΔLim(dB)                             | dBm    | Rel dB             | Abs dBm |                          |  |
| 200 kHz           | 30 kHz  | -38.17         | (-8.17)  | -21.12     | -30.00 | -65.00      | -37.45 | (-7.45)                              | -20.40 | -30.00             | -65.00  |                          |  |
| 250 kHz           | 30 kHz  | -41.06         | (-8.06)  | -24.01     | -33.00 | -65.00      | -41.24 | (-8.24)                              | -24.19 | -33.00             | -65.00  |                          |  |
| 400 kHz           | 30 kHz  | -71.32         | (-11.32) | -54.27     | -60.00 | -65.00      | -71.00 | (-11.00)                             | -53.95 | -60.00             | -65.00  |                          |  |
| 600 kHz           | 30 kHz  | -80.86         | (-20.86) | -63.81     | -60.00 | -65.00      | -80.44 | (-20.44)                             | -63.39 | -60.00             | -65.00  |                          |  |
| 1.2 MHz           | 30 kHz  | -84.15         | (-21.15) | -67.10     | -63.00 | -65.00      | -84.75 | (-21.75)                             | -67.70 | -63.00             | -65.00  |                          |  |
| 1.8 MHz           | 100 kHz | -81.56         | (-16.56) | -64.51     | -65.00 | -65.00      | -81.26 | (-16.26)                             | -64.21 | -65.00             | -65.00  |                          |  |

Figure 22: ORFS, 34dBm P<sub>OUT</sub>

### 6.3 Receive Band Noise, RXBN

Figure 23 and Figure 24 show measurements verifying the headroom in terms of noise in the appropriate receive band. In this measurement, the transmission frequency is 915MHz. The corresponding receive channel is 45MHz higher at 960MHz.

The whole plot in Figure 23 verifies the noise rejection in this band as well as the spurious noise in the adjacent channels. The several traces reflect different  $V_{IN}$  to  $V_{OUT}$  ratios at the boost converter.

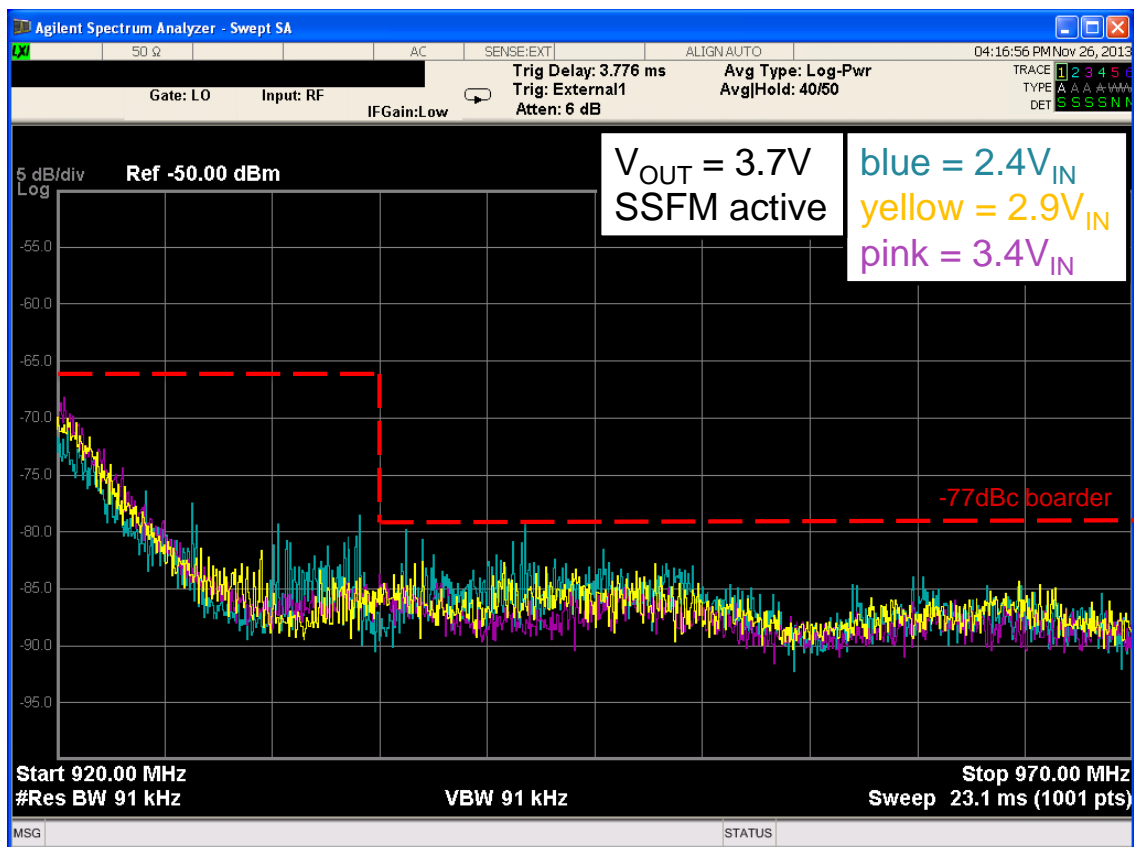


Figure 23: Receive Band Noise 34dBm  $P_{OUT}$ , several input voltages

The TPS61280 features a frequency dithering at the switching clock. This feature is called Spread Spectrum Frequency Modulation (SSFM) and expands the emitted RF spectrum over a broader frequency range. This reduces EMI peaks in the output spectrum significantly. Please refer to TPS61280 datasheet for more information's.

Figure 24 shows the noise critical RXBN measurement with this feature disabled (yellow) as well as SSFM enabled (magenta).

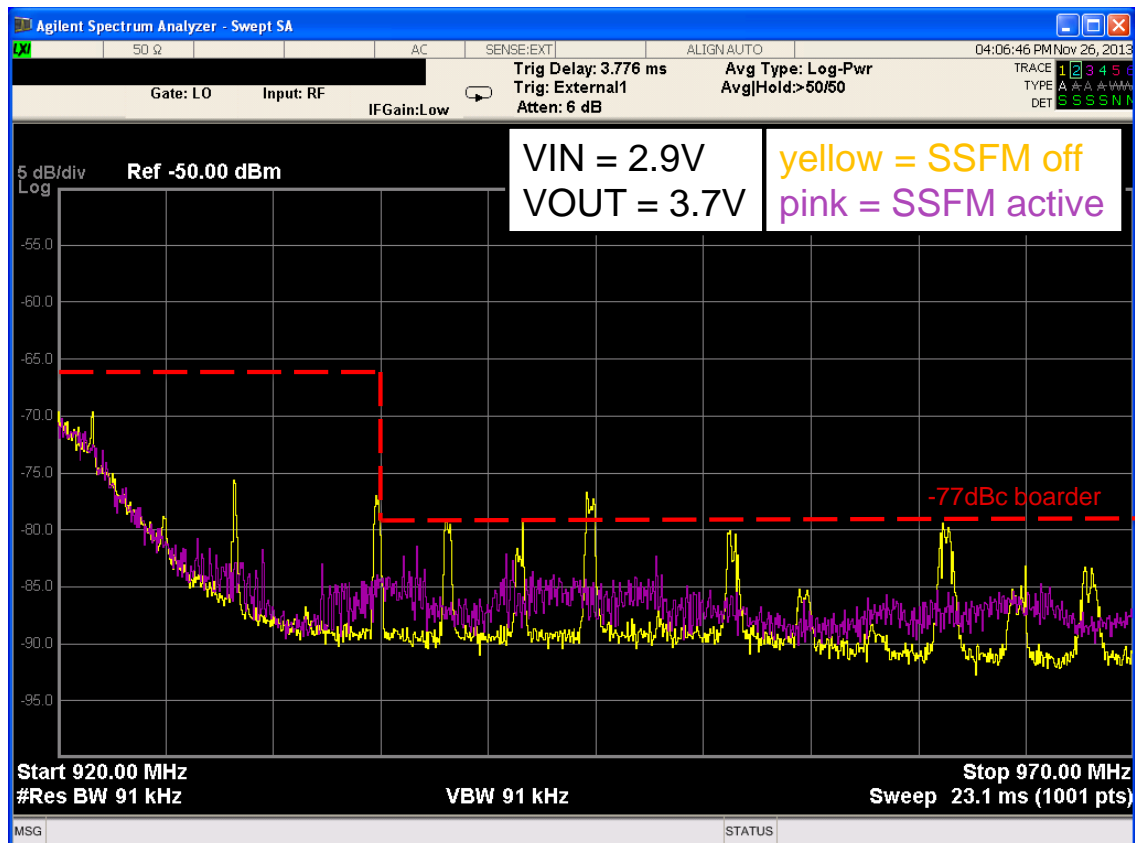


Figure 24: Receive Band Noise 34dBm  $P_{OUT}$ , Spread Spectrum effect

## 7 Appendix

### 7.1 References

- 1) TPS61280 Datasheet, Texas Instruments 2013
- 2) TPS61280EVM-585 User's Guide, Texas Instruments 2013
- 3) GSM Technical Specification, ETSI 1996

### 7.2 Related Links and Web sites

[www.ti.com/power](http://www.ti.com/power)

[www.ti.com/products/tps61280](http://www.ti.com/products/tps61280)

[http://e2e.ti.com/support/power\\_management/default.aspx](http://e2e.ti.com/support/power_management/default.aspx)

<http://www.skyworksinc.com/Product.aspx?ProductID=1623>

### 7.3 Acronyms

|       |   |
|-------|---|
| DUT   | Device under Test                       |
| EVM   | Evaluation Module                       |
| GMSK  | Gaussian Minimum Shift Keying           |
| GSM   | Global System for Mobile Communications |
| MMPA  | Multi-Mode Power Amplifier              |
| ORFS  | Output Radio Frequency Spectrum         |
| PA    | Power Amplifier                         |
| PvT   | Power versus Time                       |
| RF    | Radio Frequency                         |
| RFPA  | Radio Frequency Power Amplifier         |
| RXBN  | Receive Band Noise                      |
| SSFM  | Spread Spectrum Frequency Modulation    |
| WCDMA | Wideband Code Division Multiple Access  |



## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.