

# TIDA-00259 Test Report

Bill Johns BMS/WLPC

### **Abstract**

TI design TIDA-00259 wireless power supply transmitter is an application of the bq500212A IC in a 5W Qi compliant configuration, 5V input voltage.

Transmitter circuits are laid out in a 50mm X 50mm configuration which matches the dimensions for WPC Type A11 TX Coil.

The design is Qi certified and has been certified to WPC v1.1 standard.

TIDA-00259 is derived from the bq500212A Evaluation Module bq500212AEVM-550, both numbers may appear in documentation but refer to a single design.



Figure 1. TIDA-00259 Photo

### **Document History**

Version	Date	Author	Notes
1.0	November 2014	Bill Johns	First release



#### **WARNING: EXPORT NOTICE**

Recipient agrees to not knowingly export or re-export, directly or indirectly, any product or technical data (as defined by the U.S., EU, and other Export Administration Regulations) including software, or any controlled product restricted by other applicable national regulations, received from Disclosing party under this Agreement, or any direct product of such technology, to any destination to which such export or re-export is restricted or prohibited by U.S. or other applicable laws, without obtaining prior authorization from U.S. Department of Commerce and other competent Government authorities to the extent required by those laws. This provision shall survive termination or expiration of this Agreement.

According to our best knowledge of the state and end-use of this product or technology, and in compliance with the export control regulations of dual-use goods in force in the origin and exporting countries, this technology is classified as follows:

US ECCN: 3E991 EU ECCN: EAR99

And may require export or re-export license for shipping it in compliance with the applicable regulations of certain countries.



## 



### bq51013B EVM (bq51013BEVM-764)

The bq51013B wireless power receiver EVM (bq51013BEVM-764) was used for test with the TIDA-00259. This is a 5W Qi compliant RX that will output 5V at up to 1A out. The Vishay IWAS-4832FF-50 is 48mm X 32mm RX coil with low DCR and performs well in a 5W application. For additional information on the receiver see bq51013B product folder at TI.com.

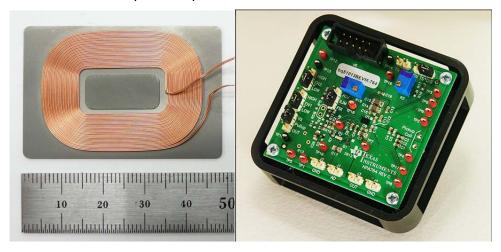


Figure 2 Test Receiver Coil and bq51013B EVM



## **Block Diagram**

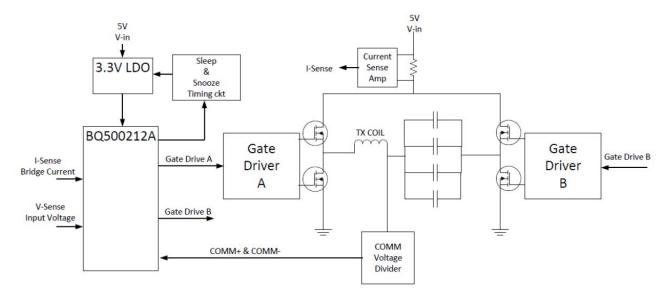


Figure 3 Block Diagram

## **Schematic**

The TIDA-00259 power schematic shown in figure 4 and bq500212A section schematic is shown in figure 5.



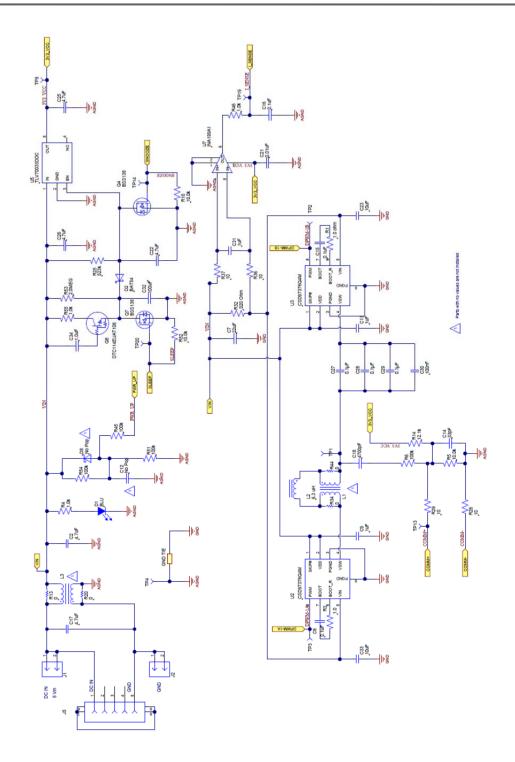


Figure 4 TIDA-00259 Schematic Power Section



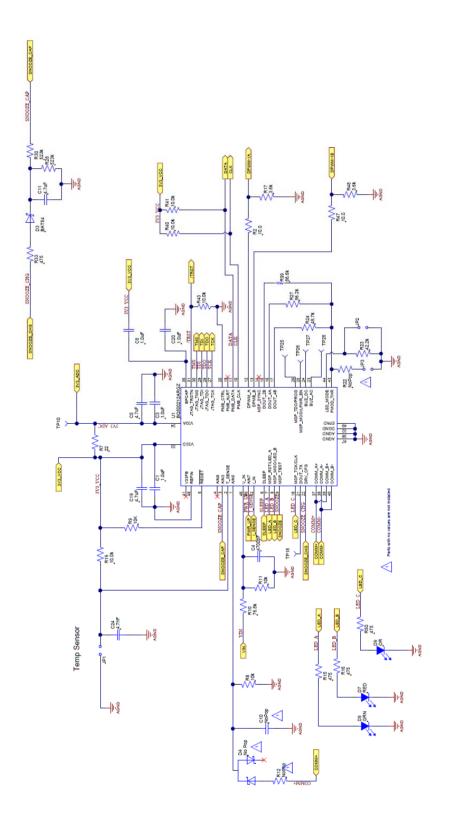


Figure 5 TIDA-00259 Schematic bq500212A Section



### **Configuration Options**

- LED\_MODE Resistor R23 (see fig 5 U1-44) controls the behavior of status LED D5, D7 and D9. The standard value is 42.2k ohms for control option 1, see data sheet for additional settings.
- NTC- Connector JP1 (see fig 5 U1-2) provides the option for connecting a negative temperature coefficient (NTC) sensor for thermal protection, see data sheet for additional settings.
- DATA / CLK / AGND I2C (see fig 5 U1-10 & 11) interface to the bq500212A can be used with software tools to monitor device operation. Consult factory for more info.
- FOD / PMOD Protection feature that is enabled and disabled using resistor R24 & R99 (see fig 5 U1-17 & 15) for FOD and R27 (see fig 5 U1-16) for PMOD, see data sheet for additional settings.
- L1 and L3 Common Mode Choke for additional input power filter or output TX Coil
  - L1 DLW5BTM101TQ2 6A, 9 m $\Omega$ , MuRata
  - L3 DLW5BTM102TQ2 2.5A,  $24m\Omega$ , MuRata

### **Test Results**

Figure 6 shows the TX and RX behavior during standby with no RX on the charging pad. The TX will ping the charging pad at about a 500ms rate set by the RC time constant associated with C22.

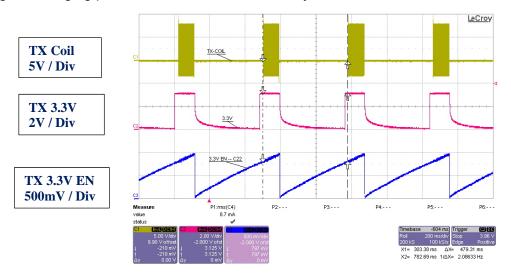


Figure 6 TX Standby Mode



Figure 7 shows a typical start up behavior for the TX and RX as the RX is placed on a TX in standby. The RX / TX can be seen transitioning from standby, note on Vrect below:

- 1.) Vrect increases above under voltage lockout, 2.7V and devices start operations
- 2.) RX sends first three packets (SS / ID / Config). Packets are decoded by TX which continues to send power.
- 3.) RX begins tuning TX operating point to V-RECT target voltage of 7.5V
- 4.) RX at target voltage and enables VOUT, 5V.



Figure 7 Start Up into 100mA load



Figure 8 shows the TX and RX behavior during Charge Complete, EPT 01. The bq51013B is configured to send EPT 01. In response TX will end power transfer and not ping for about 4 seconds.

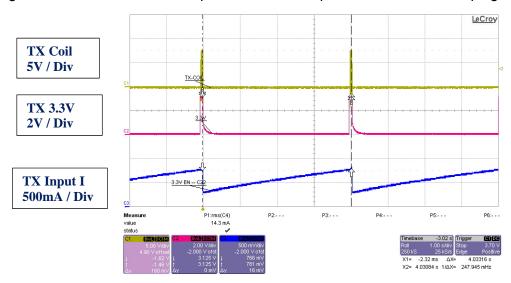


Figure 8 Charge Complete, End Power Transfer 01

Figure 9 shows the transmitter operating in power transfer mode with a load of about 5W. The coil drive signal is a 50% duty cycle signal 180 degrees out of phase. Operating freq will change with load between 110kHz and 205kHz, at this point freq is about 150kHz.



Figure 9 TX Coil Drive and C / L Tank voltage



Figure 10 shows the efficiency across the power range with the bq51013B. This is the total DC to DC system efficiency including the transmitter, coils and receiver.

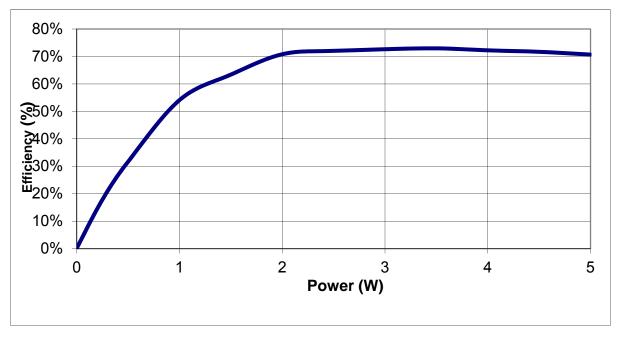


Figure 10 TIDA-00259 Efficiency with bq51013B

#### **Thermal Measurements**

The following figure shows a thermal image of the TIDA-00259 operating with the bq51013B EVM RX at 950mA output load.

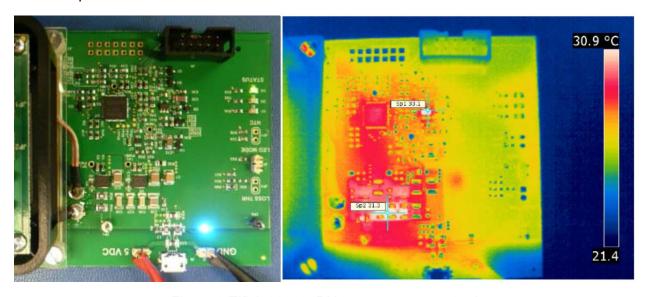


Figure 9 TIDA-00259, RX output current 950mA



## References

1. Data Sheet bq500212A Wireless Power Controller for WPC (SLUSBD6C)

#### IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design. TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have *not* been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.