

PMP10091RevA Test Results

| | | |
|-----|--|----|
| 1 | Startup | 2 |
| 2 | Shutdown | 3 |
| 3 | Efficiency | 4 |
| 4 | Load Regulation | 5 |
| 5 | Output Ripple Voltage | 6 |
| 6 | Input Ripple Voltage | 7 |
| 7 | Load Transients | 8 |
| 7.1 | Transient at the positive output | 8 |
| 7.2 | Transient at the negative output | 9 |
| 8 | Control Loop Frequency Response | 10 |
| 9 | Miscellaneous Waveforms | 11 |
| 10 | Thermal Image | 14 |

Topology: Boost with +VOUT and -VOUT

Device: TPS40210



Figure 1

1 Startup

The startup waveform is shown in the Figure 2. The input voltage was set at 5V, with 250mA load at the outputs.

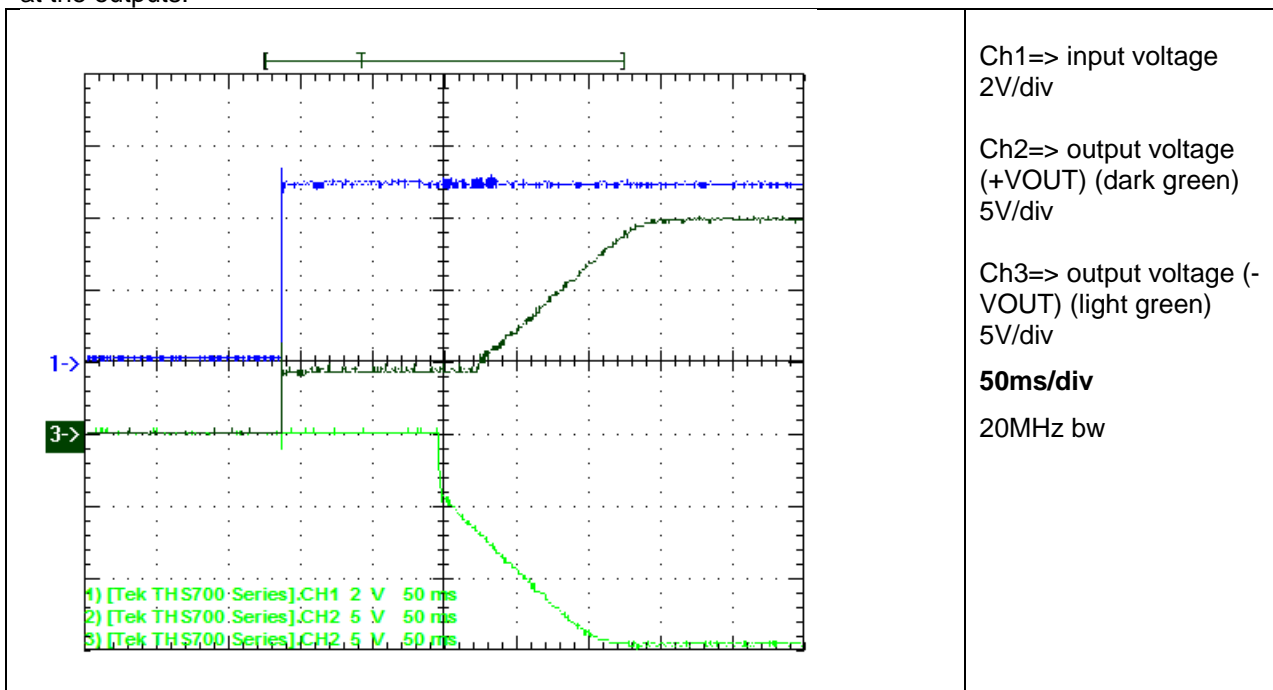


Figure 2

2 Shutdown

The shutdown waveform is shown in the Figure 3. The input voltage was set at 5V, with 250mA load on the outputs. The power supply was disconnected.

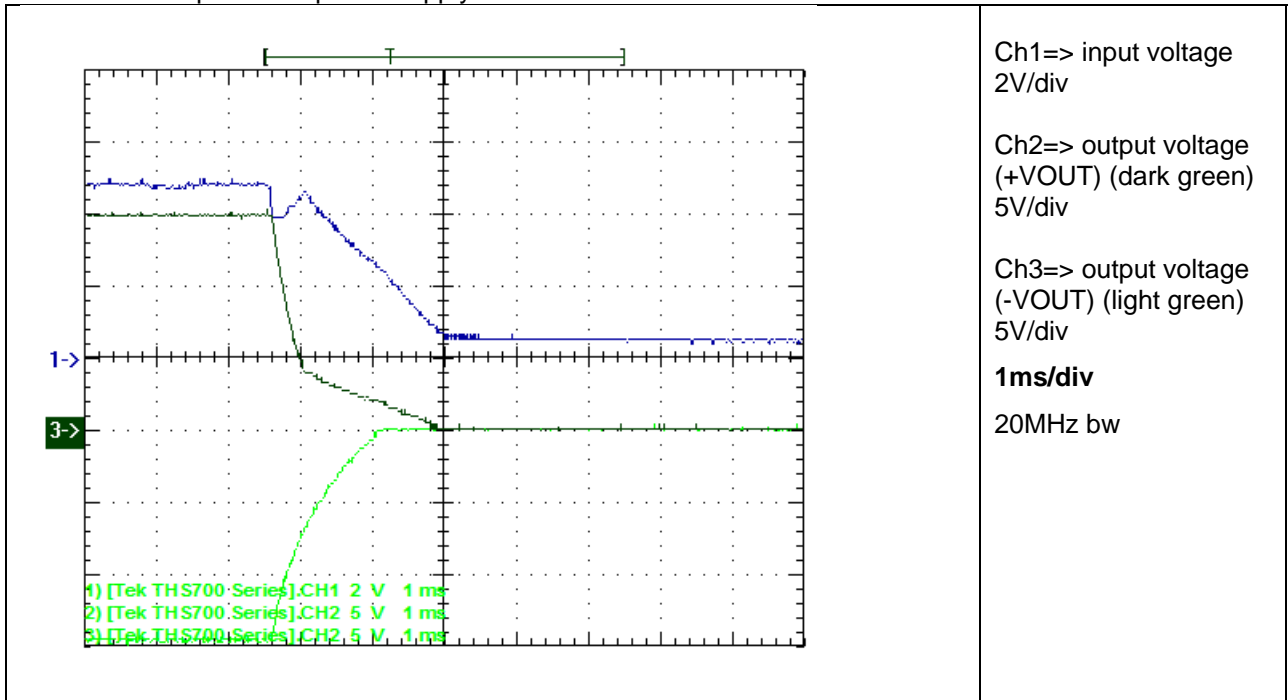


Figure 3

PMP10091RevA Test Results

3 Efficiency

The efficiency is shown in the Figure 4 below. The input voltage was set 5V.

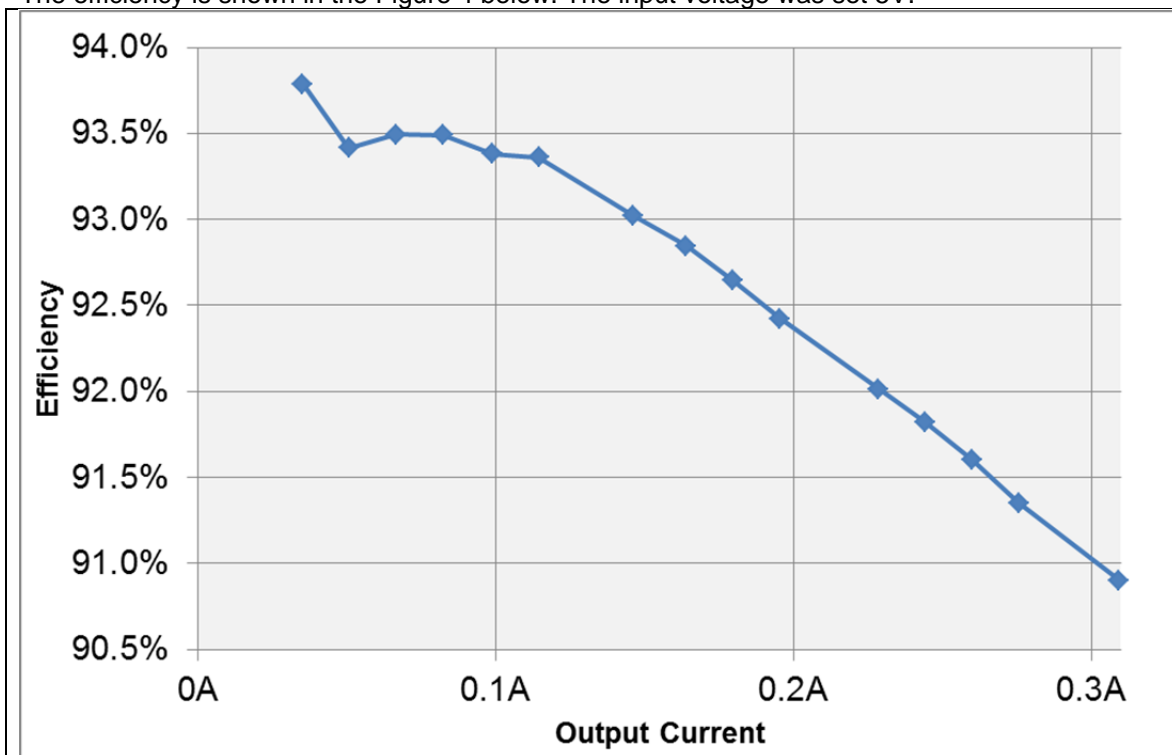


Figure 4

PMP10091RevA Test Results

4 Load Regulation

The load regulation of the output is shown in the Figure 5 below. The input voltage was set to 5V.

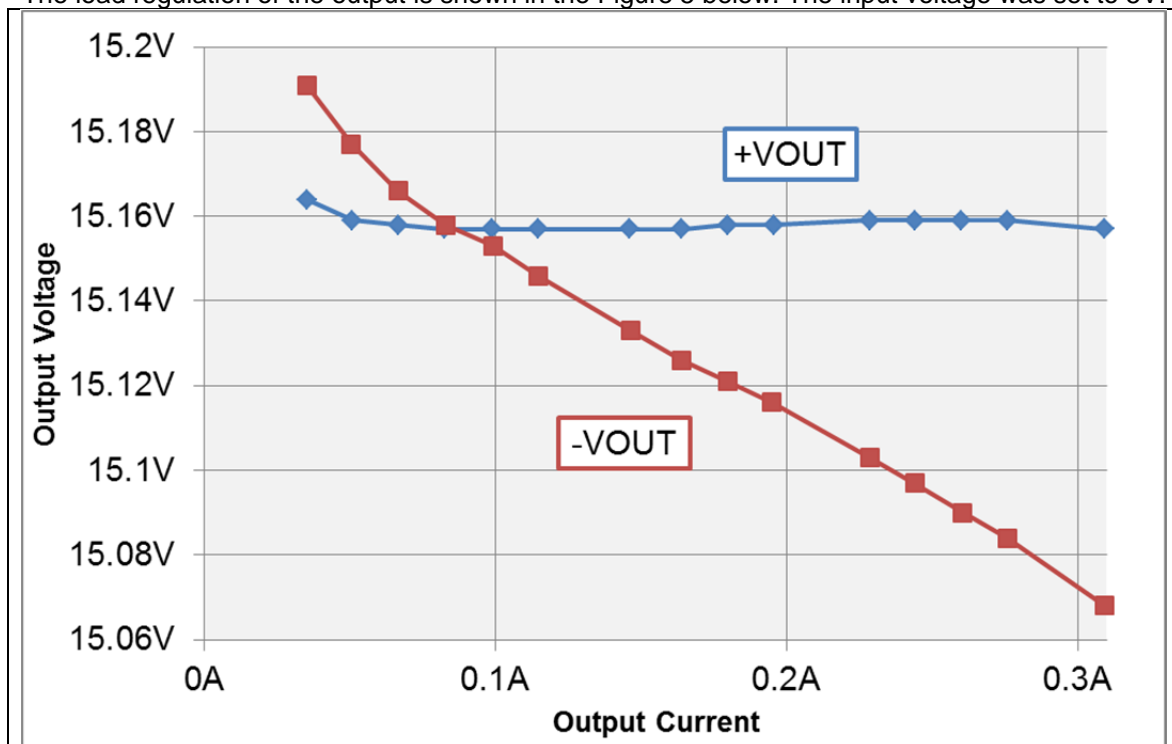


Figure 5

With no loads on the output the output voltages were +15.163V and -16.012V.

5 Output Ripple Voltage

The ripple voltage of the positive output is shown in Figure 6 (5V input, 2x300mA load).

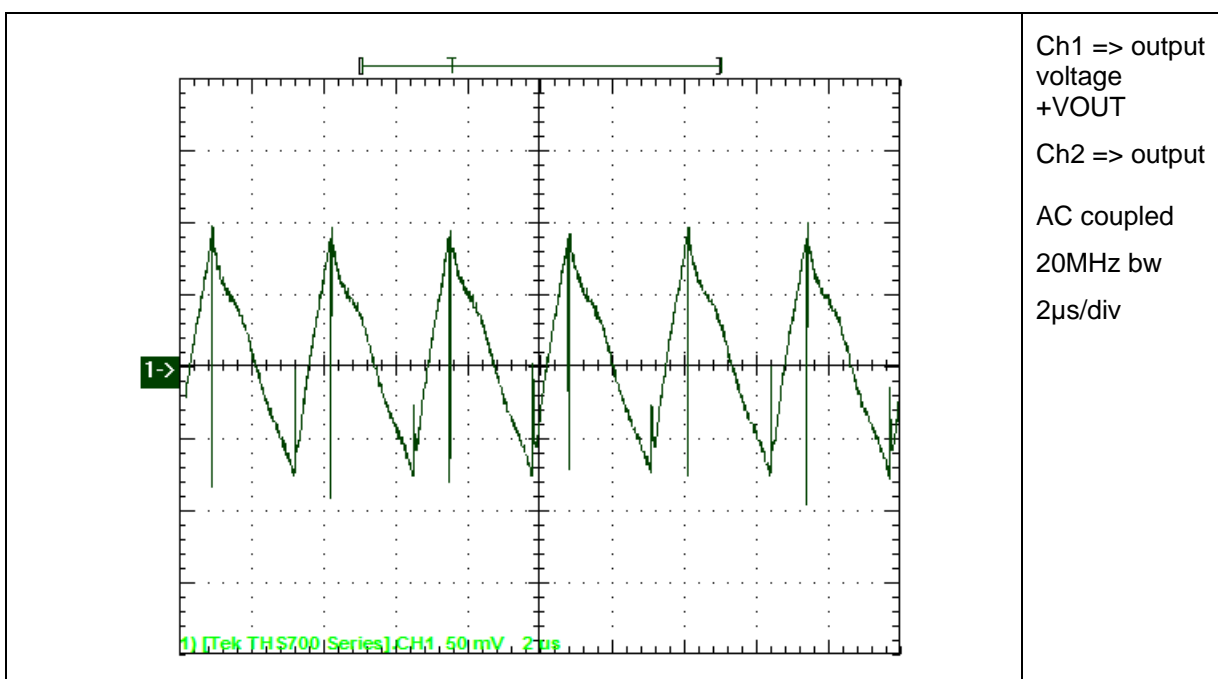


Figure 6

The ripple voltage of the negative output is shown in Figure 7 (5V input; 2x300mA output).

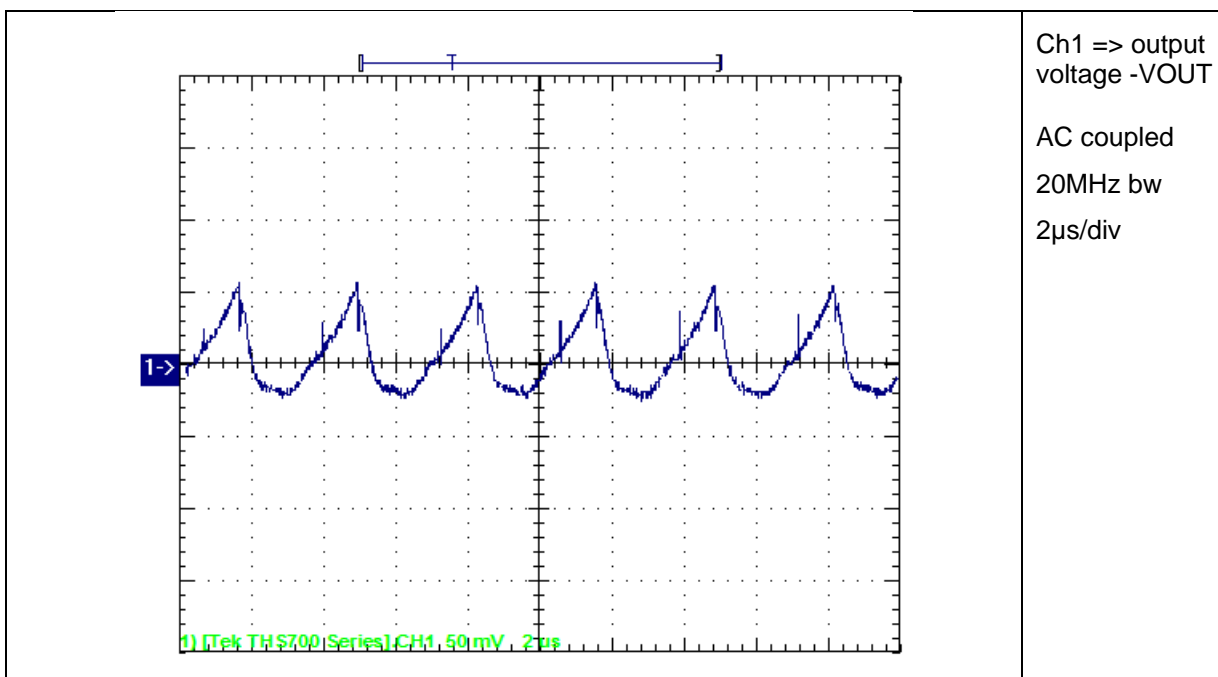


Figure 7

PMP10091RevA Test Results

6 Input Ripple Voltage

The input ripple voltage is shown in Figure 8. (5V input; 2x300mA output).

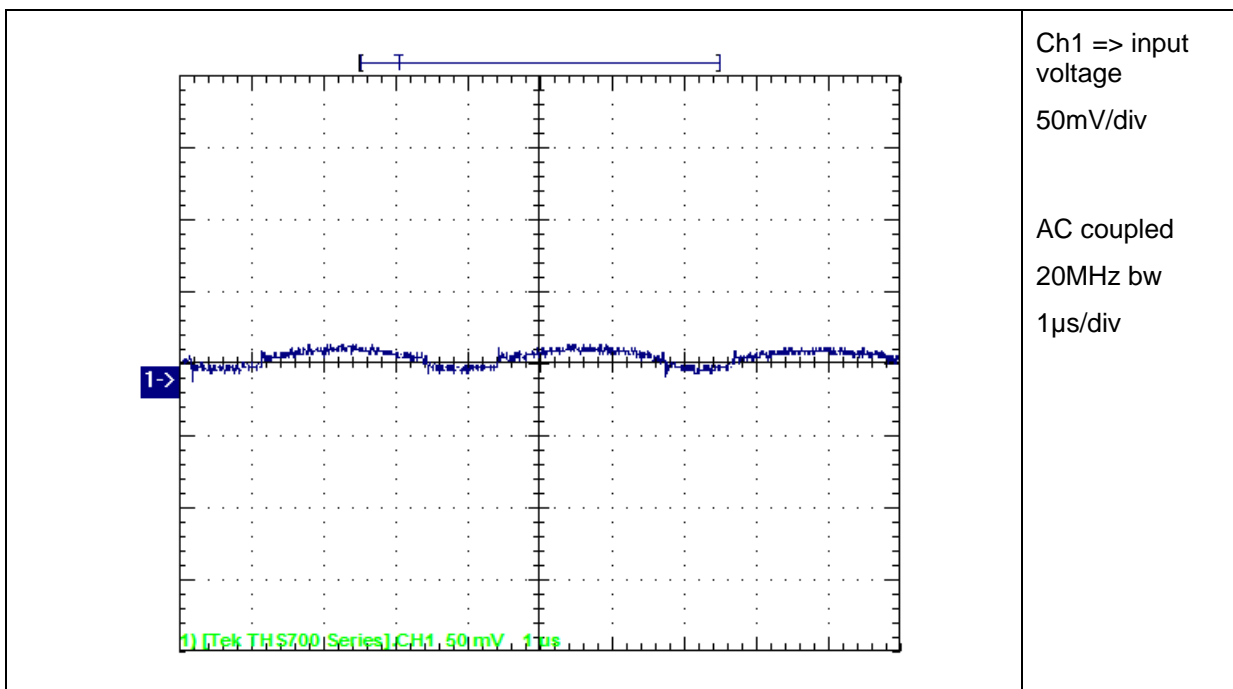


Figure 8

7 Load Transients

7.1 Transient at the positive output

The Figure 9 shows the response to load transients. The load is switching from 140mA to 410mA with a frequency of 100Hz. The input voltage was set to 5V

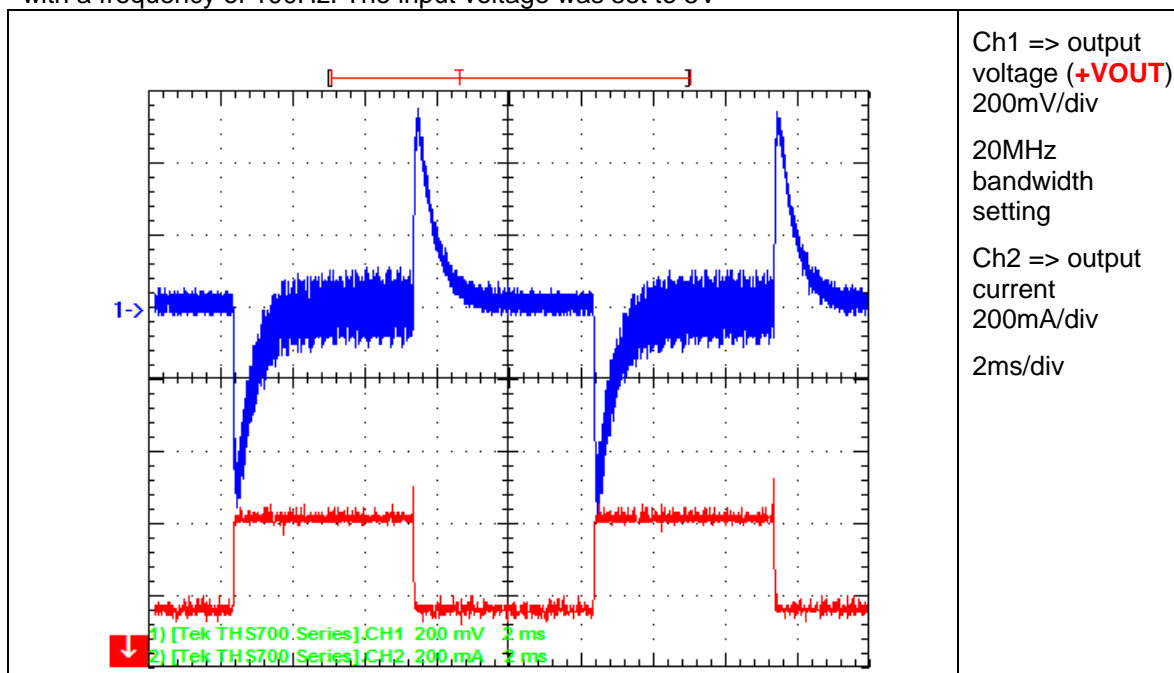


Figure 9

The Figure 10 shows the effect of a load transient at the positive output. The load is switching from 140mA to 410mA with a frequency of 100Hz. The input voltage was set to 5V

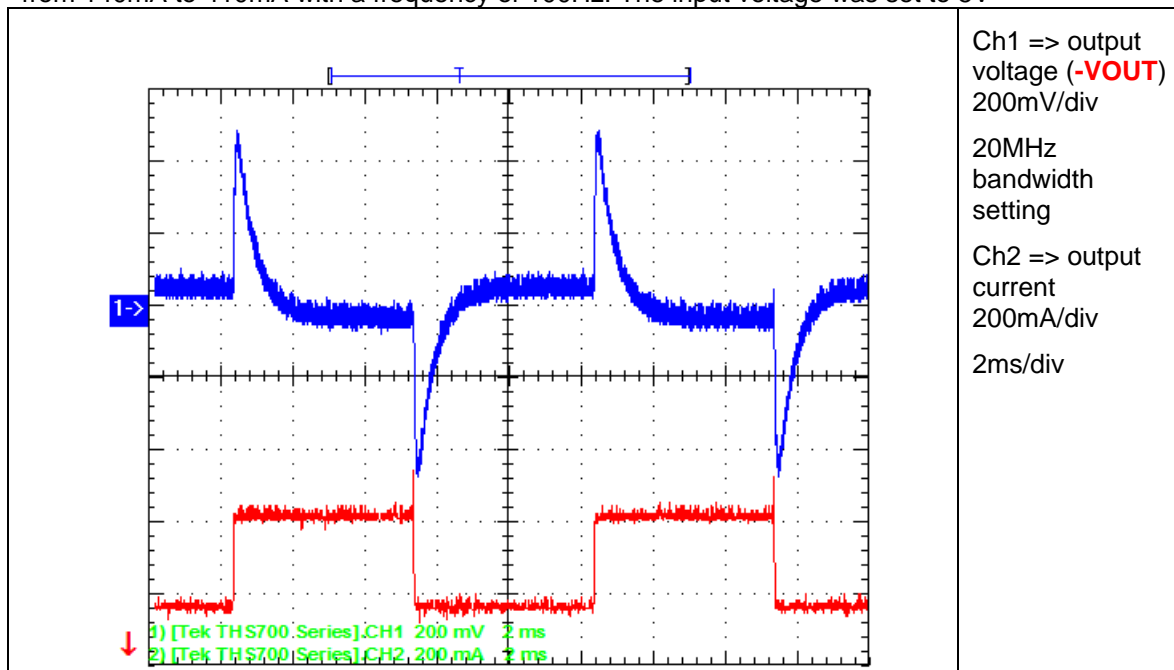


Figure 10

PMP10091RevA Test Results

7.2 Transient at the negative output

The Figure 11 shows the effect of a load transients at the negative output. The load is switching from 140mA to 410mA with a frequency of 100Hz. The input voltage was set to 5V

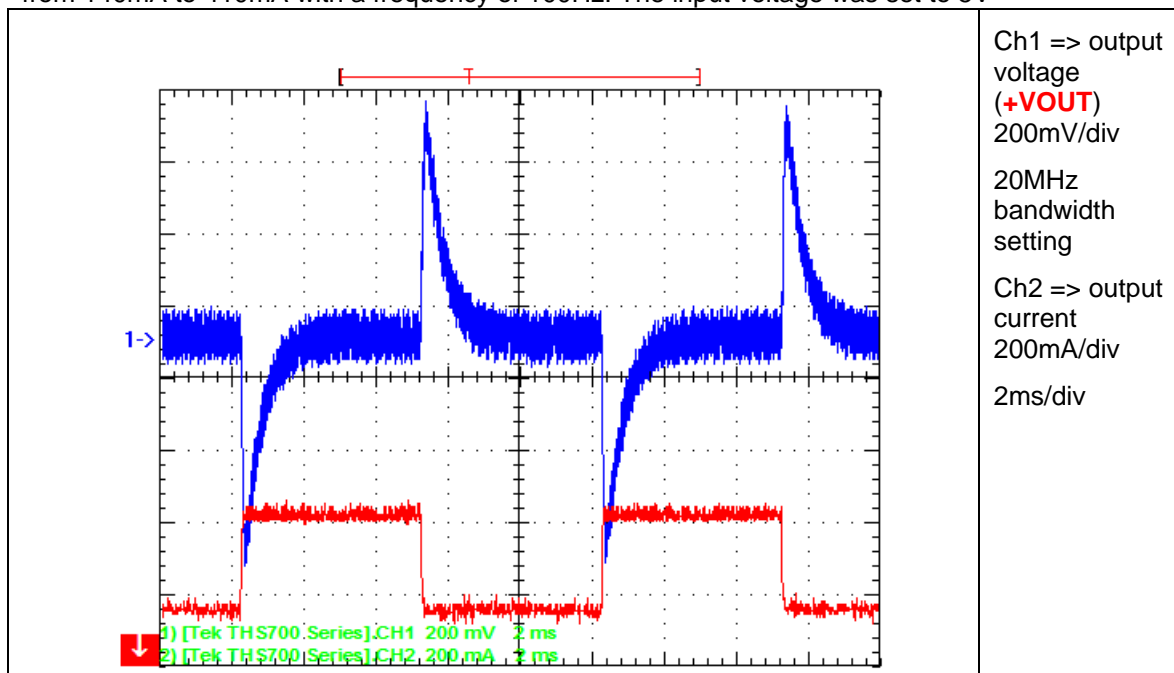


Figure 11

The Figure 12 shows the response to load transients. The load is switching from 140A to 410A with a frequency of 100Hz. The input voltage was set to 5V

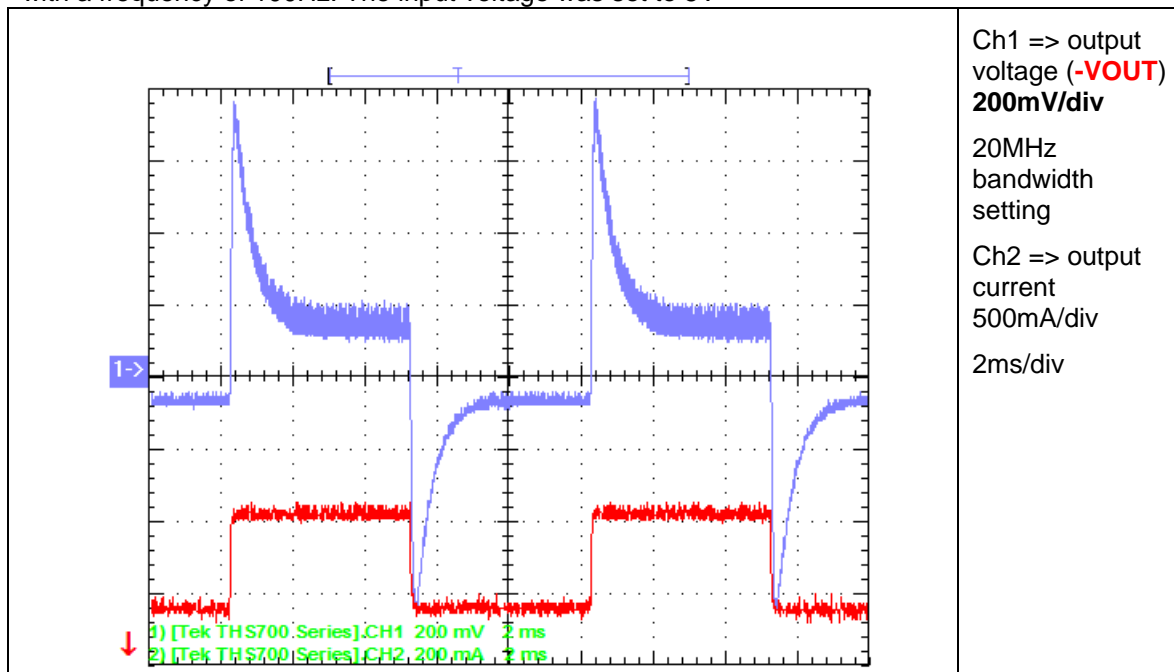


Figure 12

8 Control Loop Frequency Response

Figure 13 shows the loop response. 2x 300mA-load applied. The input voltage was set to 4.5V worst case.

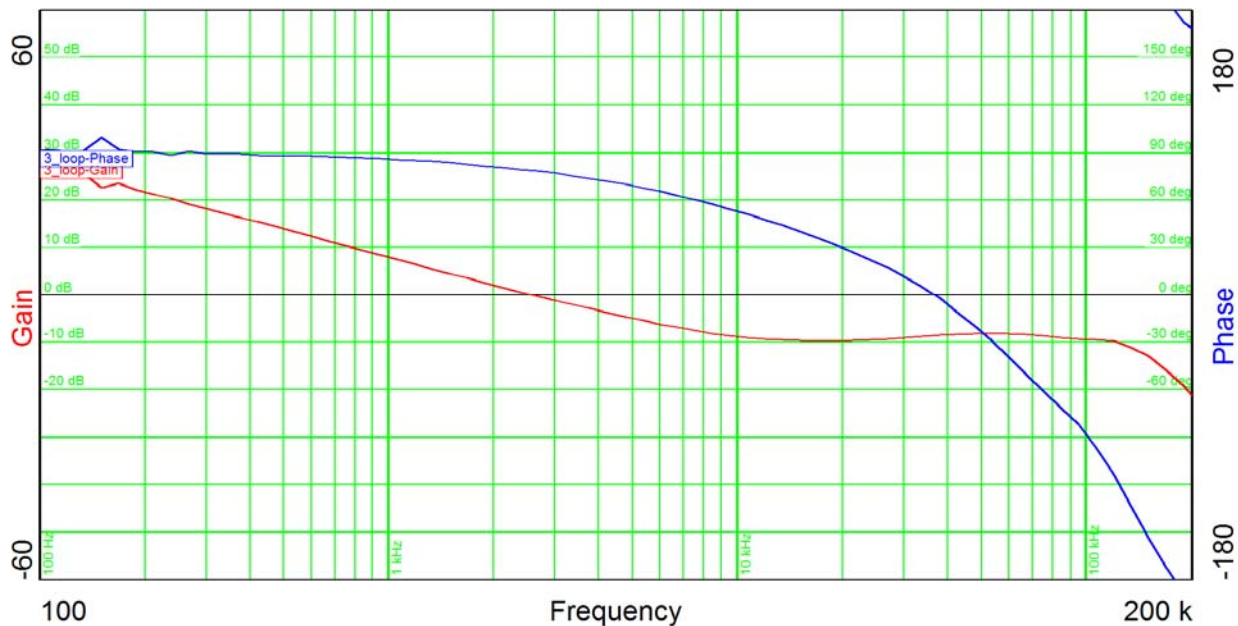


Figure 13

Table 1 summarizes the results from Figure 13.

| | |
|---------------------|-------|
| Vin | 4.5V |
| Bandwidth (kHz) | 2.58 |
| Phase margin | 78.6° |
| slope (20dB/decade) | -0.97 |
| gain margin (dB) | -8.69 |
| slope (20dB/decade) | +0.31 |
| freq (kHz) | 36.4 |

Table 1

9 Miscellaneous Waveforms

The waveform of the voltage on switchnode (drain to source) is shown in Figure 14. Input voltage was set to 5V and output current to 2 x 300mA.

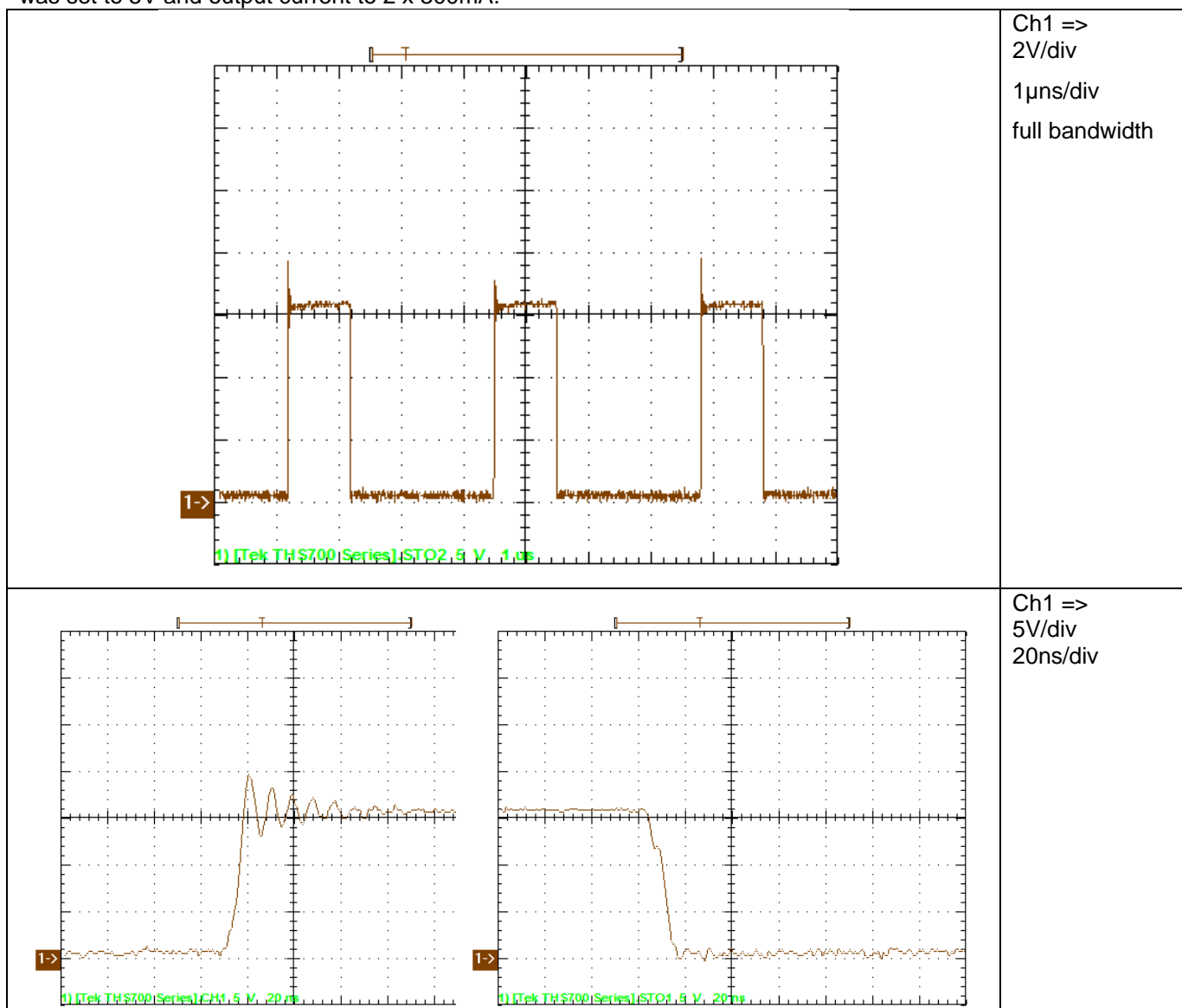


Figure 14

PMP10091RevA Test Results

The waveform of the voltage on the gate to source is shown in Figure 15. Input voltage was set to 5V and output current to 2x300mA.

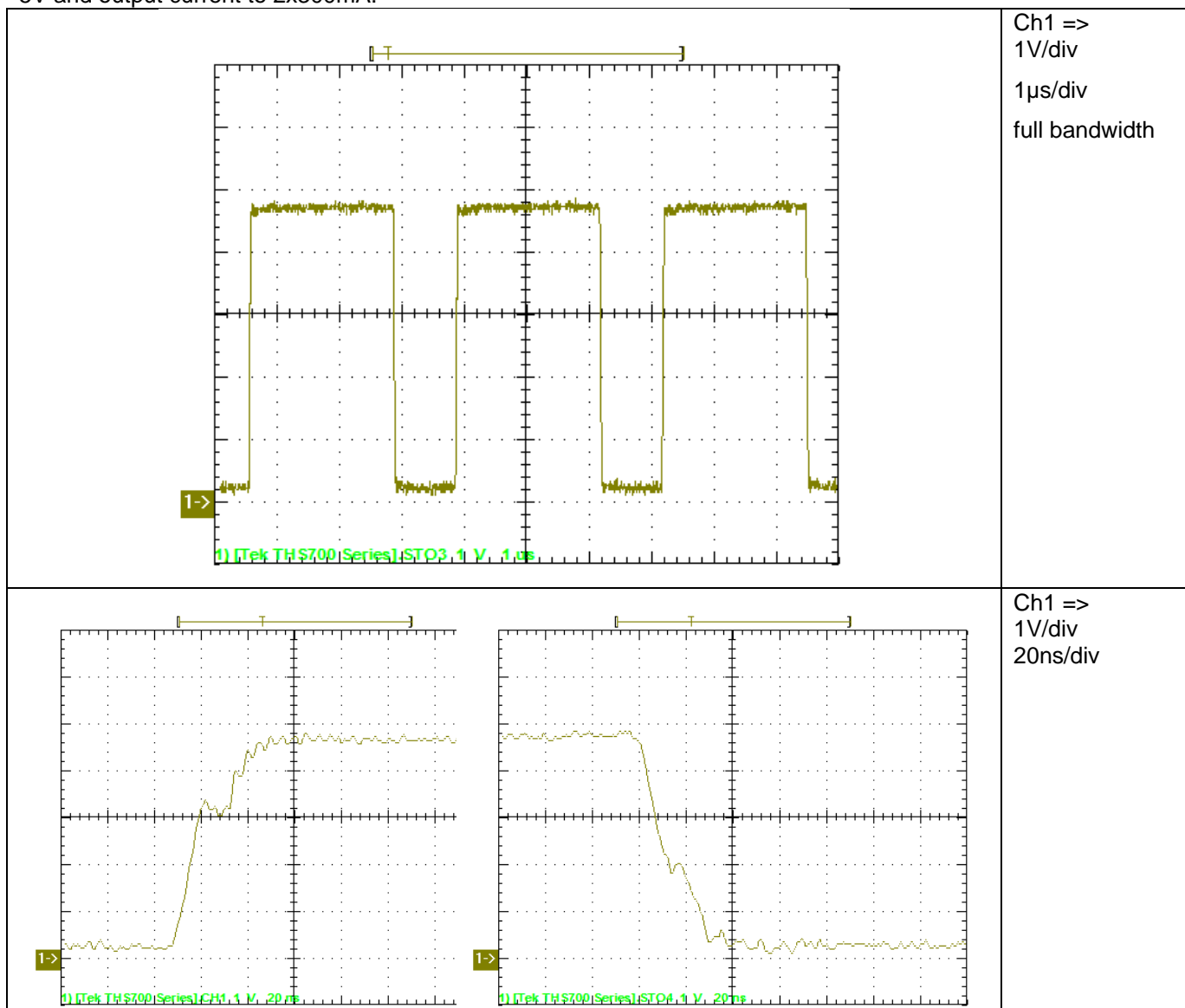


Figure 15

PMP10091RevA Test Results

The waveform of the voltage on D103 is shown in Figure 16. Input voltage was set to 5 and output current to 2x300mA.

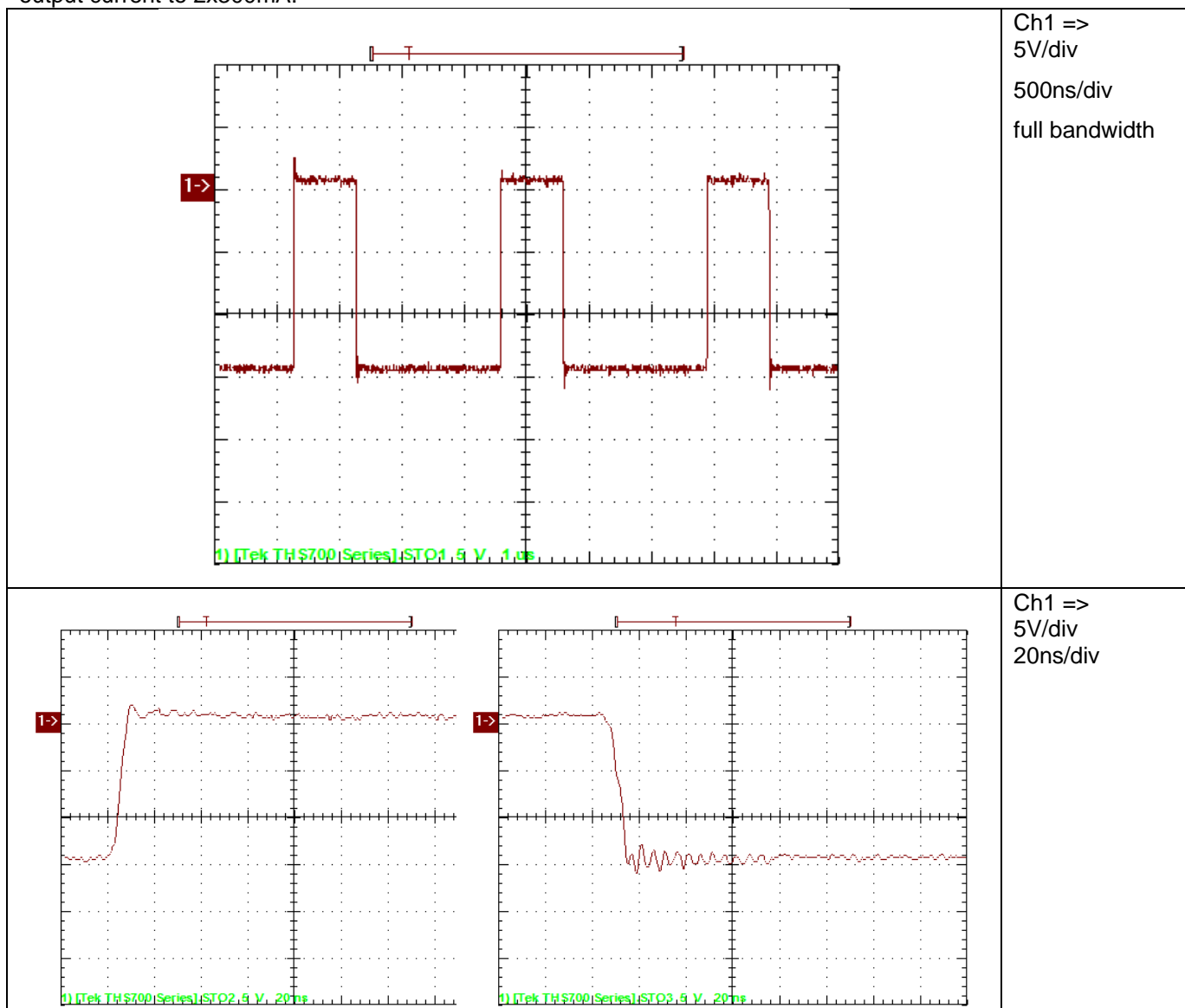


Figure 16

PMP10091RevA Test Results

10 Thermal Image

Figure 17 shows the thermal image at full load, R11 is current sense resistor:



Figure 17

| Name | Temperature |
|------|-------------|
| R11 | 52.3°C |
| L1 | 44.0°C |
| D103 | 42.1°C |
| D102 | 41.7°C |
| Q1 | 41.2°C |
| U1 | 39.0°C |
| D101 | 39.8°C |
| D1 | 40.8°C |

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.