


PMP8709RevC Test Results

1	Startup	2
2	Shutdown	4
3	Efficiency	6
4	Load Regulation	6
5	Line Regulation	7
6	Output Ripple Voltage	8
7	Input Ripple Voltage	8
8	Load Transients	9
9	Control Loop Frequency Response.....	12
10	Miscellaneous Waveforms	16
11	Thermal Image.....	25


Topology: SEPIC
Device: TPS40210

1 Startup

 The startup waveform is shown in the Figure 1. The input voltage was set at 8V, with 2A load at the output.




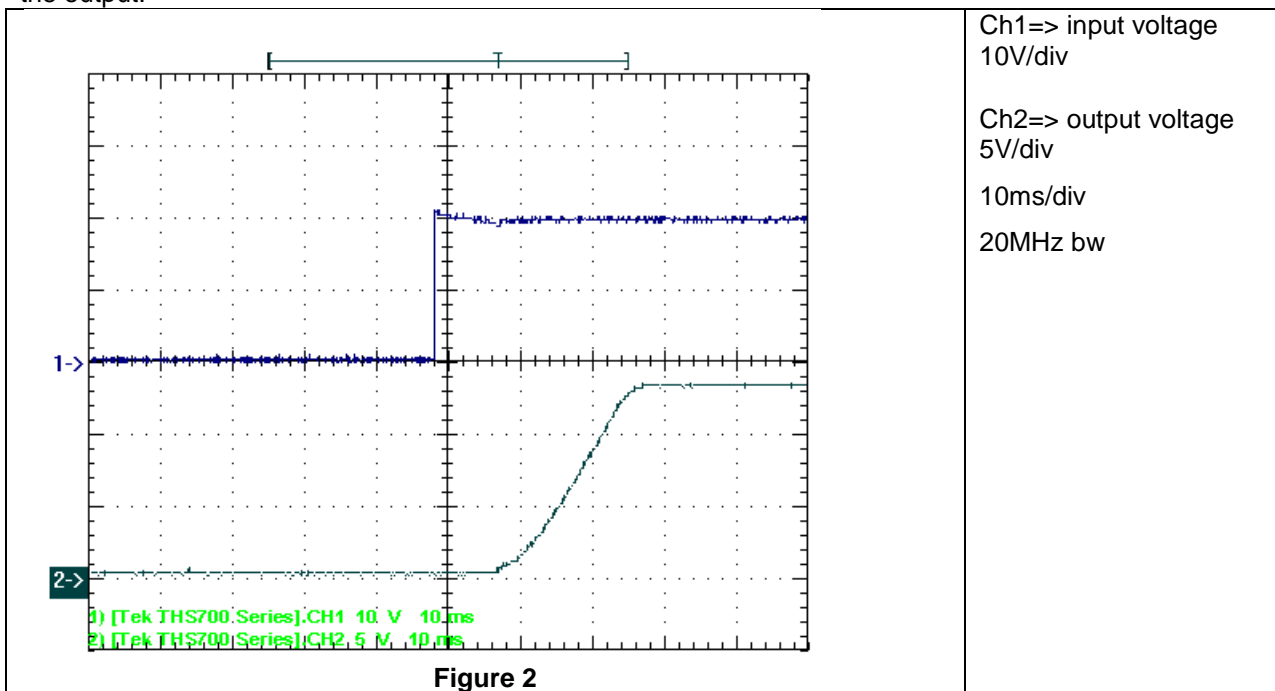The startup waveform is shown in the Figure 2. The input voltage was set at 20V, with 2A load at the output.




PMP8709RevC Test Results

 The startup waveform is shown in the Figure 3. The input voltage was set at 32V, with 2A load at the output.




2 Shutdown

 The shutdown waveform is shown in the Figure 4. The input voltage was set at 8V, with 2A load on the output. One input cable was disconnected.




 The shutdown waveform is shown in the Figure 5. The input voltage was set at 20V, with 2A load on the output. One input cable was disconnected.



PMP8709RevC Test Results

 The shutdown waveform is shown in the Figure 6. The input voltage was set at 32V, with 2A load on the output. One input cable was disconnected.



3 Efficiency

The efficiency is shown in the Figure 7 below. The input voltage was set to 8V, 20V and 32V.

 


Figure 7

4 Load Regulation

The load regulation of the output is shown in the Figure 8 below. The input voltage was set to 8V, 20V and 32V.

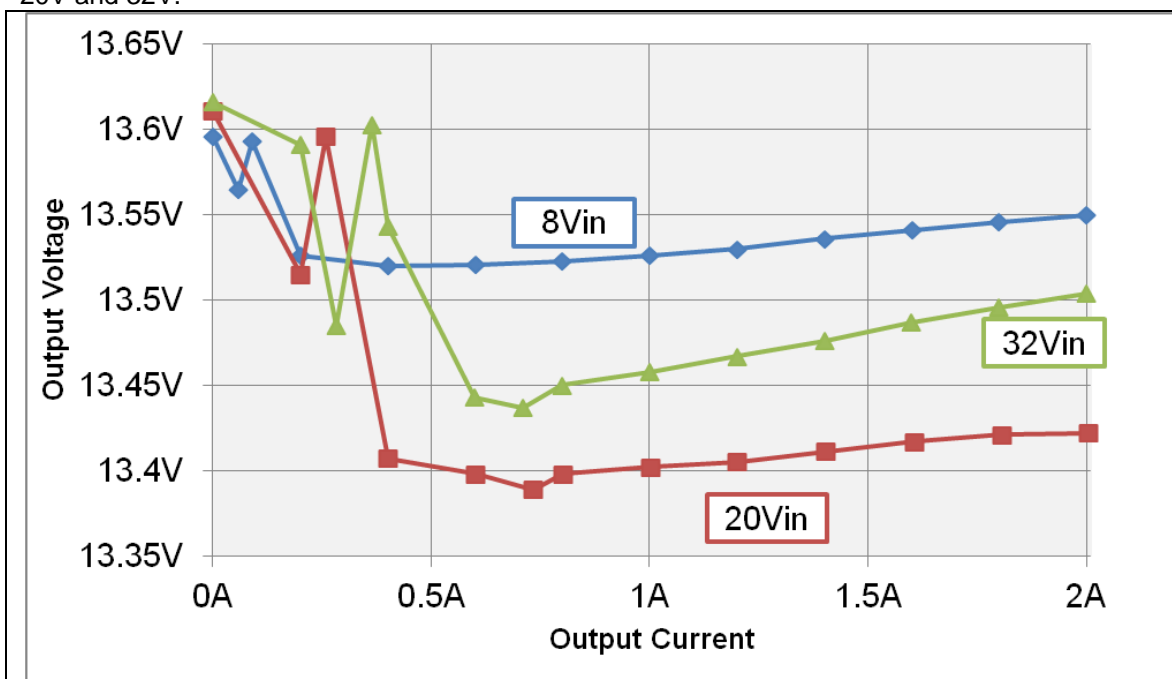


Figure 8

PMP8709RevC Test Results

5 Line Regulation

The line regulation is shown in Figure 9. The output current was set about 2A.

 


Figure 9

With the same setup the efficiencies are shown in Figure 10.


 


Figure 10


6 Output Ripple Voltage

 The output ripple voltage is shown in Figure 11. The output current was set to 2A



7 Input Ripple Voltage

 The output ripple voltage is shown in Figure 12 The output current was set to 2A



8 Load Transients

The Figure 13 shows the response to load transients. The load is switching from 1A to 2A. The input voltage was set to 8V

 


Figure 13

Upper pic shows transient response for ceramics only, lower pic w/ 1000uF added;
For use of this design powering a capacitor bank for pulsed loads **gain needs to be adjusted**.

PMP8709RevC Test Results

The Figure 14 shows the response to load transients. The load is switching from 1A to 2A. The input voltage was set to 20V

 


Figure 14

Upper pic shows transient response for ceramics only, lower pic w/ 1000uF added;
For use of this design powering a capacitor bank for pulsed loads **gain needs to be adjusted**.

The Figure 15 shows the response to load transients. The load is switching from 1A to 2A. The input voltage was set to 32V

 


Figure 15

Upper pic shows transient response for ceramics only, lower pic w/ 1000uF added;
For use of this design powering a capacitor bank for pulsed loads **gain needs to be adjusted.**

9 Control Loop Frequency Response

Figure 16 shows the loop response. 2A-load applied. The input voltage was set to 8V.

 


Figure 16

Figure 17 shows the loop response. 2A-load applied. The input voltage was set to 20V.

 


Figure 17

PMP8709RevC Test Results

Figure 18 shows the loop response. 2A-load applied. The input voltage was set to 32V.

 


Figure 18

Table 1 summarizes the results from Figure 16 Figure 17 and Figure 18.

Vin	8V	20V	32V
Bandwidth (kHz)	4.23	5.95	6.94
Phase margin	52°	58	55
slope (20dB/decade)	-0.89	-1.23	-1.34
gain margin (dB)	-6.86	-13.4	-14.9
slope (20dB/decade)	-0.54	-1.52	-1.79
freq (kHz)	12.5	18.5	20.6

Table 1

PMP8709RevC Test Results

Figure 19 and Figure 20 shows the influence of an additional output electrolytic cap (1000 μ F/25V). The input voltage was set to 20V with 2A output current..

without cap

 


Figure 19

added 1000 μ F

 


Figure 20

Upper pic shows Bode plot for ceramics only, lower pic w/ 1000 μ F added;
For use of this design powering a capacitor bank for pulsed loads **gain needs to be adjusted**.
Here in example gain has to be increased **by 20dB** to achieve bw 2kHz.
(reduce Zero to 200Hz, set Pole to 20kHz)

	no added Cap	1000 μ F
Bandwidth (kHz)	5.98	0.349
Phase margin	58°	34.3
slope (20dB/decade)	-1.19	-1.23
gain margin (dB)	-13.4	-34.9
slope (20dB/decade)	-1.45	-0.194
freq (kHz)	18.6	44.9

Table 2

10 Miscellaneous Waveforms

The waveform of the voltage on Q1 (Drain-Source) is shown in Figure 21. Input voltage was set to 8V and output current to 2A.

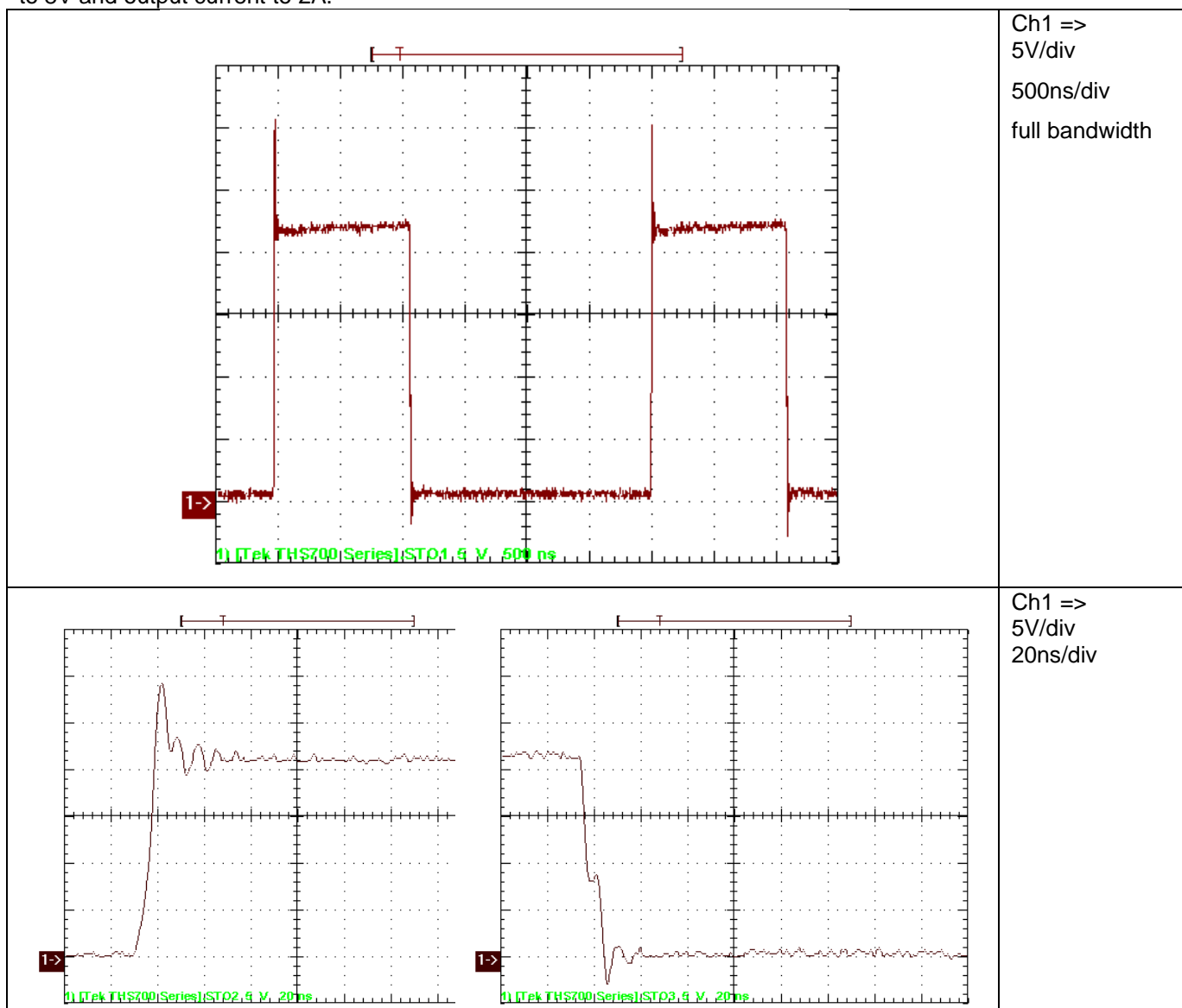


Figure 21

The waveform of the voltage on the gate to source is shown in Figure 22. Input voltage was set to 8V and output current to 2A.

 


Figure 22

PMP8709RevC Test Results

The waveform of the voltage on Q1 (Drain-Source) is shown in Figure 23. Input voltage was set to 20V and output current to 1A.

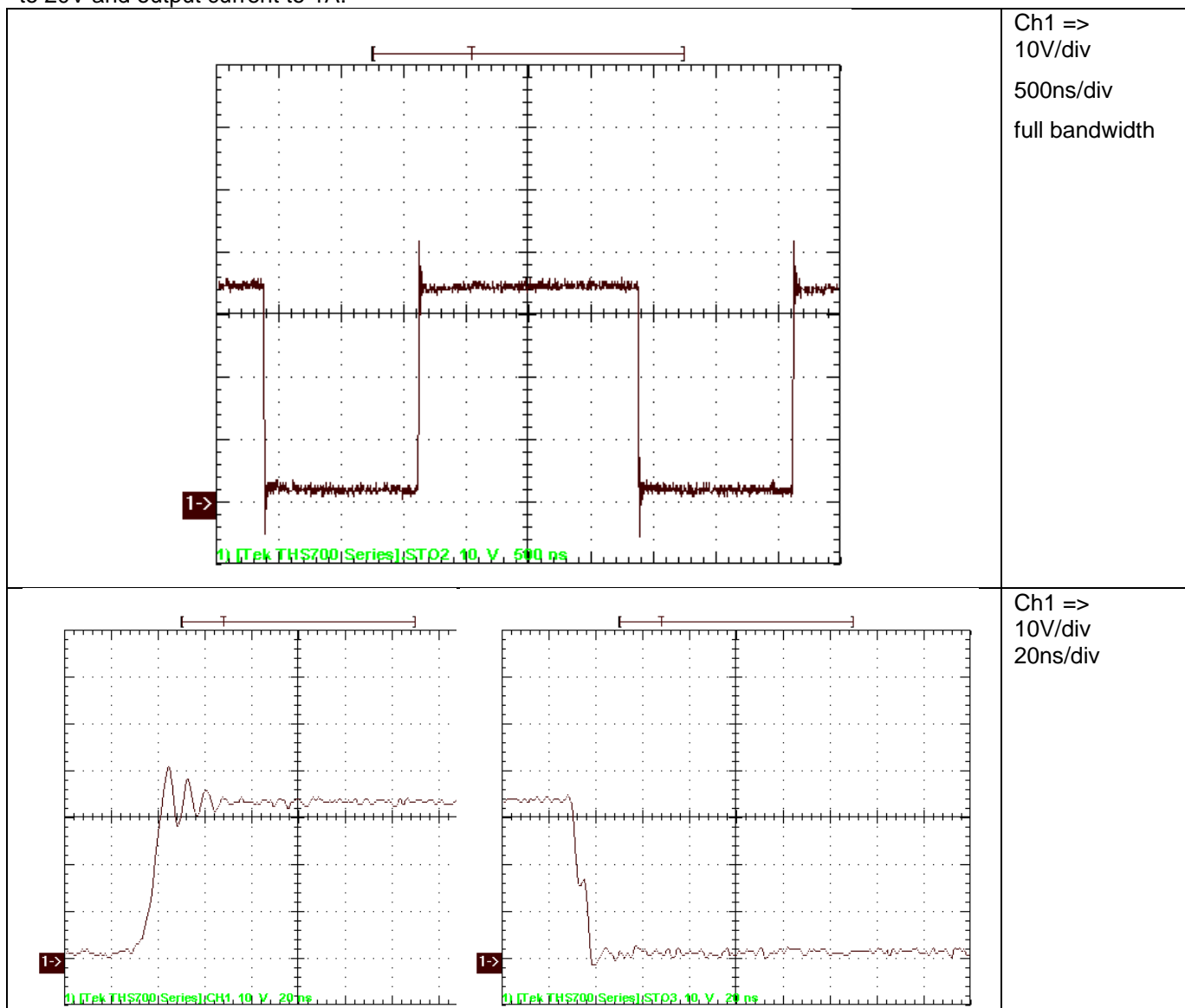


Figure 23

PMP8709RevC Test Results

The waveform of the voltage on the gate to source is shown in Figure 24. Input voltage was set to 20V and output current to 2A.

 


Figure 24

PMP8709RevC Test Results

The waveform of the voltage on Q1 (Drain-Source) is shown in Figure 25. Input voltage was set to 32V and output current to 2A.

 


Figure 25

The waveform of the voltage on the gate to source is shown in Figure 26. Input voltage was set to 32V and output current to 2A.

 


Figure 26

PMP8709RevC Test Results

The waveform of the voltage on D1 (**referenced to VOUT**) is shown in Figure 27. Input voltage was set to 8V and output current to 2A.

 


Figure 27

PMP8709RevC Test Results

The waveform of the voltage on D1 (**referenced to VOUT**) is shown in Figure 27. Input voltage was set to 20V and output current to 2A.

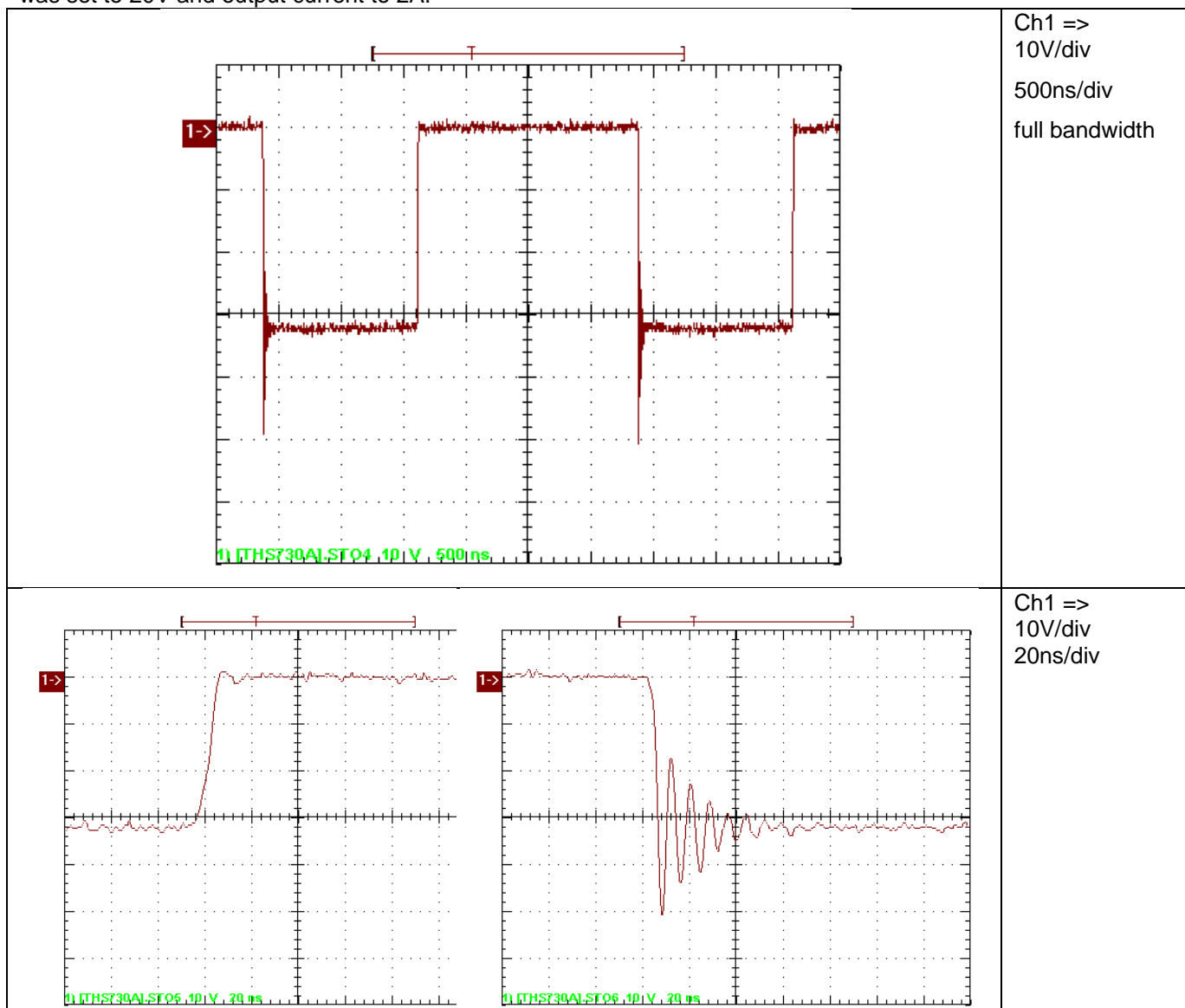


Figure 28

The waveform of the voltage on D1 (**referenced to VOUT**) is shown in Figure 29. Input voltage was set to 32V and output current to 2A.

 


Figure 29

11 Thermal Image

Figure 30 shows the thermal image at 20V input voltage and 2A output current.

 


Figure 30

Name	Temperature
D1	58.3°C
Q1	52.8°C
R5	48.8°C
U1	45.2°C
L1	51.5°C

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.