

**Test Data
For PMP10748
09/20/2015**



Table of Contents

1. Design Specifications	2
2. Circuit Description.....	3
3. Block Diagram	4
4. Board Schematic	5
5. PMP10748 Board Photos	6
6. Adjustable Overcurrent Protection Test Results	8
4.2 Waveforms.....	8
4.2.1 20A+ Overcurrent Protection.....	8
4.2.2 20A Overcurrent Protection (Ramp input)	10
4.1 Thermal Data.....	11
5. Adjustable Overvoltage Protection Test Results.....	12
5.1 Waveforms.....	12
6. Under voltage-Lockout Test Result	13
6.1 UVLO Waveform	13
6.2 UVLO and OVP Waveform	14
7. Reverse Polarity Protection Test Result.....	15
7.1 Reverse Polarity Protection Waveform 1	15
7.2 Reverse Polarity Protection Waveform 2	16
8. OR-ing Solution with LM74610-Q1	17
8.1 Waveform 1	17
8.1 Waveform 2	18

1. Design Specifications

Vin Minimum	12V
Vin Maximum	36V
Vout	12VDC
Iout	20A
Reverse Polarity Protection	Yes
Over Voltage Range	36V
Under Voltage Lockout	Not Populated
Over Current Protection	20A+
OR-ing Controller	Yes

2. Circuit Description

PMP10748 is a complete front end system protection design with the following features:

1. Reverse Polarity Protection:

The LM74610-Q1 Smart diode controller is combined with SQJ422EQ N-Channel MOSFET to provide reverse current and reverse voltage protection. The LM74610-Q1 is used to provide gate drive to the external MOSFET, and to protect the load in the case of reverse polarity by shutting down the gate within 2usec.

2. Smart Diode OR-ing Controller:

The PMP10748 replaces diode ORing for redundant power supplies with LM74610-Q1 Smart Diode Controller solution. This solution makes the OR-ing Controller device 10x more efficient.

3. Over Voltage Protection:

The LM5060 provides an over voltage and series fault protection when the input voltage surges higher than 36V. OVP can be calculated using the following expression:

$$V_{INMAX} = OVP_{TH} + \frac{R_2 \times OVP_{TH}}{R_3}$$

4. Over Current Protection:

The LM5060 uses a sense resistor to provide over current protection when the output current exceeds 20A.

5. Under Voltage Lockout (optional):

This option is not populated, but the design included an under voltage lock out. By placing appropriate resistor values for R_u and R_o , the under voltage lockout can be set to any desired value. The resistor values for under voltage lockout can be calculated using the following expression:

$$R_u = \frac{V_{INMIN} - UVLO_{TH}}{\left(UVLO_{BIAS} + \frac{UVLO_{TH}}{R_o} \right)}$$


$$V_{INMIN} = UVLO_{TH} + \left[R_u \times \left(UVLO_{BIAS} + \frac{UVLO_{TH}}{R_o} \right) \right]$$


*Pick any value for R_o and R_3 below 100kΩ

* $UVLO_{BIAS} = 5.5\mu A$, $UVLO_{TH} = 1.6V$

* $OVP_{BIAS} = 0\mu A$, $OVP_{TH} = 2.0V$


3. Block Diagram

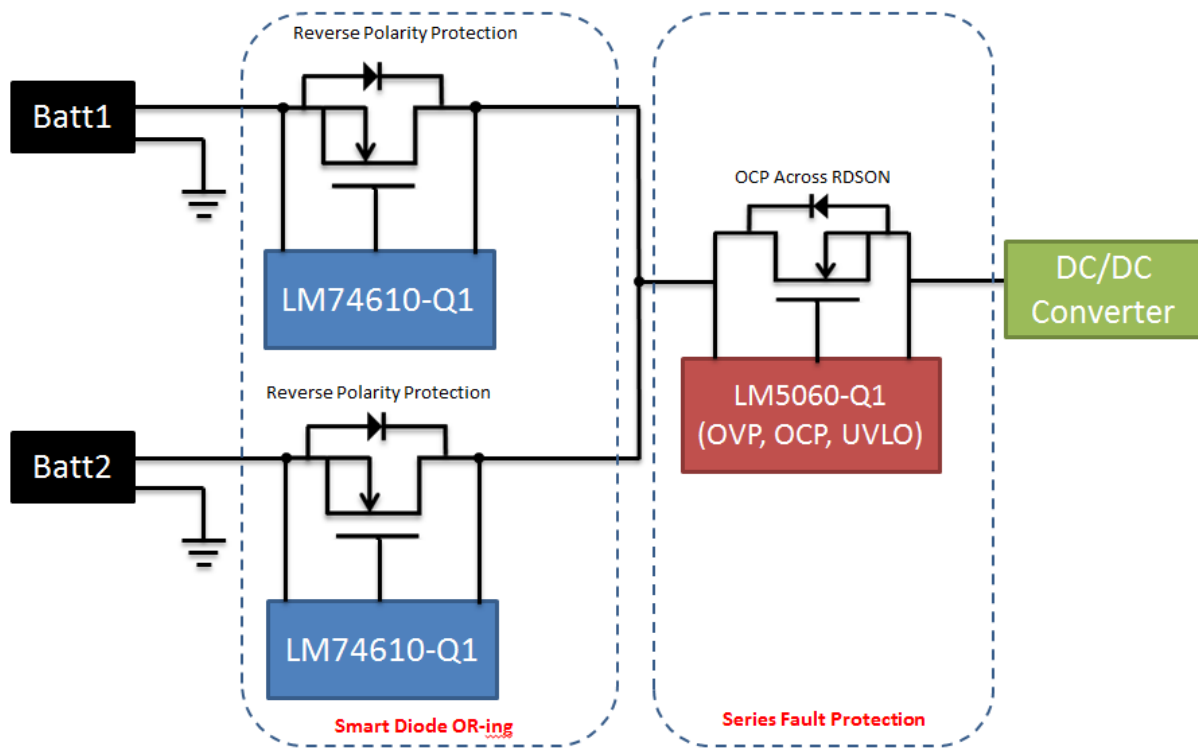

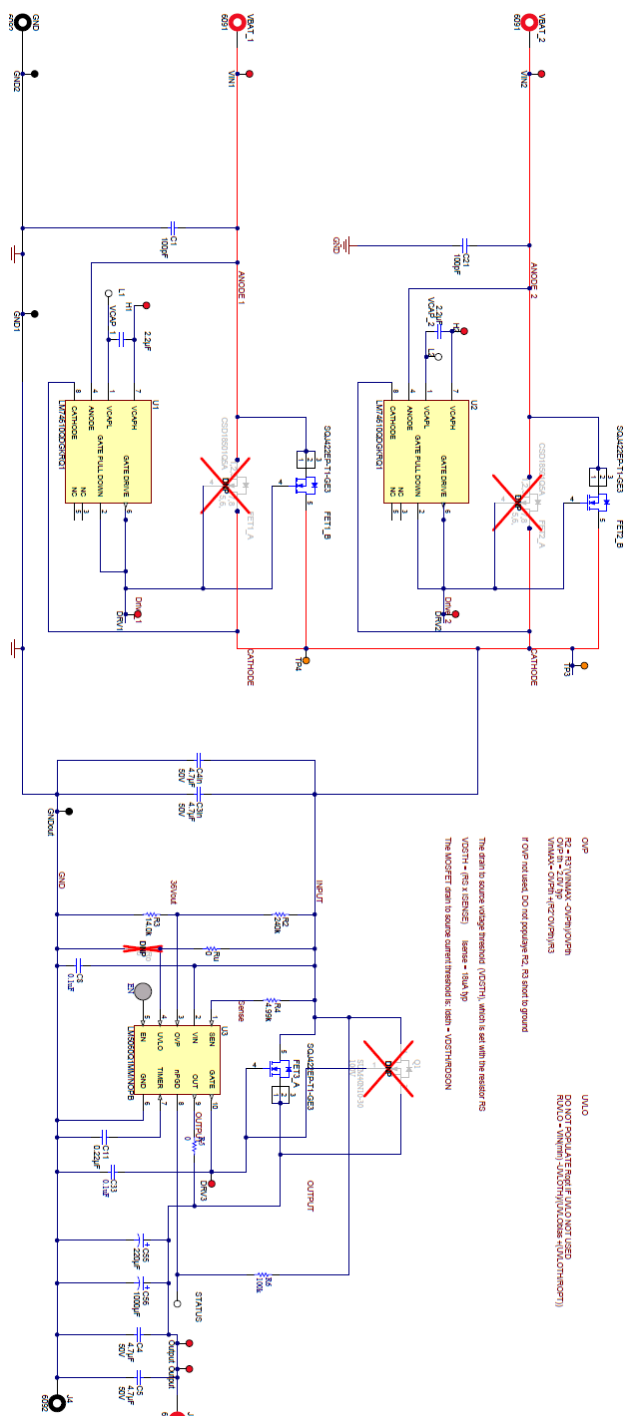



5. PMP10748 Board Photos

Board Dimensions: 4682mil *2840mil

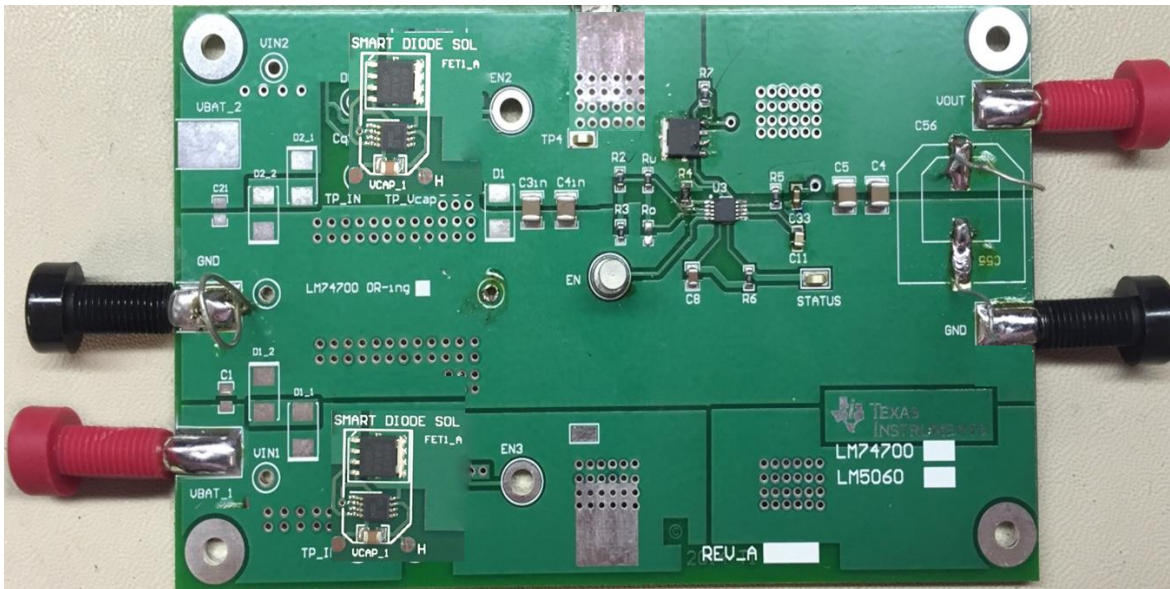


Board Photo (Top)

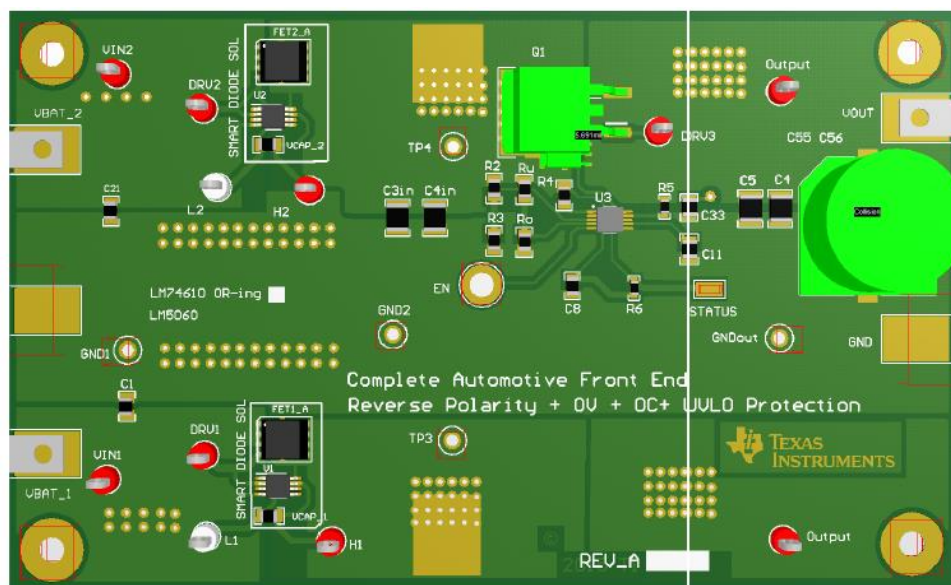

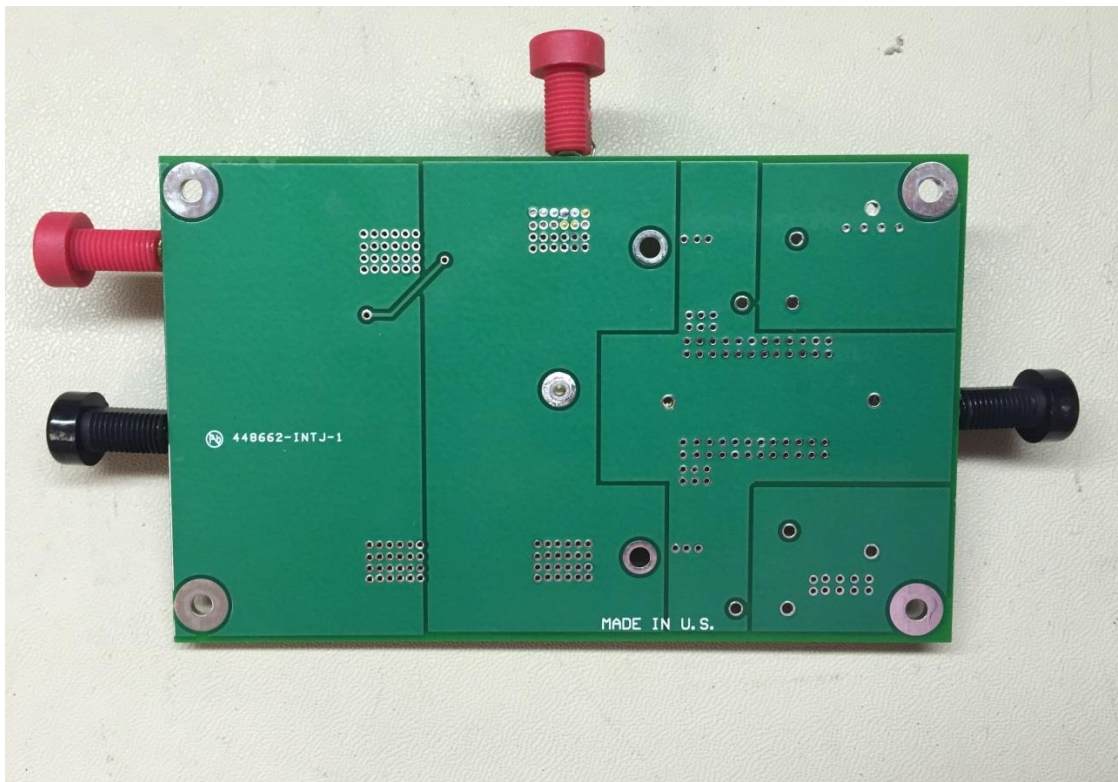

Board Photo (Bottom)

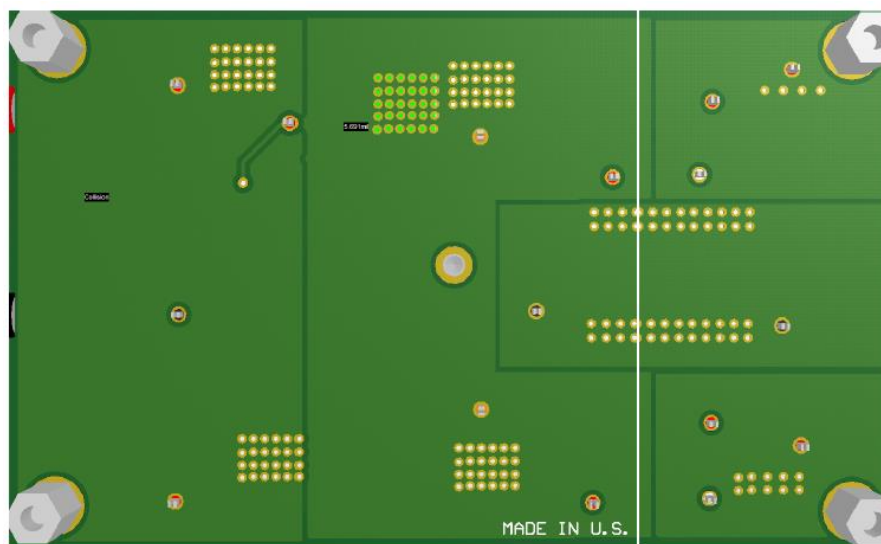


6. Adjustable Overcurrent Protection Test Results

For the test performed, the sense resistor was set at 5k Ω which allowed the Overcurrent threshold to be set around 20A.

4.2 Waveforms

4.2.1 20A+ Overcurrent Protection

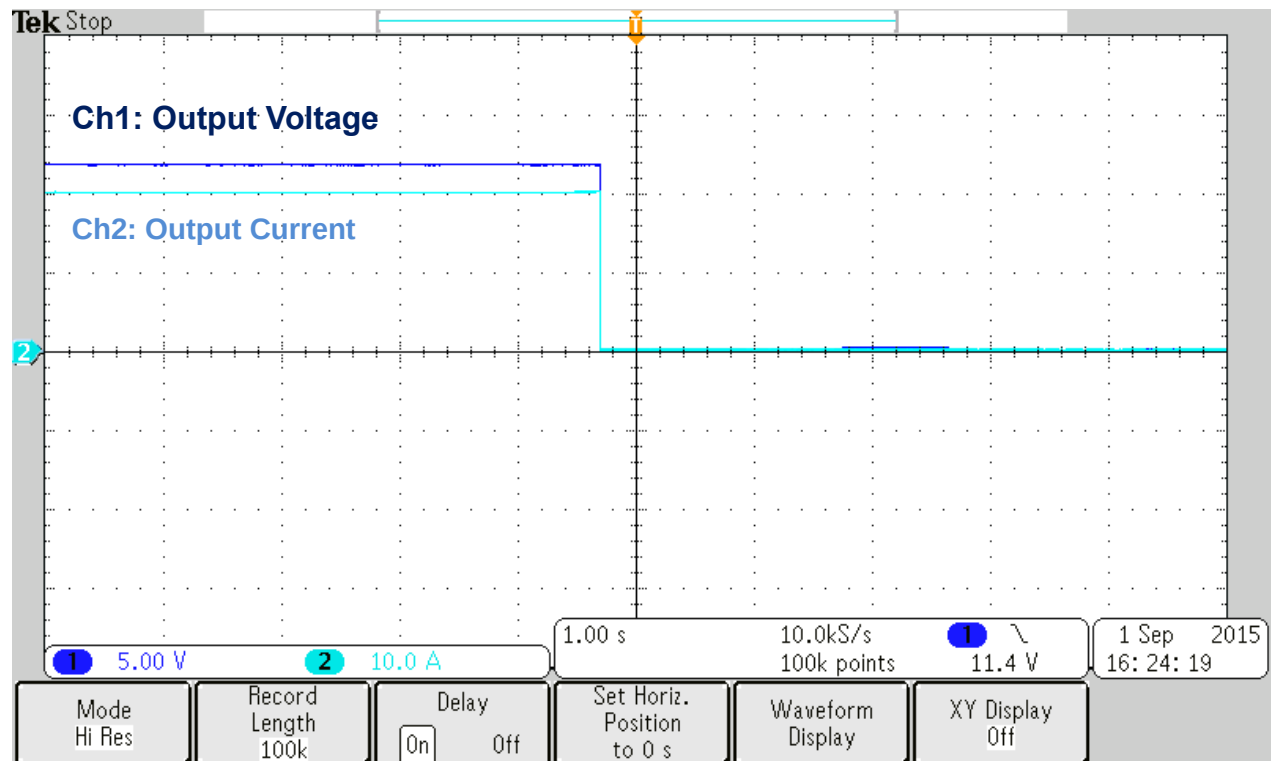


Overcurrent Protection Response: Current shift from 19.5A steady state to 20A.

$R_{\text{sense}} = 5\text{k}\Omega$.

Teal- I_{out}

Blue- V_{out}

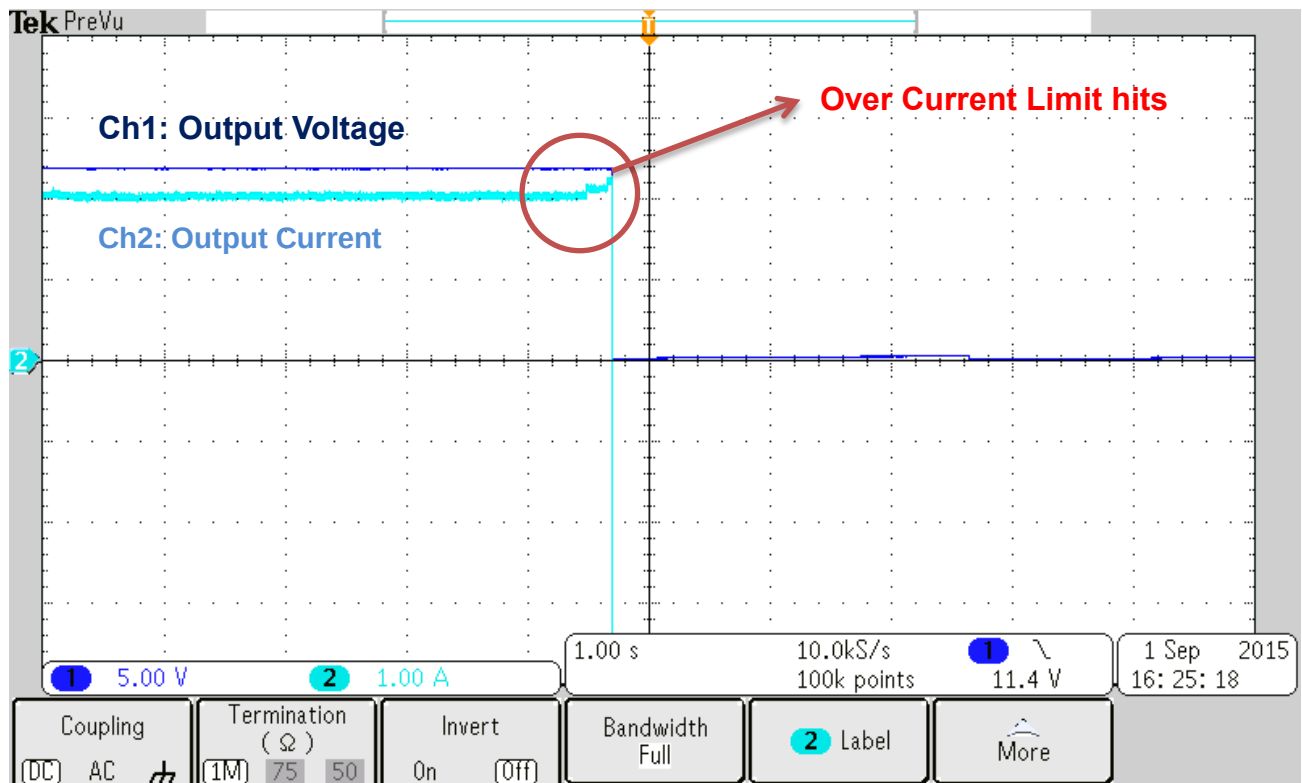

(Zoomed in)


Overcurrent Protection Response: Current shift from 19.5A steady state to 20A.

$R_{\text{sense}} = 5\text{k}\Omega$.

Teal- I_{out}

Blue- V_{out}

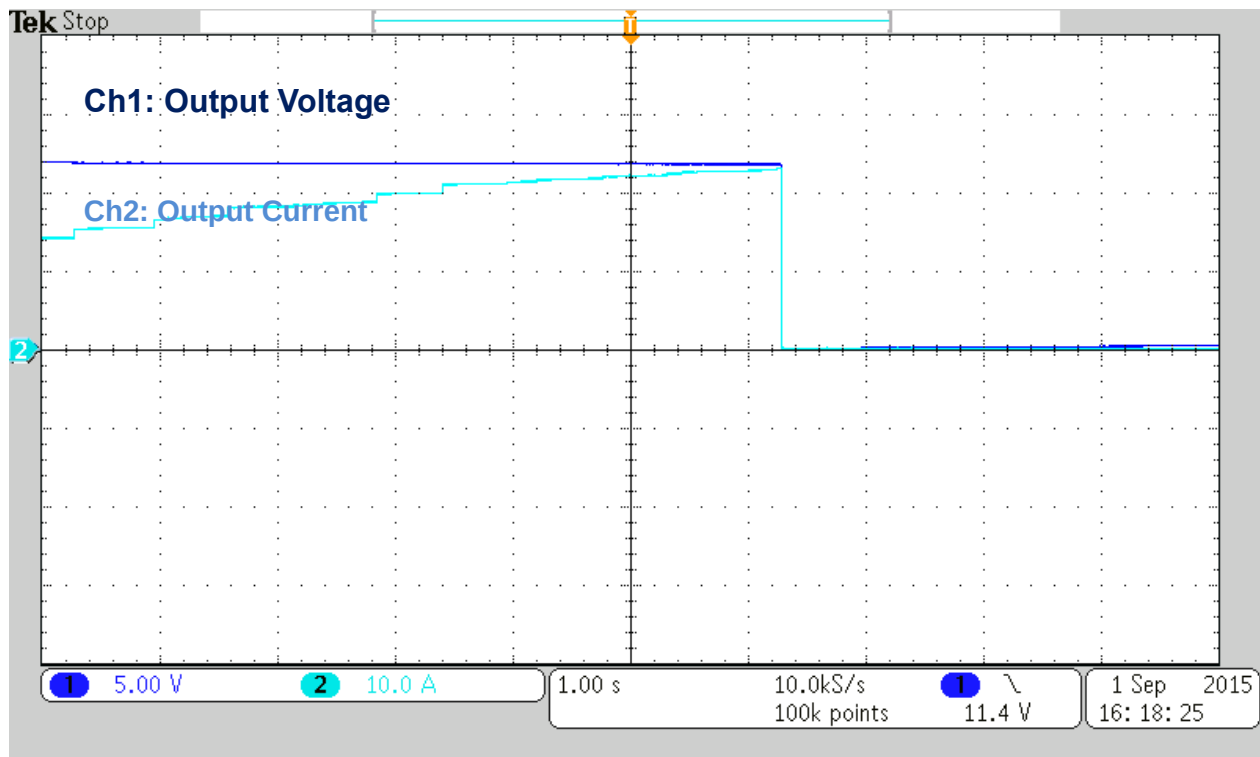4.2.2 20A Overcurrent Protection (Ramp input)




Overcurrent Protection Response: Current ramp from 0A to +20A.

$R_{\text{sense}} = 5\text{k}\Omega$.

Teal- I_{out}

Blue- V_{out}

4.1 Thermal Data

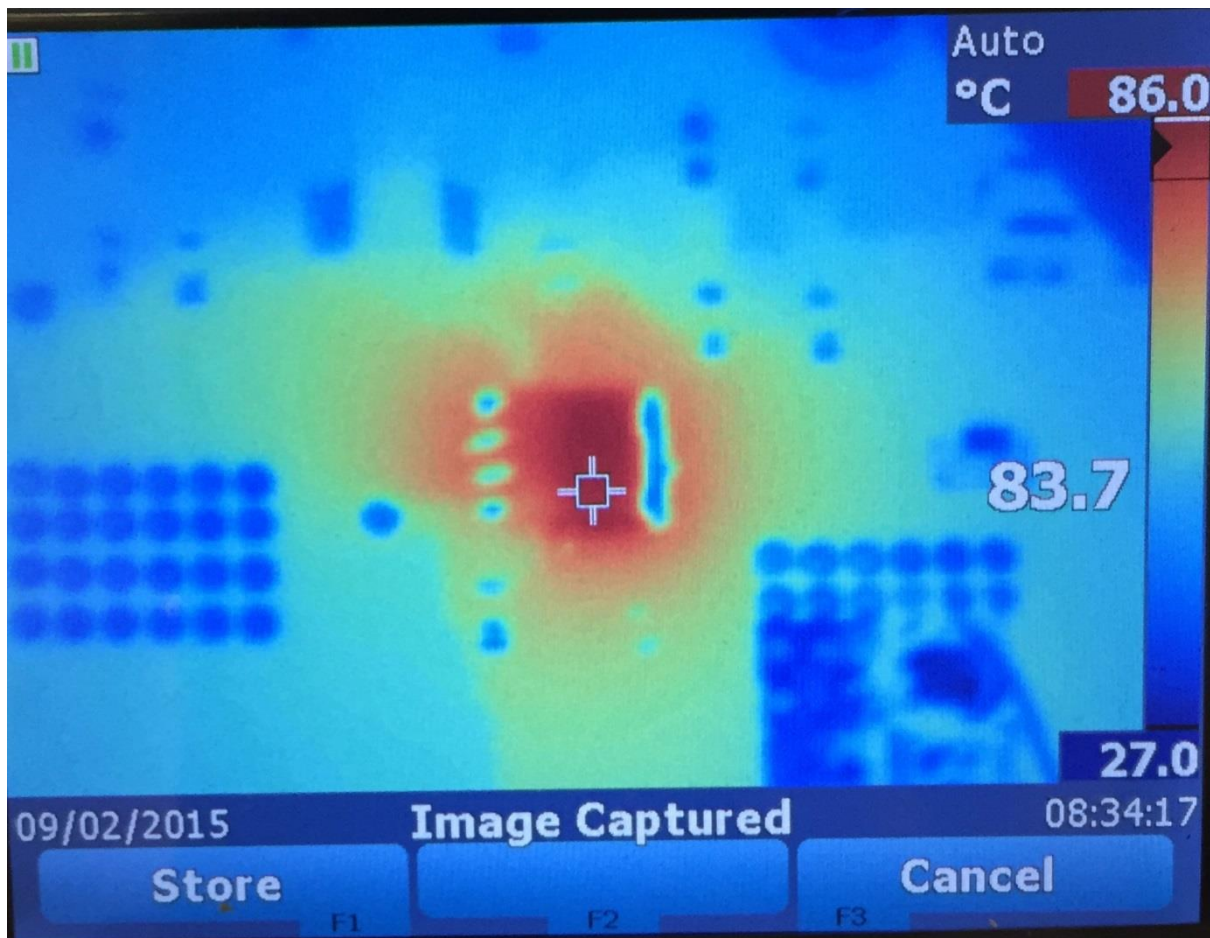


IR thermal image taken at steady state with 12V V_{in} and 20 A load.

5. Adjustable Overvoltage Protection Test Results

The Overvoltage threshold was set at 36V. This is done by.....

5.1 Waveforms

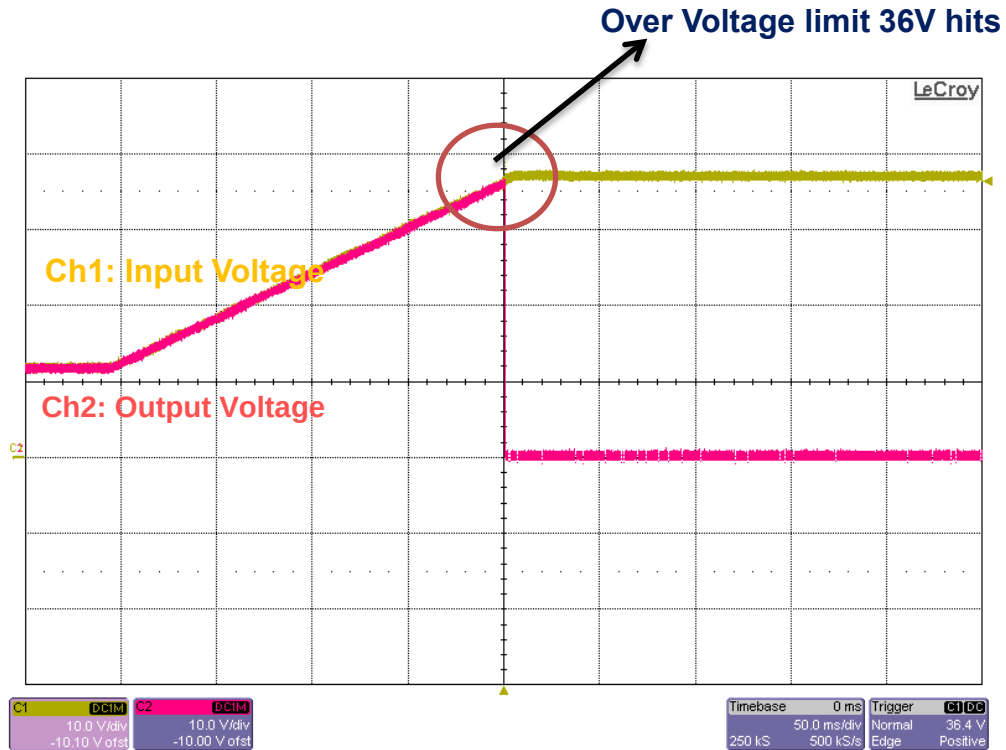

Overvoltage Protection Response: Voltage ramp from 0V to 36V.


Green- V_{in}

Red- V_{out}

6. Under voltage-Lockout Test Result

The board does not have under voltage lock out populated. The function is disabled by shorting Ru to Vin and not populating Ro, but the option is available.

6.1 UVLO Waveform

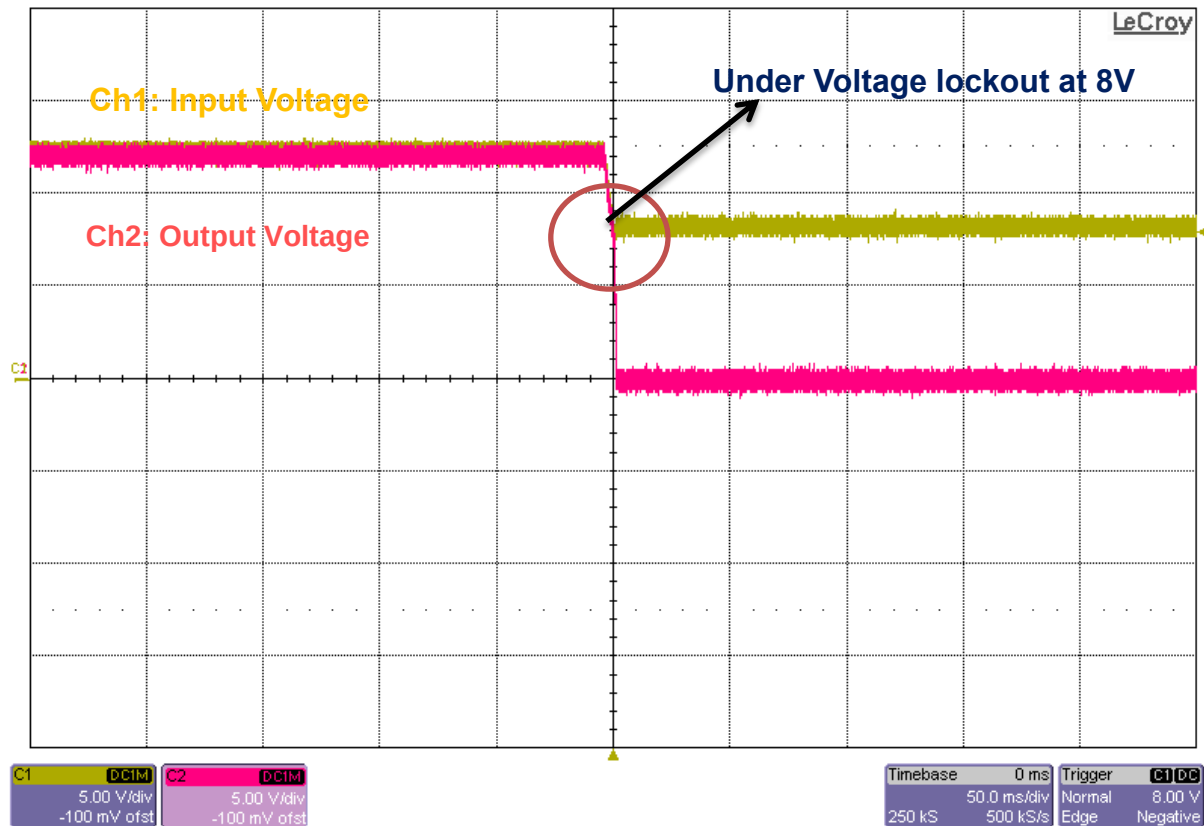


Undervoltage-Lockout Response: Voltage ramp from 12V to 8V.

Green- V_{in}

Red- V_{out}

6.2 UVLO and OVP Waveform

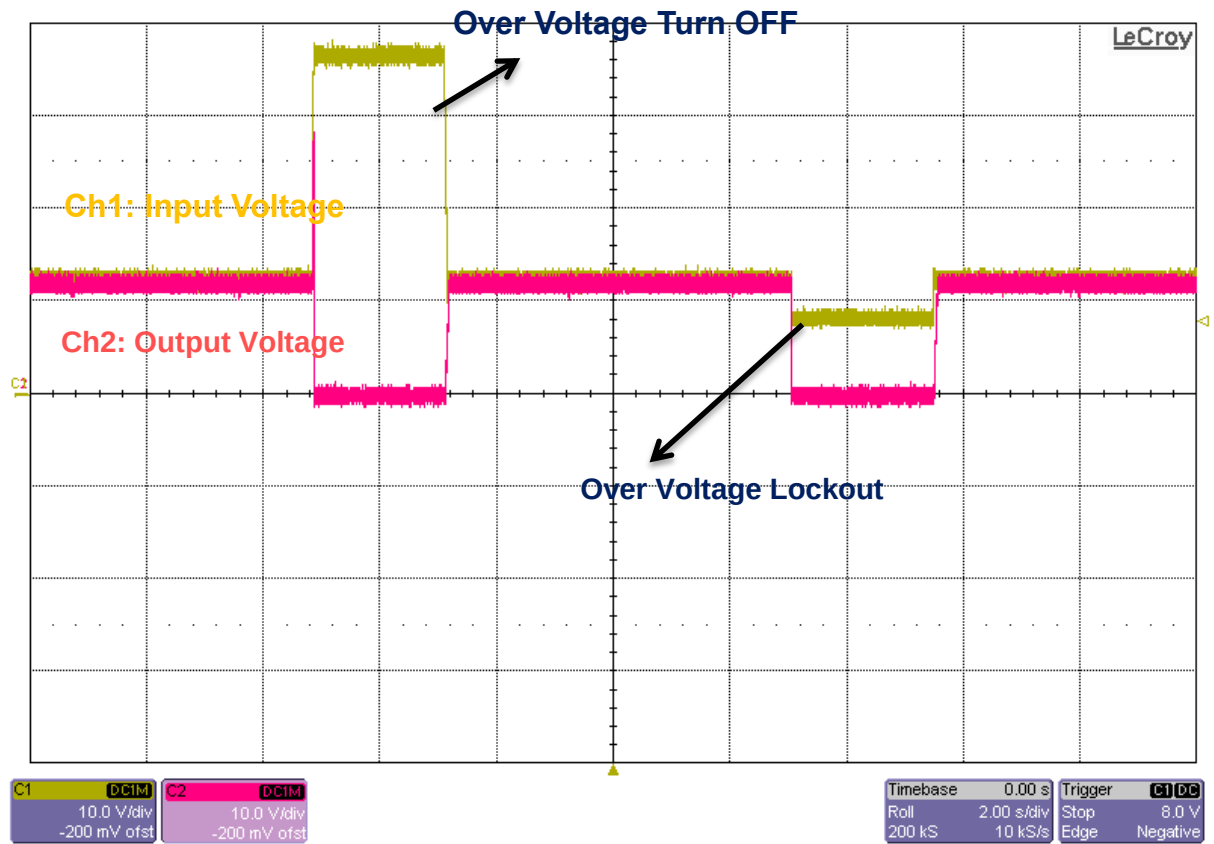

UVLO and OVP Response: Voltage pulse from 12V to 36V and a second pulse from 12V to 8V.


Green- V_{in}

Red- V_{out}

7. Reverse Polarity Protection Test Result

Using the LM74610-Q1 Smart diode in series with LM5060 the board is also given the ability to protect against reverse polarity.

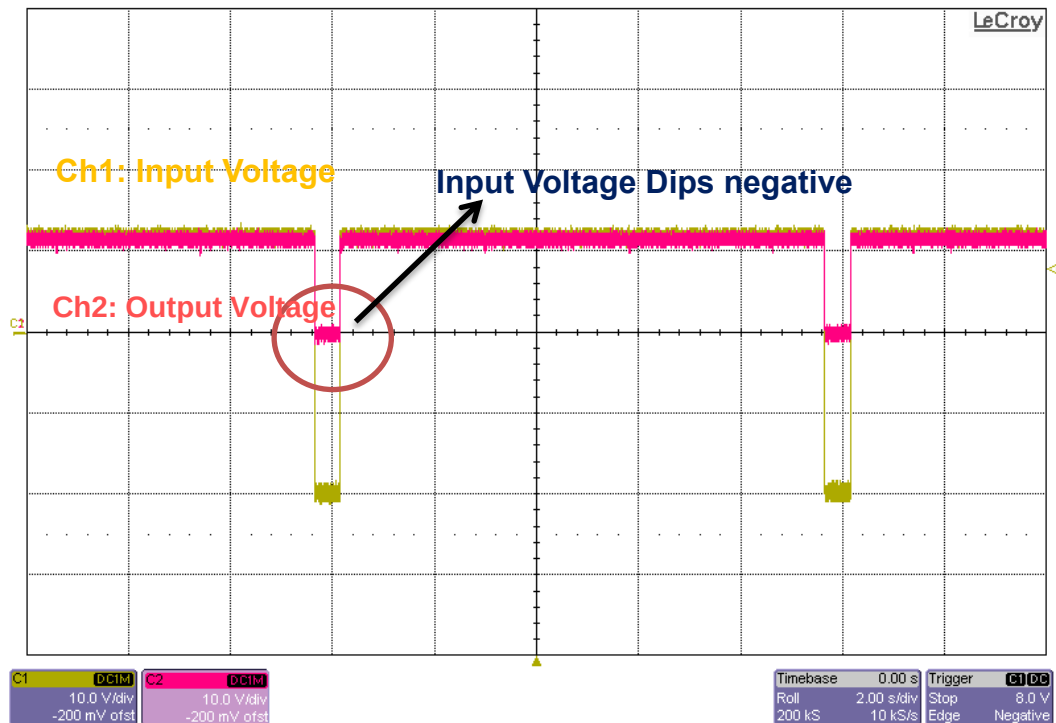7.1 Reverse Polarity Protection Waveform 1




Reverse Polarity Protection Response: Voltage pulse from 12V to -20V.

Green- V_{in}

Red- V_{out}

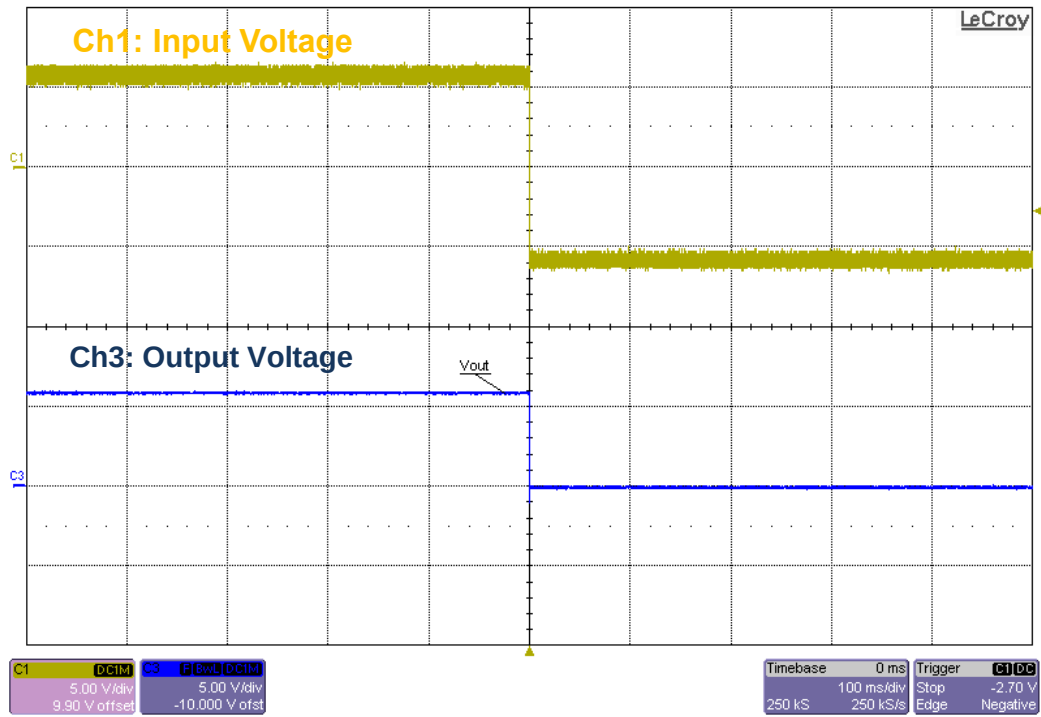7.2 Reverse Polarity Protection Waveform 2



Reverse Polarity Protection Response: Voltage pulse from 6V to -6V.


Green- V_{in}

Blue- V_{out}

8. OR-ing Solution with LM74610-Q1

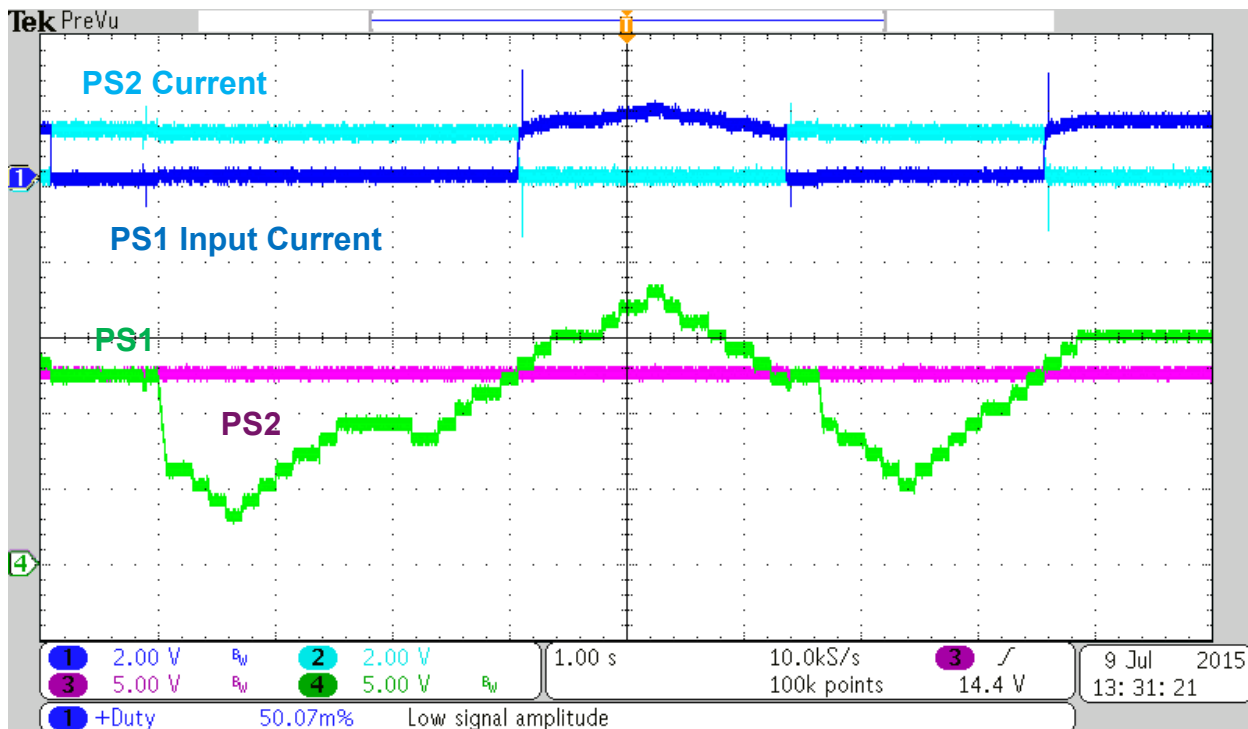8.1 Waveform 1

The following scope plot shows that changing the PS1 (Green) and PS2 (Pink) doesn't get affected. The output current is 1.5A for the following test. As the PS1 voltage increases, the input Current through PS2(light blue) immediately becomes zero after a negative current spike.



Power Supply OR-ing with PMP10748

Green- Supply 1


Pink- Supply 2

Blue- PS1 Input Current

Teal- PS3 Input Current

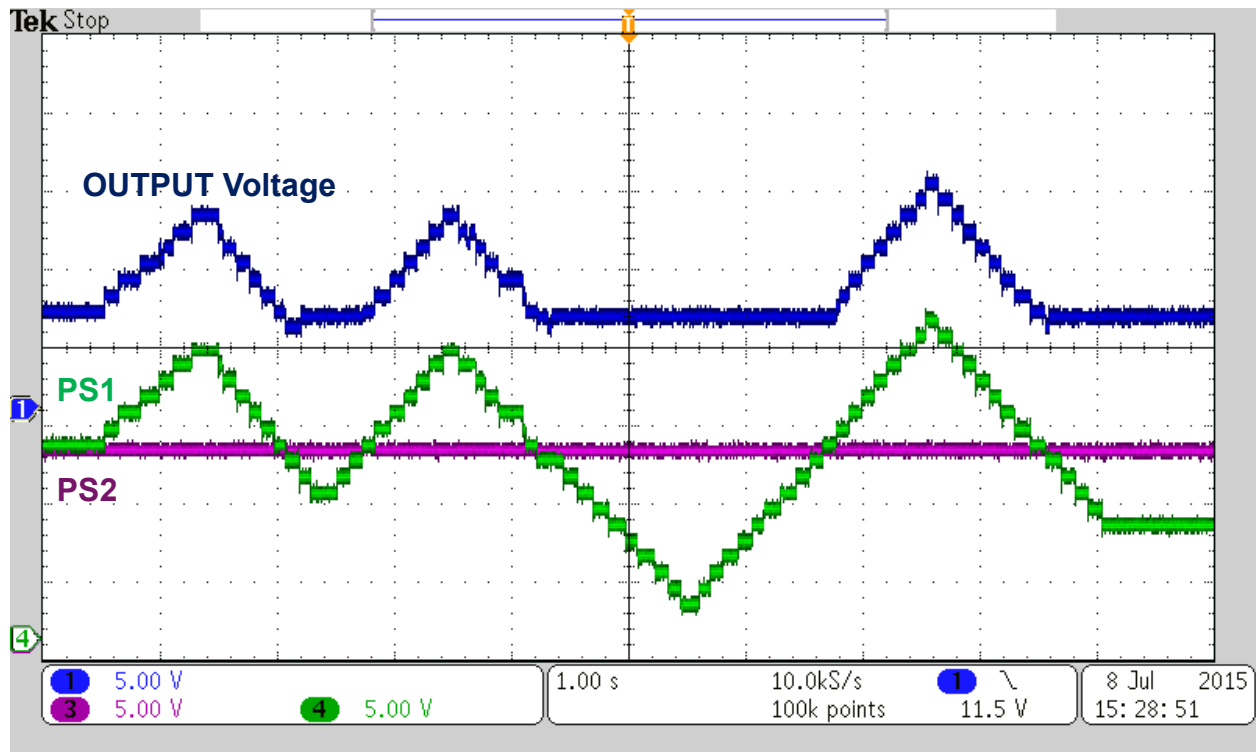8.1 Waveform 2

The following scope plot shows that voltage interruption at PS1 (Green) and PS2 (Pink) doesn't get affected. The output Voltage (Blue) follows the higher supply voltage similar to the diode ORing device. The output current is 1.5A for the following test.



Green- Supply 1

Pink- Supply 2

Blue- Output Voltage

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.