

## Fairchild Reference Design RD-440

The following reference design supports inclusion of FSFR2100 in design of an auxiliary power supply. It should be used in conjunction with the FSFR2100 datasheet as well as Fairchild's application notes and technical support team. Please visit Fairchild's website at <http://www.fairchildsemi.com>.

Application	Fairchild Device	Input Voltage Range	Rated Output Power	Output Voltage (Rated Current)	Topology
Auxiliary Power	FSFR2100	185-265 V <sub>AC</sub>	264 W	33 V (8 A)	Half-Bridge Resonant

### Key Features

- Variable Frequency Control with 50% Duty Cycle for Half-Bridge Resonant Converter Topology
- High Efficiency through Zero Voltage Switching (ZVS)
- Internal SuperFET®s with Fast-Recovery Type Body Diode (trr=120 ns)
- Fixed Dead Time (350 ns) Optimized for MOSFETs
- Up to 300 kHz Operating Frequency
- Pulse Skipping for Frequency Limit (Programmable) at Light-Load Condition
- Remote On/Off Control Using Control Pin
- Protection Functions: Over-Voltage Protection (OVP), Over-Load Protection (OLP), Over-Current Protection (OCP), Abnormal Over-Current Protection (AOCP), Internal Thermal Shutdown (TSD)

**Figure 1. Schematic**

## 2. Transformer

### 2.1. Transformer Schematic Diagram

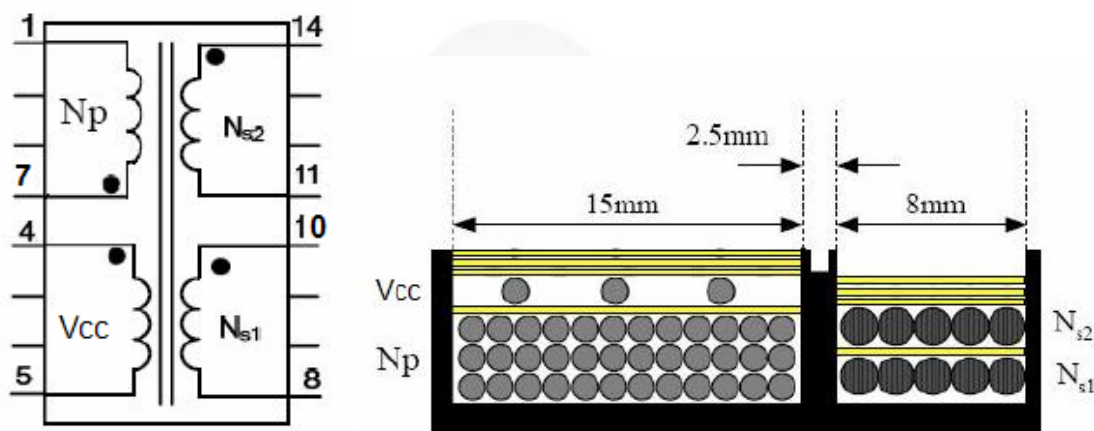


Figure 2. Transformer Configuration and Winding Stackup

### 2.2. Winding Specification

Windings	Pins (S→F)	Strands x Wire $\phi$	Turns	Layers	Winding Method
Primary	7→1	30 x 0.12 mm	36	3	Solenoid
Vcc	4→5	1 x 0.224 mm	3	1	Spaced
Sec_1	14→11	90 x 0.1 mm	6	1	Solenoid
Sec_2	10→8	90 x 0.1 mm	6	1	Solenoid

Core: EER3542 ( $A_e = 107\text{mm}^2$ )

Bobbin: EER3542 Horizontal / 14 pins

### 2.3. Electrical Characteristics

	Pin	Specification	Remark
Inductance	7→1	640 $\mu\text{H} \pm 5\%$	100 kHz, 100 mV
Leakage	7→1	110 $\mu\text{H} \pm 5\%$	Short all secondaries

### 3. Bill of Materials

Part	Value	Qty.	Note
R101	0.15	1	2W
R102	1 k	1	1/4W
R104	2.7 k	1	1/4W
R105	11 k	1	1/4W
R106	270	1	1/4W
R107	2 k	1	1/4W
R108	68	1	1/4W
R109	470	1	1/4W
R201	10 k	1	1/4W
R202	1 k	1	1/4W
R203	10 k	1	1/4W
R204	91 k	1	1/4W
R205	7.5 k	1	1/4W
R206	2 k	1	1/4W
C101	330 nF	1	Film
C102	33 nF	1	Film
C103	100 pF	1	Ceramic
C104	n.c		
C105	47 $\mu$ F	1	Electrolytic
C106	150 nF	1	Ceramic
C107	6.8 $\mu$ F	1	Electrolytic
C108	680 pF	1	Ceramic
C109	10 nF	1	Ceramic
C201	470 $\mu$ F	1	Electrolytic
C202	470 $\mu$ F	1	Electrolytic
C203	47 nF	1	Ceramic
C204	12 nF	1	Ceramic
D101	RS1J	1	
D102	FDLL4148	1	
D211	FYP2010DN	1	
D212	FYP2010DN	1	
T1	See Specs Above		
IC1	FSFR2100	1	FPS
U2	FOD81X.W	1	Opto-Coupler
U3	KA431LZ	1	Voltage-Reference
F101	3.15 A / 250 V	1	

## 4. Related Resources

[FSFR2100– Product Folder](#)

---

### Reference Design Disclaimer

Fairchild Semiconductor Corporation ("Fairchild") provides these reference design services as a benefit to our customers. Fairchild has made a good faith attempt to build for the specifications provided or needed by the customer. Fairchild provides this product "as is" and without "recourse" and MAKES NO WARRANTY, EXPRESSED, IMPLIED OR OTHERWISE, INCLUDING ANY WARRANTY OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.

Customer agrees to do its own testing of any Fairchild reference designs in order to ensure design meets the customer needs. Neither Fairchild nor Customer shall be liable for incidental or consequential damages, including but not limited to, the cost of labor, requalifications, rework charges, delay, lost profits, or loss of goodwill arising out of the sale, installation or use of any Fairchild product.

Subject to the limitations herein, Fairchild will defend any suit or proceeding brought against Customer if it is based on a claim that any product furnished hereunder constitutes an infringement of any intellectual property rights. Fairchild must be notified promptly in writing and given full and complete authority, information and assistance (at Fairchild's expense) for defense of the suit. Fairchild will pay damages and costs therein awarded against Customer but shall not be responsible for any compromise made without its consent. In no event shall Fairchild's liability for all damages and costs (including the costs of the defense by Fairchild) exceed the contractual value of the products or services that are the subject of the lawsuit. In providing such defense, or in the event that such product is held to constitute infringement and the use of the product is enjoined, Fairchild, in its discretion, shall procure the right to continue using such product, or modify it so that it becomes noninfringing, or remove it and grant Customer a credit for the depreciated value thereof. Fairchild's indemnity does not extend to claims of infringement arising from Fairchild's compliance with Customer's design, specifications and/or instructions, or the use of any product in combination with other products or in connection with a manufacturing or other process. The foregoing remedy is exclusive and constitutes Fairchild's sole obligation for any claim of intellectual property infringement and Fairchild makes no warranty that products sold hereunder will not infringe any intellectual property rights.

All solutions, designs, schematics, drawings, boards or other information provided by Fairchild to Customer are confidential and provided for Customer's own use. Customer may not share any Fairchild materials with other semiconductor suppliers.