

Fairchild Reference Design RD-481

The following reference design supports inclusion of FSQ0370RNA in design of an auxiliary power supply. It should be used in conjunction with the FSQ0370RNA datasheet as well as Fairchild's application notes and technical support team. Please visit Fairchild's website at <http://www.fairchildsemi.com>.

Application	Fairchild Device	Input Voltage Range	Rated Output Power	Output Voltage (Rated Current)	Topology
Auxiliary Power	FSQ0370RNA	150-275 V _{AC}	18 W _{nominal} 25 W _{peak}	24 V (0.675 A, 0.90 A _{peak}) 20 V (0.10 A, 0.15 A _{peak})	Flyback

Key Features

- Internal Avalanche Rugged 700 V SenseFET
- Consumes only 0.8 W at 230 V_{AC} & 0.5 W Load with Burst-Mode Operation
- Precision Fixed Operating Frequency, 100 kHz
- Internal Startup Circuit and Built-in Soft-Start
- Pulse-by-Pulse Current Limiting and Auto-Restart Mode
- Over-Voltage Protection (OVP), Overload Protection(OLP), Internal Thermal Shutdown Function (TSD)
- Under-Voltage Lockout (UVLO)
- Low Operating Current (3 mA)
- Adjustable Peak Current Limit

2. Transformer

2.1. Transformer Schematic Diagram

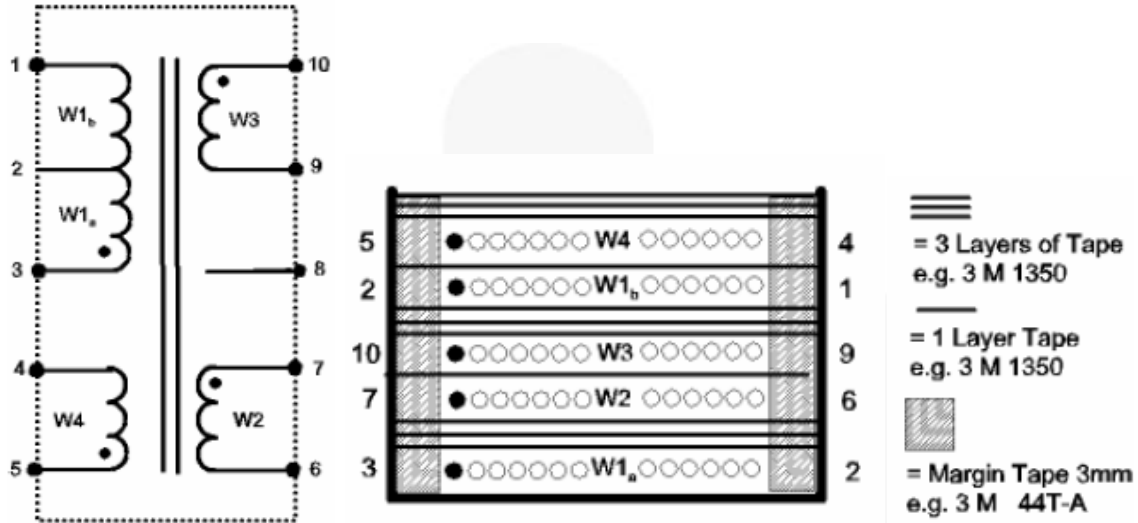


Figure 2. Transformer Configuration and Winding Stackup

2.2. Winding Specification

Winding	Pins (S→F)	Strands x Wire ϕ	Turns	Layers	Winding Method	Material
W1a	3→2	1 x 0.28 mm	39	2	Spaced	CuLL
W2	7→6	1 x 0.6 mm	16	2	Spaced	Tex E
W3	10→9	1 x 0.4 mm	15	1	Spaced	Tex E
W1b	2→1	1 x 0.28 mm	38	2	Spaced	CuLL
W4	5→4	1 x 0.15 mm	8	1	Spaced	CuLL

Core: EF 20

Material: Fi 324 (Vogt) or equivalent

Bobbin: EF 20 / 5.9 horizontal / 10-Pins

Gap in center leg: approx. 0.29 mm for A_L of 126 nH/Turns²

2.3. Electrical Characteristics

	Pin	Specification	Remark
Inductance	1→3	0.75 mH $\pm$ 5%	10 kHz, 100 mV
Leakage	1→3	<20 μ H	Short all other pins

3. Bill of Materials

Reference	Value / Specification	Qty.	Manufacturer / Series
CONN101	2 Pin	1	Phoenix Contact GMKDS 1,5
CONN202	4 Pin	1	Phoenix Contact MKDSN 1,5
C101	220 nF / 275V	1	Arcotronics R46 Series
C102	33 μ F / 400 V	1	Rubycon WA
C103	4.7 μ F / 50 V	1	SAMWHA SD
C105	3.3 nF / 400 V	1	Wima FKS 2
C106	47 nF / 25 V	1	AVX MLC X7R
C108	3.3 nF / 250 V	1	Murata DE
C201,C204	n.a.	2	e.g. Epcos B37981M
C202	33 μ F / 35 V	1	Rubycon ZL
C203,C206	n.a.	2	e.g. SAMWHA SD
C205	470 μ F / 35 V	1	Rubycon ZL
C207	22 nF / 25 V	1	AVX MLC X7R
D101	DF10S	1	Fairchild
D102	RS1K	1	Fairchild
D103	FDLL4148	1	Fairchild
D201	ES1D	1	Fairchild
D202	ES3D	1	Fairchild
FS101	230 V/T1A	1	Wickmann TR5
IC102	FOD2741BS	1	Fairchild
IC103	FSQ0370RNA	1	Fairchild
LF101	2 x 39 mH / 0,6 A	1	Epcos B82731-M
L101,L102	390 μ H / 180 mA	2	e.g. Epcos BC B78108-S
L201	n.a.	1	e.g. Epcos SBC B82141A
L202	n.a.	1	Coilcraft RFB0810
R101	100 k / 2 W	1	Any
R104	0R68 / 0,125 W	1	Any SMD0805
R105,R201,R202	n.a.	3	Any
R203	3k9 / 0.125 W	1	Any SMD0805
R204	13 k / 0.125 W	1	Any SMD0805
R205	1k5 / 0.125 W	1	Any SMD0805
R206	510 k / 0.125 W	1	Any SMD0805
R207,R208	3k3 / 0.125 W	2	Any SMD0805
T101	EF20	1	See specification
VAR101	n.a., S10K275	1	e.g. Epcos B72210S0271K101

4. Performance

4.1. Line Regulation

V_{IN} [V _{RMS}]	150	185	210	230	240	275	Min [%]	Max [%]
V_1 [V]	24,16	24,16	24,16	24,16	24,16	24,16	0,7	0,7
V_2 [V]	20,21	20,22	20,22	20,22	20,22	20,24	1,1	1,2

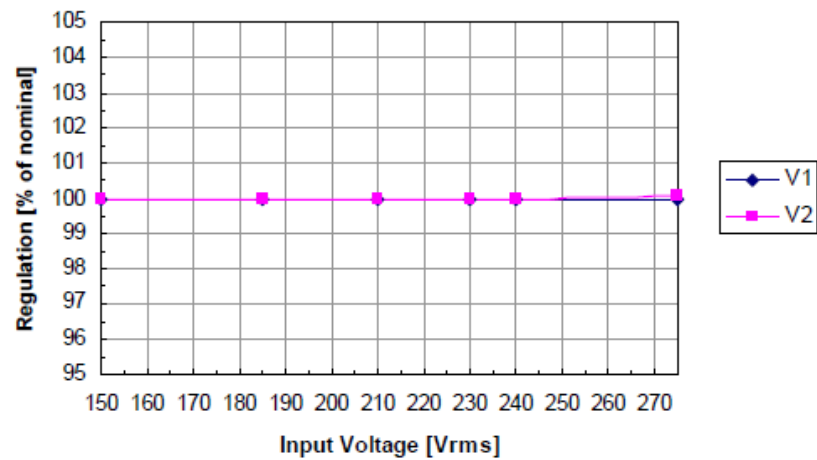


Figure 3. Line Regulation Plotted against Input Voltage

4.2. Efficiency

V_{IN} [V _{RMS}]	150	185	210	230	240	275
P_{OUT} [W]	18,33	18,33	18,33	18,33	18,33	18,33
P_{IN} [W]	20,58	20,74	20,63	20,58	20,61	20,78
Efficiency [%]	89,1	88,4	88,9	89,1	88,9	88,2

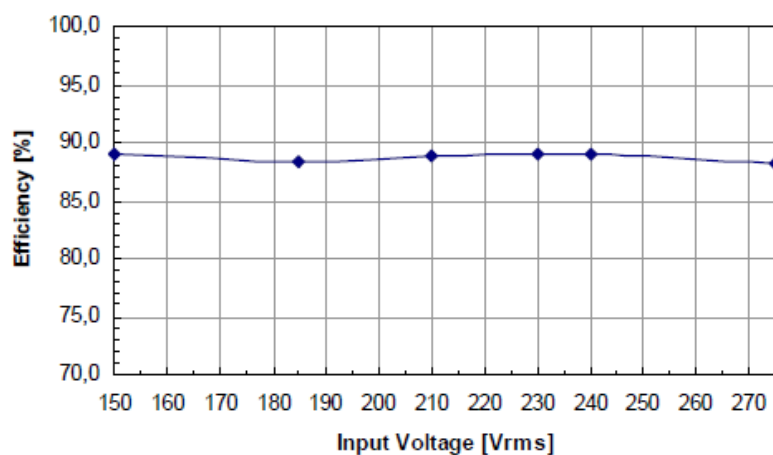


Figure 4. Efficiency Plotted Against Input Voltage

5. Related Resources

[FSQ0370RNA – Product Folder](#)

Reference Design Disclaimer

Fairchild Semiconductor Corporation ("Fairchild") provides these reference design services as a benefit to our customers. Fairchild has made a good faith attempt to build for the specifications provided or needed by the customer. Fairchild provides this product "as is" and without "recourse" and MAKES NO WARRANTY, EXPRESSED, IMPLIED OR OTHERWISE, INCLUDING ANY WARRANTY OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.

Customer agrees to do its own testing of any Fairchild reference designs in order to ensure design meets the customer needs. Neither Fairchild nor Customer shall be liable for incidental or consequential damages, including but not limited to, the cost of labor, requalifications, rework charges, delay, lost profits, or loss of goodwill arising out of the sale, installation or use of any Fairchild product.

Subject to the limitations herein, Fairchild will defend any suit or proceeding brought against Customer if it is based on a claim that any product furnished hereunder constitutes an infringement of any intellectual property rights. Fairchild must be notified promptly in writing and given full and complete authority, information and assistance (at Fairchild's expense) for defense of the suit. Fairchild will pay damages and costs therein awarded against Customer but shall not be responsible for any compromise made without its consent. In no event shall Fairchild's liability for all damages and costs (including the costs of the defense by Fairchild) exceed the contractual value of the products or services that are the subject of the lawsuit. In providing such defense, or in the event that such product is held to constitute infringement and the use of the product is enjoined, Fairchild, in its discretion, shall procure the right to continue using such product, or modify it so that it becomes noninfringing, or remove it and grant Customer a credit for the depreciated value thereof. Fairchild's indemnity does not extend to claims of infringement arising from Fairchild's compliance with Customer's design, specifications and/or instructions, or the use of any product in combination with other products or in connection with a manufacturing or other process. The foregoing remedy is exclusive and constitutes Fairchild's sole obligation for any claim of intellectual property infringement and Fairchild makes no warranty that products sold hereunder will not infringe any intellectual property rights.

All solutions, designs, schematics, drawings, boards or other information provided by Fairchild to Customer are confidential and provided for Customer's own use. Customer may not share any Fairchild materials with other semiconductor suppliers.