

Reference Design RD-356

1. Fairchild Motion SPM® 7 Series

This reference design supports design of Fairchild's Motion SPM® 7 Series. It should be used in conjunction with each datasheet as well as Fairchild's application notes and technical support team. Please visit Fairchild's website at <http://www.fairchildsemi.com>.

Application	Device Name	Max. Supply Voltage	Max. Power Rating	Topology
Home Appliance (Fan Motor)	FSB70625	200 V _{DC}	81 W	3-Phase Inverter
	FSB70325	200 V _{DC}	49 W	
	FSB70550	400 V _{DC}	110W	
	FSB70450	400 V _{DC}	110 W	
	FSB70250	400 V _{DC}	81 W	

1.1. Key Features

- 3-Phase FRFET® Inverter with High-Voltage Integrated Circuit (HVIC)
- Maximum R_{DS(ON)}: FSB70625=0.8 Ω, FSB70325=1.4 Ω, FSB70550=1.85 Ω, FSB70450=2.2 Ω, FSB70250=3.4 Ω
- High-Performance PQFN Package
- Open-Source Pins Separate from Low-Side MOSFETs for 3-Phase Current-Sensing
- Active-HIGH Interface Works with 3.3 V / 5 V Logic
- Schmitt-Trigger Input
- Optimized for Low Electromagnetic Interference (EMI)
- HVIC Temperature-Sensing for Temperature Monitoring
- HVIC for Gate Driving with Under-Voltage Protection (UVP)
- Interlock Function
- Isolation Rating: 1500 V_{RMS} / Min.
- Moisture Sensitive Level (MSL) 3
- RoHS Compliant

The internal circuit diagram is shown in Figure 1. The V_{TS} pin is from the HVIC and provides the temperature-sensing signal.

 


Figure 1. Internal Circuit Diagram

2. Pin Description

 


Figure 2. Pin Numbers and Locations in PQFN Package (Top-Through View)

Table 1. Pin Descriptions

Pin #	Name	Pin Description
1	/FO	Fault Output
2	V _{TS}	Voltage Output of HVIC Temperature
3	C _{fod}	Capacitor for Duration Time of Fault Output
4	C _{sc}	Capacitor (Low-Pass Filter) for Short-Circuit Current Detection Input
5	V _{DD}	Supply Bias Voltage for IC and MOSFETs Driving
6	IN_UH	Signal Input for High-Side U Phase
7	IN_VH	Signal Input for High-Side V Phase
8 (8a)	COM	Common Supply Ground
9	IN_WH	Signal Input for High-Side W Phase
10	IN_UL	Signal Input for Low-Side U Phase
11	IN_VL	Signal Input for Low-Side V Phase
12	IN_WL	Signal Input for Low-Side W Phase
13	N _u	Negative DC-Link Input for U Phase
14	U	Output for U Phase
15	N _v	Negative DC-Link Input for V Phase
16	V	Output for V Phase
17	W	Output for W Phase
18	N _w	Negative DC-Link Input for W Phase
19	V _{S(W)}	High-Side Bias Voltage Ground for W Phase MOSFET Driving
20	P _w	Positive DC-Link Input for W Phase
21	P _v	Positive DC-Link Input for V Phase
22	P _u	Positive DC-Link Input for U Phase

Pin #	Name	Pin Description
23(23a)	$V_{S(V)}$	High-Side Bias Voltage Ground for V Phase MOSFET Driving
24(24a)	$V_{S(U)}$	High-Side Bias Voltage Ground for U Phase MOSFET Driving
25	$V_{B(U)}$	High-Side Bias Voltage for U phase MOSFET Driving
26	$V_{B(V)}$	High-Side Bias Voltage for V phase MOSFET Driving
27	$V_{B(W)}$	High-Side Bias Voltage for W phase MOSFET Driving

3. Application Block Diagram

 


Figure 3. Block Diagram of Outdoor Fan Motor for Air-Conditioner

4. Schematic

 


Figure 4. Schematic for 3-Phase Inverter Part (Direct Coupling)

5. Key Parameter Design

5.1. Selection of Bootstrap Capacitance(C_{BS})

The current flow path of the bootstrap circuit is shown in Figure 5. When V_S is pulled down to ground (either through the low-side or the load), bootstrap capacitor C_{BS} is charged through bootstrap diode D_{BS} and resistor R_{BS} from the V_{DD} supply.

 


Figure 5. Bootstrap Circuit

The bootstrap capacitor of the Motion SPM[®] 7 Series can be calculated by:

$$C_{BS} = \frac{Q_{BS}}{\Delta V_{BS}} \quad (1)$$

where:

Q_{BS} = Total gate charge from C_{BS} ; and

ΔV_{BS} = Allowable drop voltage of the C_{BS} (voltage ripple).

Total gate charge, Q_{BS} , required by the bootstrap capacitor, can be calculated by:

$$Q_{BS} = Q_g + Q_{LS} + (I_{LK,D} + I_{LK,C} + I_{QBS}) \times t_{ON} \quad (2)$$

where:

Q_g = Gate charge to turn on the high-side MOSFET;

Q_{LS} = Level-shift charge required per cycle;

I_{LK} = Total leakage current;

$I_{LK,D}$ = Bootstrap diode leakage current;

$I_{LK,C}$ = Bootstrap capacitor leakage current, which can be ignored if it is not an electrolytic capacitor;

I_{QBS} = Quiescent current of gate driver IC; and

t_{ON} = Maximum on pulse width of high-side MOSFET.

The total leakage current can be calculated by summing all of the individual components' leakage currents. In case of FSB70325, minimum C_{BS} is calculated as:

$$C_{BS_min} = \frac{Q_{BS}}{\Delta V_{BS}} = \frac{Q_g + Q_{LS} + (I_{LK,D} + I_{LK,C} + I_{QBS}) \times t_{ON}}{\Delta V_{BS}} \quad (3)$$

$$= \frac{50 \text{ nC} + (100 \mu\text{A} + 70 \mu\text{A}) \times 200 \mu\text{s}}{0.1 \text{ V}} = 0.84 \mu\text{F}$$

→ More than two times (2X) → 2.2 μF

where:

$V_{DD} = 15 \text{ V}$

Bootstrap diode = US1J

$Q_g + Q_{LS} =$ Approximate maximum 50 nC (designed value);

$I_{LK,D} = 100 \mu\text{A}$ (maximum value from datasheet);

$I_{LK,C} = 0$ (ceramic capacitor);

$I_{QBS} = 70 \mu\text{A}$ (maximum value from datasheet);

$t_{ON} = 200 \mu\text{s}$ (depends on system);

$\Delta V_{BS} = 0.1 \text{ V}$ (depends on system);

Recommended C_{BS} is normally 2~3 times C_{BS_min} .

5.2. Initial Charging Sequence for Bootstrap Capacitor

Adequate on-time duration of the low-side MOSFET to fully charge the bootstrap capacitor is required for initial bootstrap charging. In case of the Motion SPM[®] 7 Series, the initial charging time (t_{charge}) can be calculated from the following equation:

$$t_{charge} = C_{BS} \times R_{BS} = \frac{1}{\delta} \times I_n \frac{V_{CC}}{V_{DD} - V_{BS(min)} - V_F - V_{LS}} \quad (4)$$

where:

V_F = Forward voltage drop across the bootstrap diode;

$V_{BS(min)}$ = Minimum value of the bootstrap capacitor;

V_{LS} = Voltage drop across the low-side IGBT or load; and

δ = Duty ratio of PWM.

To charge three bootstrap capacitors at the same time; theoretically, the maximum initial charging current could exceed OCP level. Therefore, initial charging time for bootstrap capacitors should be separated as shown in Figure 6.

 


Figure 6. Bootstrap Recommended Initial Bootstrap Capacitors Charging Sequence

5.3. Selection of Shunt Resistor (One Shunt)

The value of shunt resistor is calculated by the following equations.

Maximum short-circuit (SC) current trip level (depends on user selection):

$$I_{SC(max)} = 1.5 \times I_{D(max)} \quad (5)$$

SC trip reference voltage (depends on datasheet):

$$V_{SC} = \text{Min.0.45 V, Typ.0.5 V, Max.0.55 V} \quad (6)$$

Shunt resistance:

$$I_{SC(max)} = V_{SC(max)} / R_{SHUNT(min)} \rightarrow R_{SHUNT(min)} = V_{SC(max)} / I_{SC(max)} \quad (7)$$

If the deviation of the shunt resistor is limited below $\pm 5\%$:

$$R_{SHUNT(typ)} = R_{SHUNT(min)} / 0.95, R_{SHUNT(max)} = R_{SHUNT(typ)} \times 1.05 \quad (8)$$

Actual SC trip current level becomes:

$$I_{SC(typ)} = V_{SC(typ)} / R_{SHUNT(typ)}, I_{SC(min)} = V_{SC(min)} / R_{SHUNT(max)} \quad (9)$$

Inverter output power:

$$P_{OUT} = \sqrt{3} / \sqrt{2} \times MI \times V_{DC_Link} \times I_{RMS} \times PF \quad (10)$$

where:

MI = modulation index;

V_{DC_Link} = DC link voltage;

I_{RMS} = Maximum load current of inverter; and

PF = power factor;

Average DC current:

$$I_{DC_AVG} = V_{DC_Link} / (P_{out} \times Eff) \quad (11)$$

where:

Eff = inverter efficiency.

The power rating of shunt resistor is calculated by the following equation:

$$P_{SHUNT} = (I_{DC_AVG}^2 \times R_{SHUNT} \times \text{Margin}) / \text{Derating Ratio} \quad (12)$$

where:

R_{SHUNT} = Shunt resistor typical value at $T_C = 25^\circ\text{C}$

Derating Ratio = Derating ratio of shunt resistor at $T_{SHUNT} = 100^\circ\text{C}$ (from datasheet of shunt resistor); and

Margin = Safety margin (determined by customer).

Shunt Resistor Calculation Examples

Calculation Conditions:

- DUT: FSB70450, Tolerance of R_{SHUNT} : $\pm 5\%$
- SC Trip Reference Voltage:
 - $V_{SC(min)}=0.45\text{ V}$, $V_{SC(typ)}=0.50\text{ V}$, $V_{SC(max)}=0.55\text{ V}$
- Maximum Load Current of Inverter (I_{RMS}): 0.4 A_{rms}
- Maximum Peak Load Current of Inverter ($I_{D(max)}$): 0.6 A
- Modulation Index(MI): 0.9
- V_{DC} Link ($V_{DC\text{ LINK}}$): 300 V
- Power Factor (PF): 0.8
- Inverter Efficiency (Eff): 0.98
- Shunt Resistor Value at $T_C=25^\circ\text{C}$ (R_{SHUNT}): 0.25Ω
- Derating Ratio of Shunt Resistor at $T_{SHUNT}=100^\circ\text{C}$: 70%
- Safety Margin: 20%

Calculation Results:

- $I_{SC(max)}: 1.5 \times I_{D(max)} = 1.5 \times 0.6\text{ A} = 0.9\text{ A}$
- $R_{SHUNT(min)}: V_{SC(max)} / I_{SC(max)} = 0.55\text{ V} / 0.9\text{ A} = 0.61\Omega$
- $R_{SHUNT(typ)}: R_{SHUNT(min)} / 0.95 = 0.61\Omega / 0.95 = 0.64\Omega$
- $R_{SHUNT(max)}: R_{SHUNT(typ)} \times 1.05 = 0.64\Omega \times 1.05 = 0.67\Omega$
- $I_{SC(min)}: V_{SC(min)} / R_{SHUNT(max)} = 0.45\text{ V} / 0.67\Omega = 0.67\text{ A}$
- $I_{SC(typ)}: V_{SC(typ)} / R_{SHUNT(typ)} = 0.5\text{ V} / 0.64\Omega = 0.78\text{ A}$
- $P_{OUT} = \sqrt{3} / \sqrt{2} \times MI \times V_{DC\text{ Link}} \times I_{RMS} \times PF = 105.8\text{ W}$
- $I_{DC\text{ AVG}} = (P_{OUT}/\text{Eff}) / V_{DC\text{ Link}} = 0.36\text{ A}$
- $P_{SHUNT} = (I_{DC_AVG}^2 \times R_{SHUNT} \times \text{Margin}) / \text{Derating Ratio} = (0.36^2 \times 0.67 \times 1.2) / 0.7 = 0.15\text{ W}$ (therefore, recommended power rating of shunt resistor is 0.2 W)

5.4. Design of Over-Temperature Protection (OTP) Circuit

The Motion SPM[®] 7 Series provides sensing output of the temperature for the OTP circuit. The V_{TS} PIN is directly connected to the built-in temperature sensor in HVIC, as shown in the Figure 7.

Note:

1. V_{TS} is only for sensing temperature related to the module and cannot shutdown MOSFETs automatically.

 


Figure 7. Position of the Built-in Temperature Sensor

Figure 8 is V-T curve of Temperature Sensing (TS) function in Motion SPM[®] 7 Series.

 


Figure 8. V-T Curve of Temperature Sensing (TS) Function

Figure 9 is a typical application circuit for the TS function. In this reference design, the set level is 100°C ($V_{TS}=2.1$ V), the reset level is 80°C ($V_{TS}=1.72$ V), and the hysteresis temperature is 20°C (Figure 10). If using an Analog-to-Digital Converter (ADC) port, a capacitor is needed between the VTS and GND pins (Figure 11).

 


Figure 9. Temperature Sensing Circuit using I/O Port in MCU Example

 


Figure 10. Timing Chart of Temperature Sensing Circuit



Figure 11. Temperature Sensing Circuit using ADC Port in MCU Example

5.5. Interlock Function

The Motion SPM® 7 Series has an interlock function to prevent shoot-through when high- and low-side input, HIN and LIN, are placed in HIGH status at the same time.

The behavior of the interlock function, based on the one-leg diagram in Figure 12 is shown in Table 2 and Figure 13.

 


Figure 12. One-Leg Diagram of Motion SPM® 7 Series

Table 2. Logic Table for Inverter Output

HIN	LIN	Output	Status
0	0	Z	Both MOSFETs OFF
0	1	0	Low-Side MOSFET ON
1	0	V _{DC}	High-Side MOSFET ON
1	1	Forbidden	Interlock (refer to Figure 13)
Open	Open	Z	Same as (0,0)

 


Figure 13. Timing Chart for the Input and Output of HVIC

5.6. Selection of C_{FOD}

The external capacitor connected between the C_{FOD} and COM pins determines the fault output duration (t_{FOD}).

t_{FOD} can be calculated by the following approximate equation:

$$t_{FOD} = C_{FOD} / (24 \times 10^{-6}) \text{ [s]} \quad (13)$$

5.7. Printed Circuit Board (PCB) Layout Guidance

 


Figure 14. PCB Layout Guidance

Related Resources

[*AN-9077: Motion SPM® 7 Series Assembly Guide*](#)

[*AN-9078: Motion SPM® 7 Series Assembly Guide*](#)

[*FSB70325 – Motion SPM® 7 Series*](#)

[*FSB70625 – Motion SPM® 7 Series*](#)

[*FSB70250 – Motion SPM® 7 Series*](#)

[*FSB70450 – Motion SPM® 7 Series*](#)

[*FSB70550 – Motion SPM® 7 Series*](#)

[*SPM® Module Design Guide*](#)

[*Motion Control Design Tool*](#)

Reference Design Disclaimer

Fairchild Semiconductor Corporation ("Fairchild") provides these reference design services as a benefit to our customers. Fairchild has made a good faith attempt to build for the specifications provided or needed by the customer. Fairchild provides this product "as is" and without "recourse" and MAKES NO WARRANTY, EXPRESSED, IMPLIED OR OTHERWISE, INCLUDING ANY WARRANTY OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.

Customer agrees to do its own testing of any Fairchild reference designs in order to ensure design meets the customer needs. Neither Fairchild nor Customer shall be liable for incidental or consequential damages, including but not limited to, the cost of labor, requalifications, rework charges, delay, lost profits, or loss of goodwill arising out of the sale, installation or use of any Fairchild product.

Subject to the limitations herein, Fairchild will defend any suit or proceeding brought against Customer if it is based on a claim that any product furnished hereunder constitutes an infringement of any intellectual property rights. Fairchild must be notified promptly in writing and given full and complete authority, information and assistance (at Fairchild's expense) for defense of the suit. Fairchild will pay damages and costs therein awarded against Customer but shall not be responsible for any compromise made without its consent. In no event shall Fairchild's liability for all damages and costs (including the costs of the defense by Fairchild) exceed the contractual value of the products or services that are the subject of the lawsuit. In providing such defense, or in the event that such product is held to constitute infringement and the use of the product is enjoined, Fairchild, in its discretion, shall procure the right to continue using such product, or modify it so that it becomes noninfringing, or remove it and grant Customer a credit for the depreciated value thereof. Fairchild's indemnity does not extend to claims of infringement arising from Fairchild's compliance with Customer's design, specifications and/or instructions, or the use of any product in combination with other products or in connection with a manufacturing or other process. The foregoing remedy is exclusive and constitutes Fairchild's sole obligation for any claim of intellectual property infringement and Fairchild makes no warranty that products sold hereunder will not infringe any intellectual property rights.

All solutions, designs, schematics, drawings, boards or other information provided by Fairchild to Customer are confidential and provided for Customer's own use. Customer may not share any Fairchild materials with other semiconductor suppliers.