



TI reference design number: PMP9367 Rev A1

**Input: 6-40V
Nominal 12V**

Output: 5V @ 3.5A

(USB CH 1: 5V @ 1A)

(USB CH 2: 5V @ 2.1A)

DC–DC Converter Test Results

Table of Contents


1. Circuit Description	3
2. Fabrication	3
2.1 Block Diagram	5
3. Efficiency	6
4. Load Regulation	6
5. Thermal	8
Top View.....	8
6. Power Up USB CH1	9
6.1 Power Up at 6V Input – No Load Power Up at 6V Input –1A Load.....	9
6.2 Power Up at 12V Input – No Load Power Up at 12V Input –1A Load.....	9
6.3 Power Up at 36V Input – No Load Power Up at 36V Input –1A Load.....	10
Power Up USB CH2.....	11
6.4 Power Up at 6V Input – No Load Power Up at 6V Input –2.1A Load.....	11
6.5 Power Up at 12V Input – No Load Power Up at 12V Input –2.1A Load.....	11
6.6 Power Up at 36V Input – No Load Power Up at 12V Input –2.1A Load.....	12
7. Switching and Ripple.....	13
7.1 LM3150 5VOUT @ 3.1A.....	13
8. Transient Response	14
8.1 12V Input – 0.5A to 1A Step, 100mA/μs, 100 Hz. USB Ch1	14
8.2 12V Input – 1.05A to 2.1A Step, 100mA/μs, 100 Hz. USB Ch2	14
9. Current Limit Tests 12V Input.....	15
9.1 LM3150.....	15
-12Vin - No Load -12Vin - 3.5A Load	15
9.2 USB CH1	15
-12Vin - No Load -12Vin - 1A Load	15
9.3 USB CH2	16
-12Vin in - No Load -12Vin - 2.1A Load	16
10.1 Short Circuit Tests.....	17
10.1 12Vin, LM3150 No Load 12Vin, LM3150 3.1A Load	17
10.2 12Vin, USB CH1 No Load 12Vin, USB CH1 1A Load	17
10.3 12Vin, USB CH2 No Load 12Vin, USB CH2 2.1A Load	18
11. Short Circuit Recovery Tests.....	19
11.1 12Vin, LM3150 No Load 12Vin, LM3150 3.1A Load	19
11.2 12Vin, USB CH1 No Load 12Vin, USB CH1 1A Load	19
11.3 12Vin, USB CH2 No Load 12Vin, USB CH2 2.1A Load	20

1. Circuit Description

PMP9367 is a dual USB car charger. This design utilizes the LM3150, TPS2561 Dual Channel Power Switch and a TPS2513 USB Dedicated Charging Port Controller. This design operates from 6 to 40V in. The outputs is set to 5V, channel one has a 1A current limit and channel two has a 2.1A current limit. This design has a switching frequency of 300 kHz.

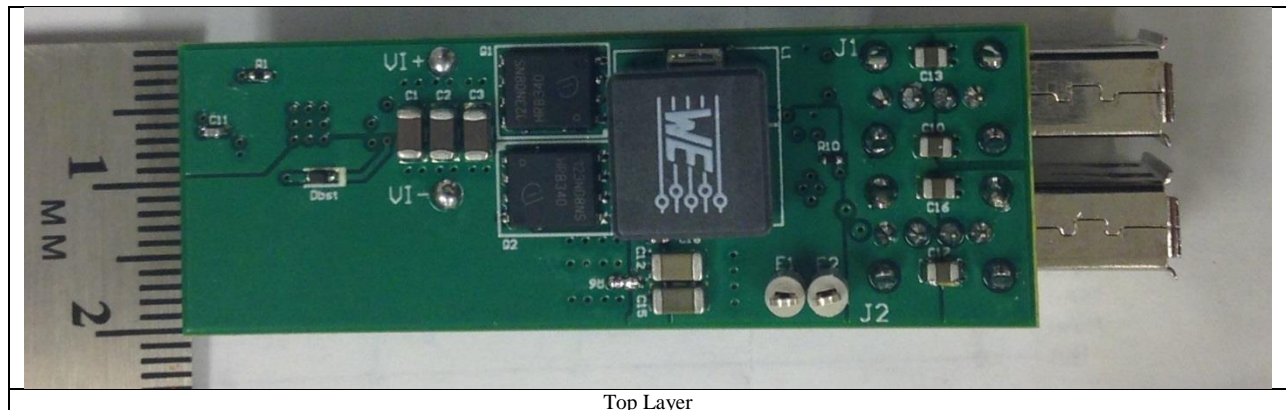
2. Fabrication

The PMP9367 is a four layer board with overall dimensions of 0.713" (18mm) x 2.2" (55mm). The copper weight is 1oz on the outer layers and 0.5oz the inner layers.




Top Layer

USB Direct Charging Port

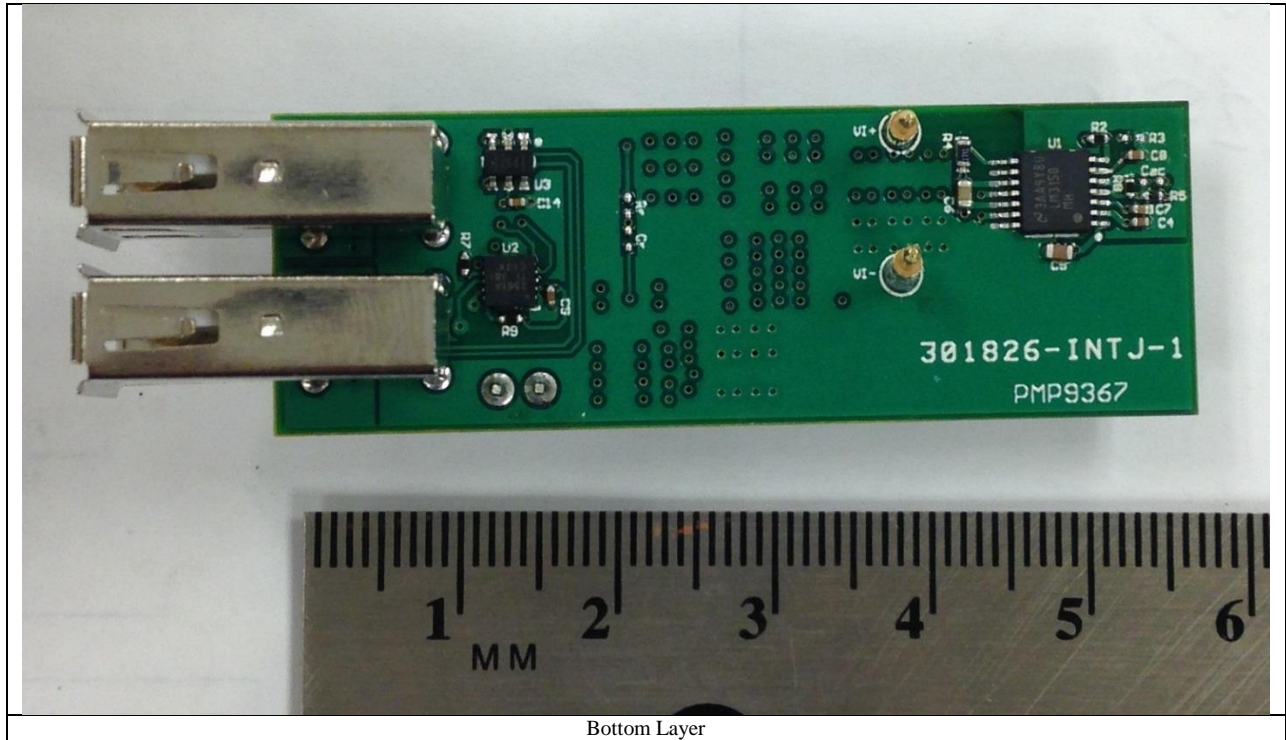


USB Direct Charging Port


2.1 Block Diagram

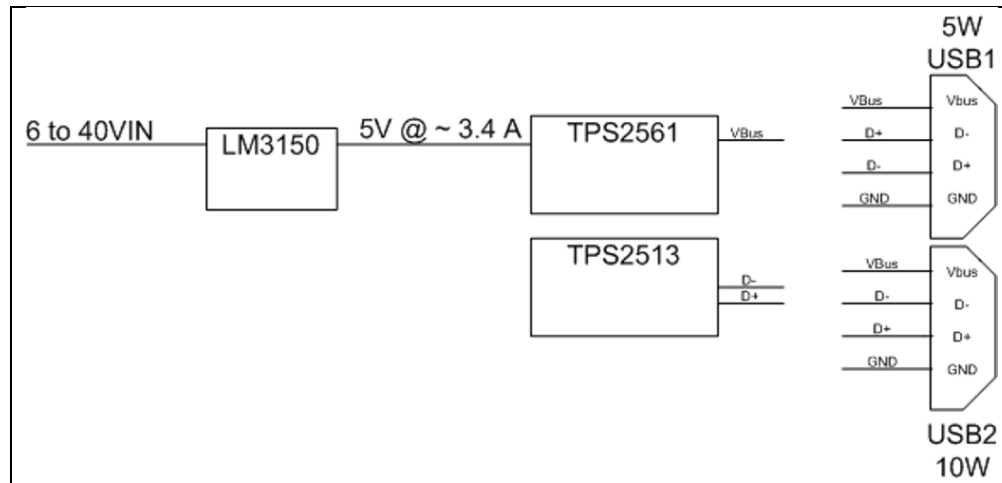


3. Efficiency

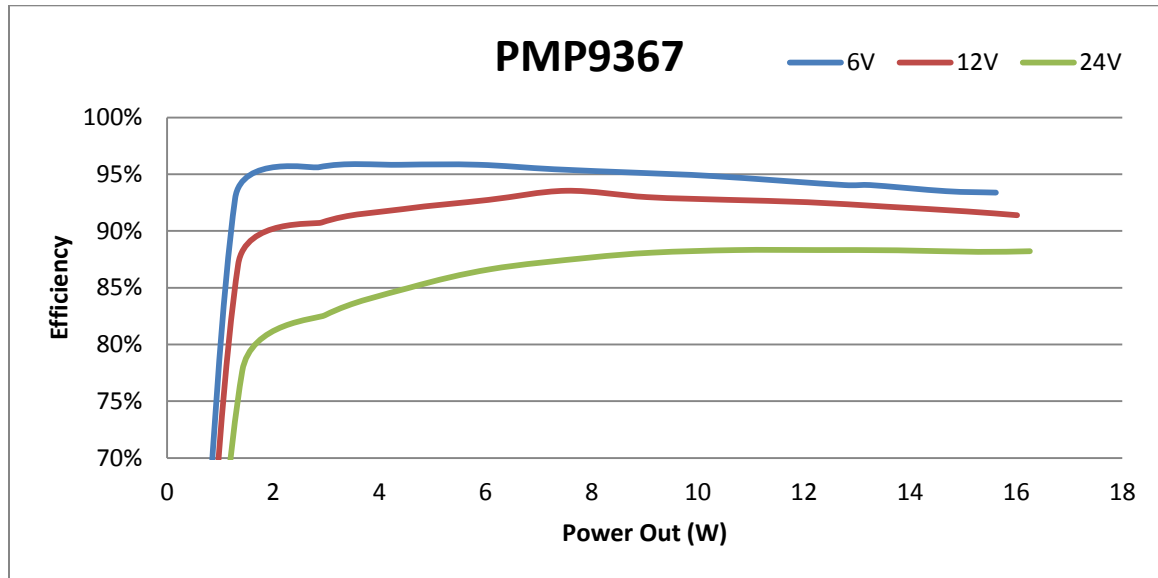


4. Load Regulation

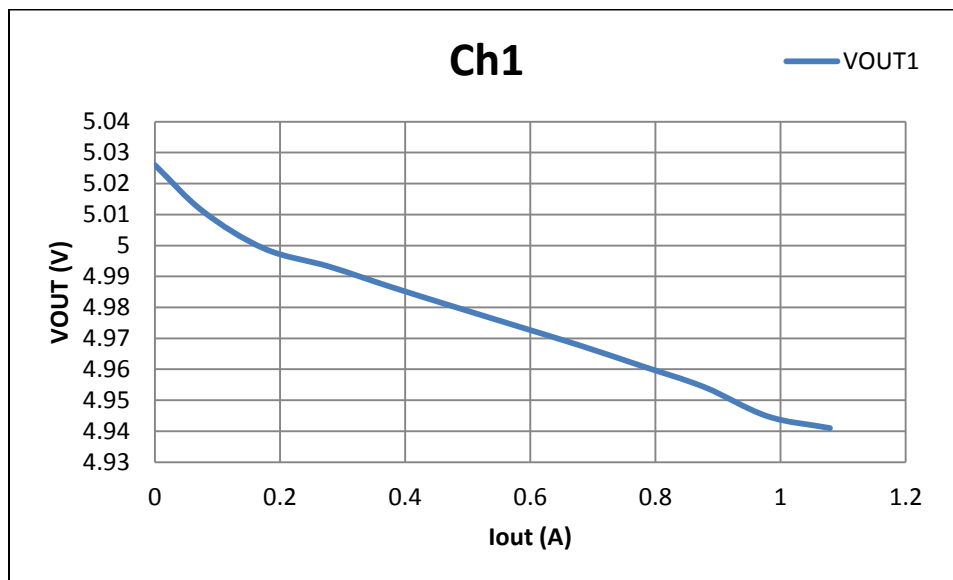

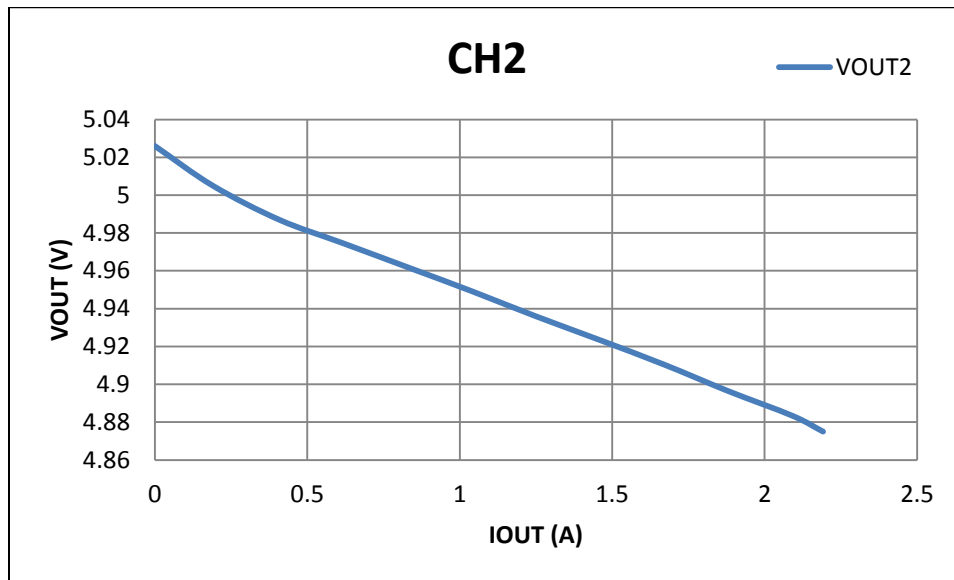

5. Thermal

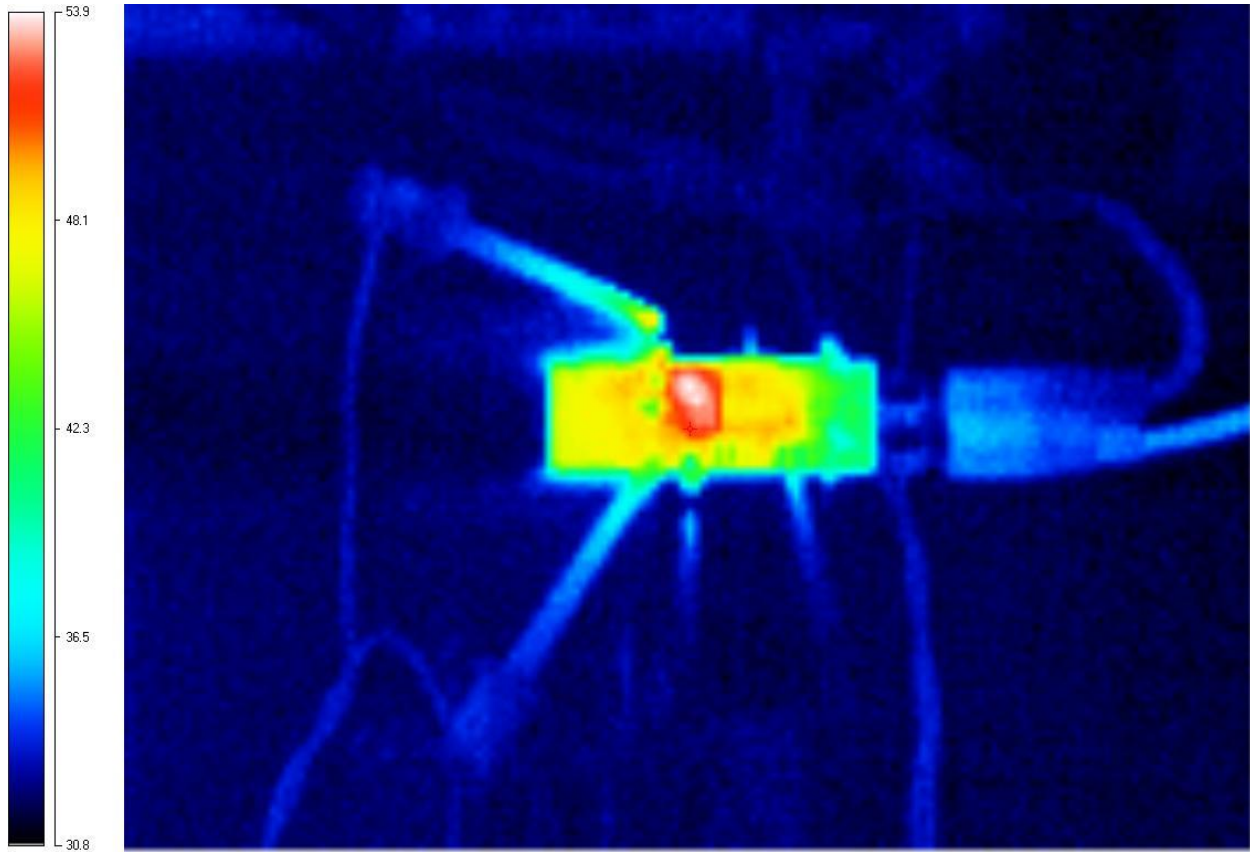5.1 Steady State Temperature, 12Vin and 15.5W out.




Top View

The warmest component on the module is the inductor. This image displays a 28°C temperature rise.

6. Power Up USB CH1

6.1 Power Up at 6V Input – No Load


Power Up at 6V Input – 1A Load

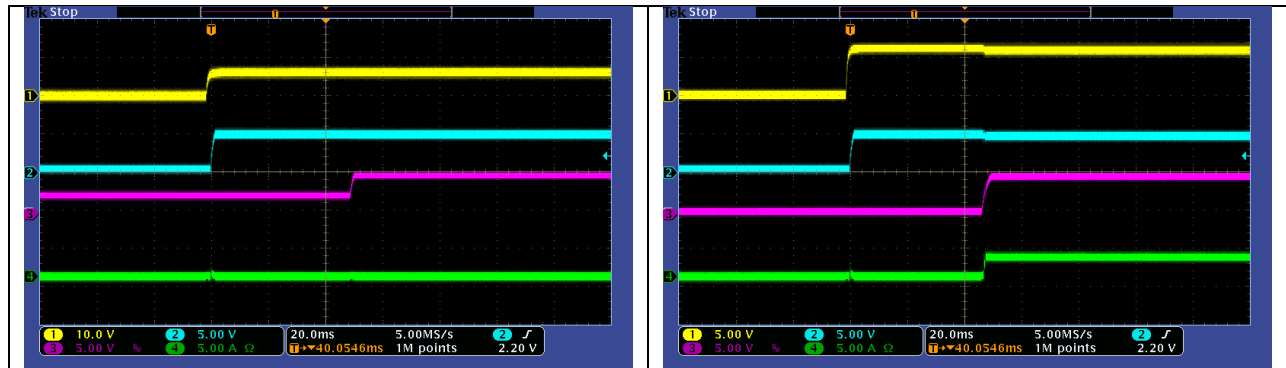


Channel 1 VIN
Channel 2 5Vout LM3150
Channel 3 J1 5Vout
Channel 4 IIN

6.2 Power Up at 12V Input – No Load

Power Up at 12V Input – 1A Load

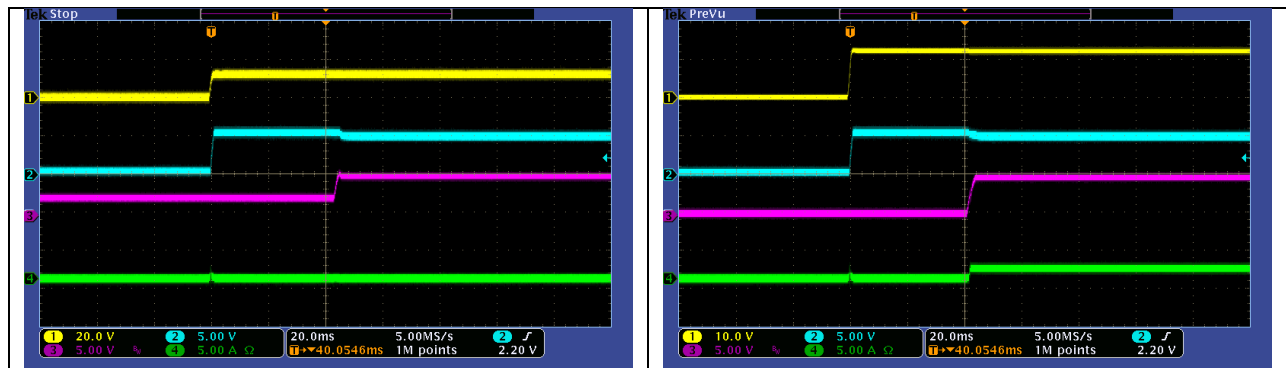

Channel 1 VIN
Channel 2 5Vout LM3150
Channel 3 J1 5Vout
Channel 4 IIN

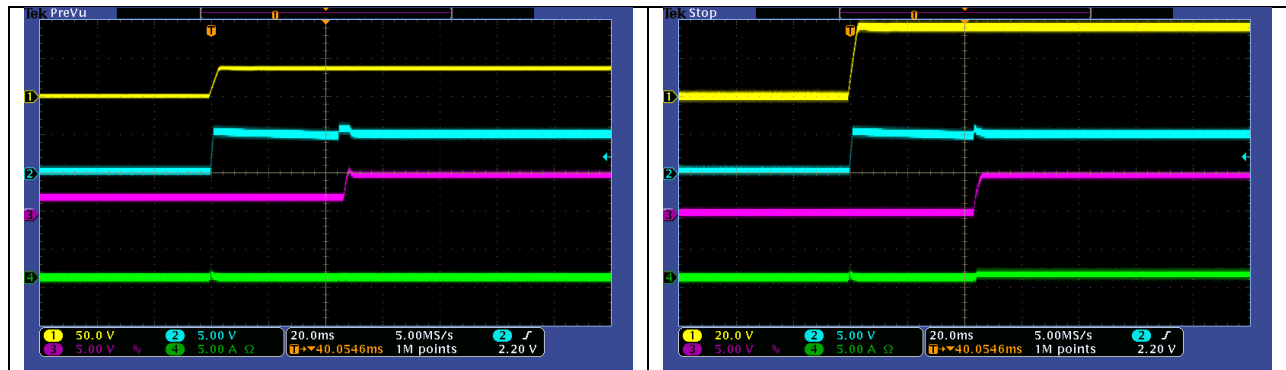
6.3 Power Up at 36V Input – No Load**Power Up at 36V Input – 1A Load**

Channel 1 VIN
 Channel 2 5Vout LM3150
 Channel 3 J1 5Vout
 Channel 4 IIN

Power Up USB CH2

6.4 Power Up at 6V Input – No Load


Power Up at 6V Input – 2.1A Load

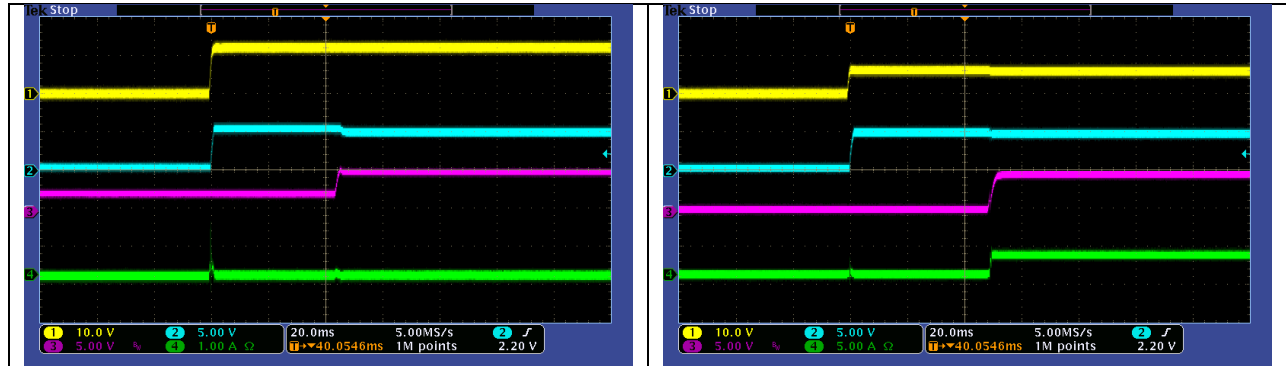


Channel 1 VIN
Channel 2 5Vout LM3150
Channel 3 J2 5Vout
Channel 4 IIN

6.5 Power Up at 12V Input – No Load

Power Up at 12V Input – 2.1A Load

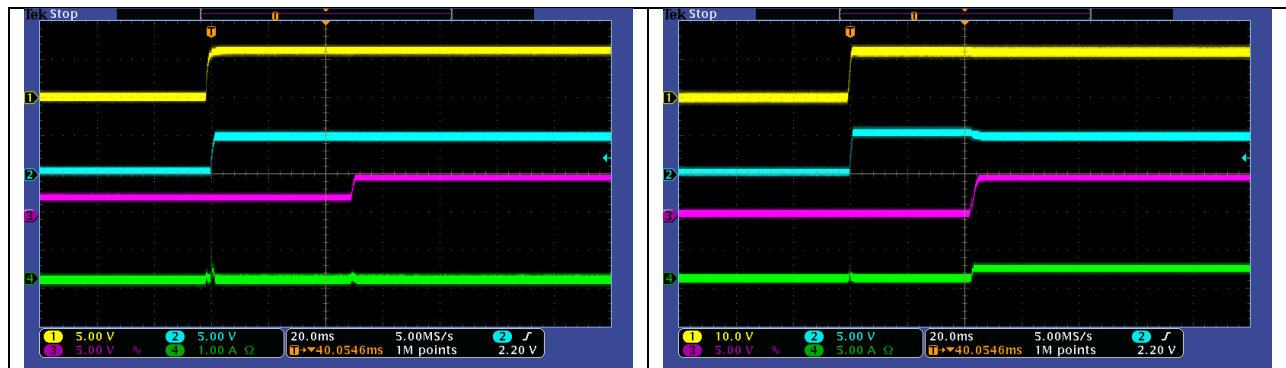


Channel 1 VIN
Channel 2 5Vout LM3150
Channel 3 J2 5Vout
Channel 4 IIN

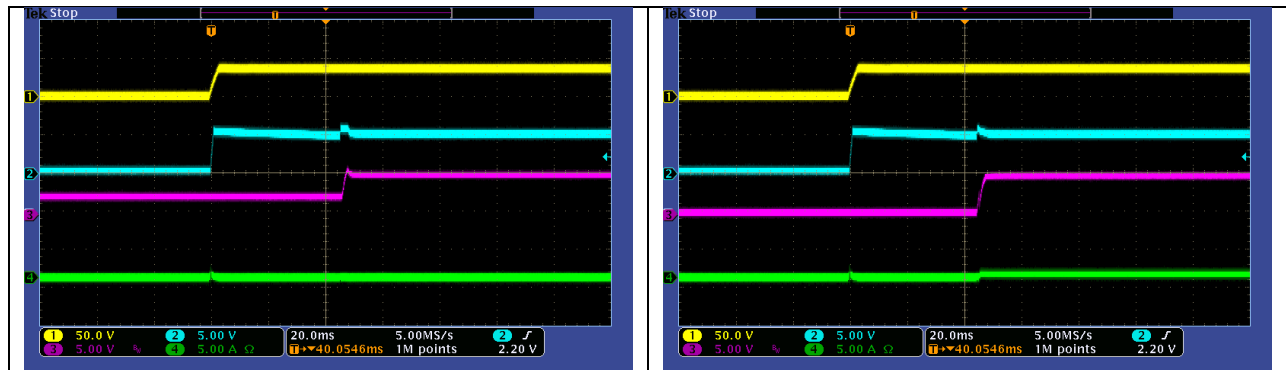6.6 Power Up at 36V Input – No Load**Power Up at 12V Input – 2.1A Load**

7. Switching and Ripple

7.1 LM3150 5VOUT @ 3.1A

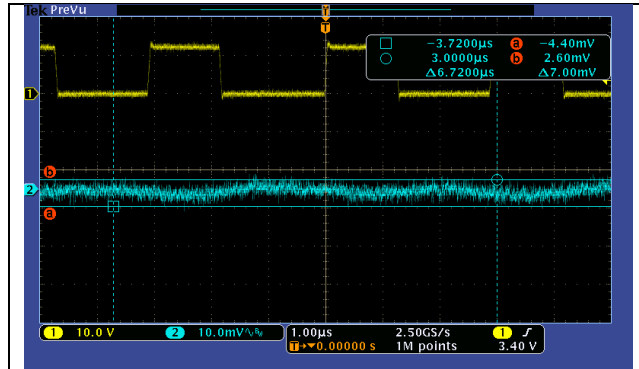


The cursors indicate 7mV ripple.

Channel 1 VSW
Channel 2 5Vout

8. Transient Response


A load step was applied to each channel and the transient response of the controller was monitored.

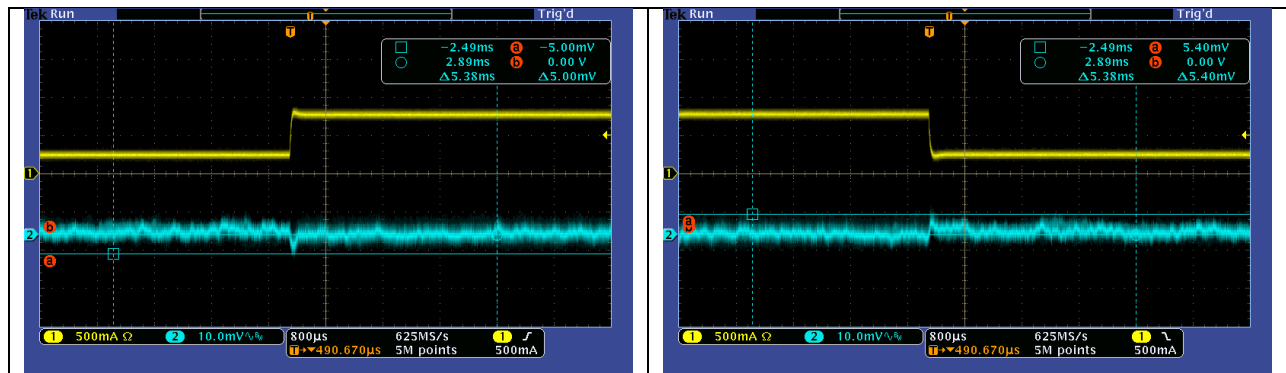8.1 12V Input – 0.5A to 1A Step, 100mA/ μ s, 100 Hz. USB Ch1



Cursors indicate ~5mV deviation across output capacitor.

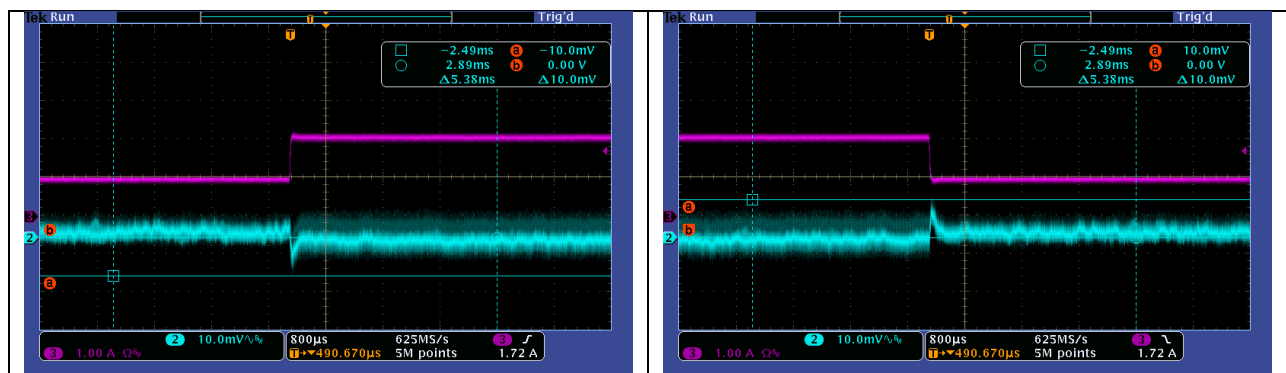
8.2 12V Input – 1.05A to 2.1A Step, 100mA/ μ s, 100 Hz. USB Ch2



Cursors indicate ~10mV deviation across output capacitor.


9. Current Limit Tests 12V Input

9.1 LM3150

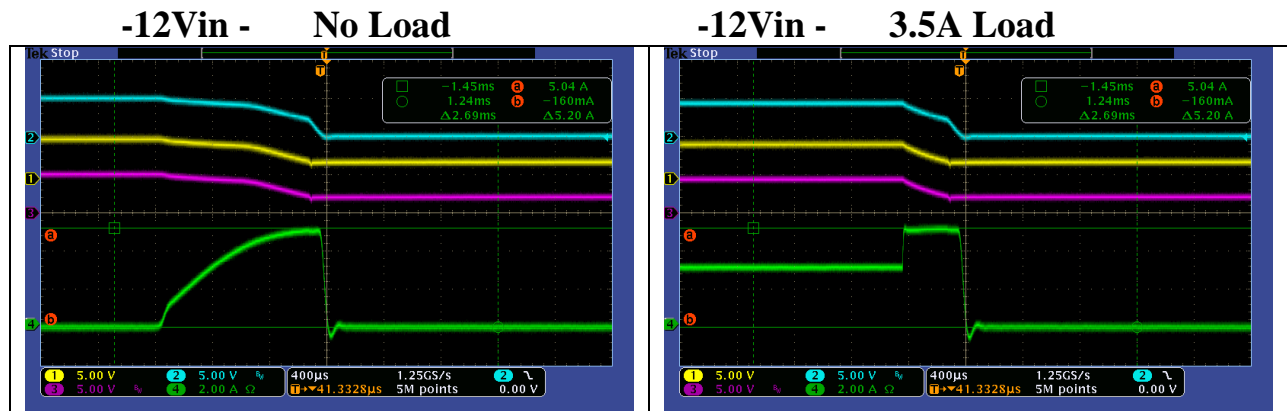


Channel 1 USB CH2
Channel 2 LM3150
Channel 3 USB CH1
Channel 4 IOUT

9.2 USB CH1

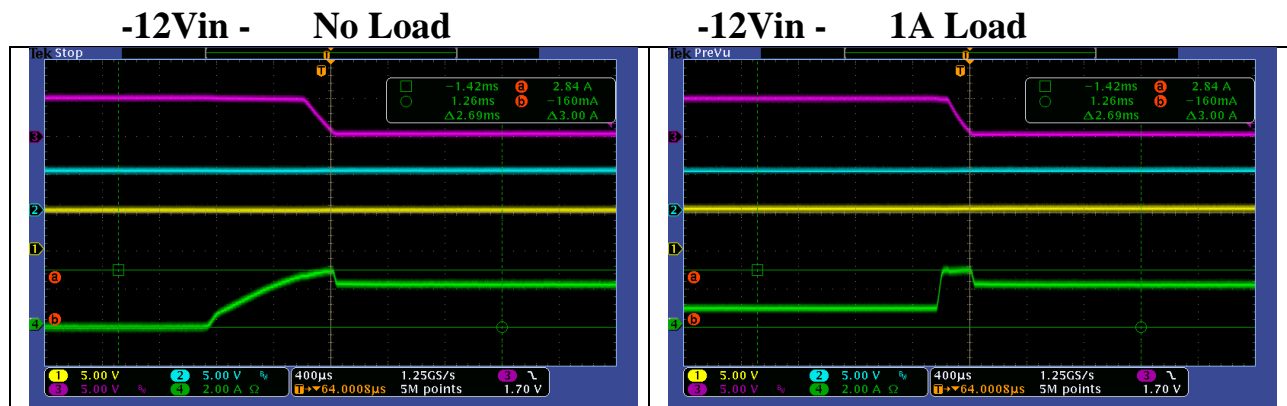

Channel 1 USB CH 1
Channel 2 LM3150
Channel 3 USB CH 2
Channel 4 IOUT


9.3 USB CH2

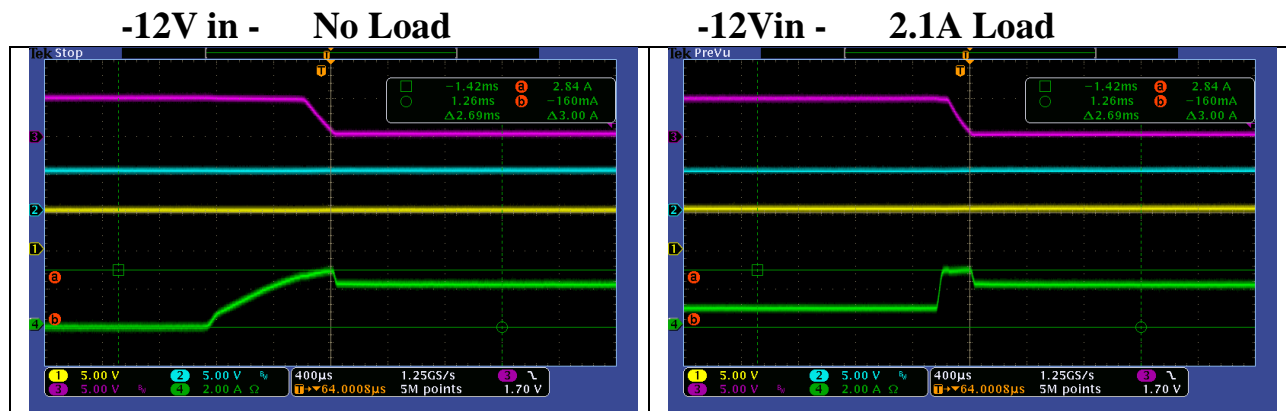


Channel 1 USB CH 1
 Channel 2 LM3150
 Channel 3 USB CH 2
 Channel 4 IOUT

10.1 Short Circuit Tests

10.1 12Vin, LM3150 No Load

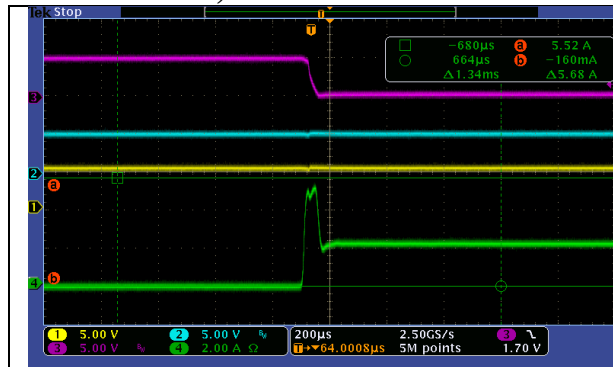


12Vin, LM3150 3.1A Load

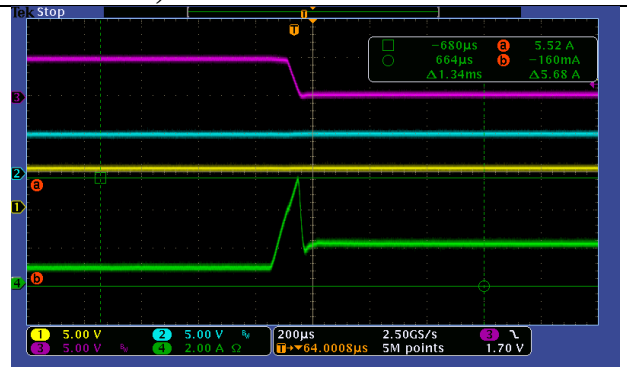


Channel 1 USB CH 1
Channel 2 LM3150
Channel 3 USB CH 2
Channel 4 IOUT



10.2 12Vin, USB CH1 No Load

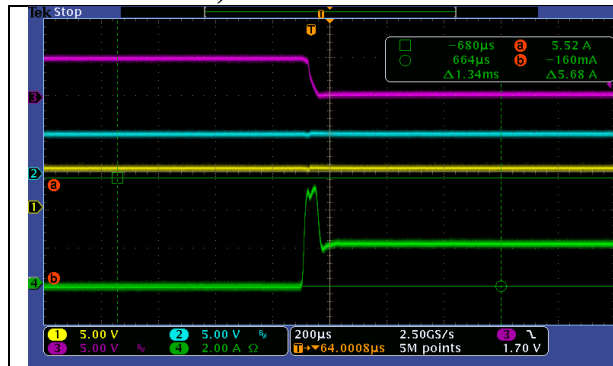

12Vin, USB CH1 1A Load

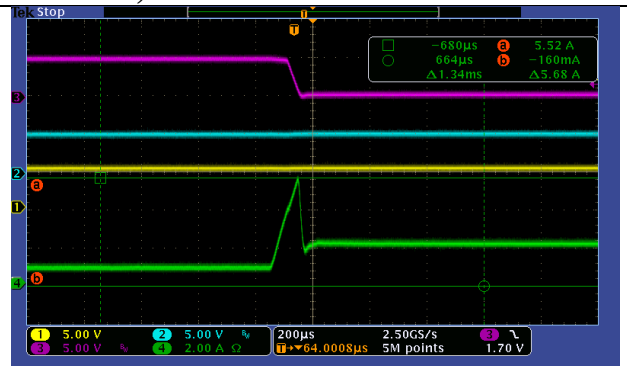


Channel 1 USB CH 1
Channel 2 LM3150
Channel 3 USB CH 2
Channel 4 IOUT

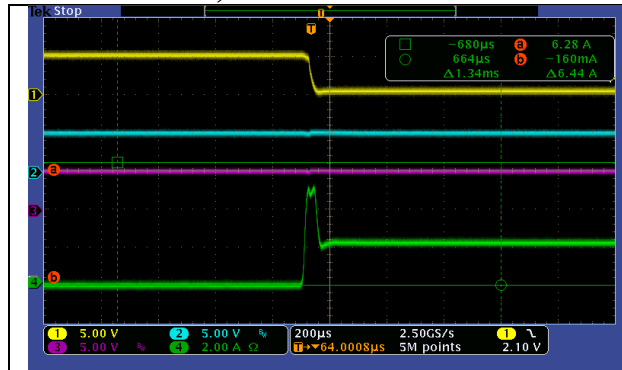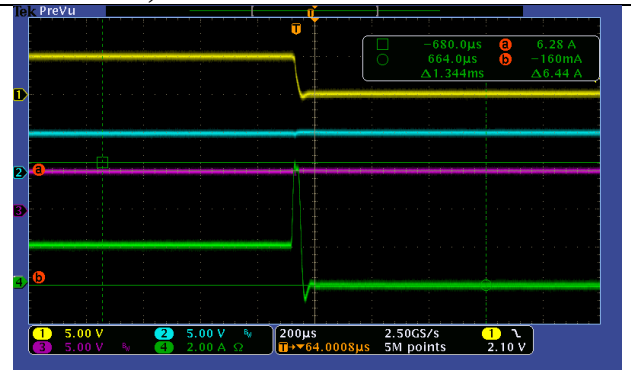10.3 12Vin, USB CH2 No Load**12Vin, USB CH2 2.1A Load**


Channel 1 USB CH 1
 Channel 2 LM3150
 Channel 3 USB CH 2
 Channel 4 IOUT

11. Short Circuit Recovery Tests

11.1 12Vin, LM3150 No Load

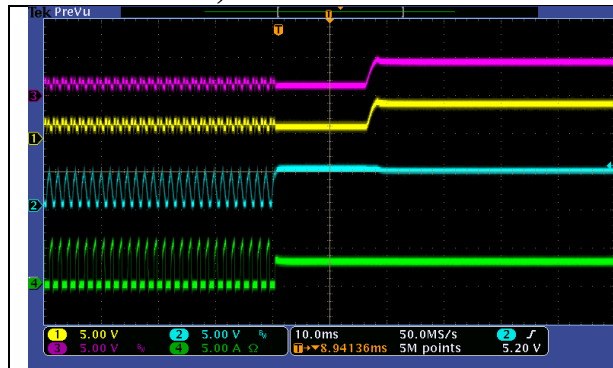


12Vin, LM3150 3.1A Load

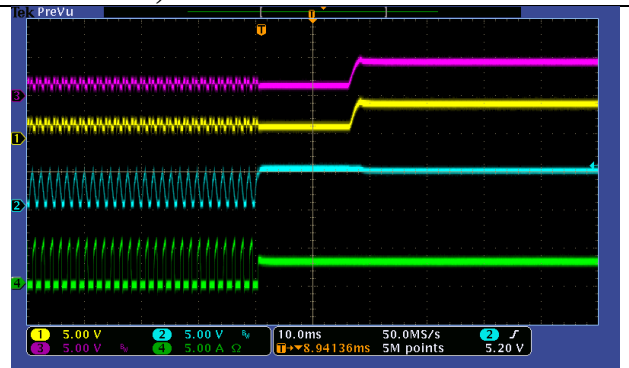


Channel 3 VOUT
Channel 4 IOUT



11.2 12Vin, USB CH1 No Load

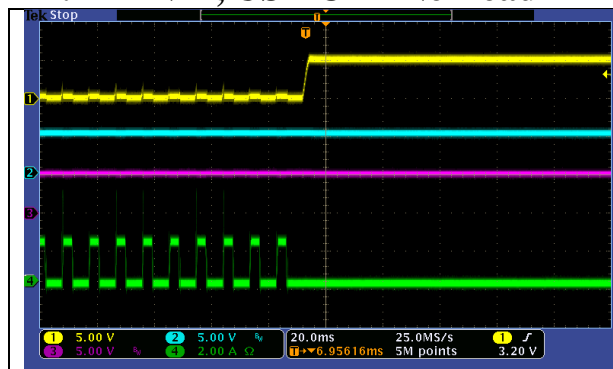

12Vin, USB CH1 1A Load

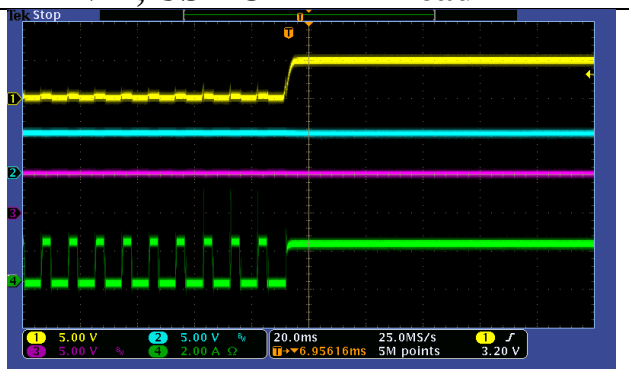

Channel 3 VOUT
Channel 4 IOUT

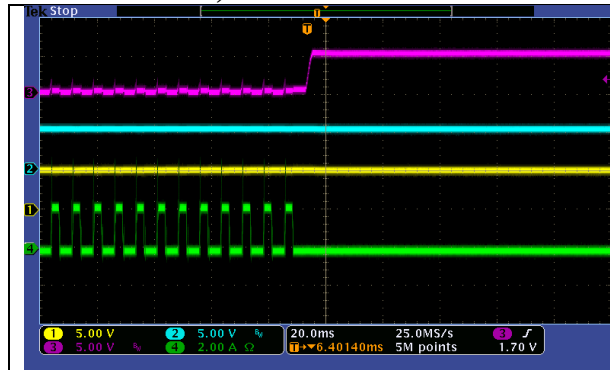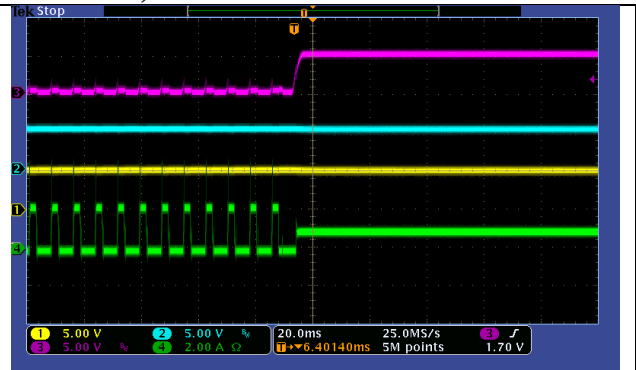11.3 12Vin, USB CH2 No Load**12Vin, USB CH2 2.1A Load**

Channel 3 VOUT
Channel 4 IOU

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.