

TEXAS INSTRUMENTS INCORPORATED

# PMP11438 Rev A

---

## Power Design Services Test Report

**Ryan Manack**

**4/8/2016**

PMP11438 REVA is a power evaluation module showcasing three different implementations for a 12V input, 1.2V output power supply at 6-10A. The board contains three non-isolated buck power supplies controlled by TPS54A20, TPS62184 and TPS53515. Each design is optimized for various parameters including size, efficiency, and transient response to name a few. The output filters have been designed to satisfy DC regulation of  $\pm 3\%$  and DC+AC regulation of  $\pm 5\%$ .

# PMP11438 Rev A Test Results

## Table of Contents

1	PMP11438 Board Photos .....	3
2	PMP11438 REVA 1.2V/10A – TPS54A20 .....	5
2.1	Board Photos.....	5
2.2	Efficiency and Power Loss .....	6
2.3	Load Regulation .....	6
2.4	Thermal .....	7
2.5	Startup .....	8
2.6	Shutdown .....	8
2.7	Output Ripple.....	9
2.8	Transient response.....	10
2.9	Synchronous Rectifier Stress.....	11
2.10	Frequency Characteristics.....	12
2.11	Loop Response .....	13
3	PMP11438 REVA 1.2V/6A – TPS62184 .....	14
3.1	Board Photos.....	14
3.2	Efficiency and Power Loss .....	15
3.3	Load Regulation .....	15
3.4	Thermal .....	16
3.5	Startup .....	17
3.6	Shutdown .....	17
3.7	Output Ripple.....	18
3.8	Transient response.....	20
3.9	Synchronous Rectifier Stress.....	20
3.10	Frequency Characteristics.....	21
3.11	Loop Response .....	22
4	PMP11438 REVA 1.2V/6A – TPS53515 .....	23
4.1	Board Photos.....	23
4.2	Efficiency and Power Loss .....	24
4.3	Load Regulation .....	24
4.4	Thermal .....	25
4.5	Startup .....	26


**PMP11438 Rev A Test Results**

4.6	Shutdown .....	26
4.7	Output Ripple .....	27
4.8	Transient response.....	29
4.9	Synchronous Rectifier Stress.....	29
4.10	Frequency Characteristics.....	30
4.11	Loop Response .....	31

# PMP11438 Rev A Test Results

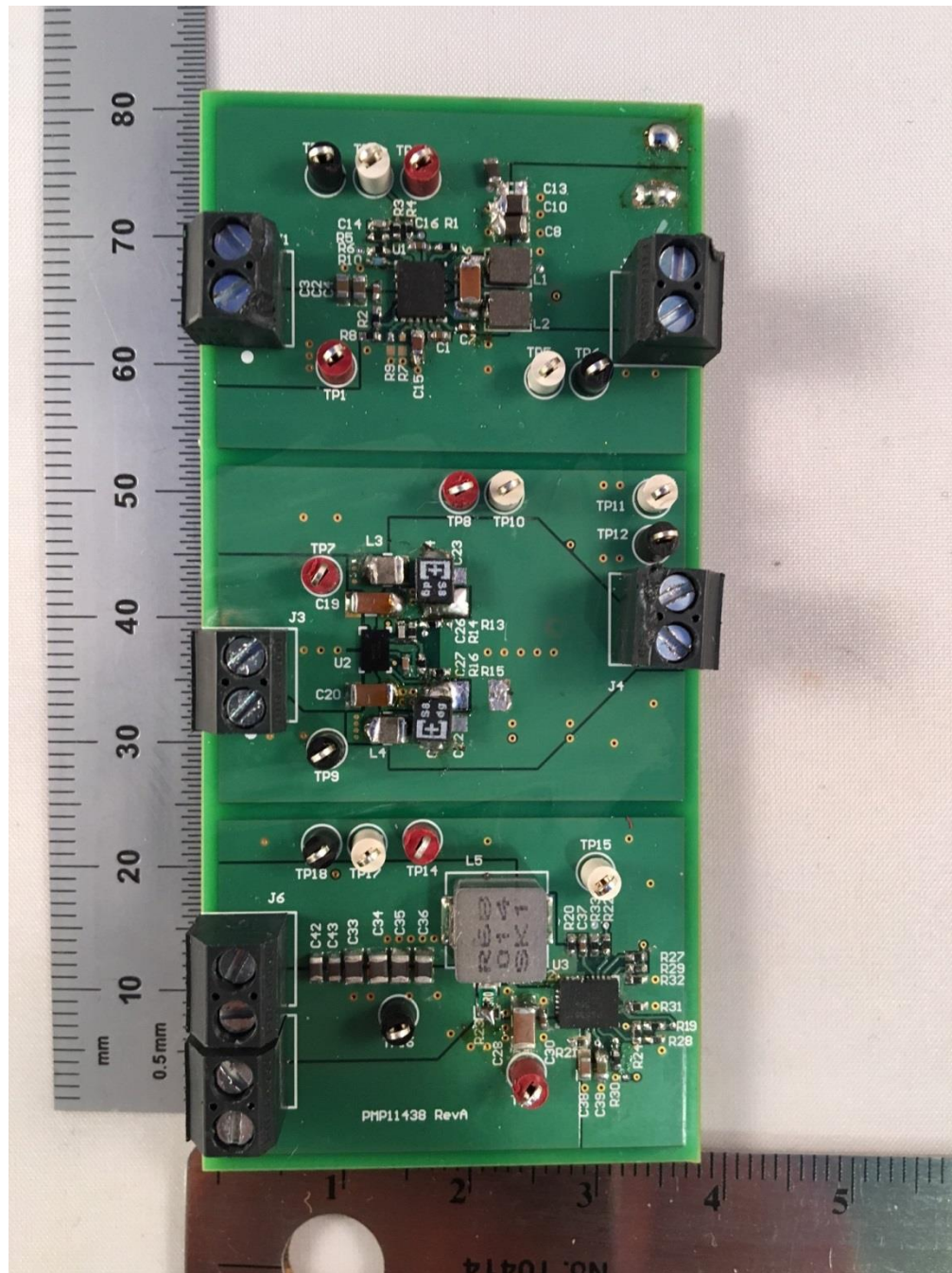
## 1 PMP11438 Board Photos

The front and back photos of PMP11438 are shown below. The board measures 3.2" x 1.5" and each circuit lies upon the same amount of PCB copper.



4/08/2016

# PMP11438 Rev A Test Results

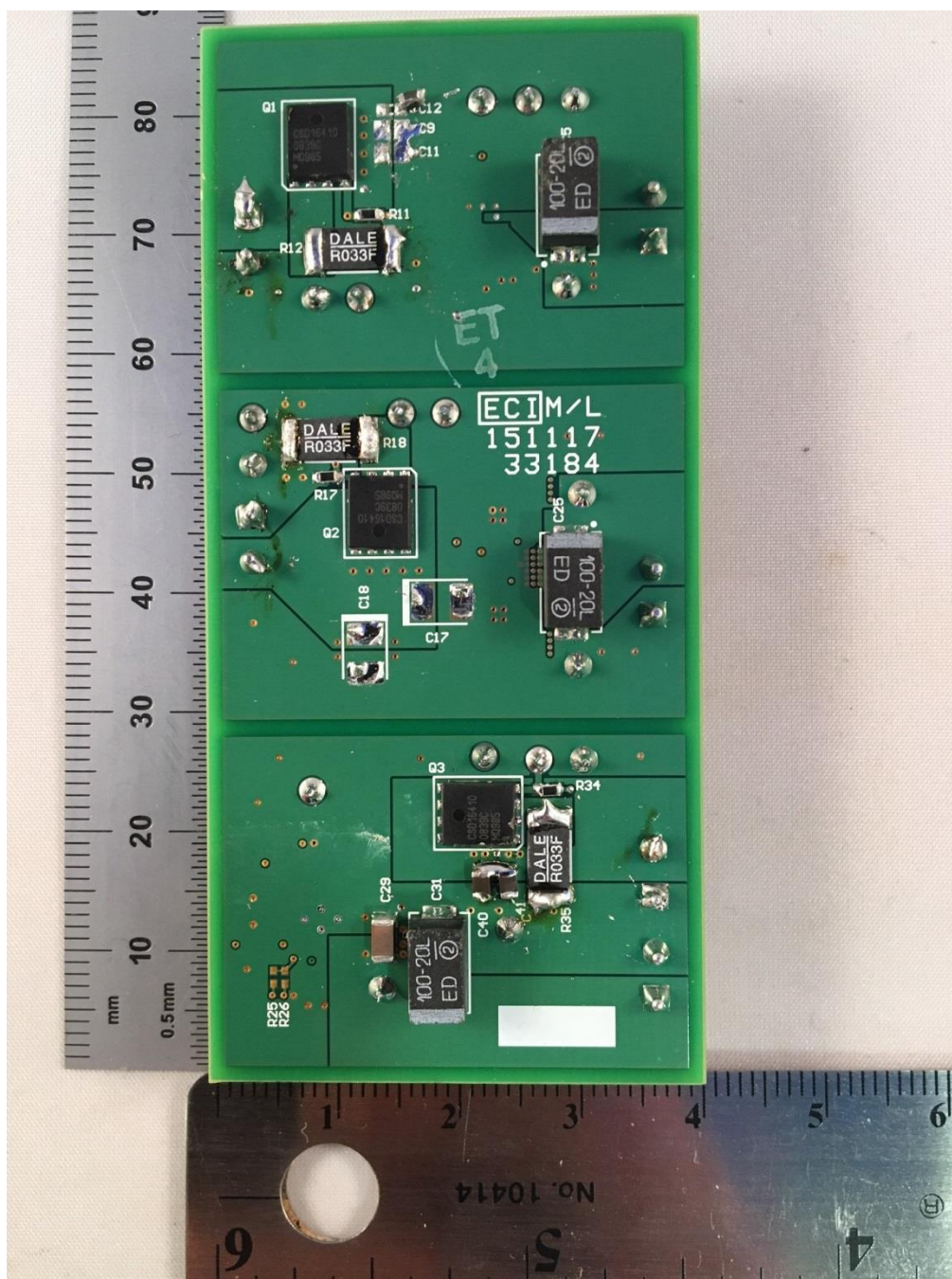





## PMP11438 Rev A Test Results

### 2 PMP11438 REVA 1.2V/10A - TPS54A20
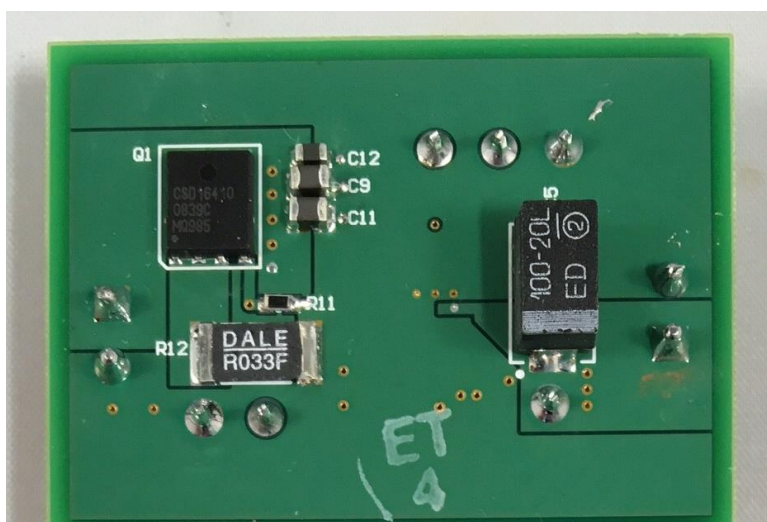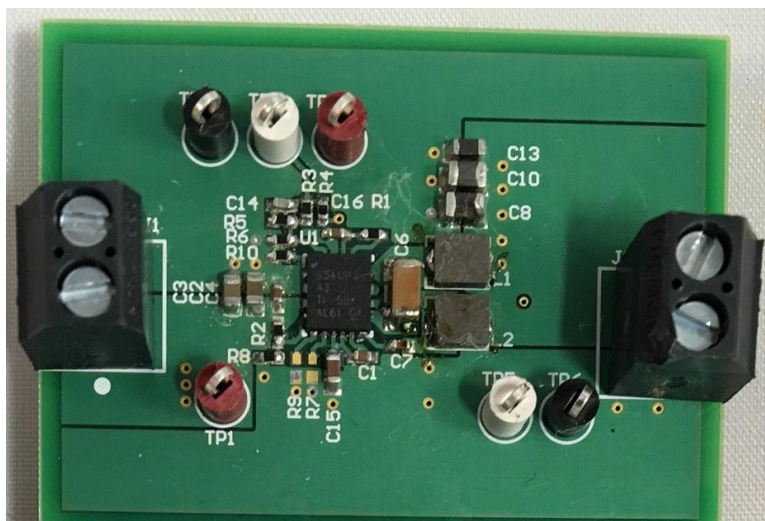
#### 2.1 Board Photos


The top and bottom images of PMP11438 TPS54A20 are shown below.



## PMP11438 Rev A Test Results

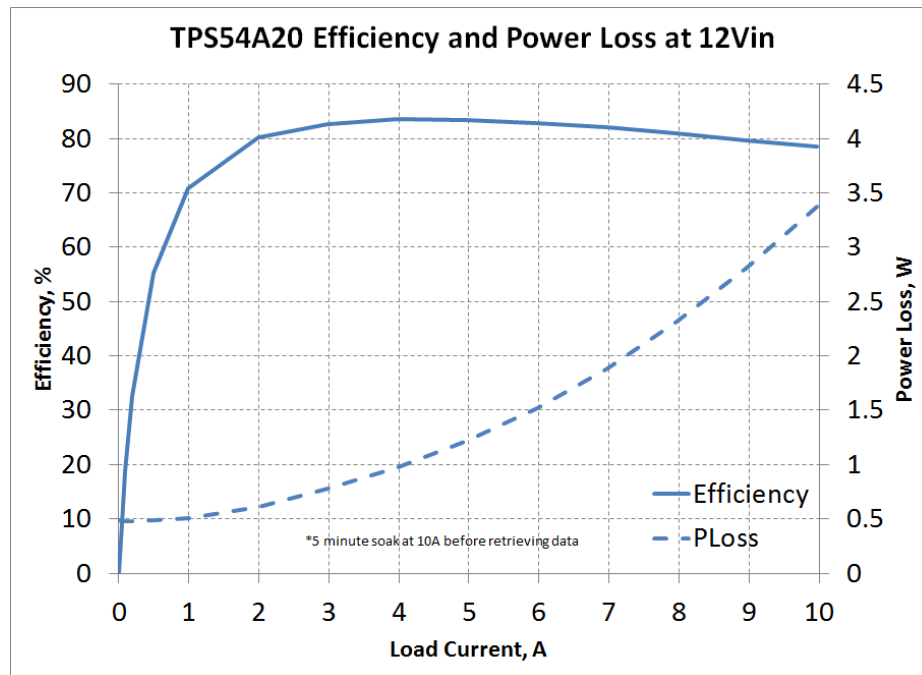
### 2.2 Efficiency and Power Loss

The efficiency and power loss of the power supply is shown below at 12Vin with natural convection.


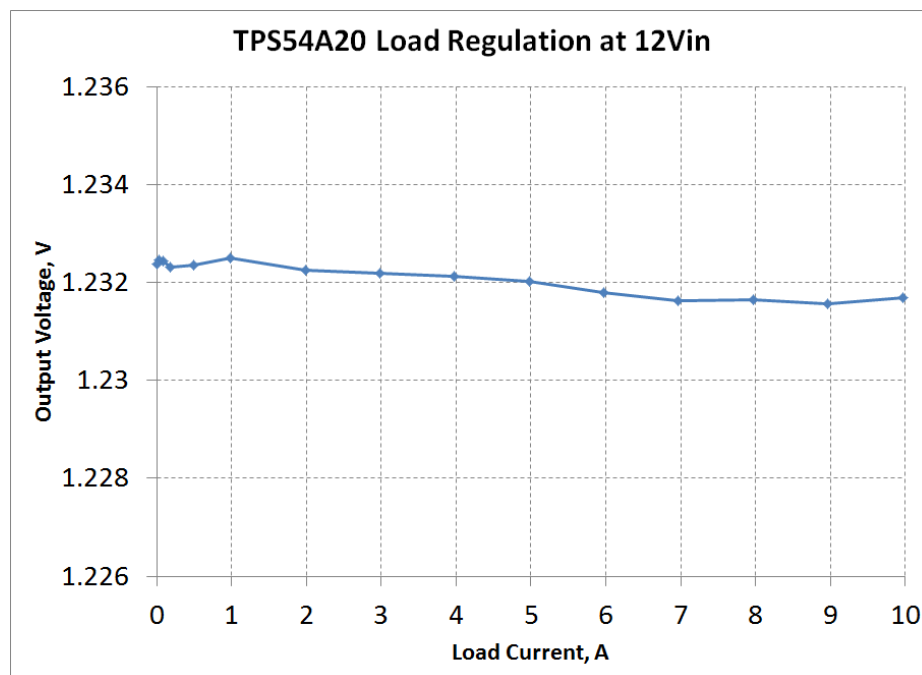
### 2.3 Load Regulation


The load regulation of the power supply is shown below at 12Vin.



## PMP11438 Rev A Test Results
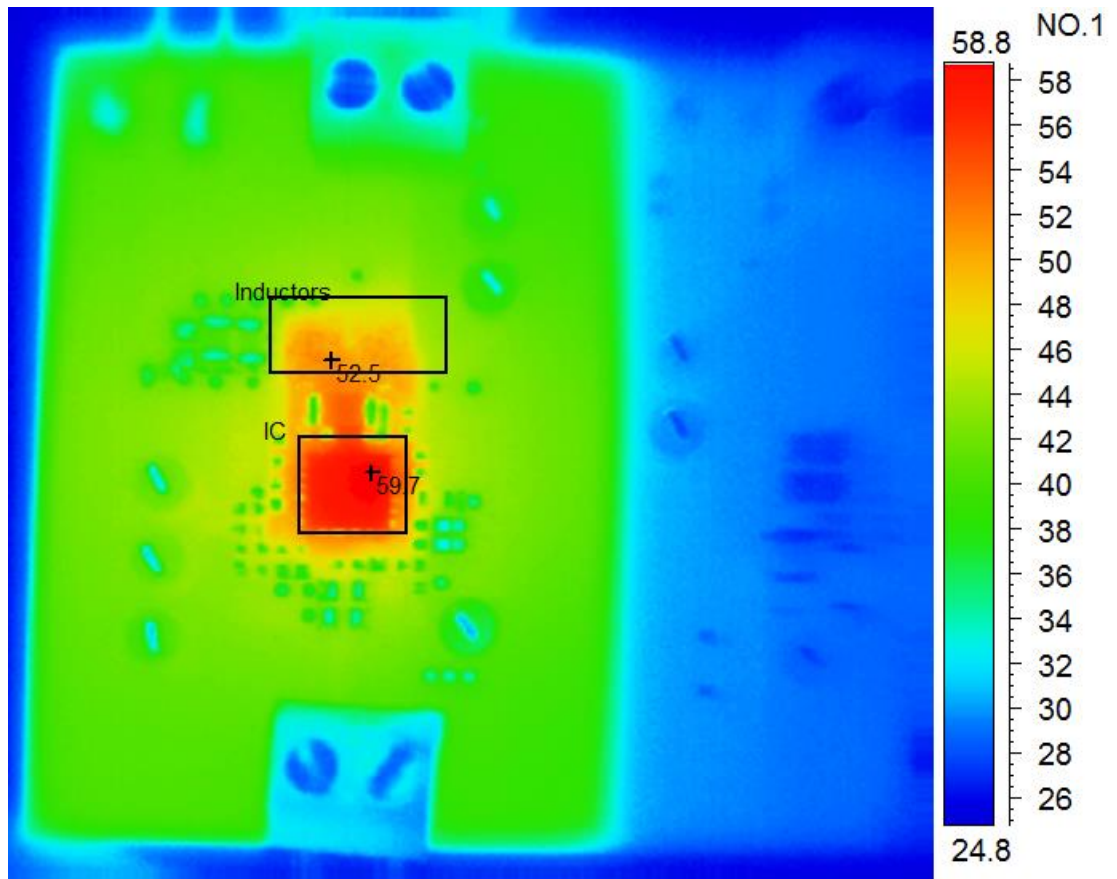
### 2.4 Thermal

The thermal image of the power supply is shown at room temperature with 12Vin, 6Aout, and natural convection. The power supply soaked for 10min at 6A before the measurement was taken. The IC, which has integrated MOSFETs, is the hottest component at 59.7°C.




Area analysis	Value	NO.1
IC Max	59.7°C	
Inductors Max	52.5°C	



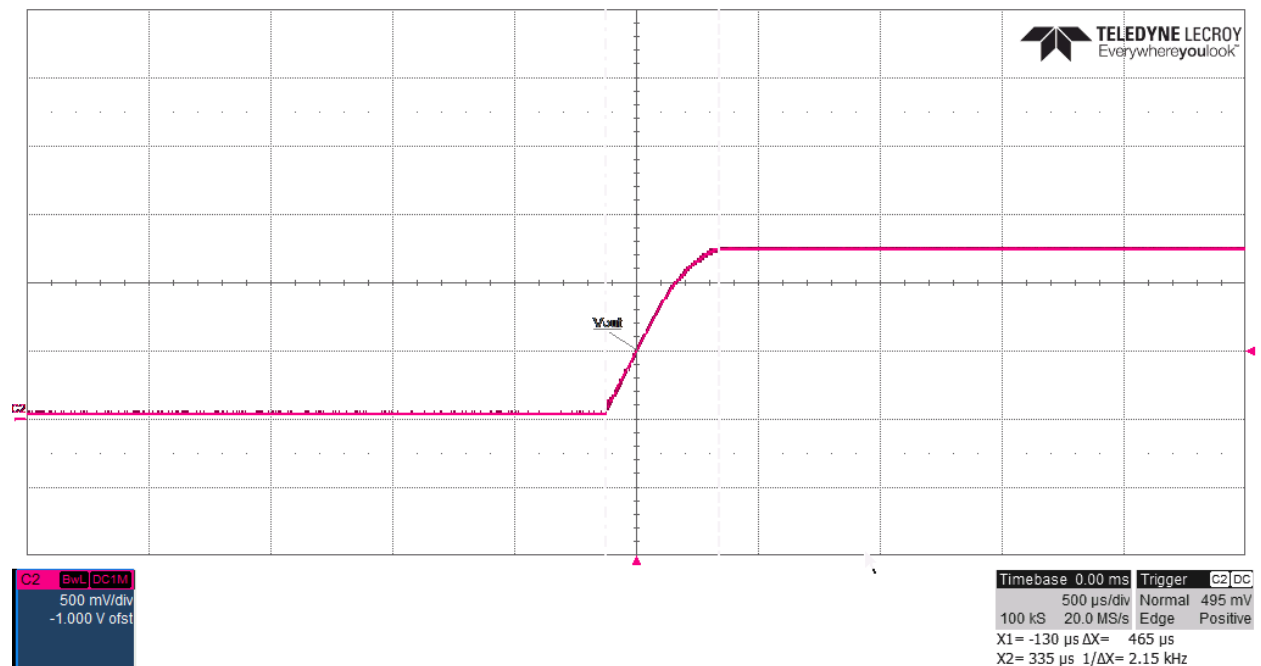
## 2.5 Startup

The power supply startup at 0A is shown below. The startup time is 500 $\mu$ s.


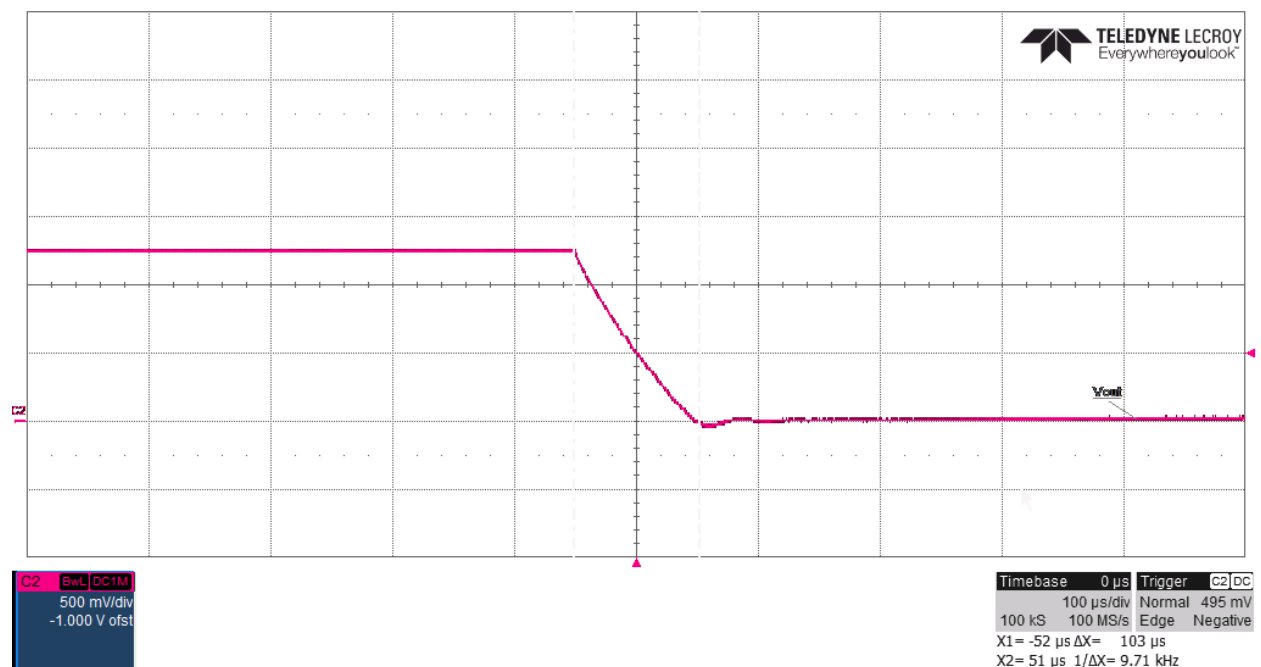
## 2.6 Shutdown

The shutdown of the power supply with 1.2 $\Omega$  constant-resistance load is shown below.





4/08/2016


## PMP11438 Rev A Test Results


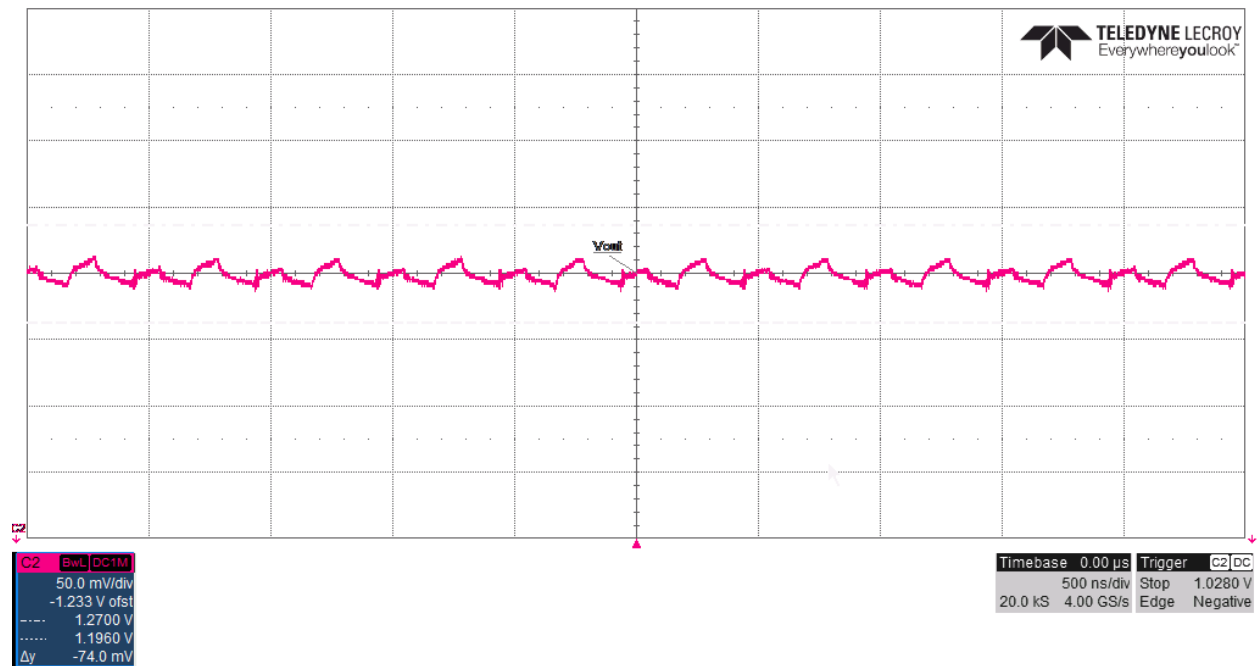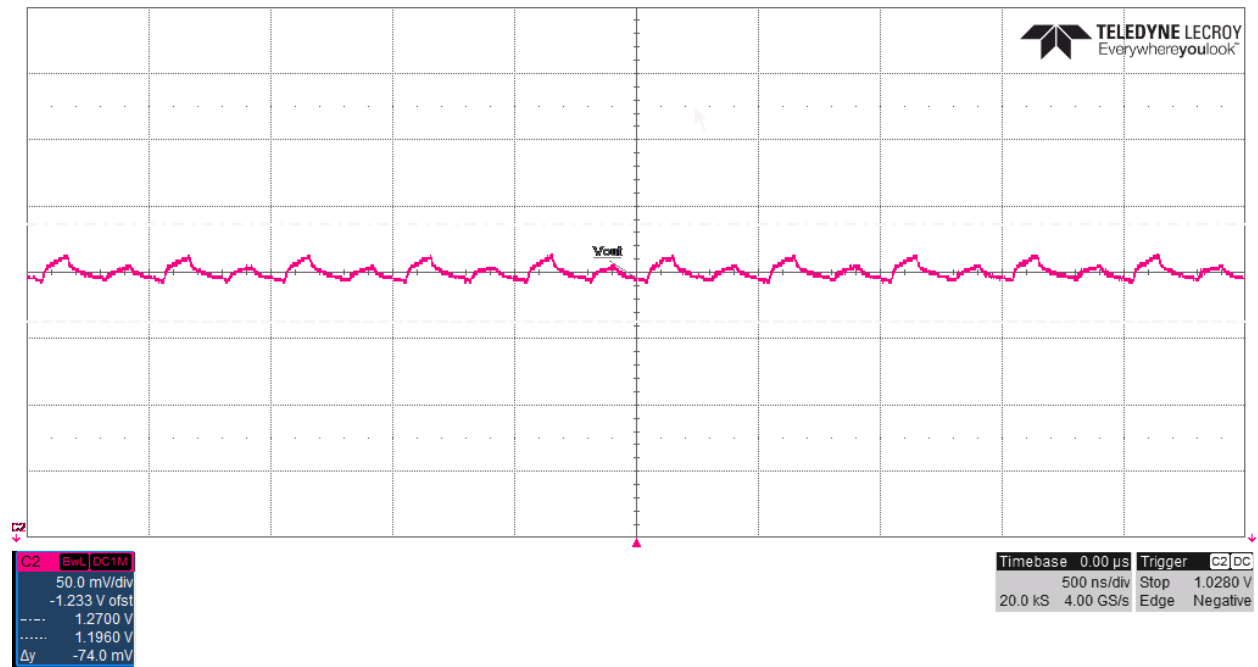
### 2.7 Output Ripple


The 1.2V output ripple is shown in red below, DC coupled with offset, for 0A, 6A and 10A, respectively.



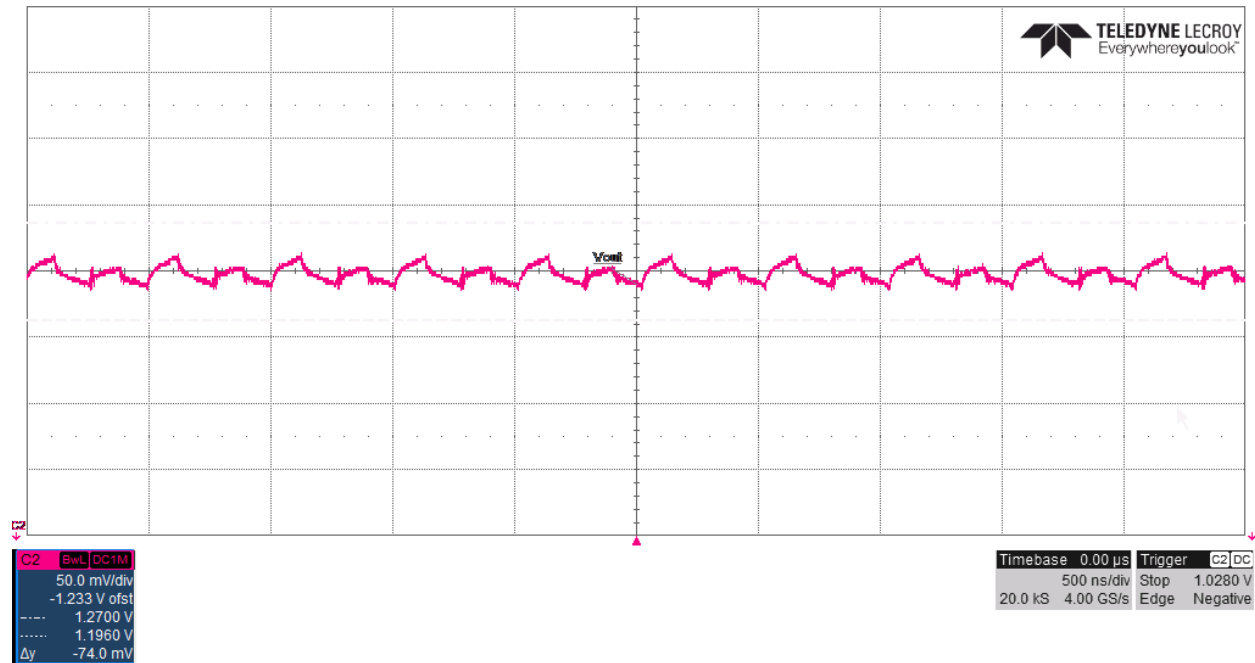
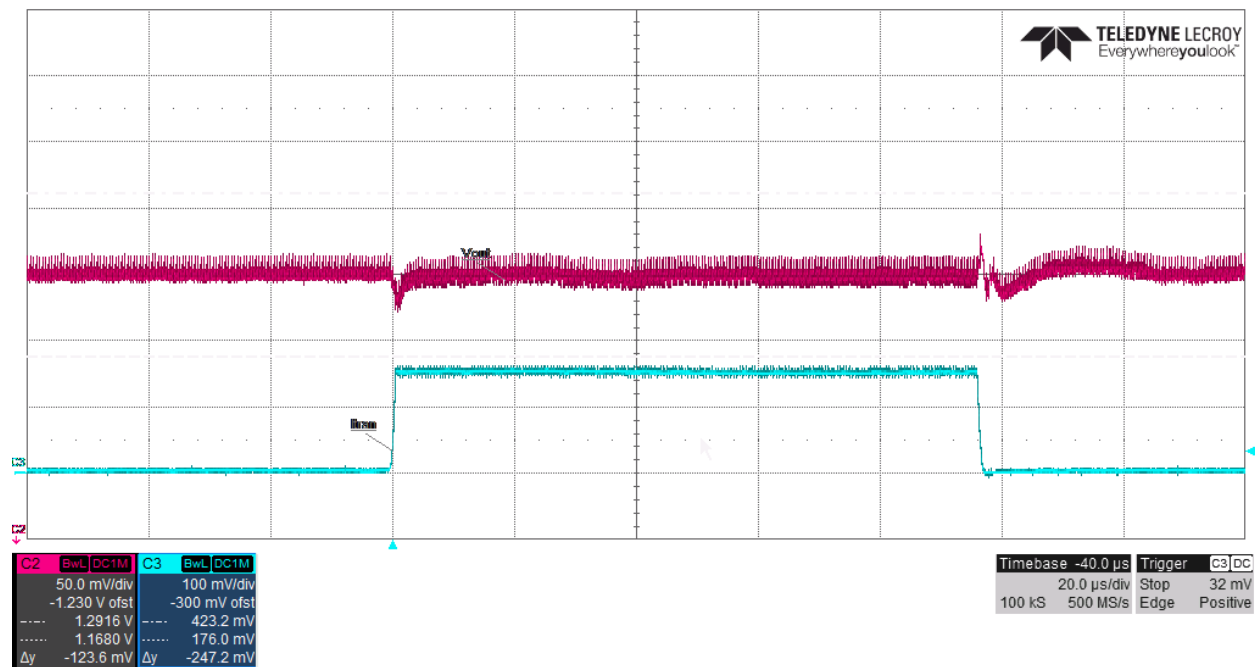
## 2.8 Transient response


The transient response is shown in the plot below where the red trace is the DC offset output voltage. The current step is 1A-6A-1A at 5A/ $\mu$ s slew rate.



## PMP11438 Rev A Test Results
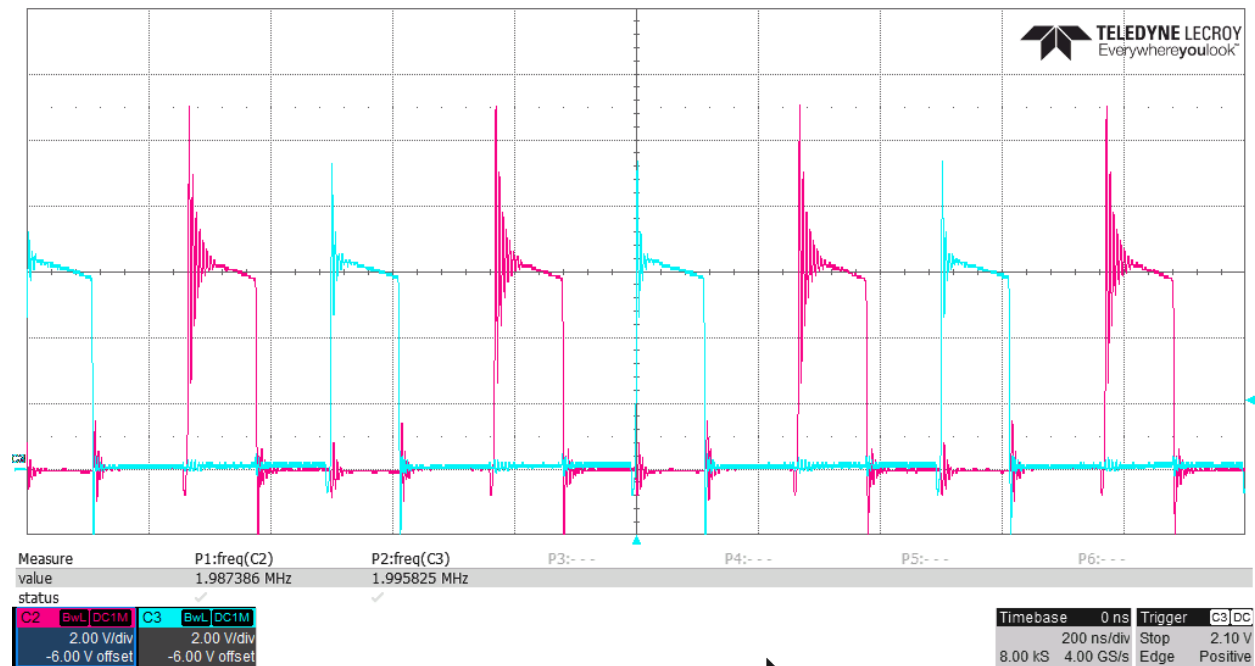
### 2.9 Synchronous Rectifier Stress



The voltage stresses on the synchronous MOSFETs are shown below. The image is taken at 12Vin and 6A with 200MHz of bandwidth limit.



## PMP11438 Rev A Test Results
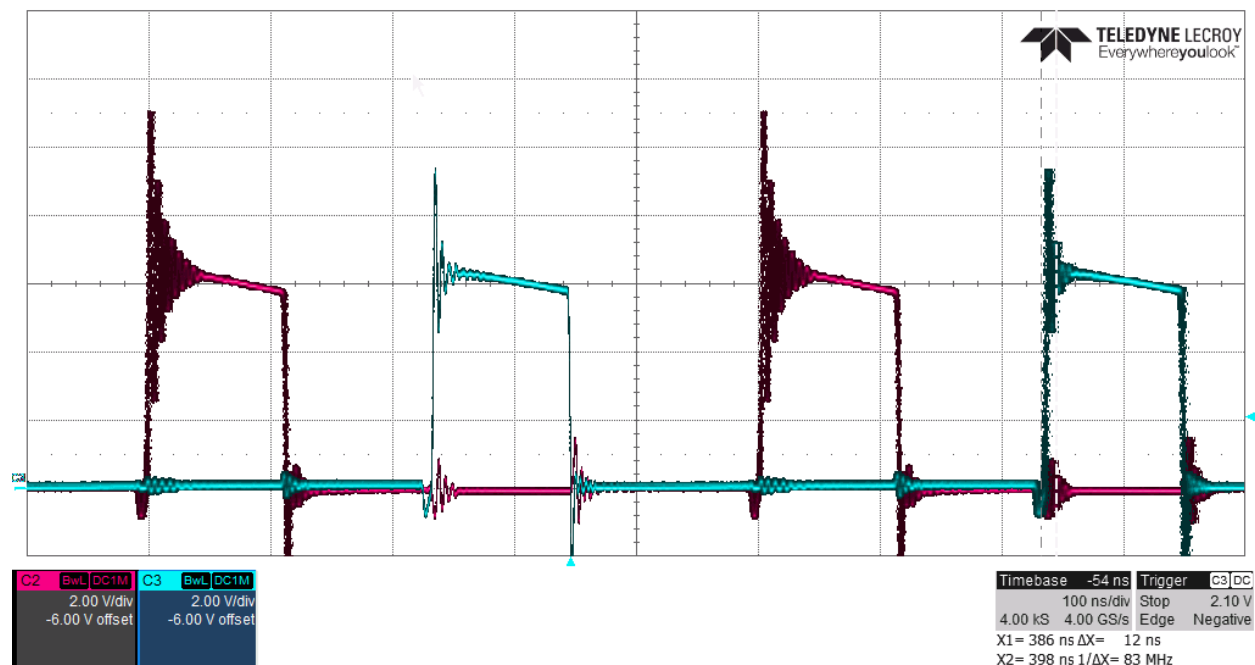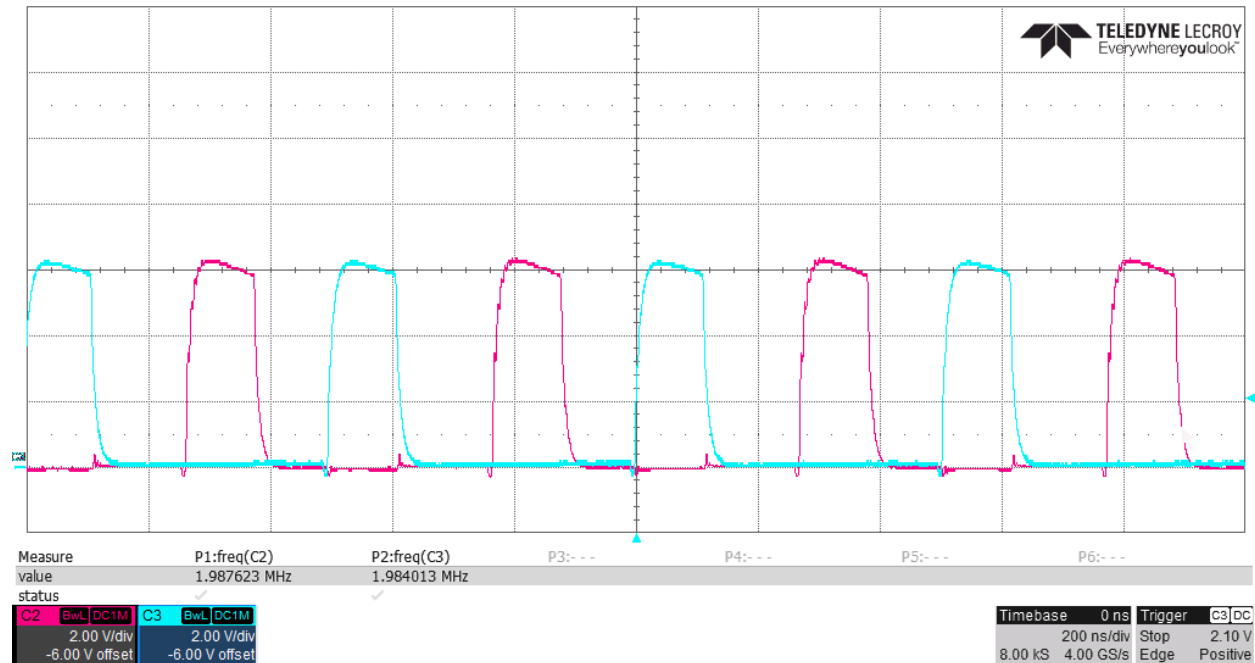
### 2.10 Frequency Characteristics

The switch nodes are shown below in blue and red and measured on the inductor. The first image illustrates the power supply switching frequency of ~2MHz per phase. The second image shows frequency jitter of 12ns. Both images are taken with 12V<sub>in</sub> and 6A<sub>out</sub>.






## PMP11438 Rev A Test Results
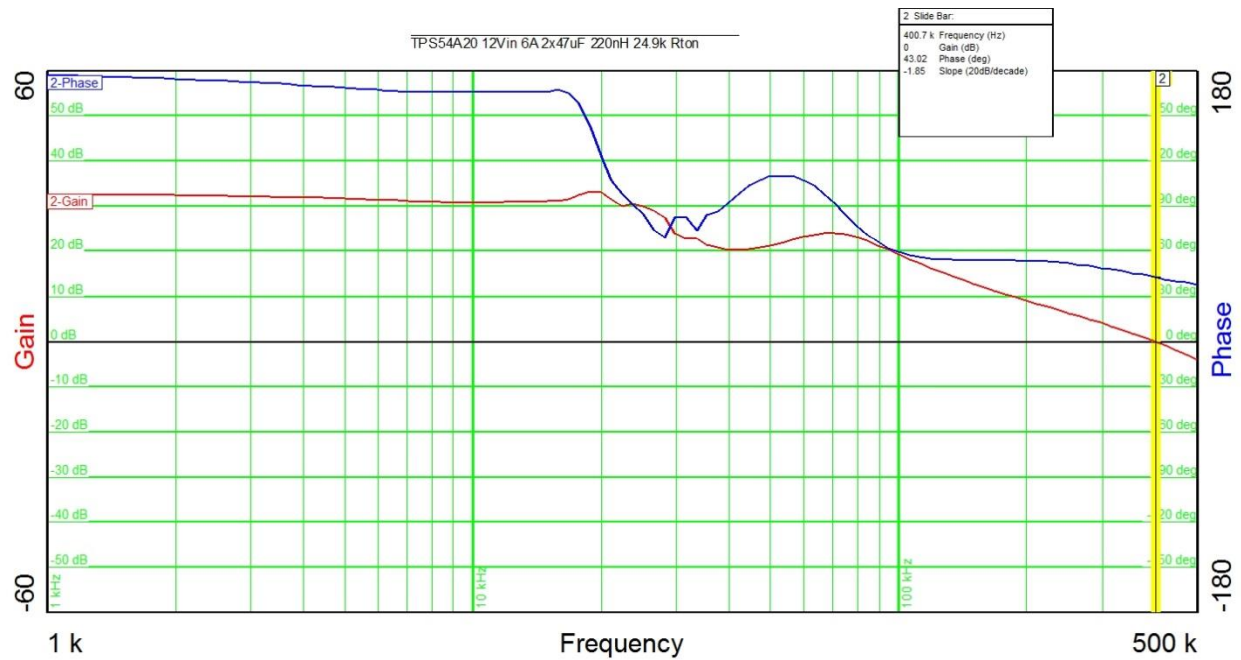
### 2.11 Loop Response

The loop response of the power supply at 12Vin and 6A load current is shown below. The bandwidth is 400kHz with  $\sim 45^\circ$  of phase margin.





## PMP11438 Rev A Test Results

### 3 PMP11438 REVA 1.2V/6A - TPS62184
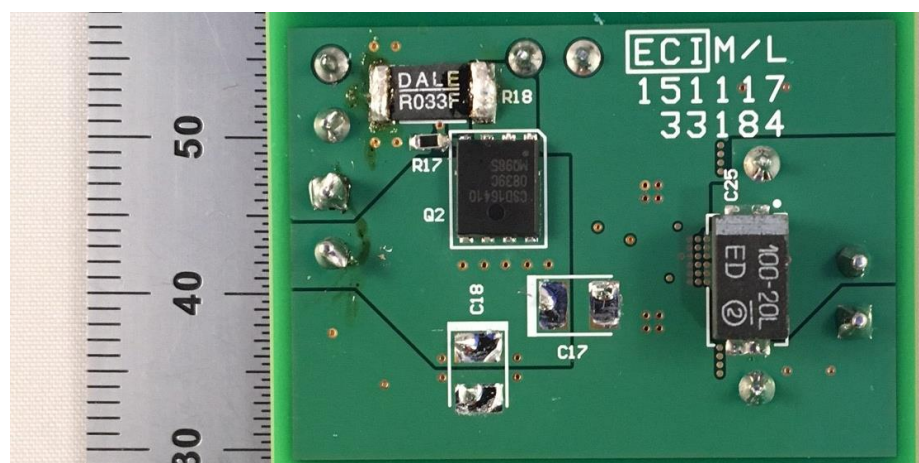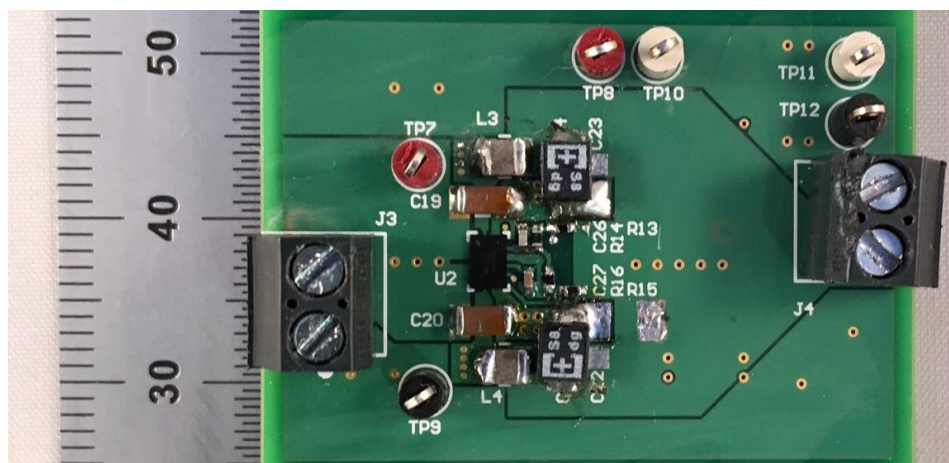
#### 3.1 Board Photos


The top and bottom images of PMP11438 TPS62184 are shown below.



## PMP11438 Rev A Test Results

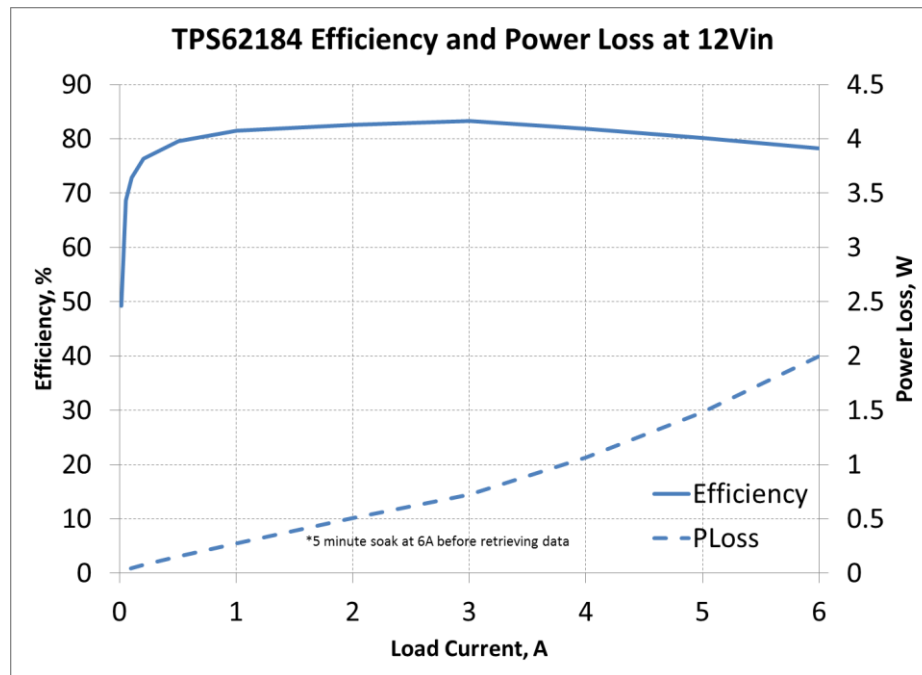
### 3.2 Efficiency and Power Loss

The efficiency and power loss of the power supply is shown below at 12Vin with natural convection.


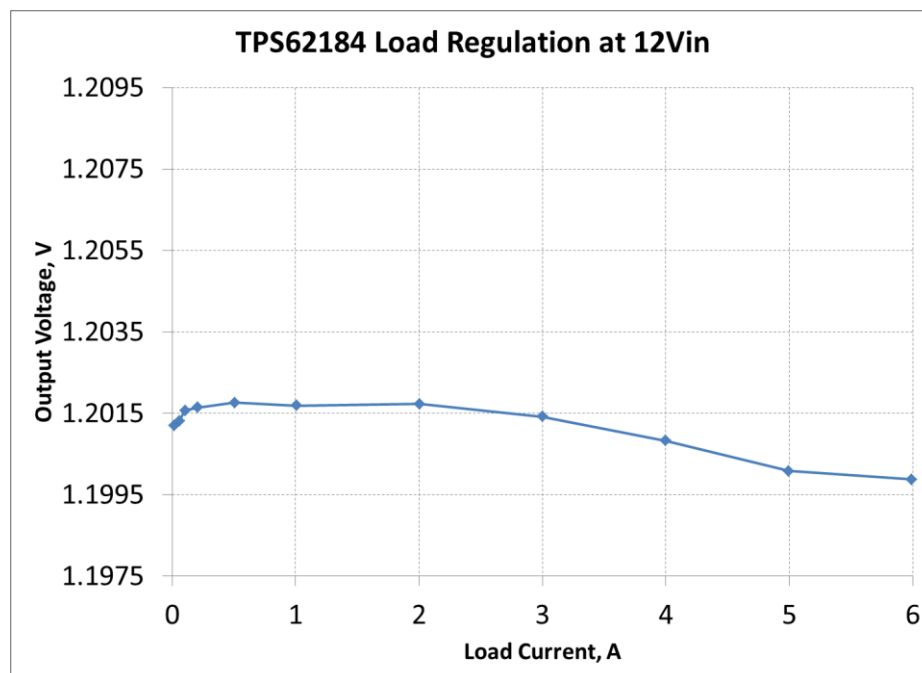
### 3.3 Load Regulation


The load regulation of the power supply is shown below at 12Vin.



## PMP11438 Rev A Test Results
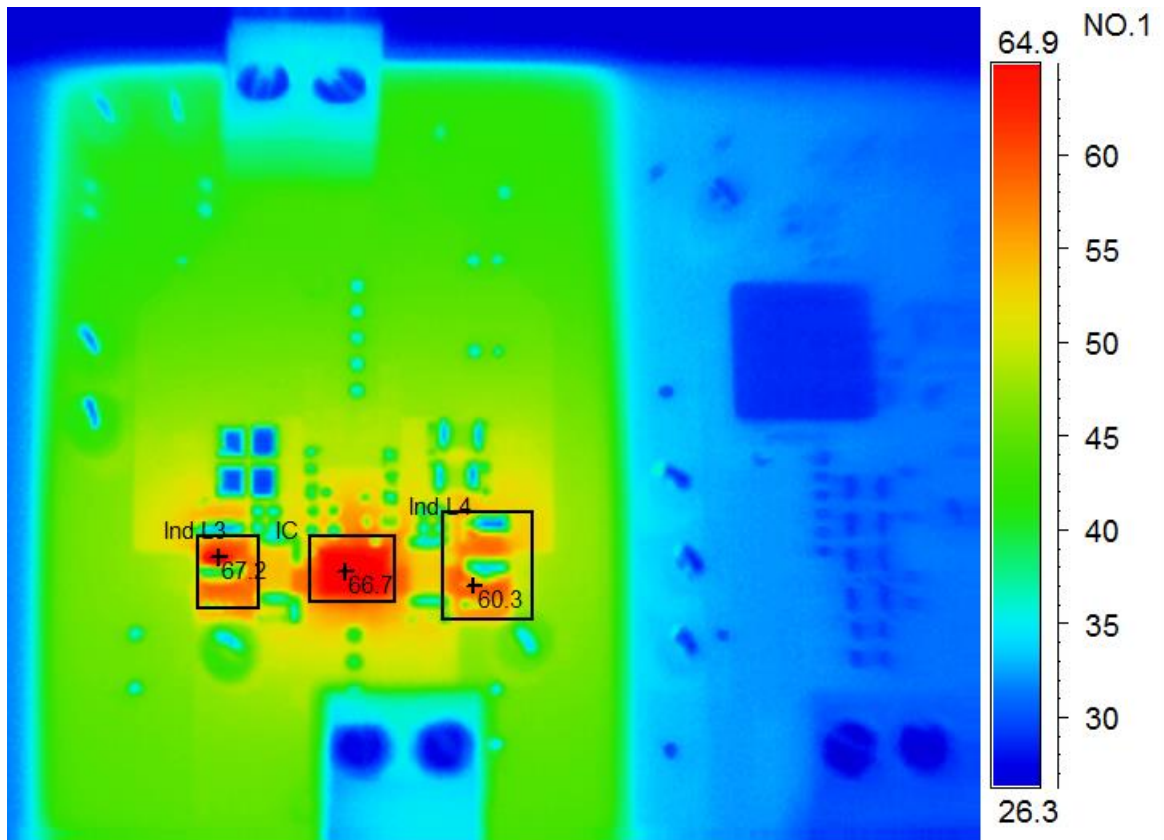
### 3.4 Thermal

The thermal image of the power supply is shown at room temperature with 12Vin, 6Aout, and natural convection. The power supply soaked for 10min at 6A before the measurement was taken. The IC, which has integrated MOSFETs, is one of the hottest components at 66.7°C.




Area analysis	Value
IC Max	66.7°C
Ind L3 Max	67.2°C
Ind L4 Max	60.3°C

NO.1

## PMP11438 Rev A Test Results

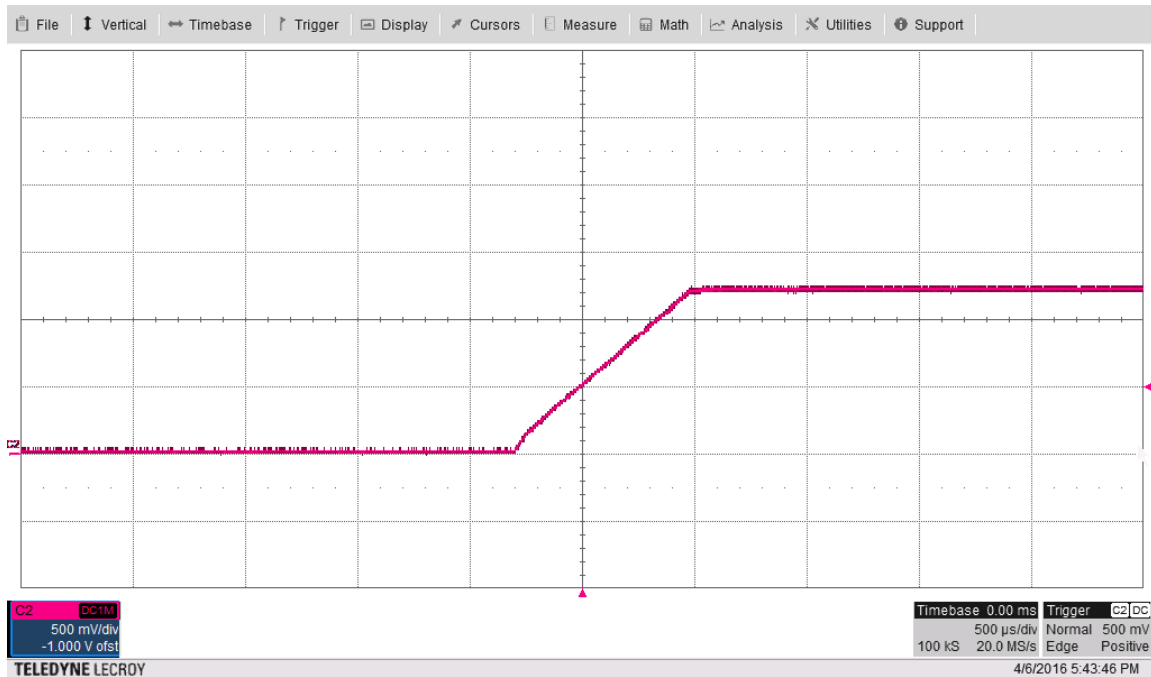
### 3.5 Startup

The power supply startup at 0A is shown below. The startup time is 750 $\mu$ s.


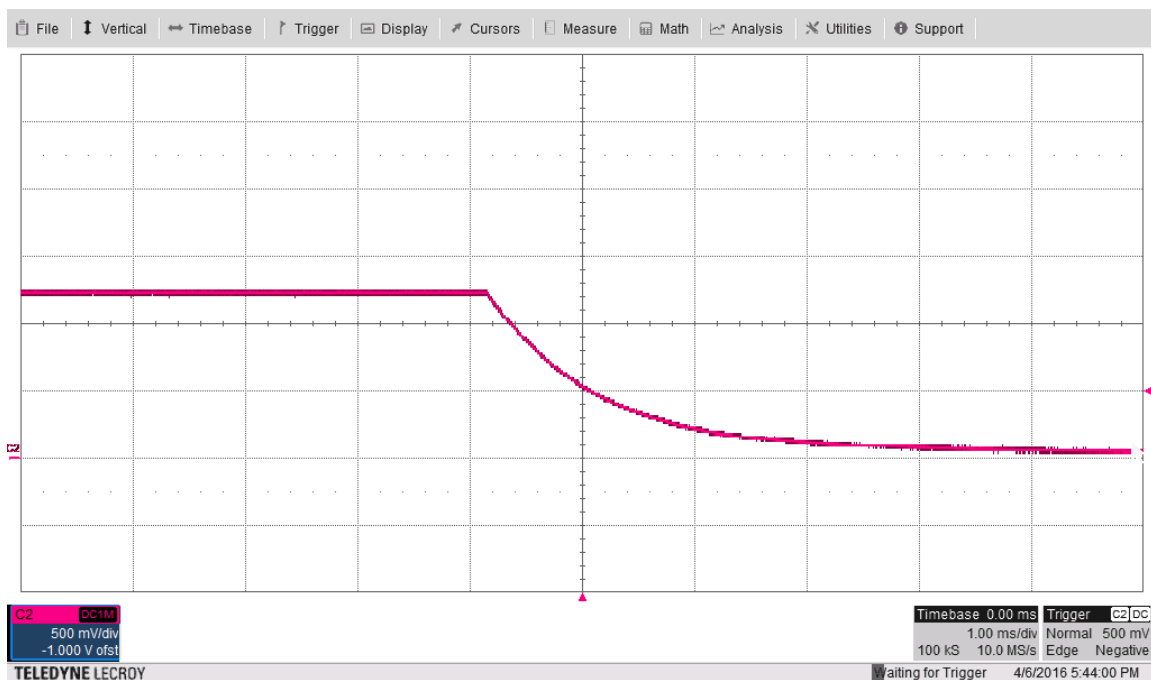
### 3.6 Shutdown

The shutdown of the power supply with 1.2 $\Omega$  constant-resistance load is shown below.







## PMP11438 Rev A Test Results

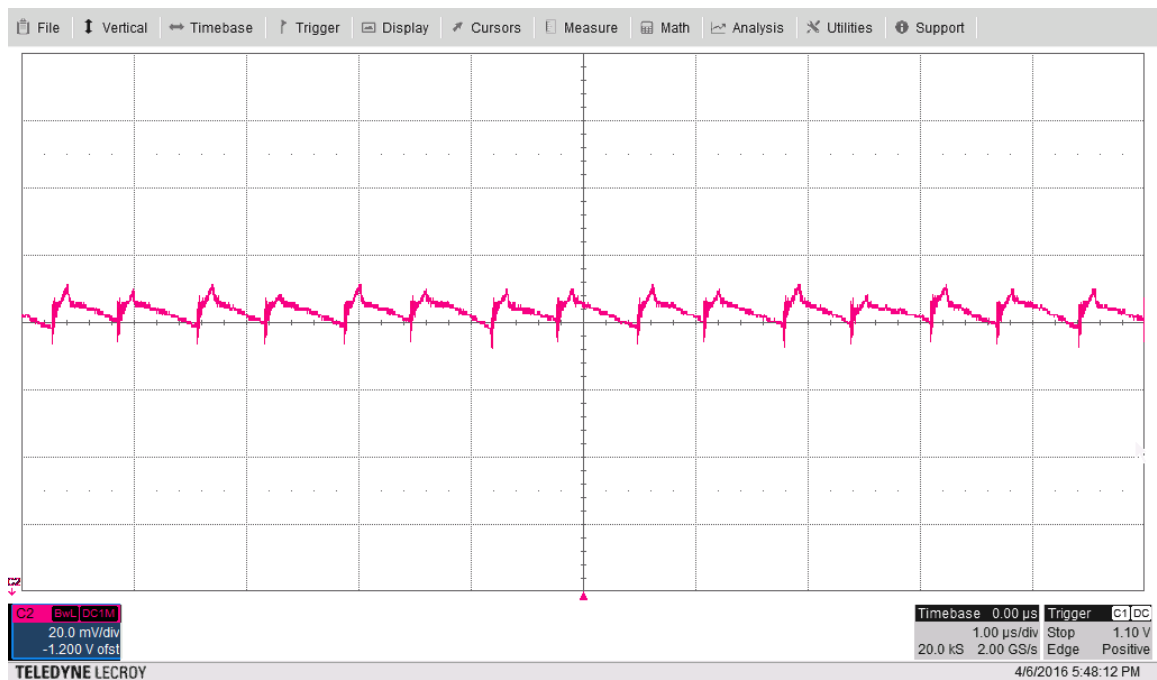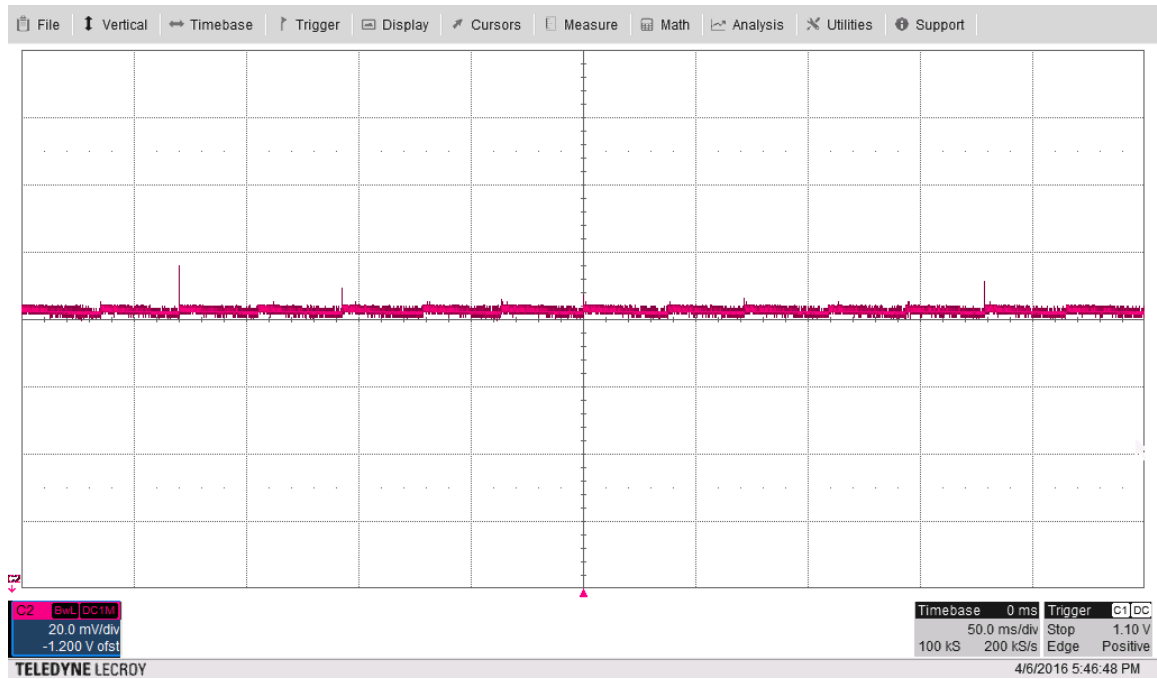
### 3.7 Output Ripple

The 1.2V output ripple is shown in red below, DC coupled with offset, for 0A, 3A and 6A, respectively.



4/08/2016


# PMP11438 Rev A Test Results

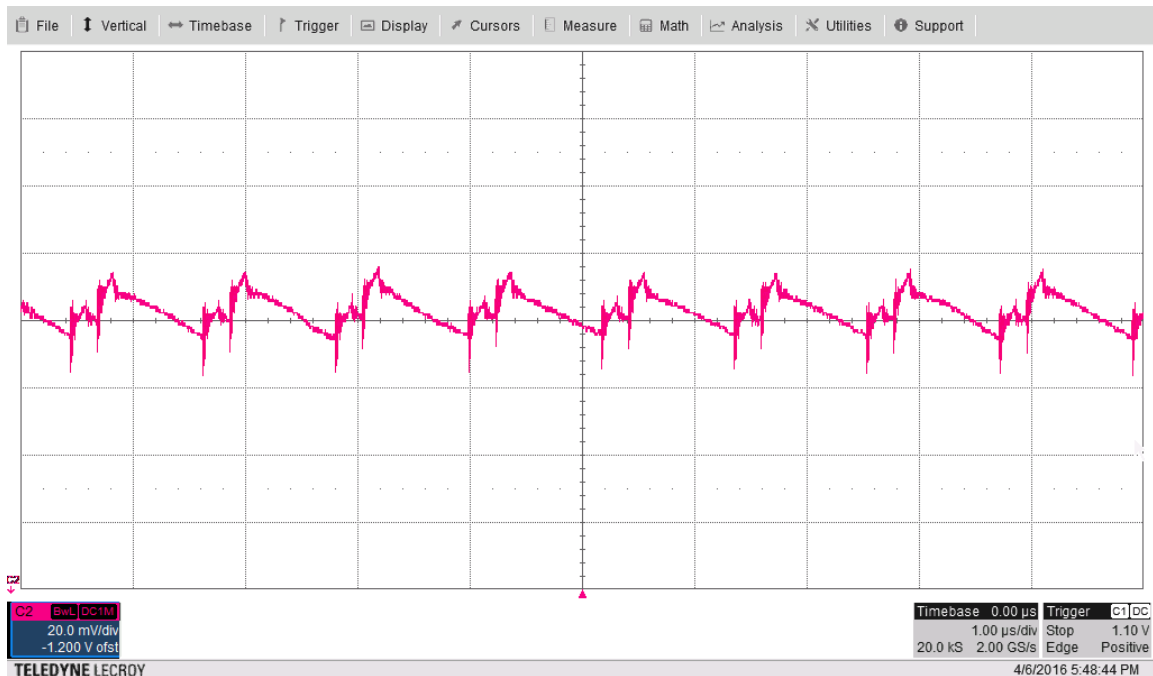

## PMP11438 Rev A Test Results

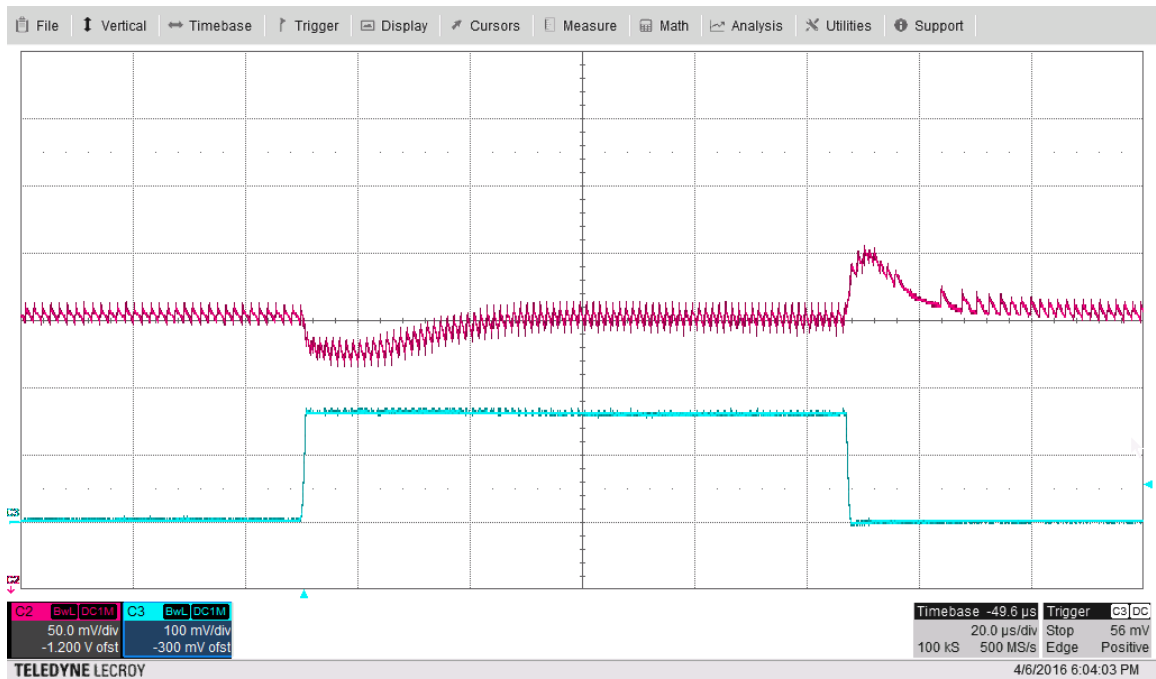
### 3.8 Transient response

The transient response is shown in the plot below where the red trace is the DC offset output voltage. The current step is 1A-6A-1A at 5A/ $\mu$ s slew rate.


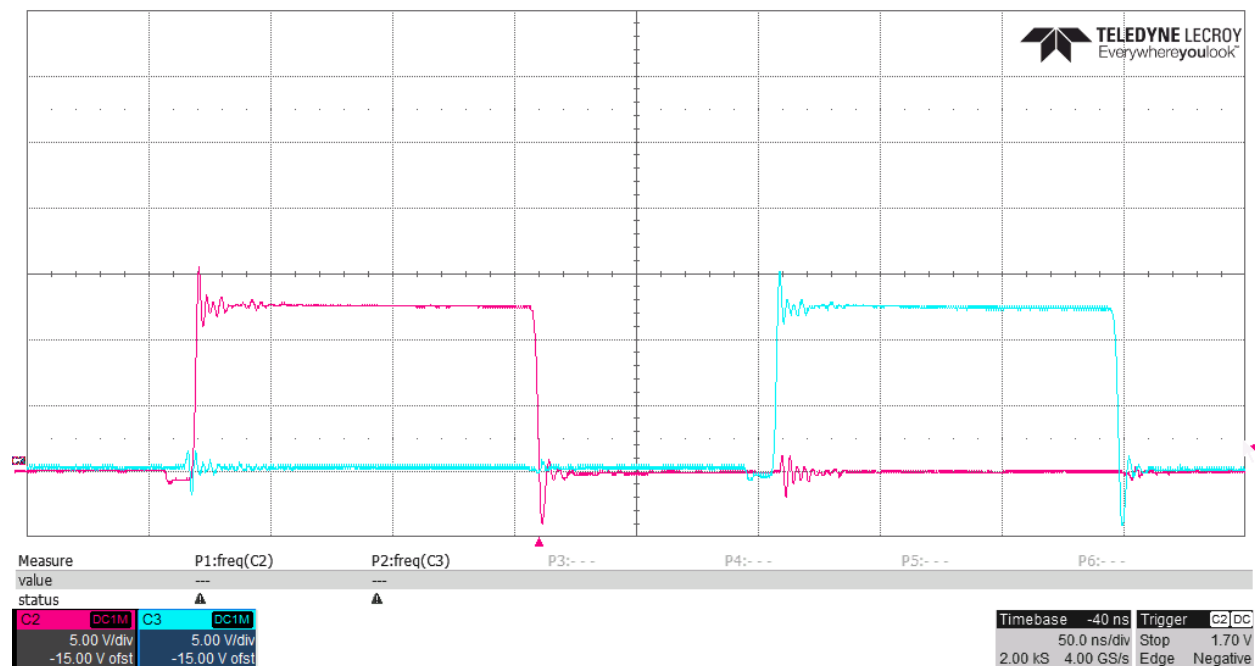
### 3.9 Synchronous Rectifier Stress



The voltage stresses on the synchronous MOSFETs are shown below. The image is taken at 12Vin and 6A with 200MHz of bandwidth limit.



## PMP11438 Rev A Test Results
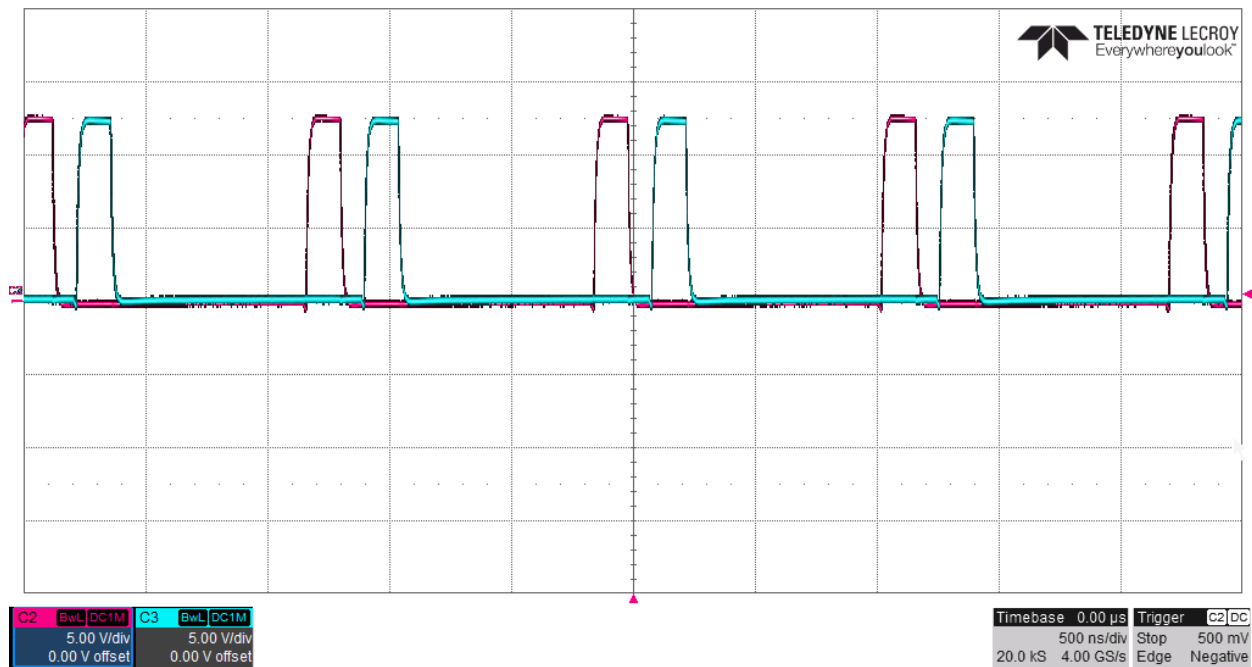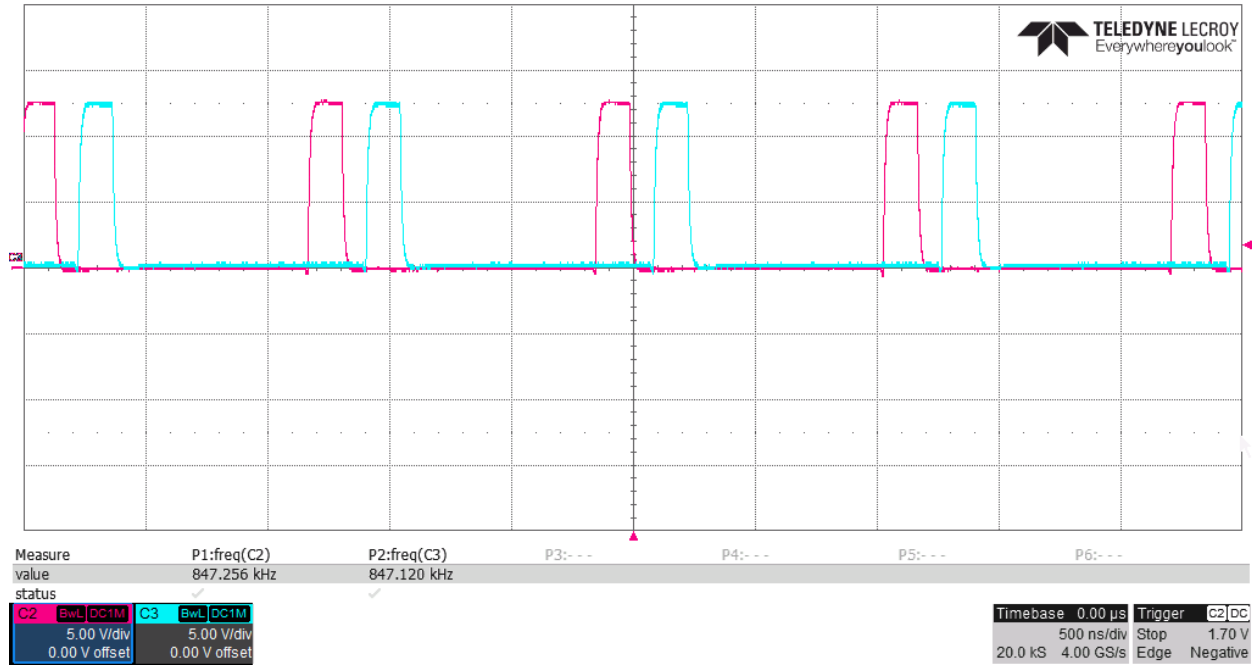
### 3.10 Frequency Characteristics


The switch nodes are shown below in blue and red and measured on the inductor. The first image illustrates the power supply switching frequency of ~850kHz per phase. The second image shows negligible frequency jitter. Both images are taken with 12Vin and 6Aout.



## PMP11438 Rev A Test Results
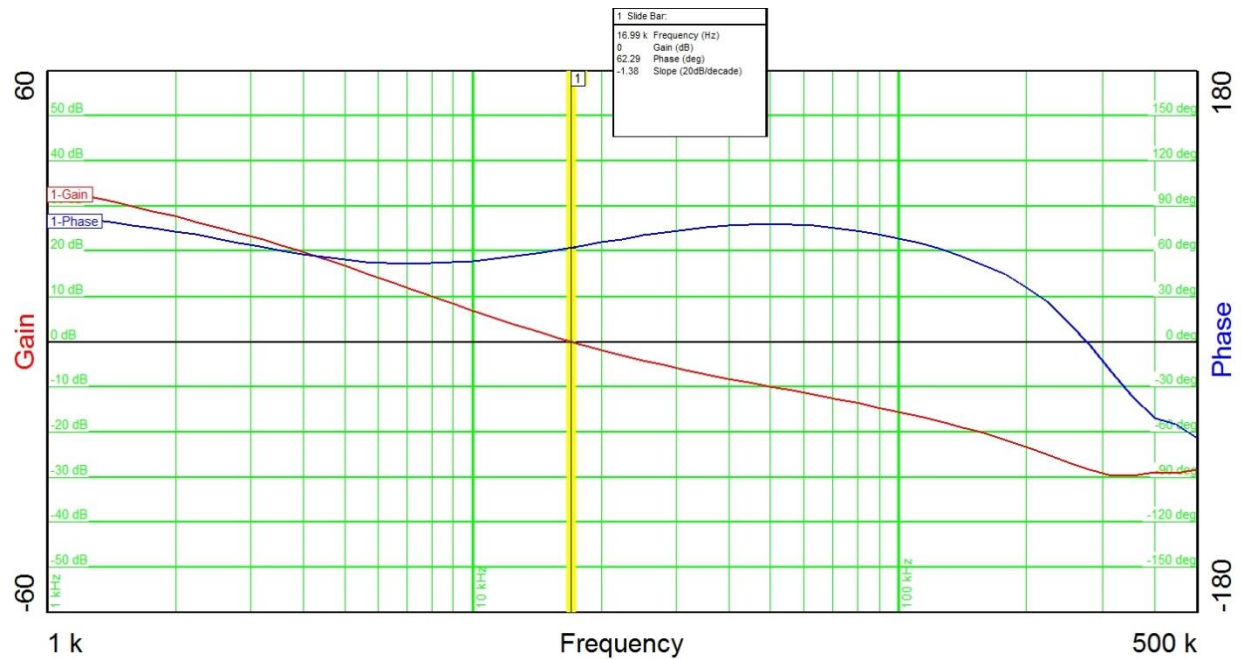
### 3.11 Loop Response

The loop response of the power supply at 12Vin and 6A load current is shown below. The bandwidth is 17kHz with  $\sim 62^\circ$  of phase margin.







## PMP11438 Rev A Test Results

### 4 PMP11438 REVA 1.2V/6A - TPS53515
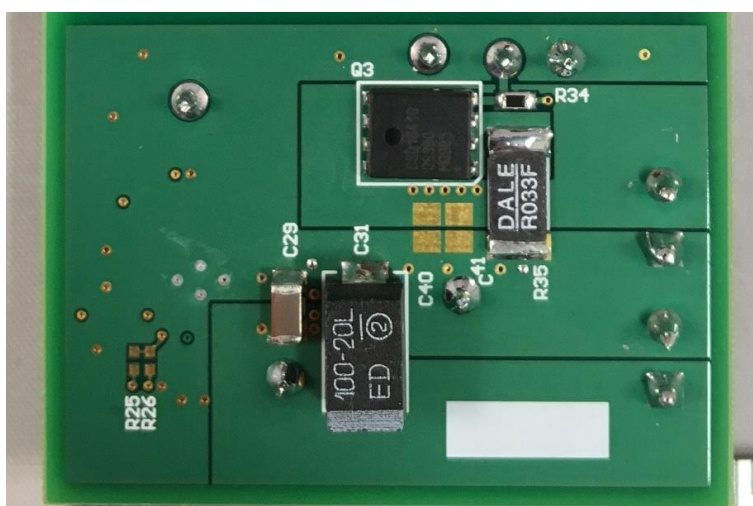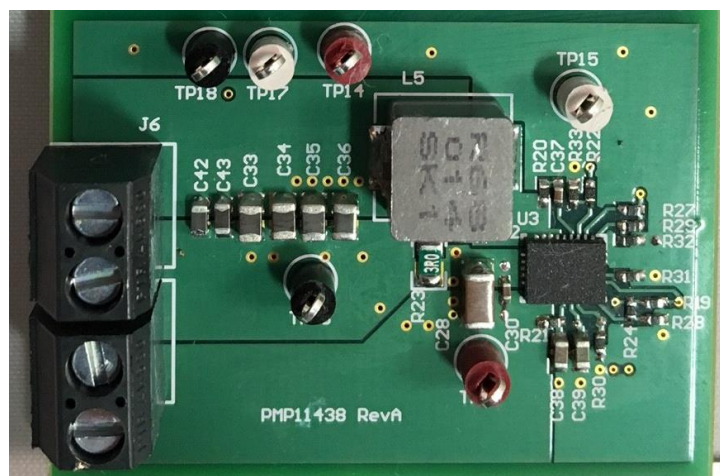
#### 4.1 Board Photos


The top and bottom images of PMP11438 TPS53515 are shown below.



## PMP11438 Rev A Test Results

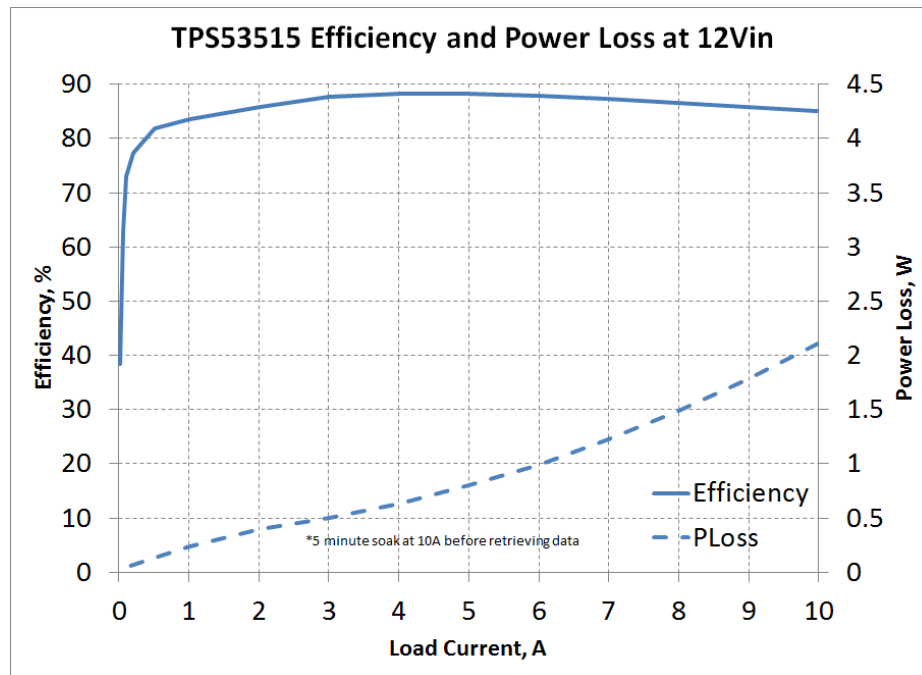
### 4.2 Efficiency and Power Loss

The efficiency and power loss of the power supply is shown below at 12Vin with natural convection.


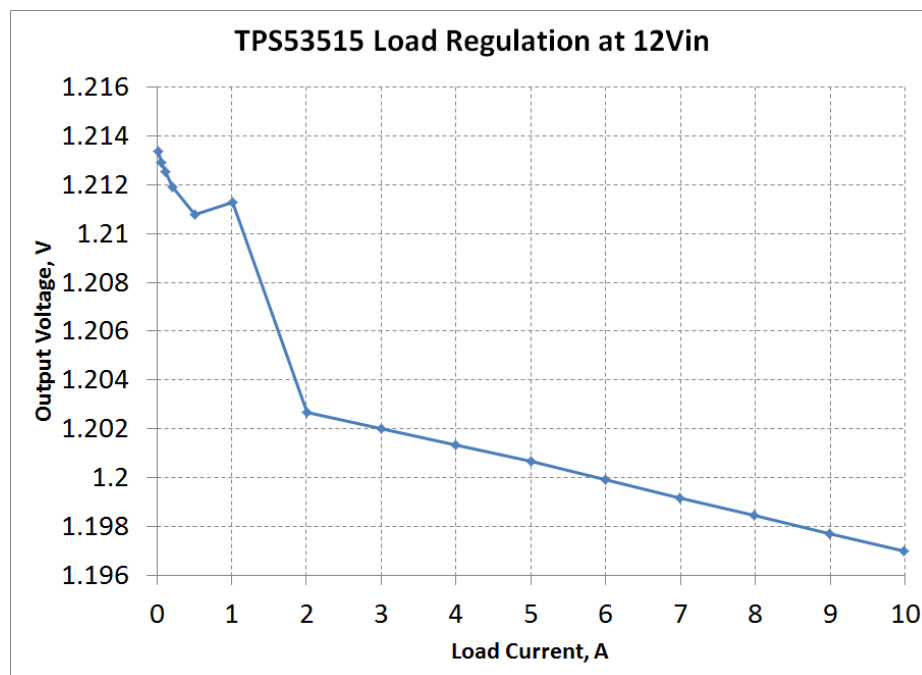
### 4.3 Load Regulation


The load regulation of the power supply is shown below at 12Vin.



## PMP11438 Rev A Test Results

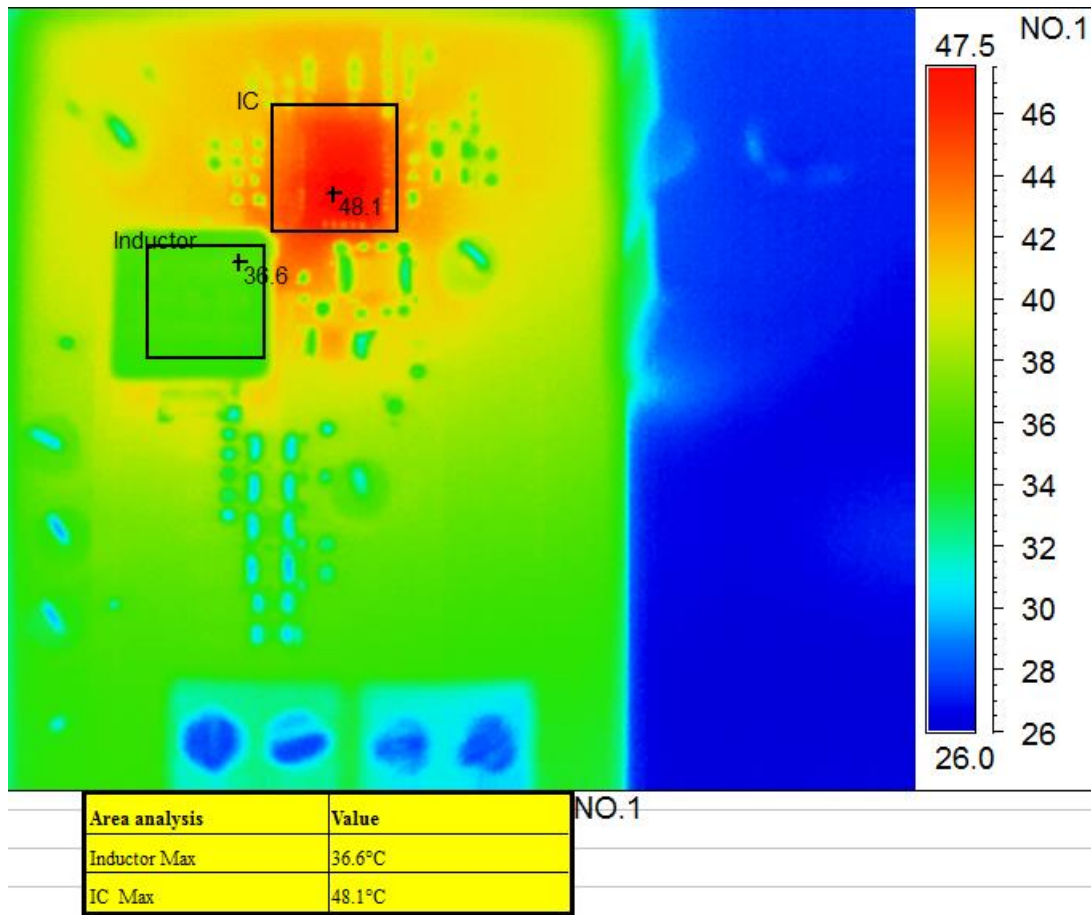
### 4.4 Thermal

The thermal image of the power supply is shown at room temperature with 12Vin, 6Aout, and natural convection. The power supply soaked for 10min at 6A before the measurement was taken. The IC, which has integrated MOSFETs, is one of the hottest components at 48.1°C.



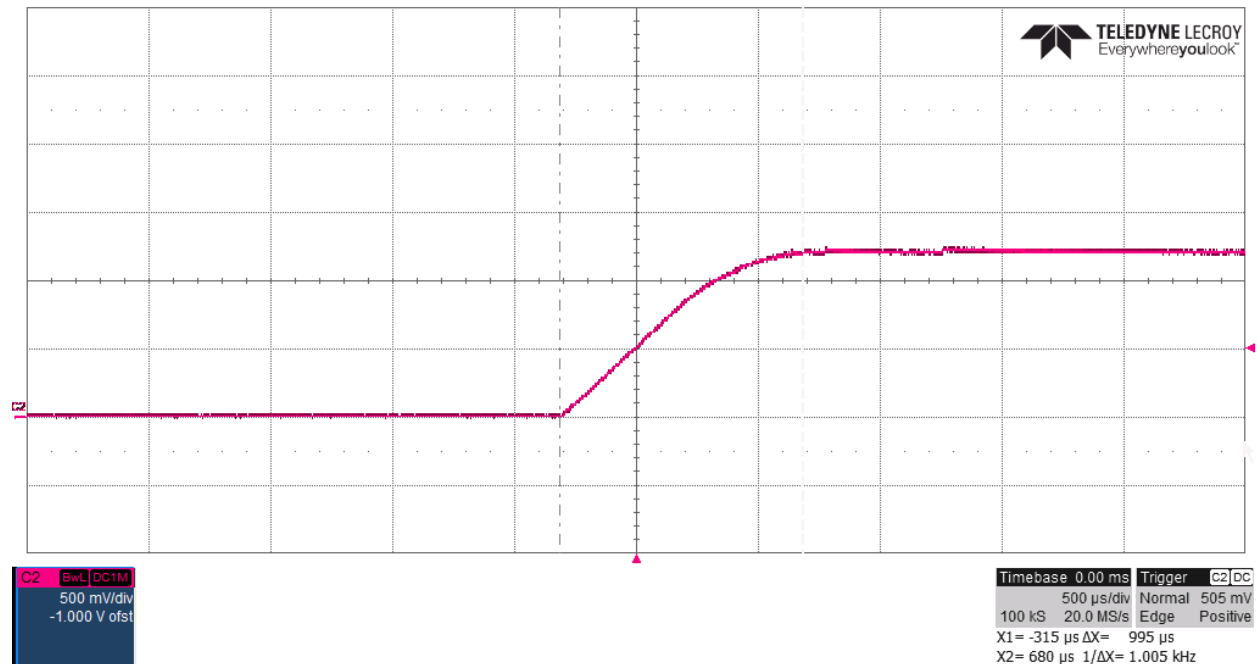
## 4.5 Startup

The power supply startup at 0A is shown below. The startup time is 750 $\mu$ s.


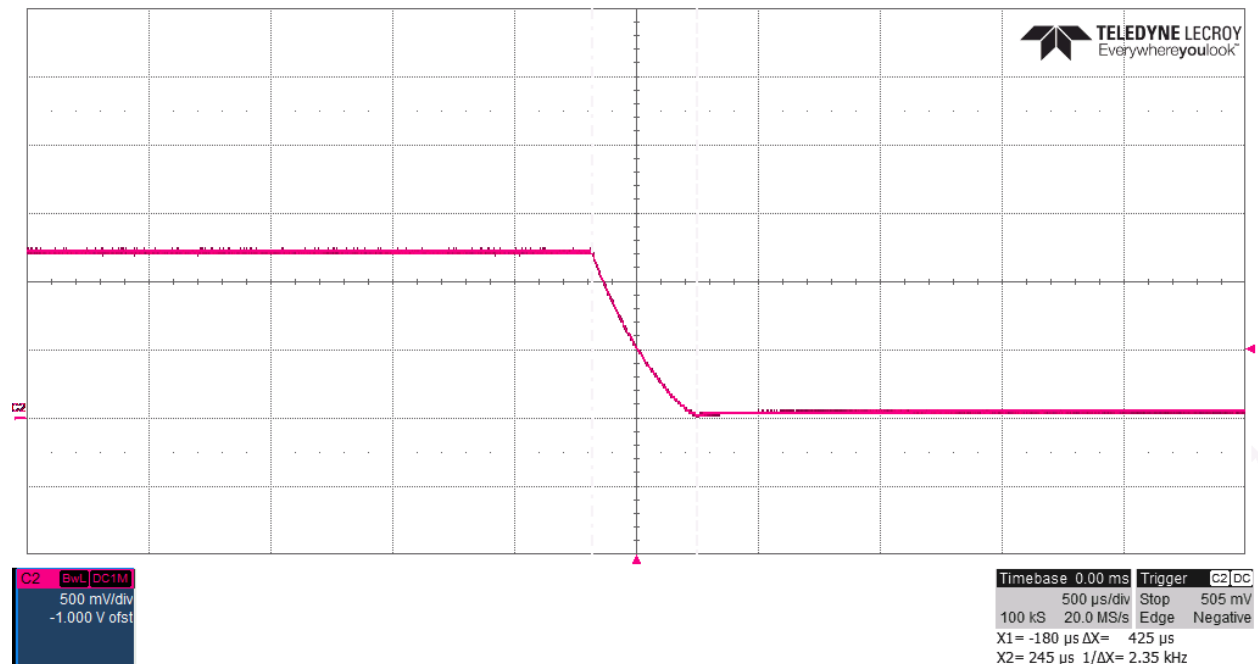
## 4.6 Shutdown

The shutdown of the power supply with 1.2 $\Omega$  constant-resistance load is shown below.





4/08/2016

## PMP11438 Rev A Test Results


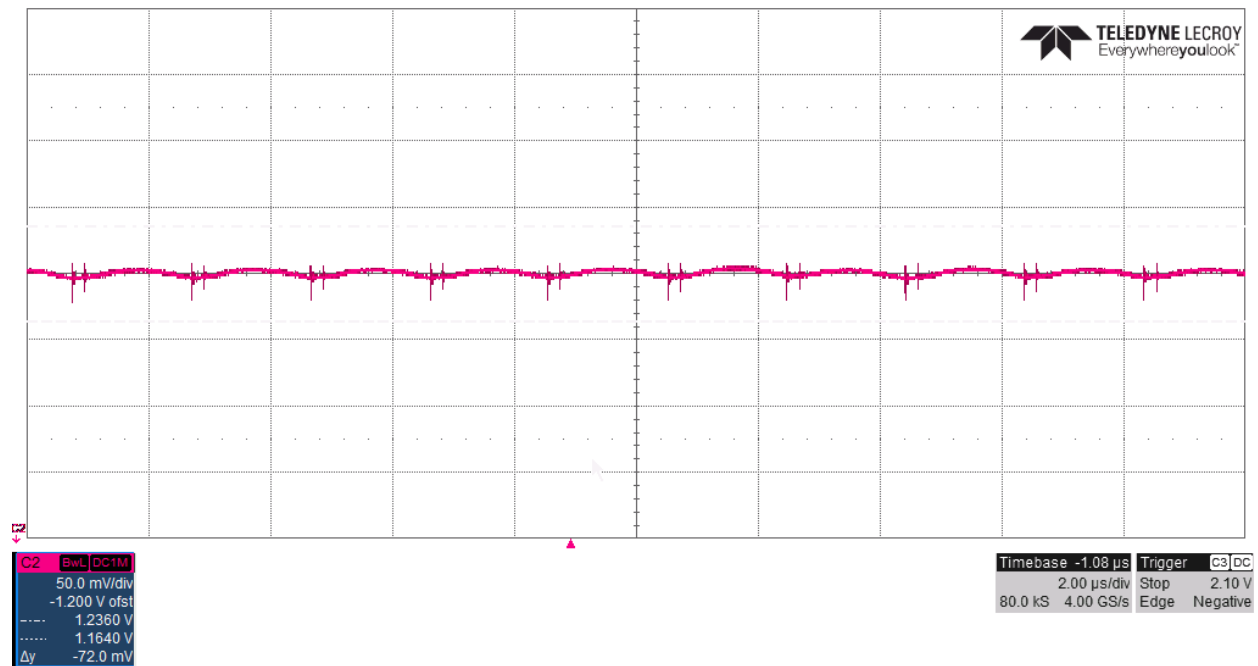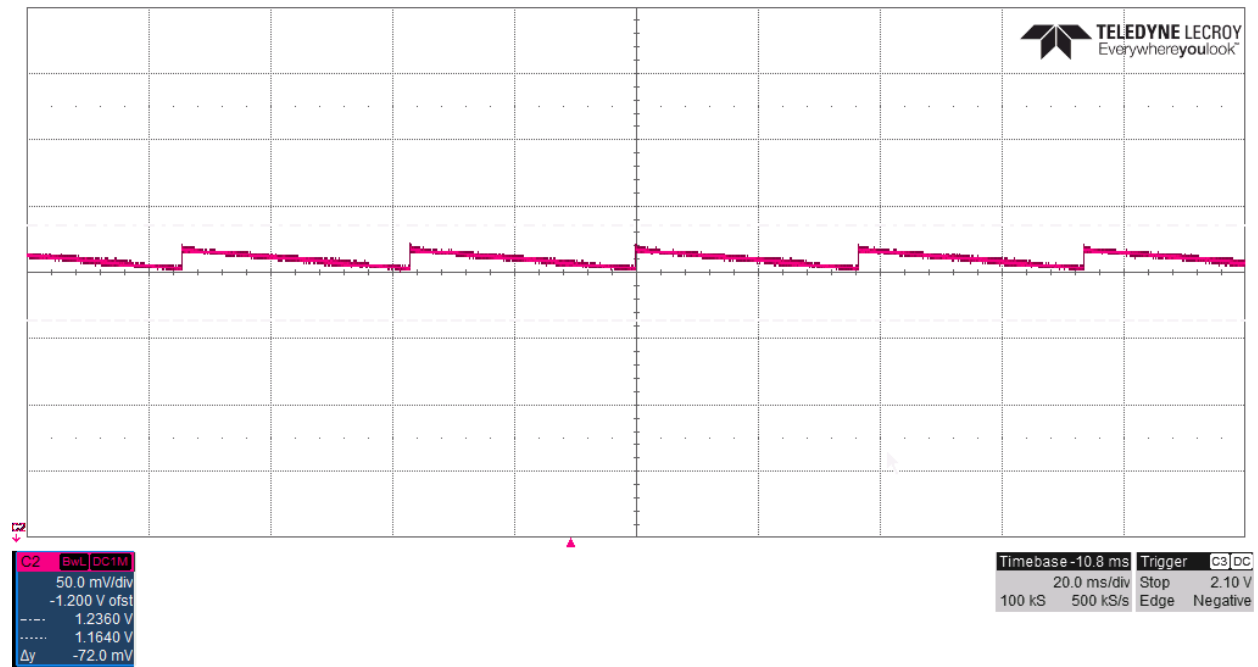
### 4.7 Output Ripple


The 1.2V output ripple is shown in red below, DC coupled with offset, for 0A, 6A and 10A, respectively.





4/08/2016


# PMP11438 Rev A Test Results

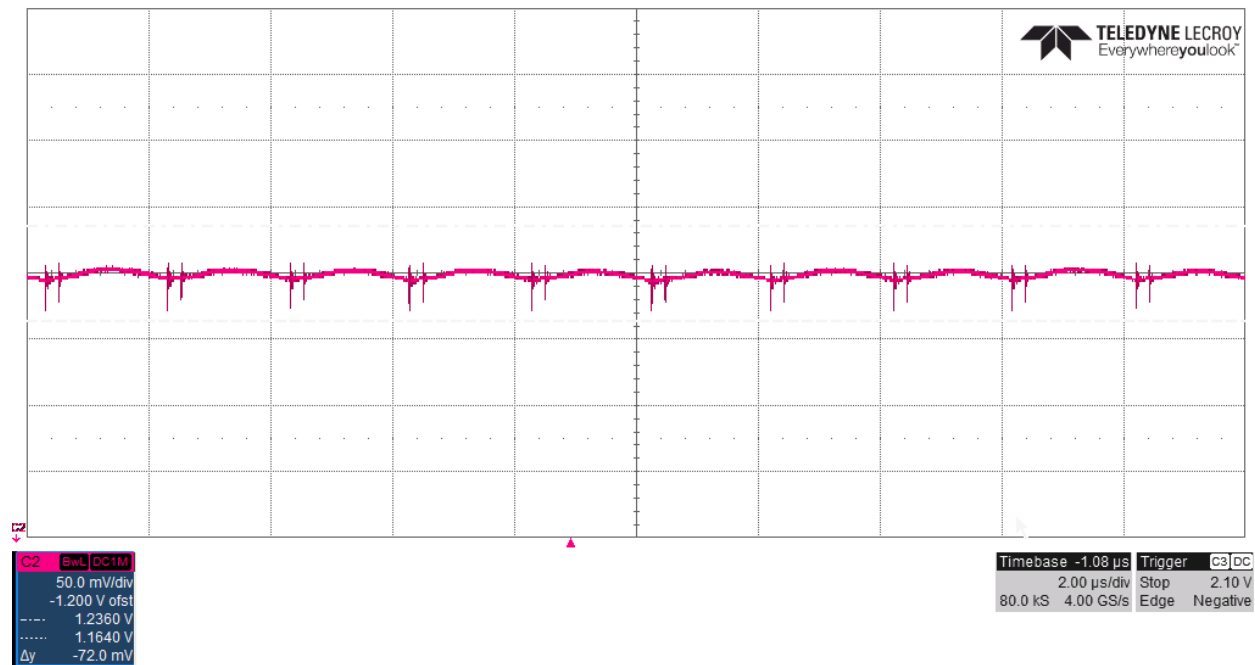

## PMP11438 Rev A Test Results

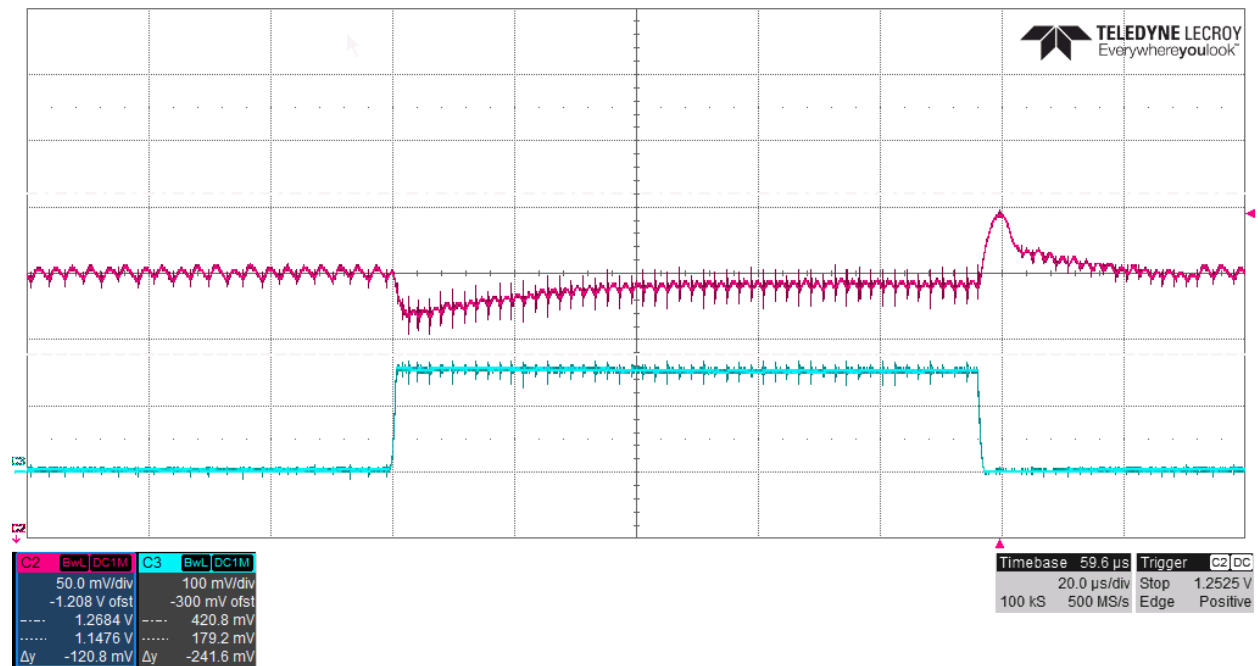
### 4.8 Transient response

The transient response is shown in the plot below where the red trace is the DC offset output voltage. The current step is 1A-6A-1A at 5A/ $\mu$ s slew rate.


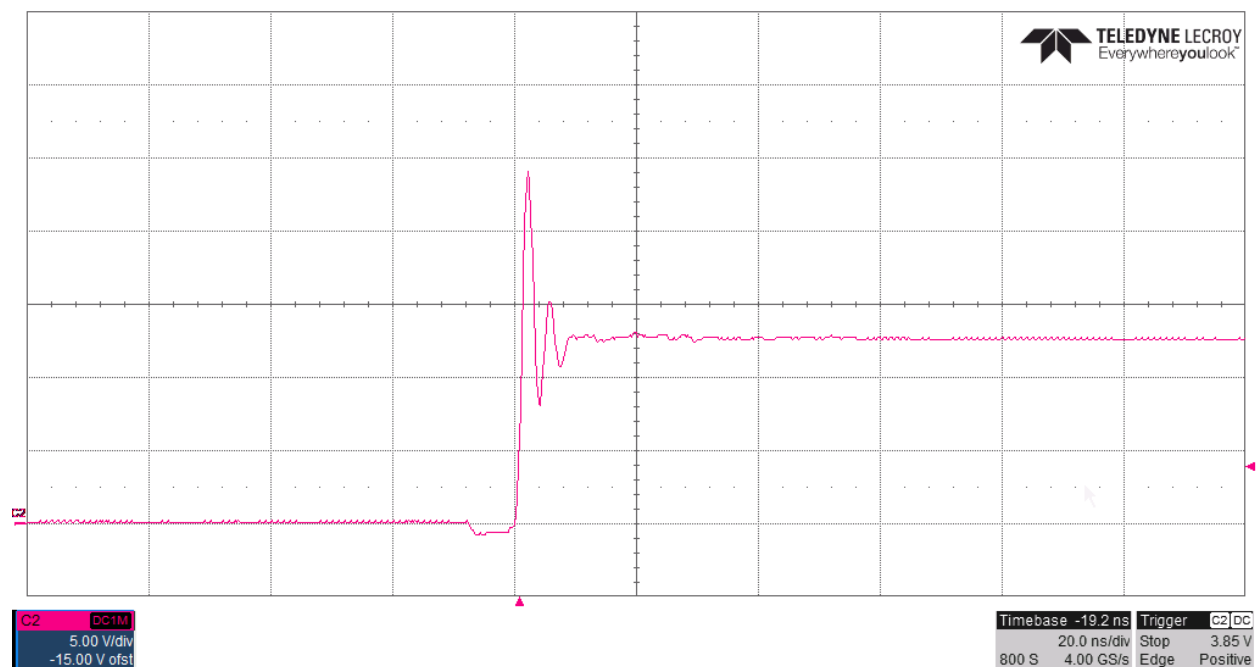
### 4.9 Synchronous Rectifier Stress



The voltage stresses on the synchronous MOSFETs are shown below. The image is taken at 12Vin and 6A with 200MHz of bandwidth limit.



## PMP11438 Rev A Test Results
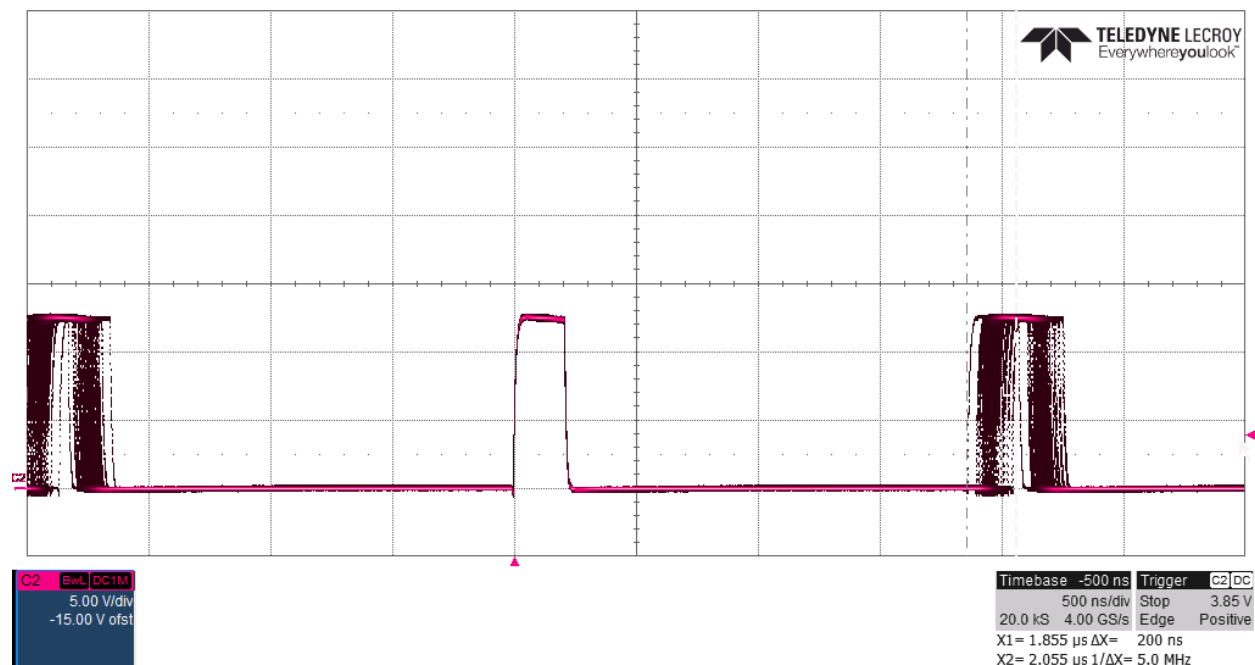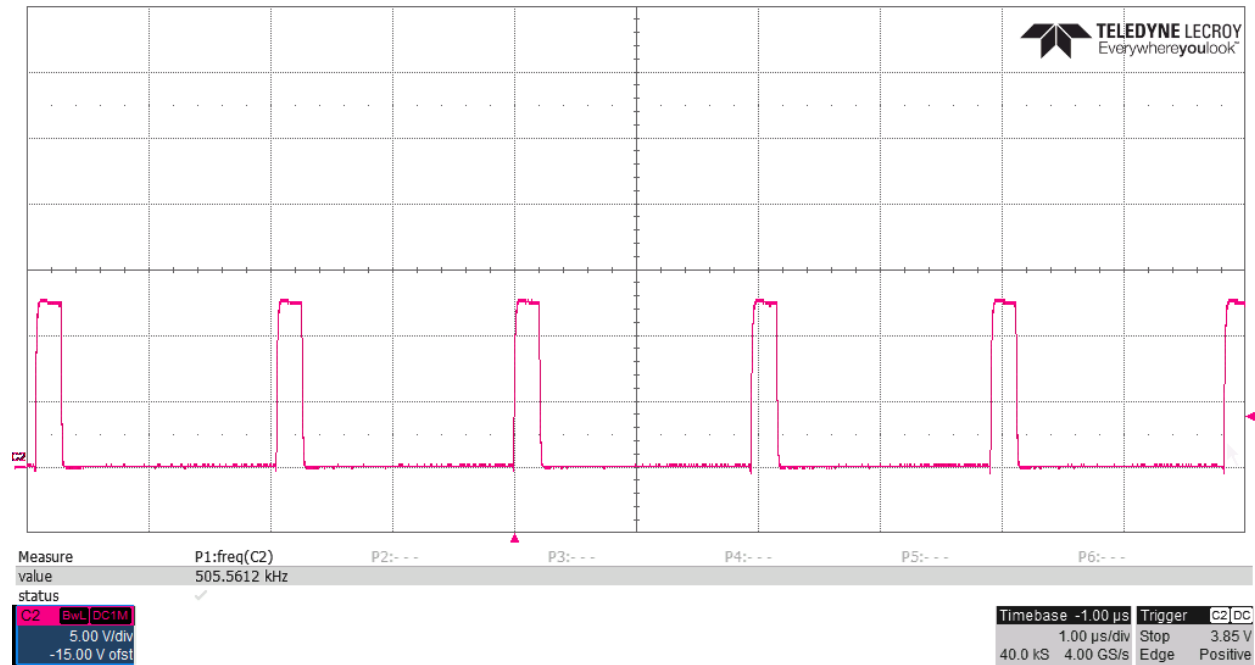
### 4.10 Frequency Characteristics


The switch node is shown below in red and measured on the inductor. The first image illustrates the power supply switching frequency of  $\sim 500\text{kHz}$  per phase. The second image shows  $\sim 200\text{ns}$  of frequency jitter. Both images are taken with  $12\text{V}_{\text{in}}$  and  $6\text{A}_{\text{out}}$ .



## PMP11438 Rev A Test Results

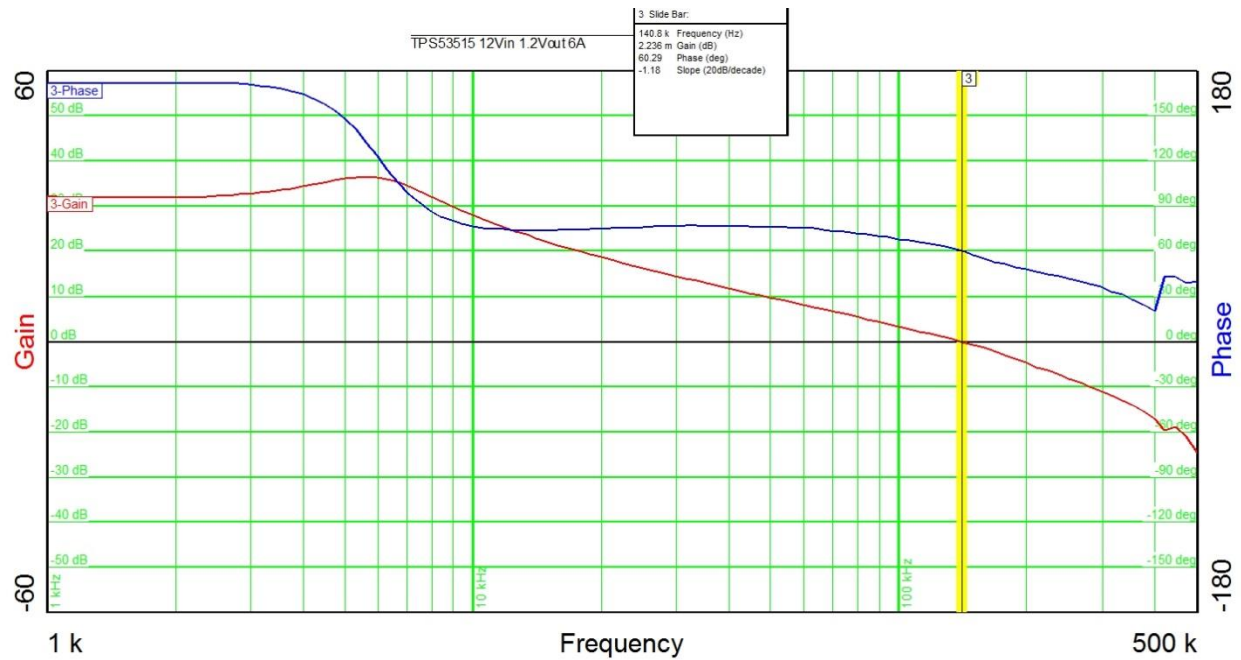**4.11 Loop Response**

The loop response of the power supply at 12Vin and 6A load current is shown below. The bandwidth is 140kHz with  $\sim 60^\circ$  of phase margin.



## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.