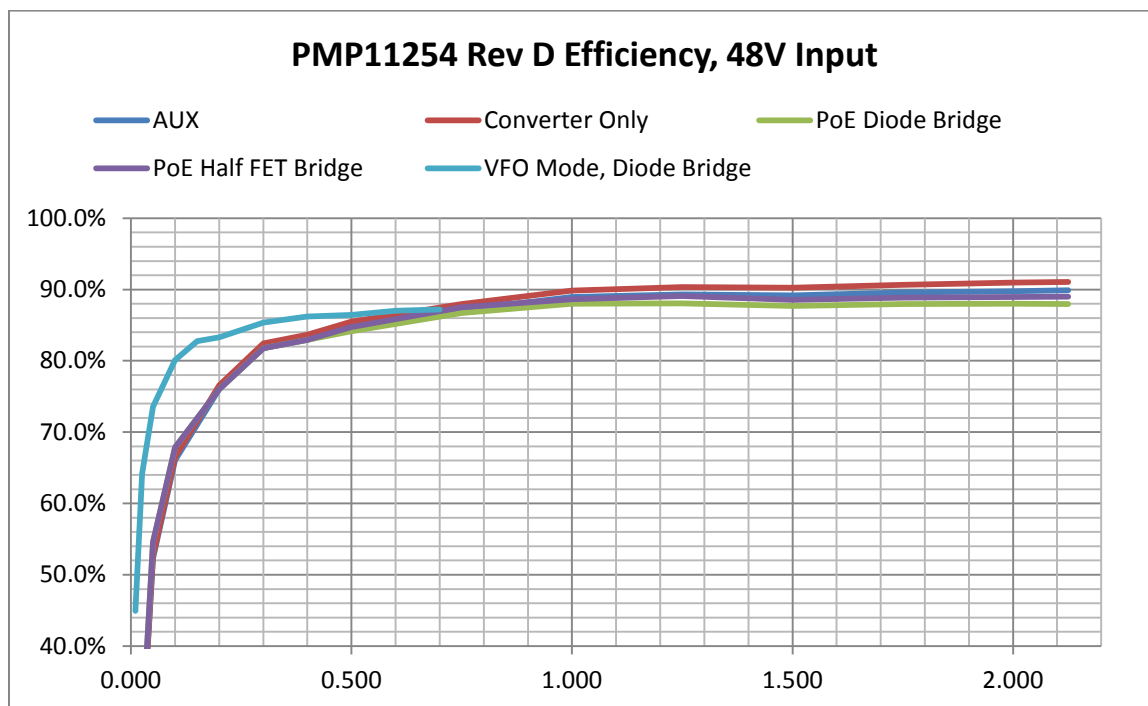


All measurements taken with a 48V input, 2.125A load and 20MHz BW, unless noted.

Efficiency



						VDD to PWRGND	
		AUX	AUX	AUX	Conv	Conv	
J6	J6	J5	J5	J5	Only	Only	
Iout	Vout	Iin	Vin	Eff	Vin	Eff	
0.000	12.05	0.006	48.00	0.0%	47.73	0.0%	
0.050	12.05	0.024	48.00	52.3%	47.68	52.7%	
0.100	12.05	0.038	48.00	66.1%	47.66	66.5%	
0.200	12.04	0.066	48.00	76.0%	47.64	76.6%	
0.300	12.04	0.092	48.00	81.8%	47.61	82.5%	
0.400	12.04	0.121	48.00	82.9%	47.58	83.7%	
0.500	12.04	0.148	48.00	84.7%	47.57	85.5%	
0.750	12.04	0.216	48.00	87.1%	47.52	88.0%	
1.000	12.04	0.282	48.00	88.9%	47.52	89.8%	
1.250	12.04	0.351	48.00	89.3%	47.46	90.3%	
1.500	12.04	0.422	48.00	89.2%	47.42	90.2%	
1.750	12.04	0.490	48.00	89.6%	47.44	90.6%	
2.000	12.04	0.559	48.00	89.7%	47.35	91.0%	
2.125	12.04	0.593	48.00	89.9%	47.39	91.0%	

		PoE	PoE	PoE	PoE	PoE	PoE
		Diode	Diode	Diode	Half FET	Half FET	Half FET
		Bridge	Bridge	Bridge	Bridge	Bridge	Bridge
J6	J6	J1	J1	J1	J1	J1	J1
I _{out}	V _{out}	I _{in}	V _{in}	Eff	I _{in}	V _{in}	Eff
0.000	12.05	0.005	48.00	0.0%	0.005	48.00	0.0%
0.050	12.05	0.023	48.00	54.6%	0.023	48.00	54.6%
0.100	12.05	0.037	48.00	67.8%	0.037	48.00	67.8%
0.200	12.04	0.066	48.00	76.0%	0.066	48.00	76.0%
0.300	12.04	0.092	48.00	81.8%	0.092	48.00	81.8%
0.400	12.04	0.121	48.00	82.9%	0.121	48.00	82.9%
0.500	12.04	0.149	48.00	84.2%	0.148	48.00	84.7%
0.750	12.04	0.217	48.00	86.7%	0.215	48.00	87.5%
1.000	12.04	0.285	48.00	88.0%	0.283	48.00	88.6%
1.250	12.04	0.356	48.00	88.1%	0.352	48.00	89.1%
1.500	12.04	0.429	48.00	87.7%	0.425	48.00	88.5%
1.750	12.04	0.499	48.00	88.0%	0.494	48.00	88.9%
2.000	12.04	0.570	48.00	88.0%	0.564	48.00	88.9%
2.125	12.04	0.606	48.00	88.0%	0.599	48.00	89.0%


VFO Mode

1. R38=100k ohms, R39=28.7k ohms, C35=0.1uF
2. Converter loses primary bias below 10mA output load and operates in hiccup mode.
3. A 25mA output load is required to provide the 10mA input current for PoE MPS.
4. With increasing load current the converter switches from VFO mode to PWM mode at approximately 0.8A.
5. With decreasing load current the converter switches from PWM mode to VFO mode at approximately 0.7A


		PoE	PoE	PoE	PoE	PoE	PoE	PoE	PoE	PoE
		Diode	Diode	Diode	Diode	Diode	Diode	Diode	Diode	Diode
		Bridge	Bridge	Bridge	Bridge	Bridge	Bridge	Bridge	Bridge	Bridge
J6	J6	J1	J1	J1	J1	J1	J1	J1	J1	J1
I _{out}	V _{out}	I _{in}	V _{in}	Eff	I _{in}	V _{in}	Eff	I _{in}	V _{in}	Eff
0.010	12.075	0.0062	42.50	45.8%	0.0056	48.00	44.9%	0.0048	57.00	44.1%
0.025	12.075	0.0109	42.50	65.2%	0.0098	48.00	64.2%	0.0084	57.00	63.0%
0.050	12.075	0.0191	42.50	74.4%	0.0171	48.00	73.6%	0.0146	57.00	72.5%
0.100	12.075	0.0353	42.50	80.5%	0.0314	48.00	80.1%	0.0268	57.00	79.0%
0.150	12.075	0.0513	42.50	83.1%	0.0456	48.00	82.8%	0.0388	57.00	81.9%
0.200	12.075	0.0679	42.50	83.7%	0.0604	48.00	83.3%	0.0513	57.00	82.6%
0.300	12.075	0.0995	42.50	85.7%	0.0884	48.00	85.4%	0.0751	57.00	84.6%
0.400	12.074	0.1318	42.50	86.2%	0.1167	48.00	86.2%	0.0993	57.00	85.3%
0.500	12.074	0.1637	42.50	86.8%	0.1455	48.00	86.4%	0.1239	57.00	85.5%
0.600	12.074	0.1969	42.50	86.6%	0.1734	48.00	87.0%	0.1479	57.00	85.9%
0.700	12.073	0.2277	42.50	87.3%	0.2019	48.00	87.2%	0.1731	57.00	85.7%

Ripple and Noise

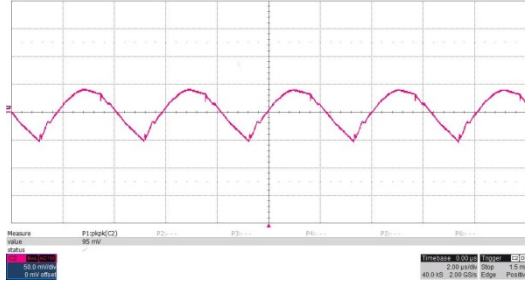Output Ripple (C24)
 50mV/div, 2usec/div
 Measured 95mVpk-pk:




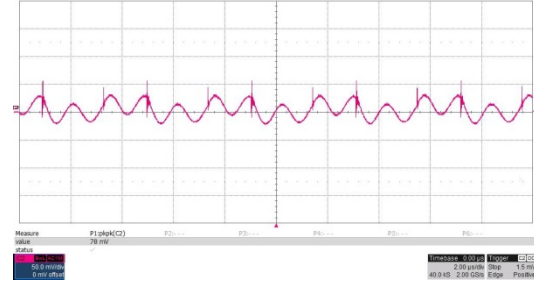Input Ripple (C10)
 50mV/div, 2usec/div
 Measured 78mVpk-pk:




Dynamic Loading

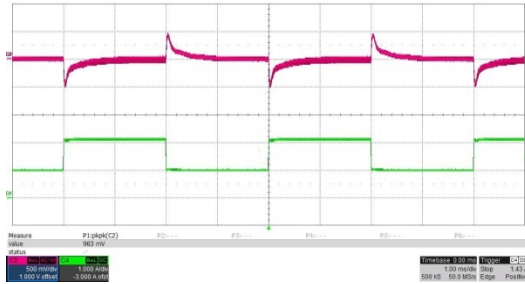Load Step, 1A to 2.125A, 200mA/usec slew rate, 500mV/div, 1A/div, 1msec/div
 Measured 983mVpp:




Turn On Response


2.125A Load, 2V/div, 1msec/div:

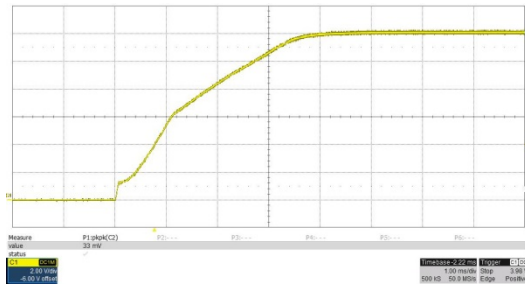

0A Load, 2V/div, 1msec/div:

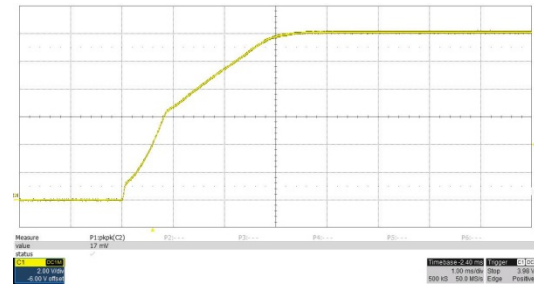

Stability

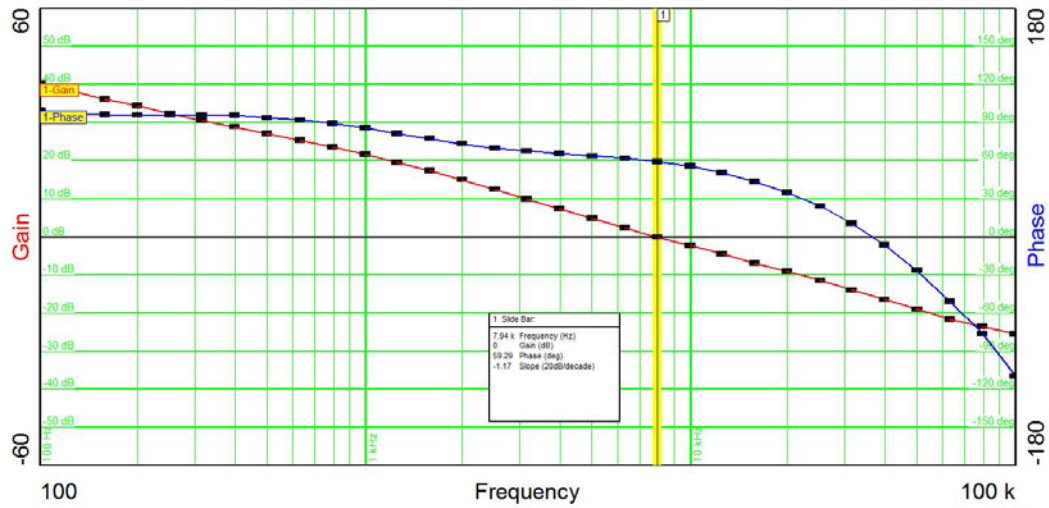


BW=7.9KHz

PM=59 degrees


GM=15dB.

Photo:

Top:

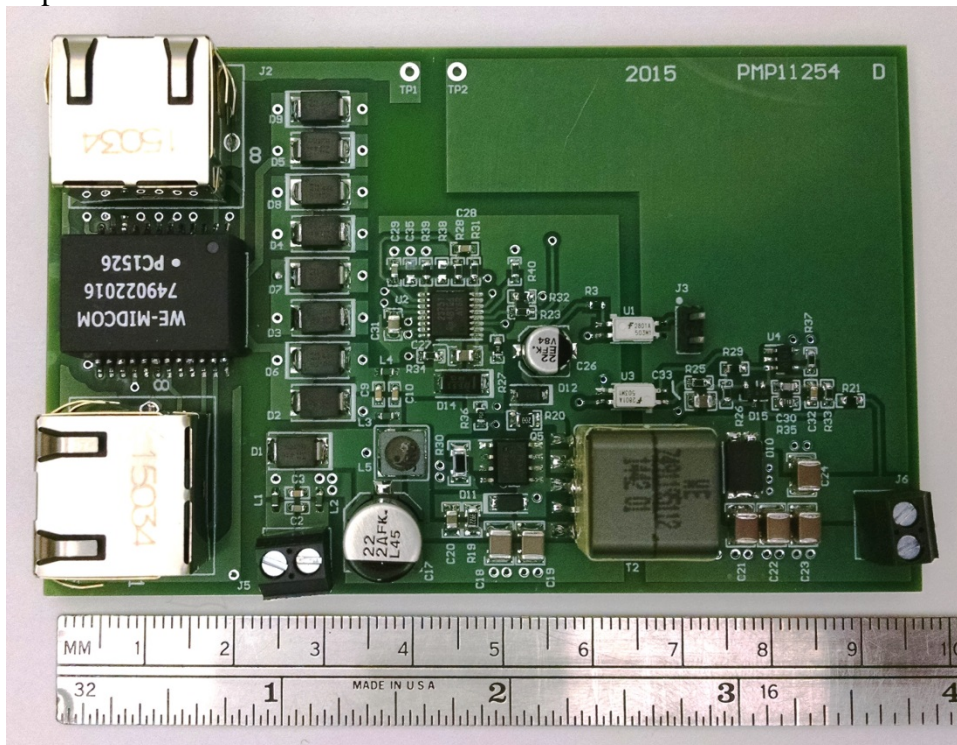


Bottom:

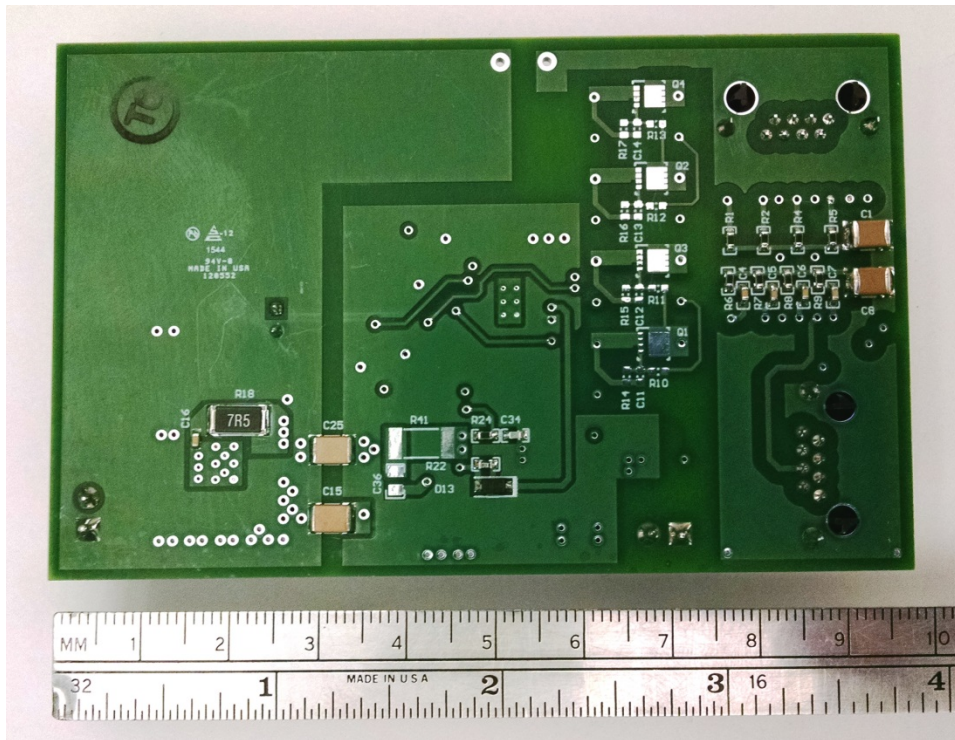


Thermal Plots:

Top:

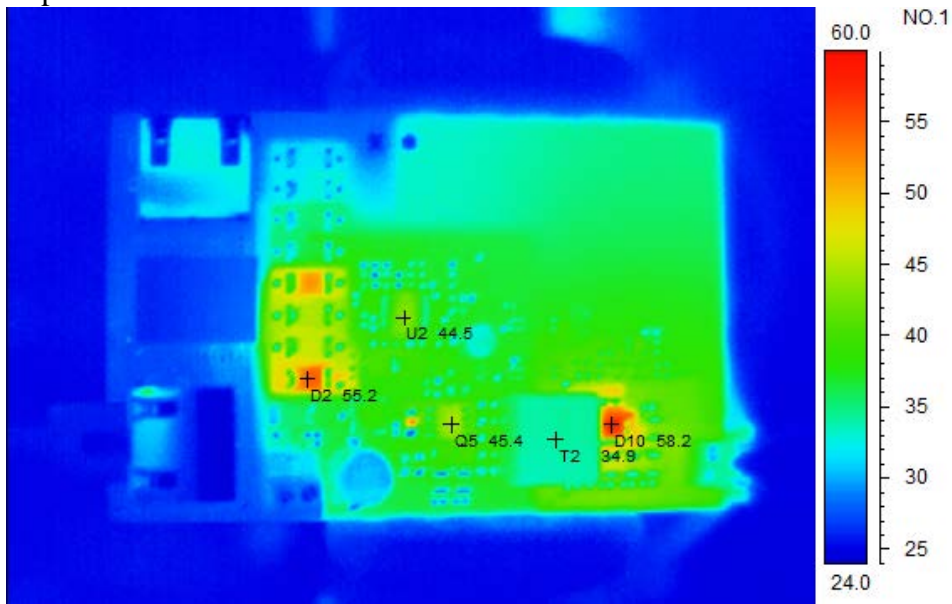

Bottom:

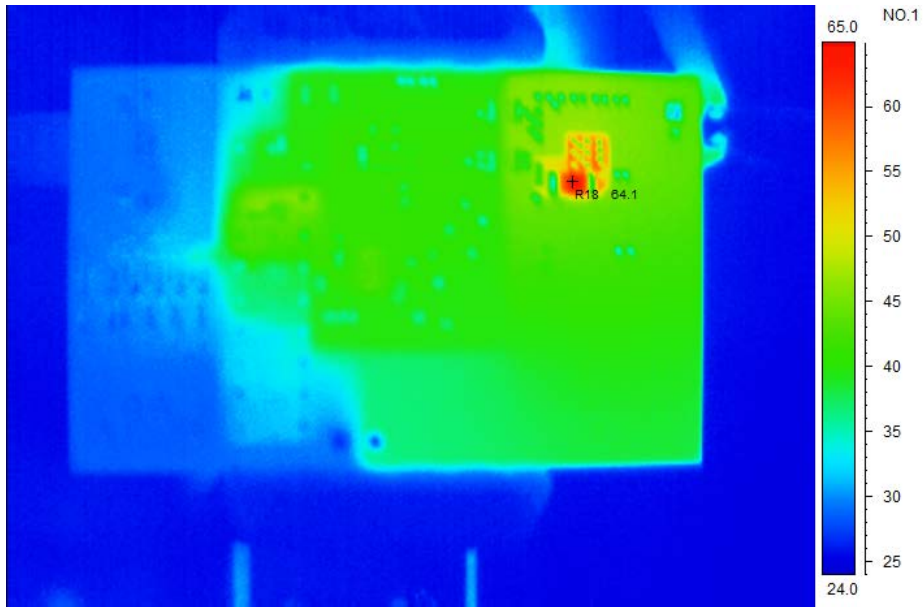

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Designer(s)") who are developing systems that incorporate TI products. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.

TI's provision of reference designs and any other technical, applications or design advice, quality characterization, reliability data or other information or services does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such reference designs or other items.

TI reserves the right to make corrections, enhancements, improvements and other changes to its reference designs and other items.

Designer understands and agrees that Designer remains responsible for using its independent analysis, evaluation and judgment in designing Designer's systems and products, and has full and exclusive responsibility to assure the safety of its products and compliance of its products (and of all TI products used in or for such Designer's products) with all applicable regulations, laws and other applicable requirements. Designer represents that, with respect to its applications, it has all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. Designer agrees that prior to using or distributing any systems that include TI products, Designer will thoroughly test such systems and the functionality of such TI products as used in such systems. Designer may not use any TI products in life-critical medical equipment unless authorized officers of the parties have executed a special contract specifically governing such use. Life-critical medical equipment is medical equipment where failure of such equipment would cause serious bodily injury or death (e.g., life support, pacemakers, defibrillators, heart pumps, neurostimulators, and implantables). Such equipment includes, without limitation, all medical devices identified by the U.S. Food and Drug Administration as Class III devices and equivalent classifications outside the U.S.

Designers are authorized to use, copy and modify any individual TI reference design only in connection with the development of end products that include the TI product(s) identified in that reference design. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of the reference design or other items described above may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS AND OTHER ITEMS DESCRIBED ABOVE ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY DESIGNERS AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS AS DESCRIBED IN A TI REFERENCE DESIGN OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

TI's standard terms of sale for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>) apply to the sale of packaged integrated circuit products. Additional terms may apply to the use or sale of other types of TI products and services.

Designer will fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of Designer's non-compliance with the terms and provisions of this Notice.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2016, Texas Instruments Incorporated