


#### 1 Photo

The photograph below shows the PMP4028 Rev B demo board. The circuit is built on a PMP3023 Rev A PWB.


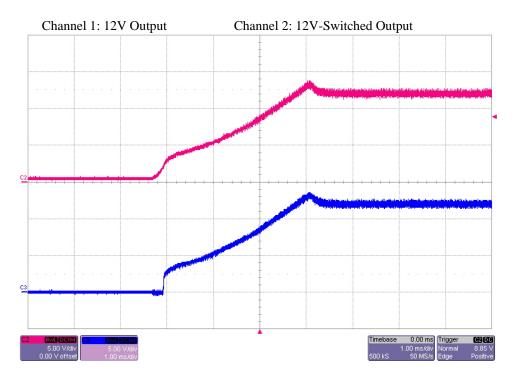
# 2 Startup


The output voltages at startup are shown in the image below. The input was 48VDC and both outputs were unloaded.




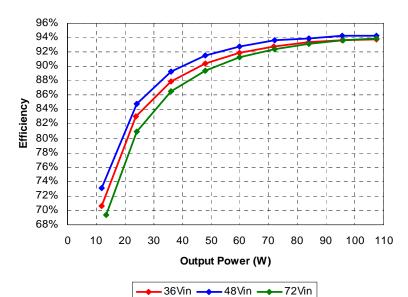
# 3 Efficiency

The efficiency data is shown in the tables and graph below.



12V		12V-Switched						
lout	Vout	lout	Vout	Vin	lin	Pout	Losses	Efficiency
0.000	12.04	0.000	12.04	36.00	0.143	0.00	5.148	0.0%
0.499	12.03	0.491	12.02	36.01	0.468	11.90	4.948	70.6%
1.000	12.03	0.995	12.00	36.01	0.801	23.97	4.874	83.1%
1.497	12.02	1.501	11.98	35.99	1.137	35.98	4.945	87.9%
2.000	12.02	1.996	11.97	35.99	1.473	47.93	5.081	90.4%
2.500	12.02	2.500	11.95	36.00	1.812	59.93	5.307	91.9%
2.996	12.02	3.005	11.94	36.00	2.152	71.89	5.580	92.8%
3.500	12.02	3.512	11.92	36.00	2.498	83.93	5.995	93.3%
3.998	12.01	4.004	11.91	36.01	2.839	95.70	6.529	93.6%
4.501	12.01	4.500	11.89	36.01	3.185	107.56	7.130	93.8%


12V		12V-Switched						
lout	Vout	lout	Vout	Vin	lin	Pout	Losses	Efficiency
0.000	12.04	0.000	12.04	48.00	0.096	0.00	4.608	0.0%
0.503	12.04	0.497	12.03	48.00	0.343	12.04	4.429	73.1%
1.001	12.04	0.999	12.01	48.00	0.591	24.05	4.318	84.8%
1.498	12.03	1.494	11.99	48.00	0.839	35.93	4.338	89.2%
1.999	12.03	2.002	11.98	48.00	1.094	48.03	4.480	91.5%
2.498	12.03	2.502	11.96	48.00	1.347	59.97	4.681	92.8%
3.003	12.03	3.000	11.95	48.00	1.602	71.98	4.920	93.6%
3.500	12.02	3.504	11.93	48.00	1.860	83.87	5.407	93.9%
4.000	12.02	3.998	11.91	48.00	2.115	95.70	5.824	94.3%
4.496	12.02	4.500	11.90	48.00	2.377	107.59	6.504	94.3%

12V		12V-Switched						
lout	Vout	lout	Vout	Vin	lin	Pout	Losses	Efficiency
0.000	12.31	0.000	12.32	72.0	0.088	0.00	6.336	0.0%
0.496	12.14	0.606	12.13	71.9	0.268	13.37	5.897	69.4%
0.994	12.06	0.999	12.03	72.0	0.412	24.01	5.658	80.9%
1.495	12.05	1.502	12.01	72.0	0.579	36.05	5.634	86.5%
2.000	12.04	1.999	11.99	72.0	0.746	48.05	5.664	89.5%
2.497	12.04	2.493	11.97	72.0	0.912	59.91	5.759	91.2%
2.997	12.04	2.998	11.96	72.0	1.081	71.94	5.892	92.4%
3.499	12.03	3.502	11.94	72.0	1.251	83.91	6.165	93.2%
3.994	12.03	4.003	11.92	72.0	1.420	95.76	6.476	93.7%
4.492	12.03	4.500	11.91	72.0	1.592	107.63	6.990	93.9%



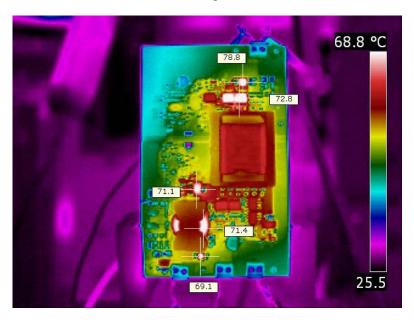
# 4 Thermal Image

The image below shows a thermal image of the board. The ambient temperature was 26°C with no forced air flow. The input was 48VDC, the 12V output was loaded with 4.5A, and the 12V switched output was loaded with 4.5A. The primary current sense resistor (R4) was the hottest component on the board and measured 78.8°C.


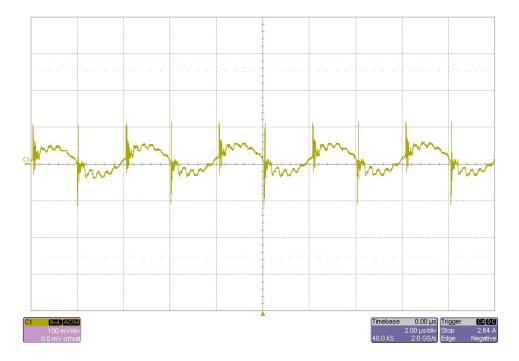
## 5 Output Ripple Voltage


The 12Voutput ripple voltage is shown in the plot below. The input was set to 48VDC and both outputs were loaded with 4.5A.





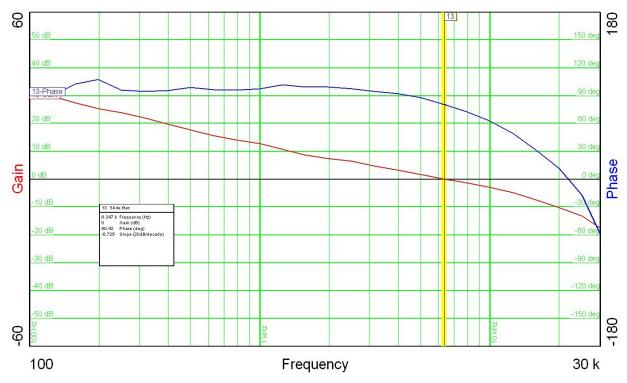
### 6 Frequency Response

The frequency response of the feedback loop is shown below. The input was set to 48VDC and both outputs were loaded with 4.5A.


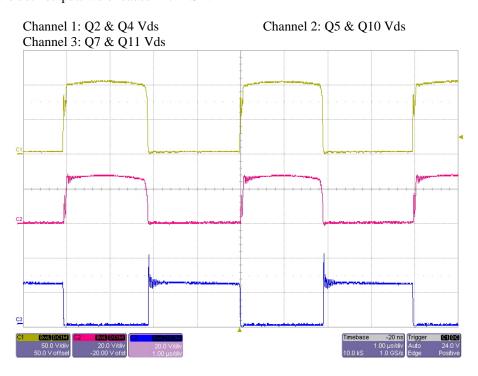
#### 7 Switching Waveforms

The image below shows the drain-to-source voltage waveforms on the switching MOSFETs. The input was set to 48VDC, and the both outputs were loaded with 4.5A.



#### IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

**Applications** 

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

**Products** 

**OMAP Mobile Processors** 

Wireless Connectivity

www.ti.com/omap

www.ti.com/wirelessconnectivity

Audio	www.ti.com/audio	Automotive and Transportation	www.ti.com/automotive
Amplifiers	amplifier.ti.com	Communications and Telecom	www.ti.com/communications
Data Converters	dataconverter.ti.com	Computers and Peripherals	www.ti.com/computers
DLP® Products	www.dlp.com	Consumer Electronics	www.ti.com/consumer-apps
DSP	dsp.ti.com	Energy and Lighting	www.ti.com/energy
Clocks and Timers	www.ti.com/clocks	Industrial	www.ti.com/industrial
Interface	interface.ti.com	Medical	www.ti.com/medical
Logic	logic.ti.com	Security	www.ti.com/security
Power Mgmt	power.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video
RFID	www.ti-rfid.com		

TI E2E Community Home Page

e2e.ti.com