
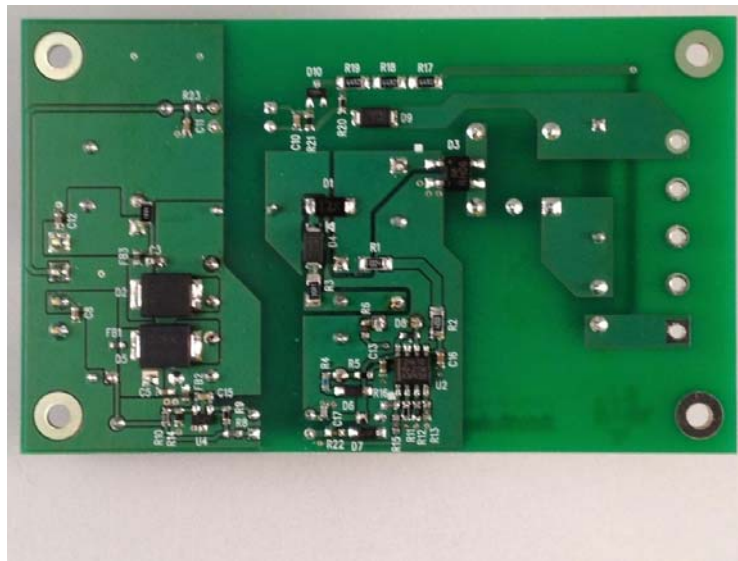

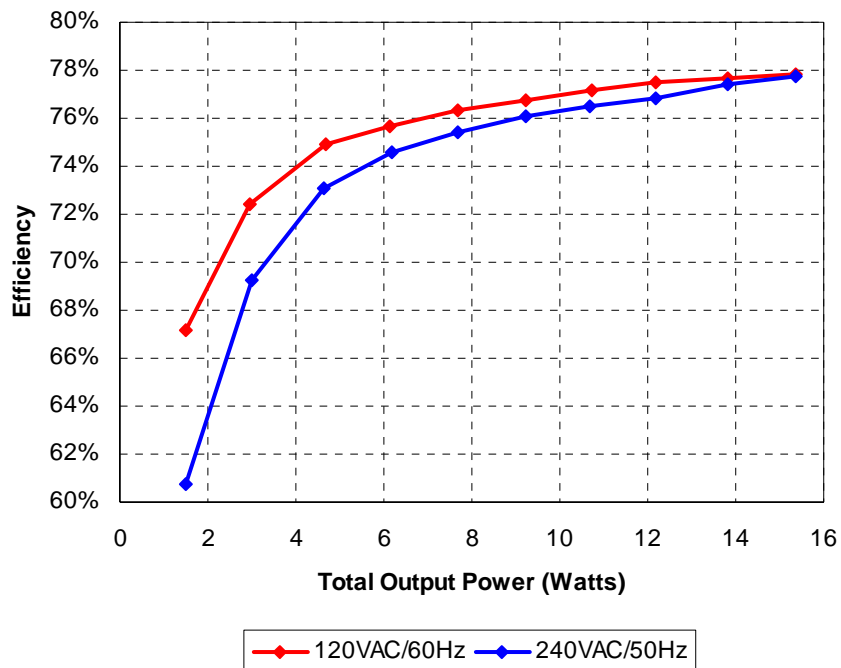
## 1 Photo

The photographs below show the PMP8362 assembly. This circuit was built on a PMP8259 Rev A PCB.



## 2 Efficiency



### 120VAC/60Hz

7.5V		12V		Vin	Iin (A)	Pin	PF	Pout	Losses	Efficiency
Iout	Vout	Iout	Vout							
0.000	7.52	0.000	11.85	120.0	0.01	0.32	0.29	0.00	0.32	0.0%
0.129	7.52	0.042	13.03	120.0	0.05	2.26	0.39	1.52	0.74	67.1%
0.257	7.52	0.079	13.13	120.0	0.08	4.10	0.43	2.97	1.13	72.4%
0.392	7.53	0.130	13.15	120.0	0.11	6.22	0.46	4.66	1.56	74.9%
0.518	7.53	0.171	13.16	120.0	0.14	8.13	0.49	6.15	1.98	75.7%
0.652	7.53	0.211	13.18	120.0	0.17	10.07	0.51	7.69	2.38	76.4%
0.781	7.53	0.252	13.19	120.0	0.19	11.99	0.52	9.20	2.79	76.8%
0.913	7.53	0.291	13.20	120.0	0.22	13.89	0.54	10.72	3.17	77.1%
1.040	7.54	0.330	13.20	120.0	0.24	15.74	0.55	12.20	3.54	77.5%
1.170	7.54	0.379	13.19	120.0	0.27	17.79	0.56	13.82	3.97	77.7%
1.302	7.54	0.421	13.19	120.0	0.29	19.74	0.57	15.37	4.37	77.9%


### 240VAC/50Hz


7.5V		12V		Vin	Iin (A)	Pin	PF	Pout	Losses	Efficiency
Iout	Vout	Iout	Vout							
0.000	7.53	0.000	11.92	240.0	0.01	0.62	0.24	0.00	0.62	0.0%
0.129	7.53	0.042	13.04	240.0	0.03	2.50	0.31	1.52	0.98	60.8%
0.261	7.53	0.079	13.15	240.0	0.05	4.34	0.33	3.00	1.34	69.2%
0.391	7.53	0.130	13.16	240.0	0.07	6.37	0.36	4.66	1.71	73.1%
0.520	7.53	0.172	13.18	240.0	0.09	8.29	0.37	6.18	2.11	74.6%
0.652	7.53	0.211	13.19	240.0	0.11	10.20	0.39	7.69	2.51	75.4%
0.782	7.53	0.252	13.19	240.0	0.13	12.11	0.40	9.21	2.90	76.1%
0.910	7.53	0.291	13.20	240.0	0.14	13.98	0.41	10.69	3.29	76.5%
1.040	7.53	0.330	13.20	239.9	0.16	15.86	0.42	12.19	3.67	76.8%
1.171	7.54	0.379	13.20	240.0	0.17	17.87	0.44	13.83	4.04	77.4%
1.302	7.54	0.421	13.20	240.0	0.19	19.78	0.44	15.37	4.41	77.7%

### 3 Thermal Images

The ambient temperature was 25°C with no forced air flow. The outputs were loaded with 7.5V/1.3A and 12V/0.42A.

#### 3.1 120VAC/60Hz Input

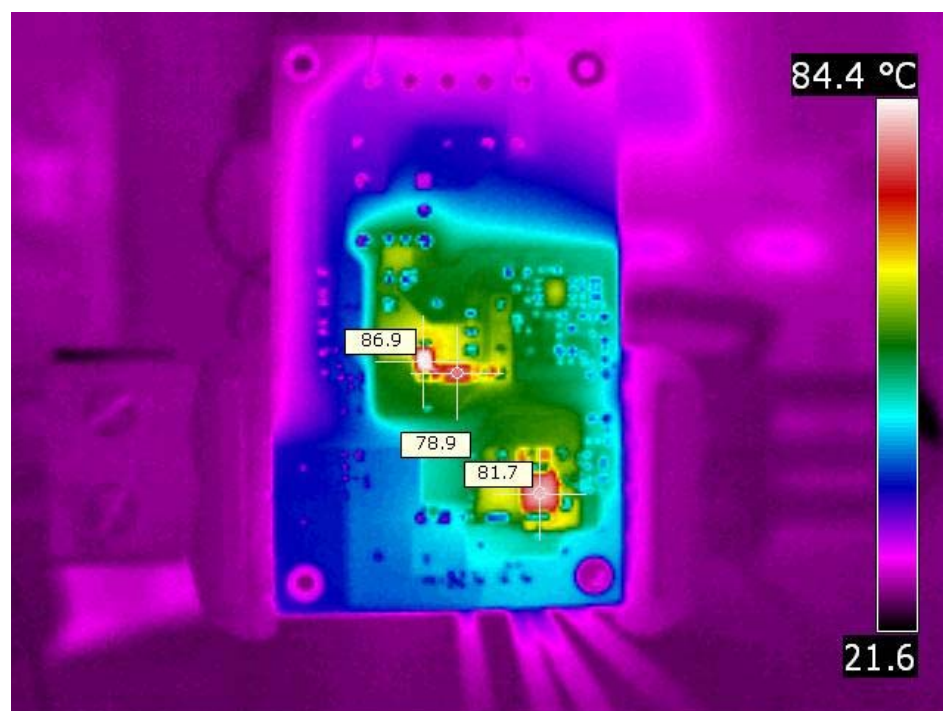


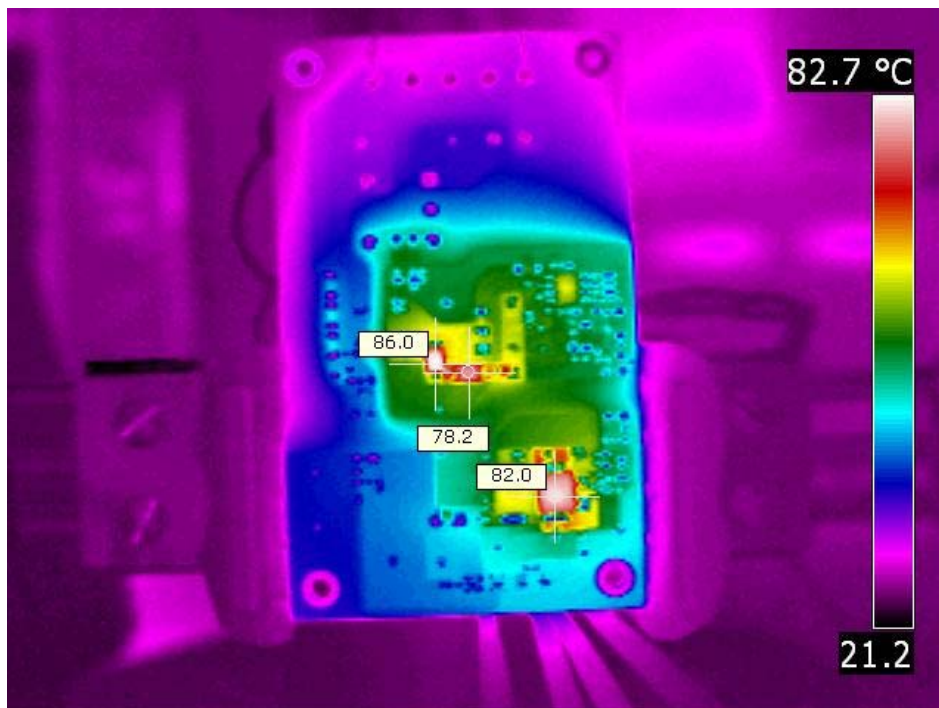**3.2 240VAC/50Hz Input**


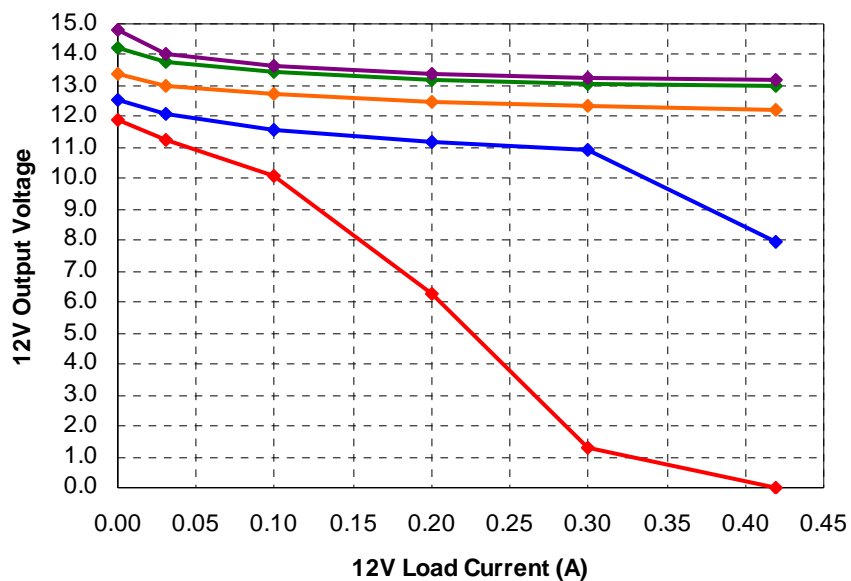
## 4 Cross-Regulation


The chart below shows the 12V output voltage versus 12V load current for different loading conditions on the 7.5V output. The input was 120VAC/60Hz.





## 5 Startup


The output voltages at startup are shown in the images below. The input was 120VAC/60Hz.

### 5.1 120VAC/60Hz Input; No Load

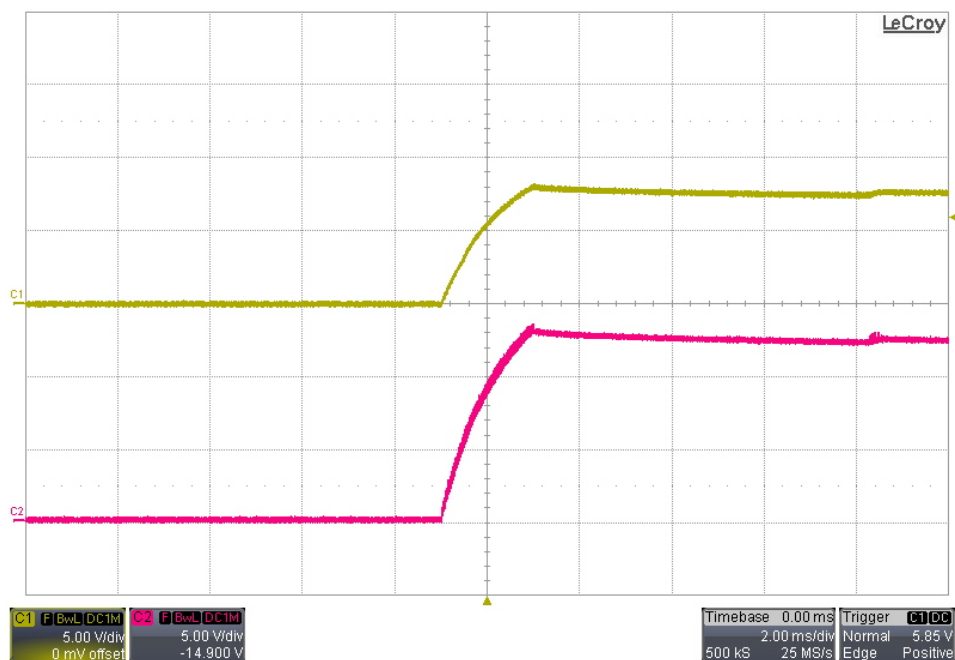

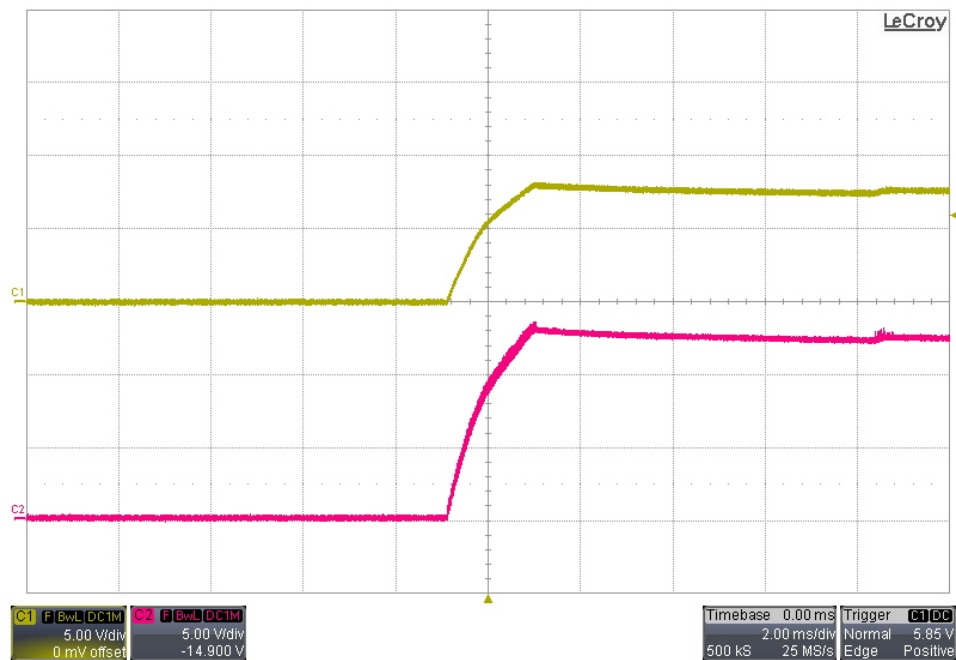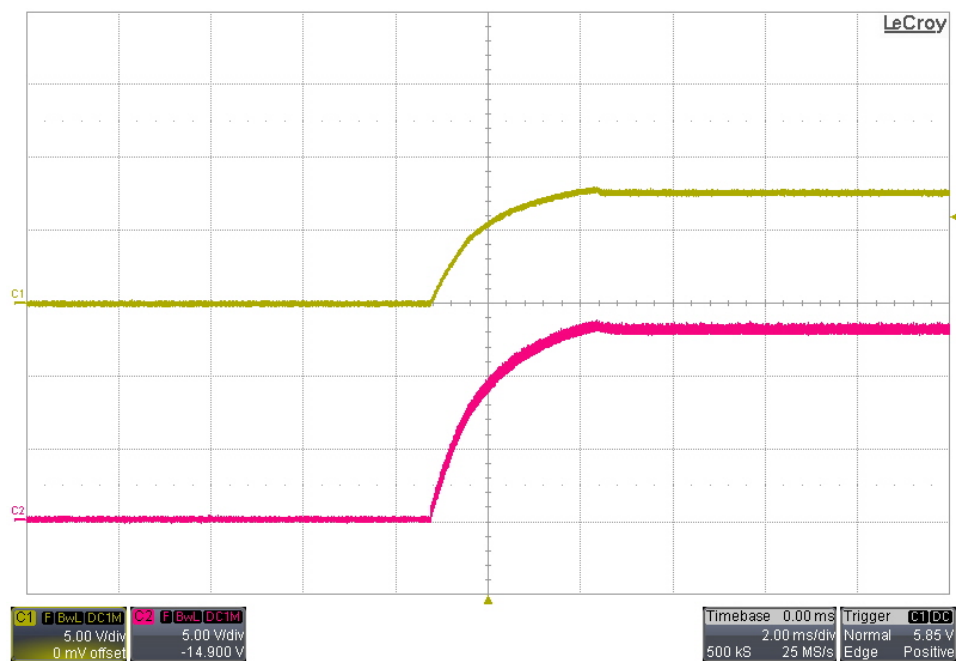**5.2 240VAC/50Hz Input; No Load****5.3 120VAC/60Hz Input; 7.5V/6 $\Omega$ , 12V/28 $\Omega$** 

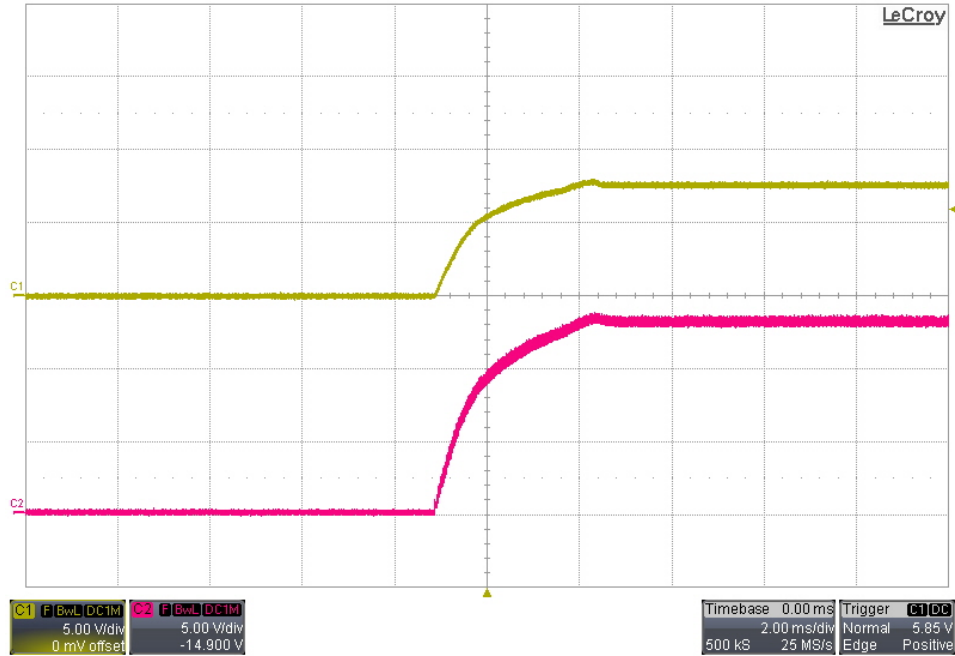
#### 5.4 240VAC/50Hz Input; 7.5V/6 $\Omega$ , 12V/28 $\Omega$




## 6 7.5V Output Ripple Voltage

The output ripple voltage on the 7.5V output is shown in the plots below. The outputs were loaded with 7.5V/1.3A and 12V/0.42A.

### 6.1 120VAC/60Hz Input

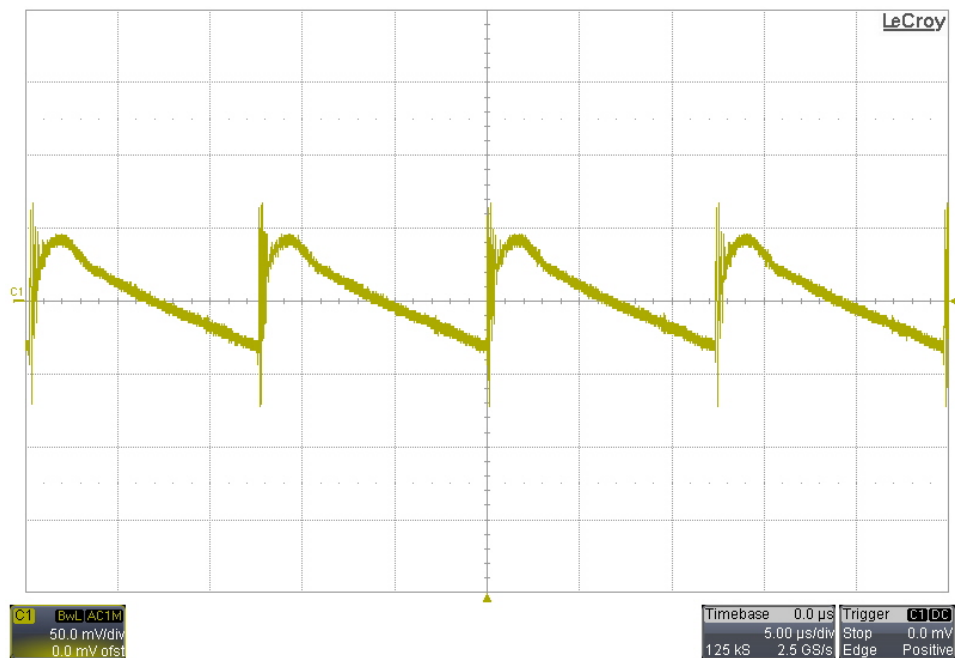


## 6.2 240VAC/50Hz Input

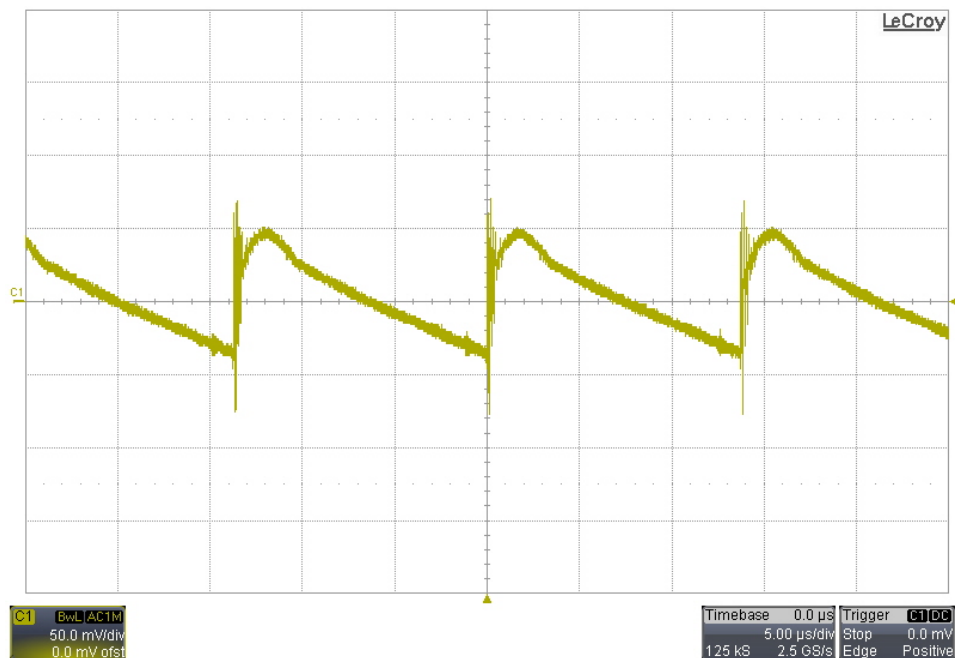

## 7 12V Output Ripple Voltage


The output ripple voltage on the 12V output is shown in the plots below. The outputs were loaded with 7.5V/1.3A and 12V/0.42A.

### 7.1 120VAC/60Hz Input

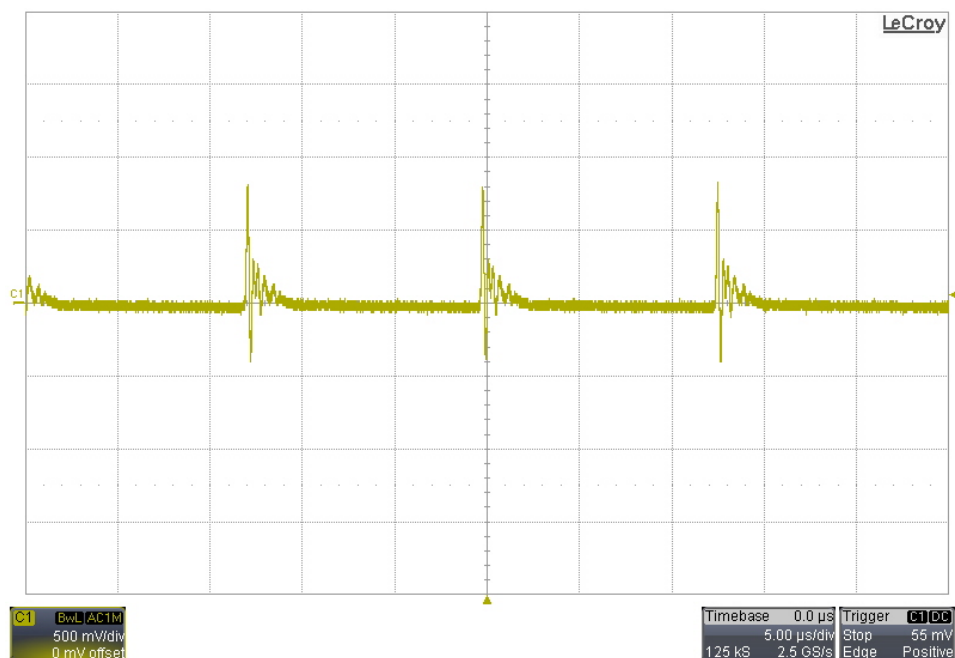




## 7.2 240VAC/50Hz Input

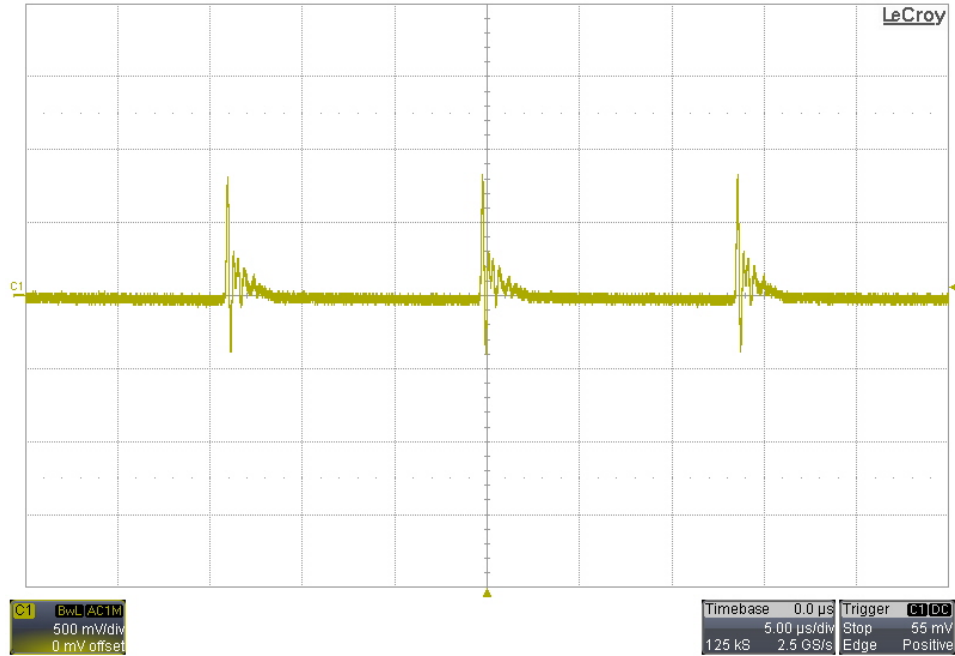
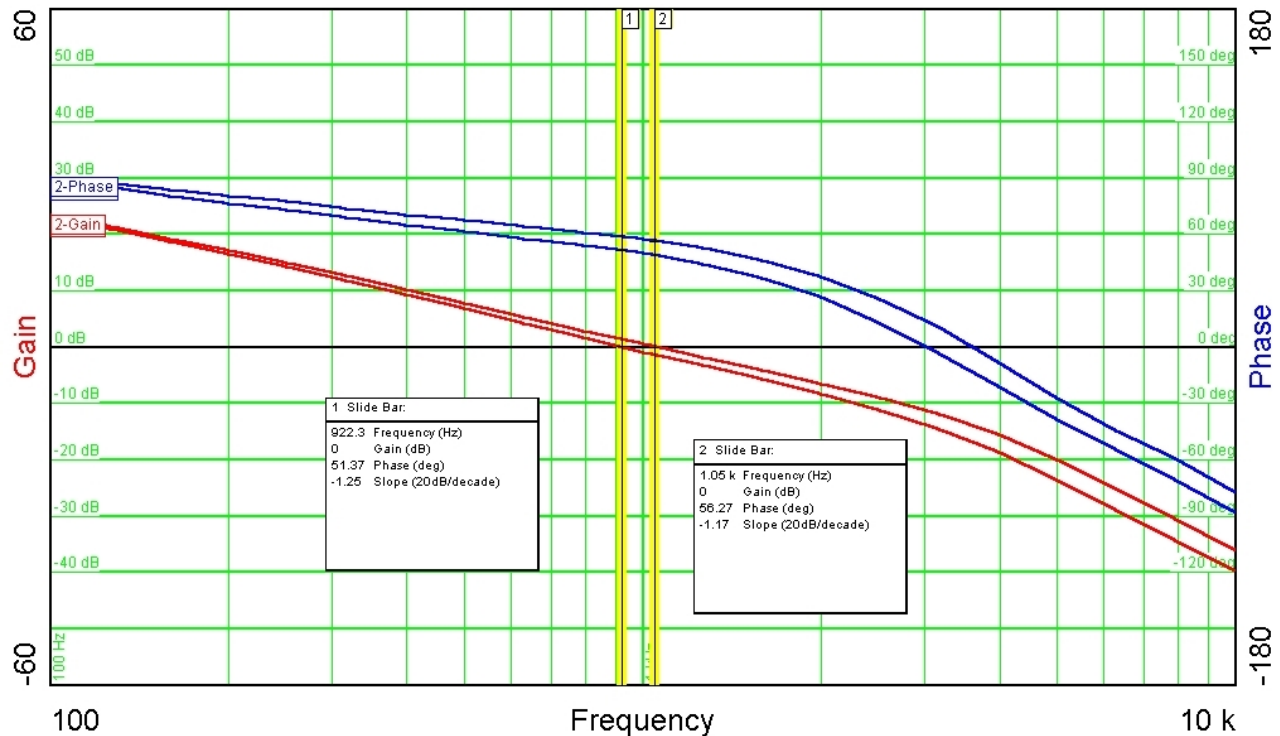
## 8 Loop Response


The frequency response of the feedback loop is shown in the image below. The outputs were loaded with 7.5V/1.3A and 12V/0.42A. For gain/phase plot #1, the input was 120VAC/60Hz. For gain/phase plot #2, the input was 240VAC/50Hz.




## 9 7.5V Load Transients

The images below show the response to a 0.5A to 1A load transient on the 7.5V output. The 12V output was loaded with 50Ω. Channel 1 shows the 7.5V output voltage (ac coupled). Channel 2 shows the 12V output voltage (ac coupled). Channel 4 shows the 7.5V load current.

### 9.1 120VAC/60Hz Input

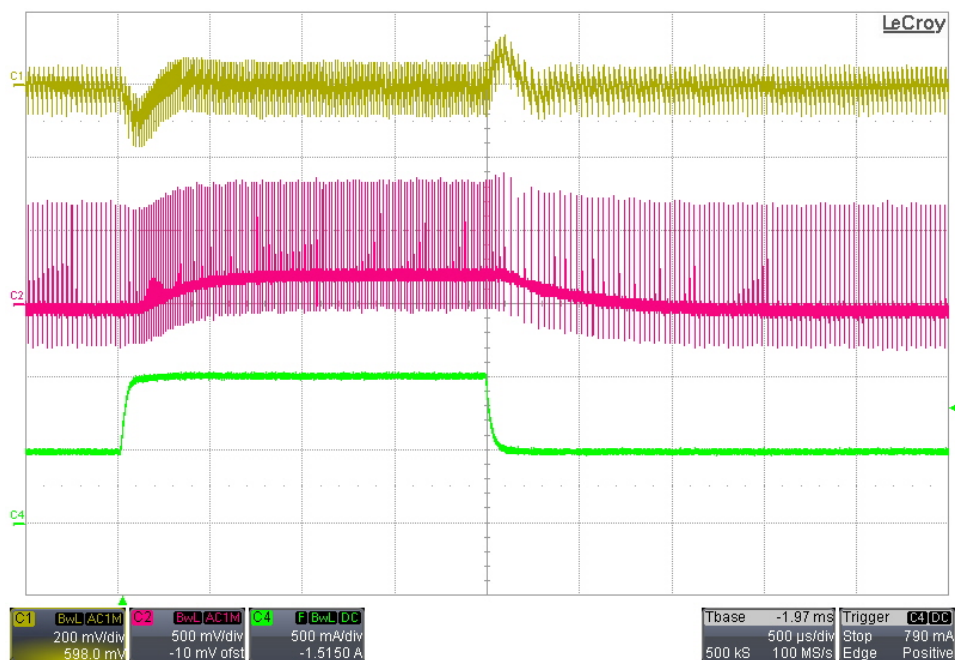


### 9.2 240VAC/50Hz Input

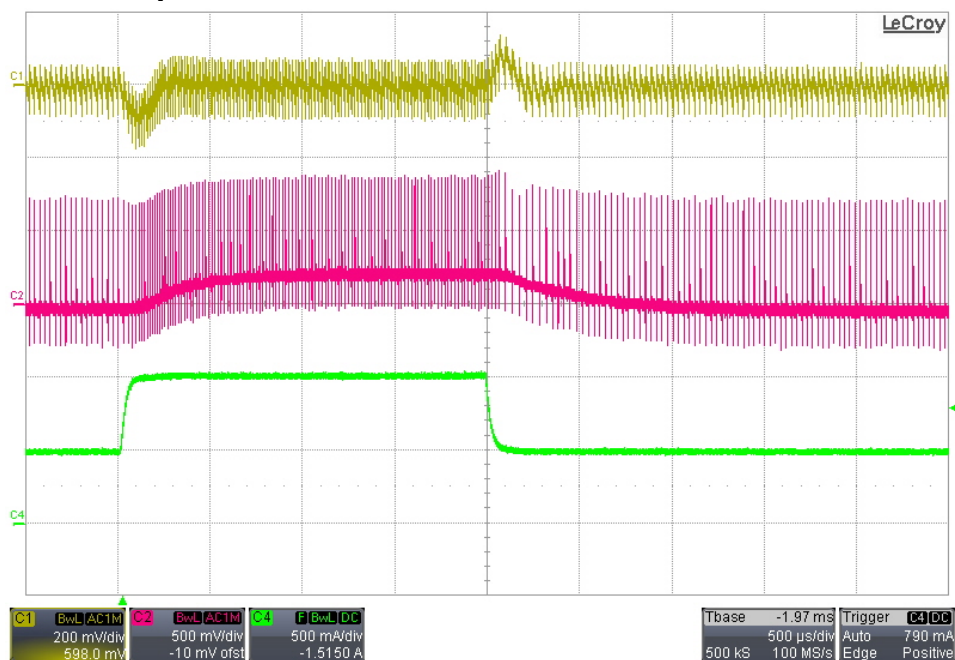


## 10 12V Load Transients

The images below show the response to a 0A to 0.42A load transient on the 12V output. The 7.5V output was loaded with 10 $\Omega$ . Channel 1 shows the 7.5V output voltage (ac coupled). Channel 2 shows the 12V output voltage (ac coupled). Channel 4 shows the 12V load current.

### 10.1 120VAC/60Hz Input

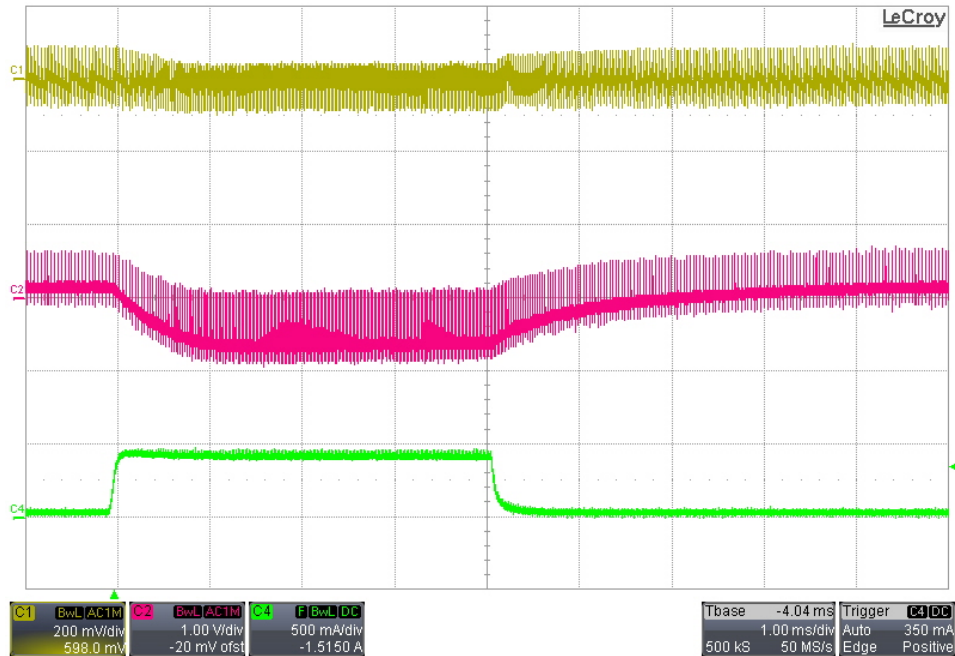


### 10.2 240VAC/50Hz Input

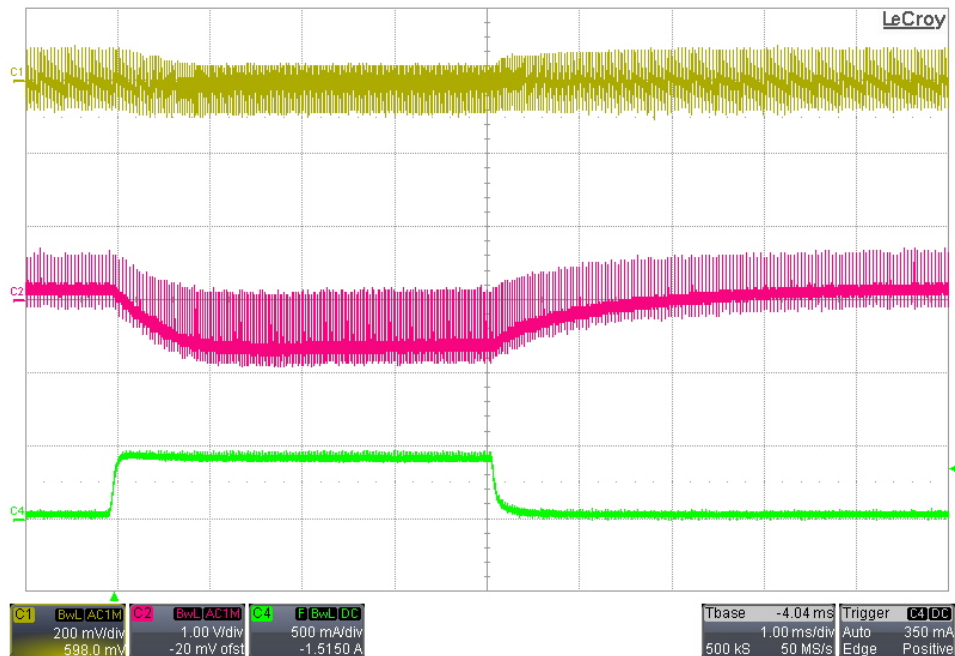

## 11 Switching Waveforms

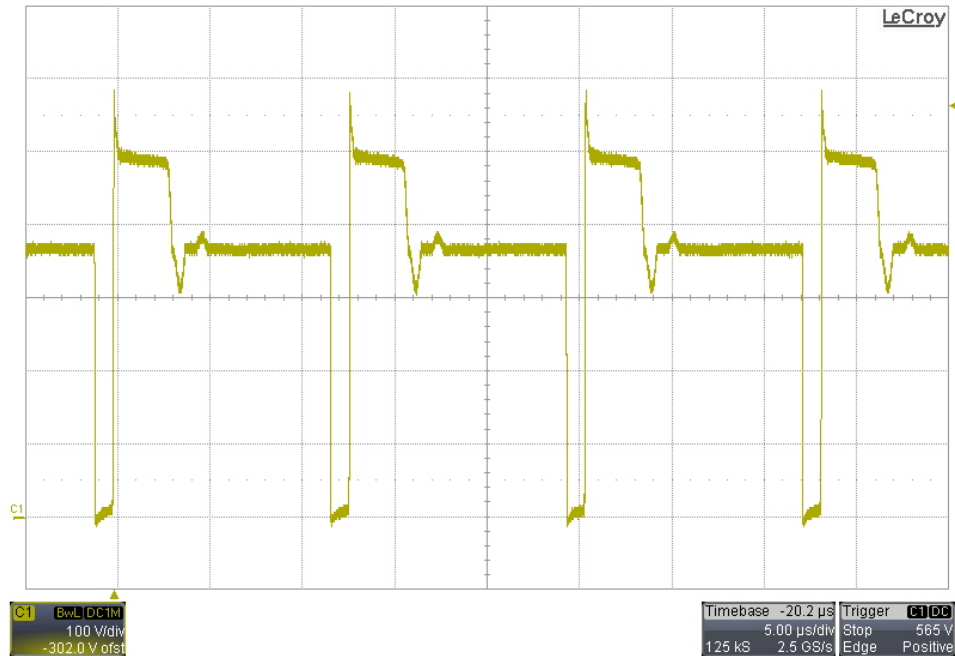
### 11.1 Primary FET

The image below shows the drain-to-source voltage on the primary MOSFET (Q1). The outputs were loaded with 7.5V/1.3A and 12V/0.42A. The input was set to 264VAC/50Hz.



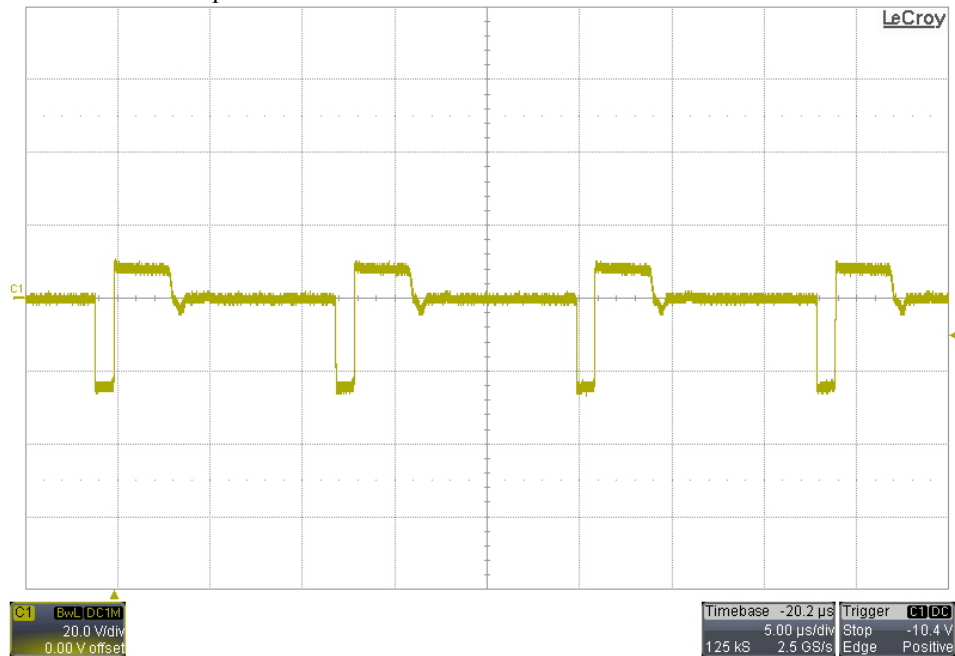
### 11.2 7.5V Diode

The image below shows the voltage on the anode of the 7.5V output diode (D5). The outputs were loaded with 7.5V/1.3A and 12V/0.42A. The input was set to 264VAC/50Hz.


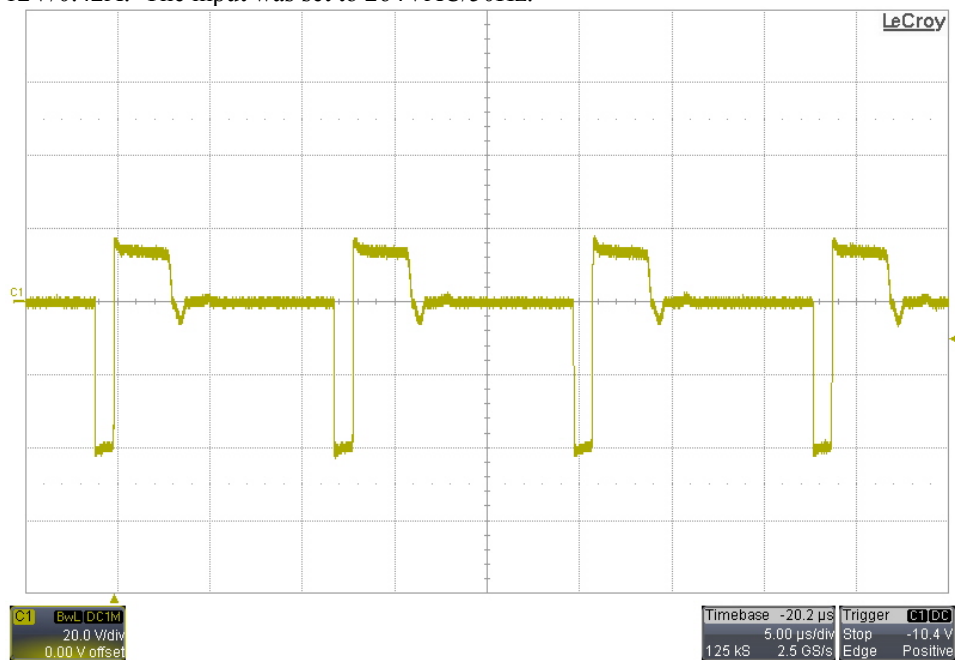
### 11.3 12V Diode

The image below shows the voltage on the anode of the 12V output diode (D2). The outputs were loaded with 7.5V/1.3A and 12V/0.42A. The input was set to 264VAC/50Hz.





## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46C and to discontinue any product or service per JESD48B. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components which meet ISO/TS16949 requirements, mainly for automotive use. Components which have not been so designated are neither designed nor intended for automotive use; and TI will not be responsible for any failure of such components to meet such requirements.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)