
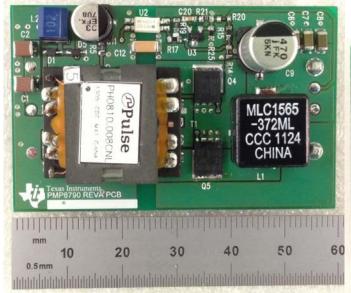



1 Photo

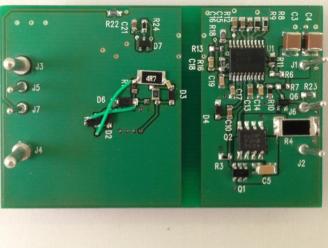The photographs below show the top and bottom views of the PMP8790 Rev B demo board. The circuit is built on a PMP8790 Rev A PWB.





2 Efficiency

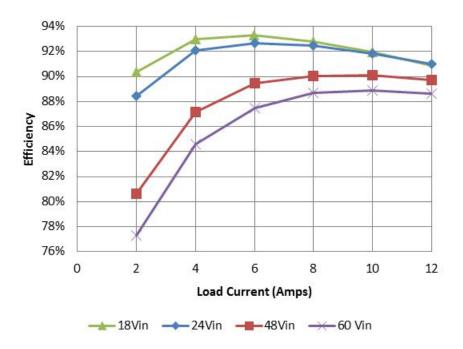



				T		
lout	Vout	Vin	lin	Pout	Losses	Efficiency
0.000	3.316	18.0	0.033	0.00	0.594	0.0%
2.001	3.315	18.0	0.408	6.63	0.711	90.3%
4.000	3.314	18.0	0.792	13.26	1.000	93.0%
5.996	3.313	18.0	1.183	19.86	1.429	93.3%
8.00	3.312	18.0	1.587	26.50	2.070	92.8%
10.00	3.311	18.0	2.001	33.11	2.908	91.9%
12.01	3.310	18.0	2.430	39.75	3.987	90.9%

lout	Vout	Vin	lin	Pout	Losses	Efficiency
0.000	3.315	24.0	0.029	0.00	0.696	0.0%
2.004	3.314	24.0	0.313	6.64	0.871	88.4%
4.007	3.314	24.0	0.601	13.28	1.145	92.1%
6.000	3.313	24.0	0.894	19.88	1.578	92.6%
8.00	3.312	24.0	1.194	26.50	2.160	92.5%
10.00	3.311	24.0	1.502	33.11	2.938	91.8%
12.00	3.310	24.0	1.819	39.72	3.936	91.0%

lout	Vout	Vin	lin	Pout	Losses	Efficiency
0.000	3.316	48.0	0.024	0.00	1.152	0.0%
1.997	3.315	48.0	0.171	6.62	1.588	80.7%
4.001	3.314	48.0	0.317	13.26	1.957	87.1%
6.002	3.313	48.0	0.463	19.88	2.339	89.5%
8.00	3.312	48.0	0.613	26.50	2.928	90.0%
10.00	3.312	48.0	0.766	33.12	3.648	90.1%
12.00	3.311	48.0	0.923	39.73	4.572	89.7%


lout	Vout	Vin	lin	Pout	Losses	Efficiency
0.000	3.317	60.0	0.023	0.00	1.380	0.0%
2.001	3.315	60.0	0.143	6.63	1.947	77.3%
3.998	3.314	60.0	0.261	13.25	2.411	84.6%
6.002	3.314	60.0	0.379	19.89	2.849	87.5%
8.00	3.313	60.0	0.498	26.50	3.376	88.7%
10.00	3.312	60.0	0.621	33.12	4.140	88.9%
12.00	3.311	60.0	0.747	39.73	5.088	88.6%




3 Thermal Images

The ambient temperature was 25C with no forced air flow. The output was loaded with 12A.

3.1 24V Input

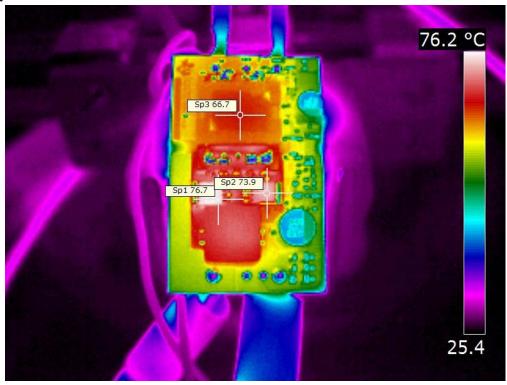


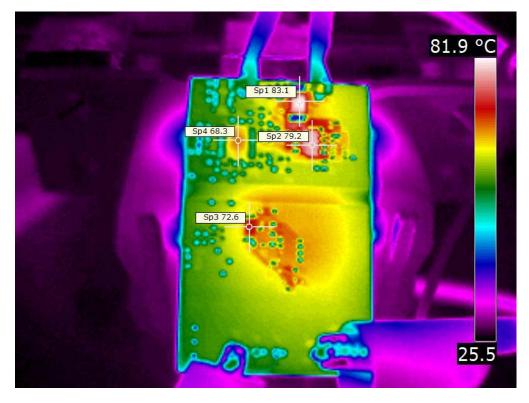




3.2 48V Input



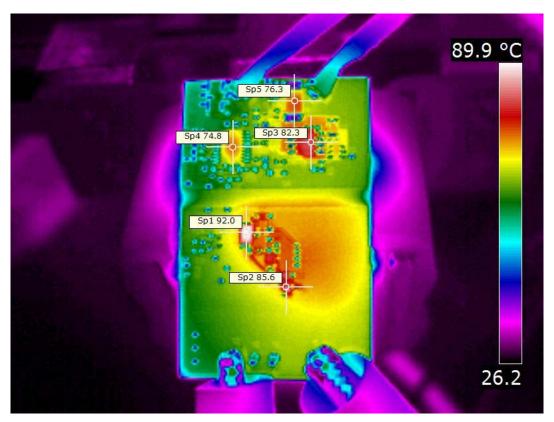




4 Startup – 18V Input, No Load

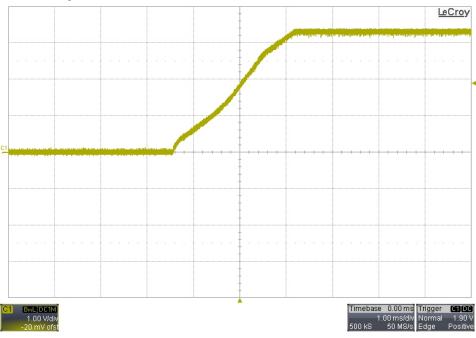


5 Startup – 60V Input, No Load

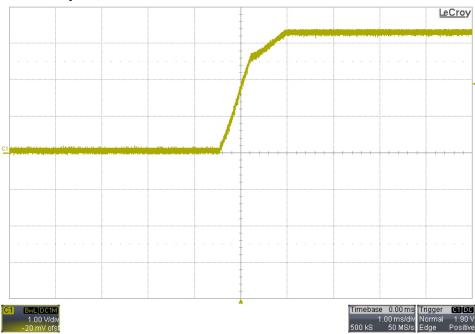




6 Startup – 18V Input, 0.3Ω Load

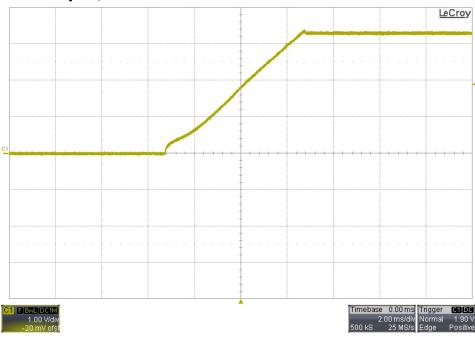

7 Startup – 60V Input, 0.3Ω Load

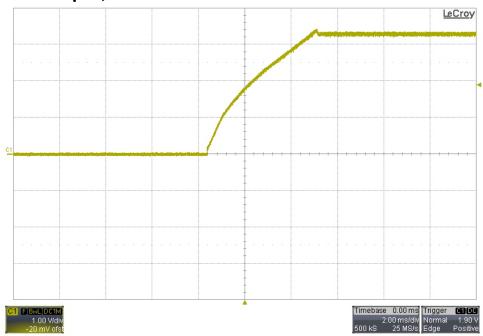





8 Output Ripple Voltage

The output ripple voltage is shown in the plots below. The output was loaded with 12A.

8.1 18V Input

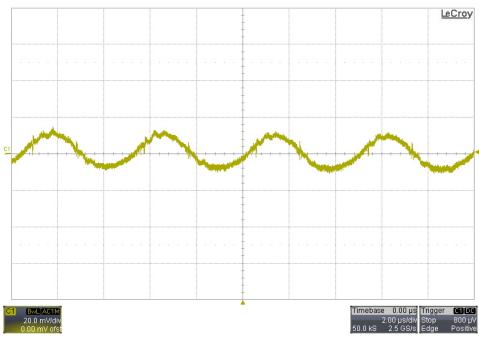

8.2 60V Input

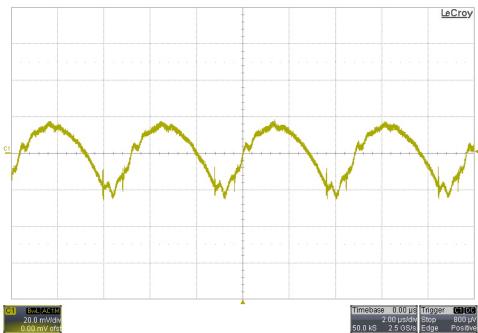





9 Frequency Response

The frequency response of the feedback loop is shown below. For the gain/phase plot #1, the input was set to 18V. For the gain/phase plot #2, the input was set to 60V. The output was loaded with 12A.

9.1 Measured Across R14

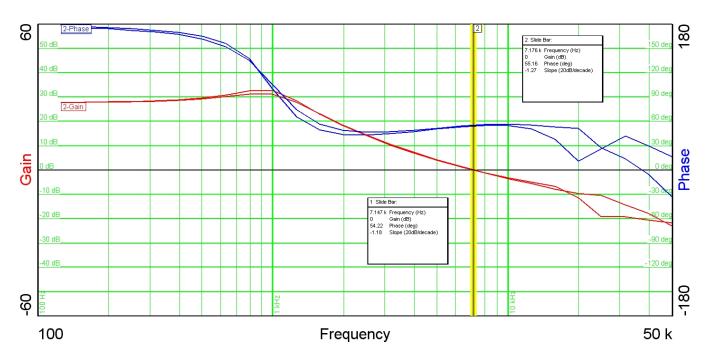

9.2 Measured Across R15

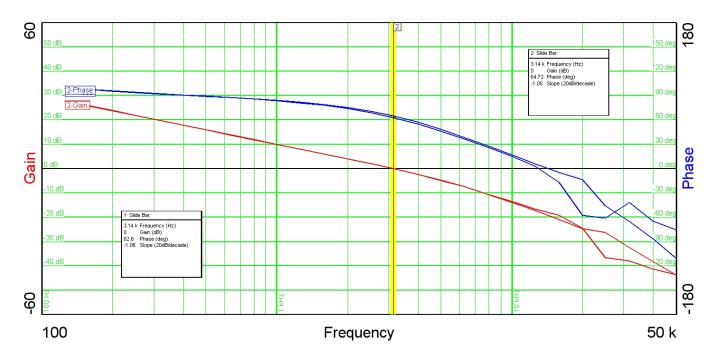





10 Load Transients

The response to a load step from 6A to 12A is shown in the images below. Channel 1: Vout (ac coupled); Channel 4: Iout

10.1 18V Input

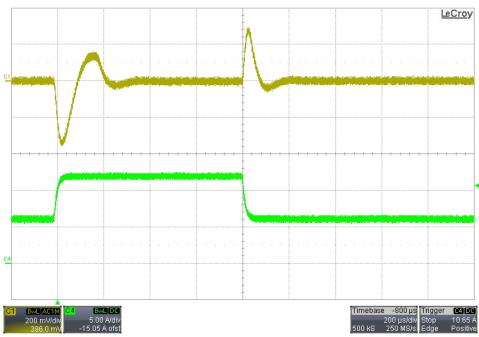

10.2 60V Input

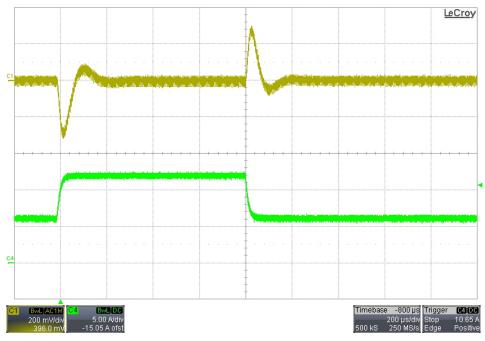

11 Input Under-Voltage Lock-Out

The turn-on and turn-off input voltages were measured and recorded below.


Turn-On	17.3 V
Turn-Off	17.0 V



12 Switching Waveforms


For the images below show the output was loaded with 12A.

12.1 Primary FET (Q2) Vds - 60V Input

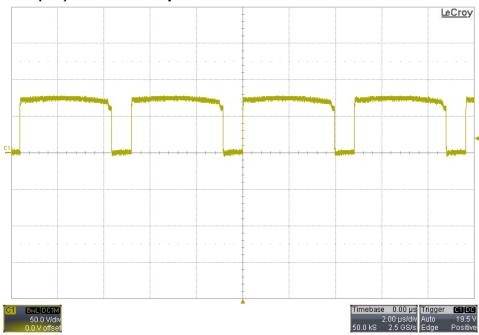

12.2 Q4 & Q5 Synchronous FETs - 18V Input

Channel 1 – Q5 Vds; Channel 2 – Q4 Vds

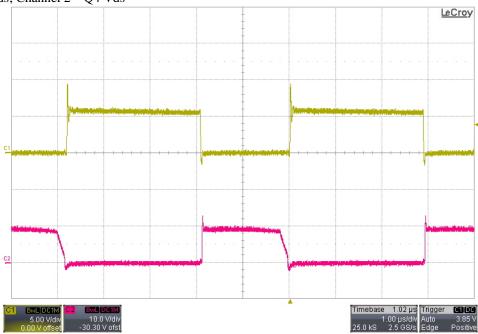


PMP8790 Rev B Test Results



12.3 Q4 & Q5 Synchronous FETs - 60V Input

Channel 1 – Q5 Vds; Channel 2 – Q4 Vds

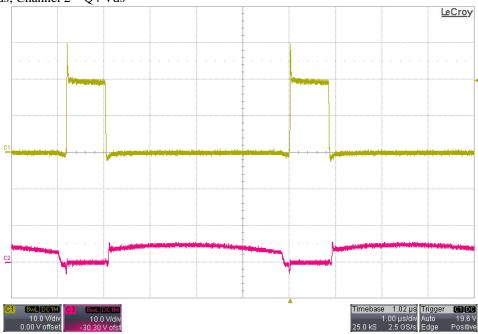

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products Applications

Audio www.ti.com/audio Automotive and Transportation www.ti.com/automotive Communications and Telecom **Amplifiers** amplifier.ti.com www.ti.com/communications **Data Converters** dataconverter.ti.com Computers and Peripherals www.ti.com/computers **DLP® Products** www.dlp.com Consumer Electronics www.ti.com/consumer-apps

DSP **Energy and Lighting** dsp.ti.com www.ti.com/energy Clocks and Timers www.ti.com/clocks Industrial www.ti.com/industrial Interface interface.ti.com Medical www.ti.com/medical logic.ti.com Logic Security www.ti.com/security

Power Mgmt power.ti.com Space, Avionics and Defense www.ti.com/space-avionics-defense

Microcontrollers <u>microcontroller.ti.com</u> Video and Imaging <u>www.ti.com/video</u>

RFID www.ti-rfid.com

OMAP Applications Processors www.ti.com/omap TI E2E Community e2e.ti.com

Wireless Connectivity <u>www.ti.com/wirelessconnectivity</u>