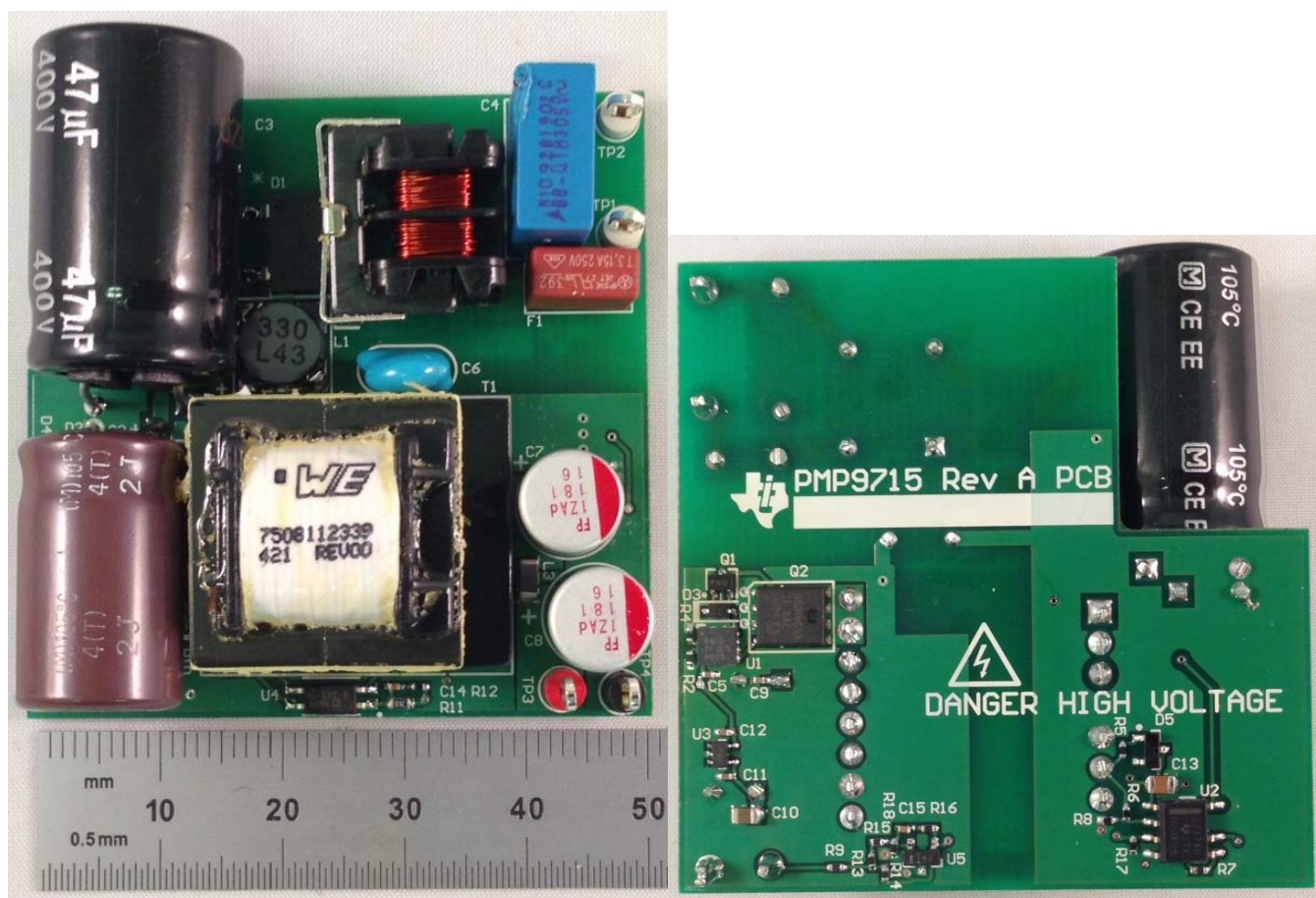


1 Photos


The photograph below shows the PMP9715 Rev A prototype assembly.



2 Standby Power

With no load attached to the output of the supply, the unit draws 89mW of input power with an 115VAC/60Hz input, and 103mW with a 230VAC/50Hz input.

3 Efficiency

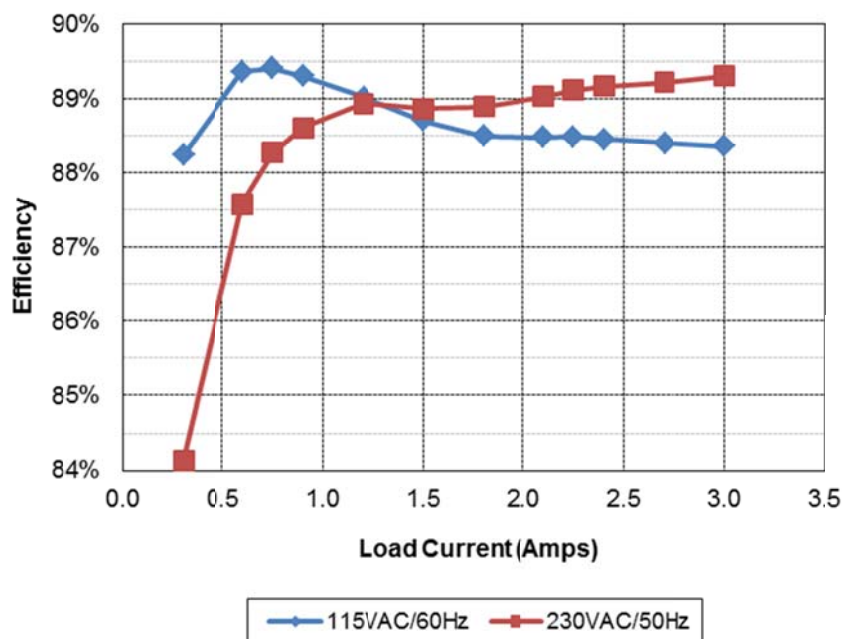


115VAC/60Hz								
I _{out}	V _{out}	V _{in}	I _{in}	P _{in}	PF	P _{out}	Losses	Efficiency
0.000	12.10	115.0	0.0058	0.089		0.00	0.09	
0.299	12.10	114.9	0.104	4.10	0.34	3.62	0.48	88.2%
0.599	12.10	114.9	0.188	8.11	0.38	7.25	0.86	89.4%
0.750	12.10	114.9	0.226	10.15	0.39	9.08	1.08	89.4%
0.899	12.10	114.9	0.262	12.18	0.40	10.88	1.30	89.3%
1.200	12.10	114.9	0.330	16.31	0.43	14.52	1.79	89.0%
1.500	12.10	114.9	0.393	20.46	0.45	18.15	2.31	88.7%
1.800	12.10	114.9	0.455	24.61	0.47	21.78	2.83	88.5%
2.101	12.10	114.9	0.514	28.73	0.49	25.42	3.31	88.5%
2.251	12.10	114.9	0.543	30.78	0.49	27.24	3.54	88.5%
2.400	12.10	114.8	0.571	32.83	0.50	29.04	3.79	88.5%
2.701	12.10	114.8	0.628	36.97	0.51	32.68	4.29	88.4%
3.000	12.10	114.8	0.684	41.08	0.52	36.30	4.78	88.4%

230VAC/50Hz								
I _{out}	V _{out}	V _{in}	I _{in}	P _{in}	PF	P _{out}	Losses	Efficiency
0.000	12.11	229.7	0.0071	0.103		0.00	0.10	
0.299	12.10	229.7	0.067	4.30	0.28	3.62	0.68	84.1%
0.600	12.10	229.7	0.115	8.29	0.31	7.26	1.03	87.6%
0.750	12.10	229.7	0.139	10.28	0.32	9.08	1.21	88.3%
0.900	12.10	229.7	0.163	12.29	0.33	10.89	1.40	88.6%
1.201	12.10	229.7	0.209	16.34	0.34	14.53	1.81	88.9%
1.499	12.10	229.7	0.254	20.41	0.35	18.14	2.27	88.9%
1.800	12.10	229.7	0.297	24.50	0.36	21.78	2.72	88.9%
2.103	12.10	229.7	0.368	28.58	0.37	25.45	3.13	89.0%
2.250	12.10	229.7	0.358	30.55	0.37	27.23	3.33	89.1%
2.401	12.10	229.7	0.377	32.58	0.38	29.05	3.53	89.2%
2.701	12.10	229.7	0.414	36.63	0.39	32.68	3.95	89.2%
3.001	12.10	229.7	0.450	40.66	0.39	36.31	4.35	89.3%

Vin	Pin	Vout	Iout	Load	Efficiency	Avg. Eff.
115VAC/60Hz	10.15	12.10	0.750	25%	89.41%	88.74%
	20.46	12.10	1.500	50%	88.71%	
	30.78	12.10	2.251	75%	88.49%	
	41.08	12.10	3.000	100%	88.36%	
230VAC/50Hz	10.28	12.10	0.750	25%	88.28%	88.89%
	20.41	12.10	1.499	50%	88.87%	
	30.55	12.10	2.250	75%	89.12%	
	40.66	12.10	3.001	100%	89.31%	

4 Current Limit


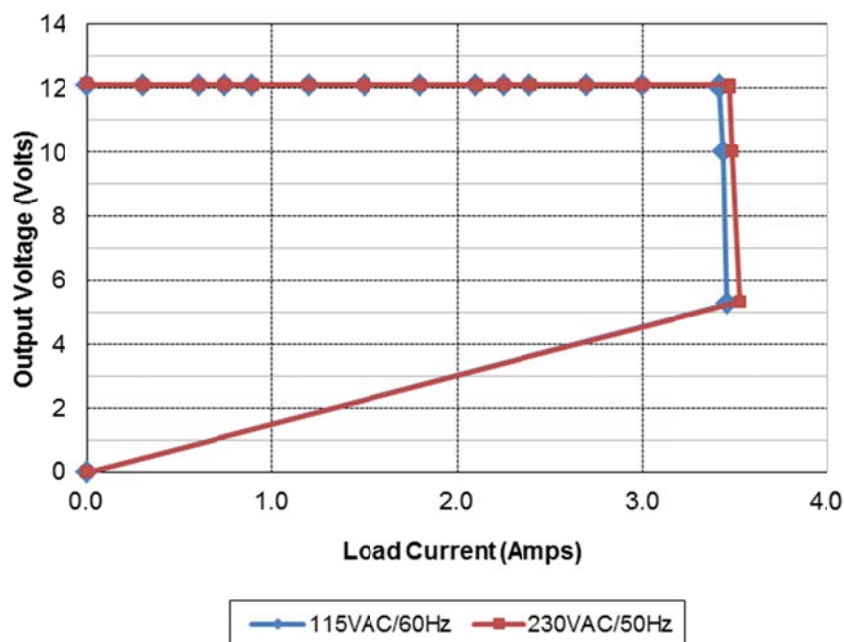
A plot of the output voltage versus load current is shown below.




5 Thermal Images

The ambient temperature was 25°C. The output was loaded with 3A.

5.1 115VAC/60Hz Input

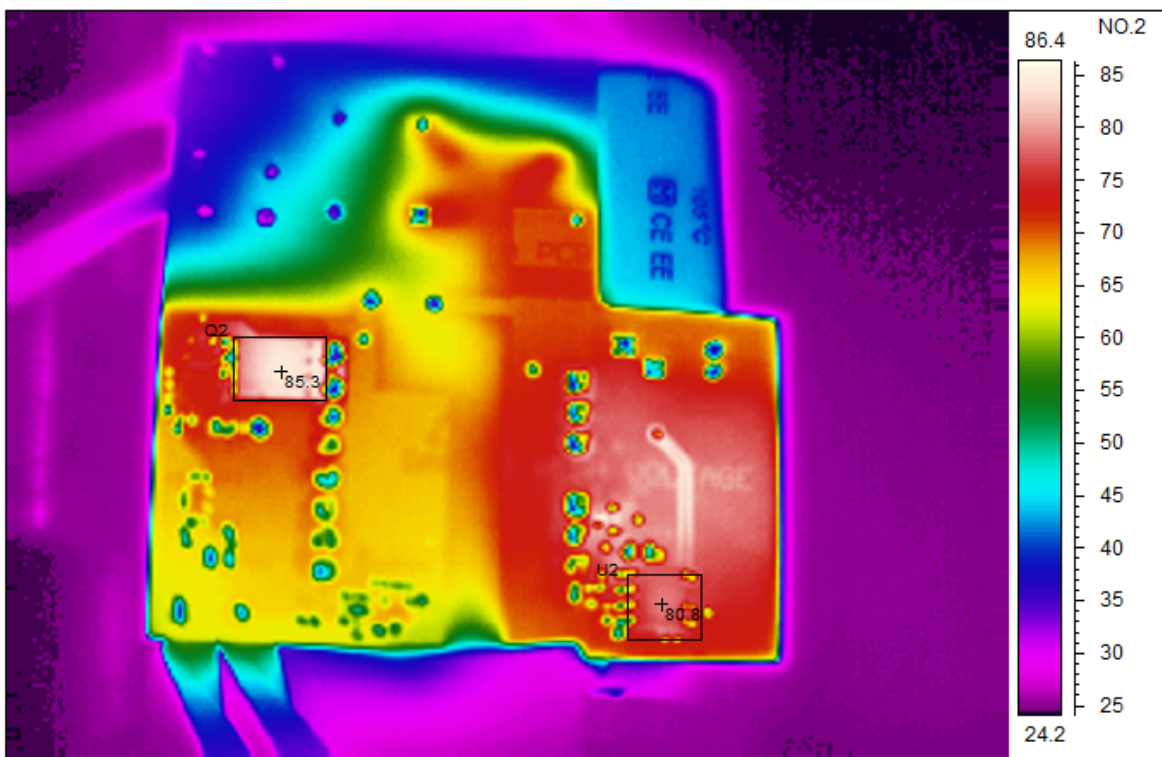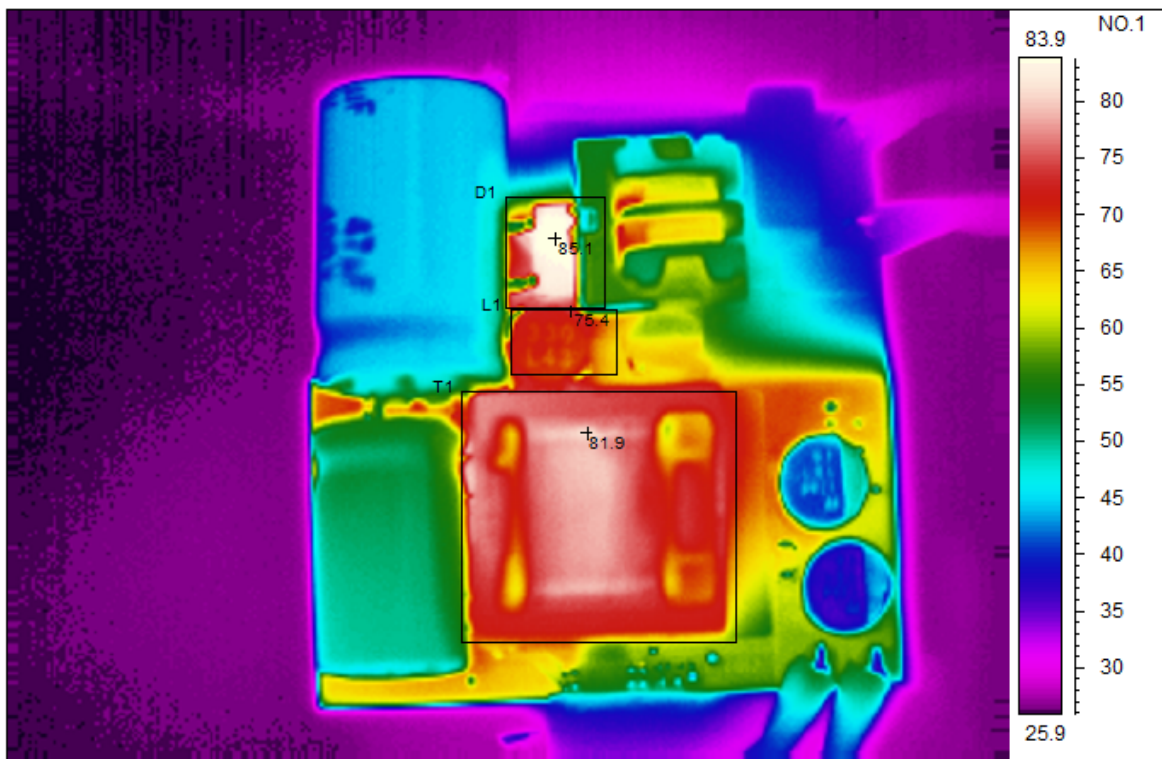


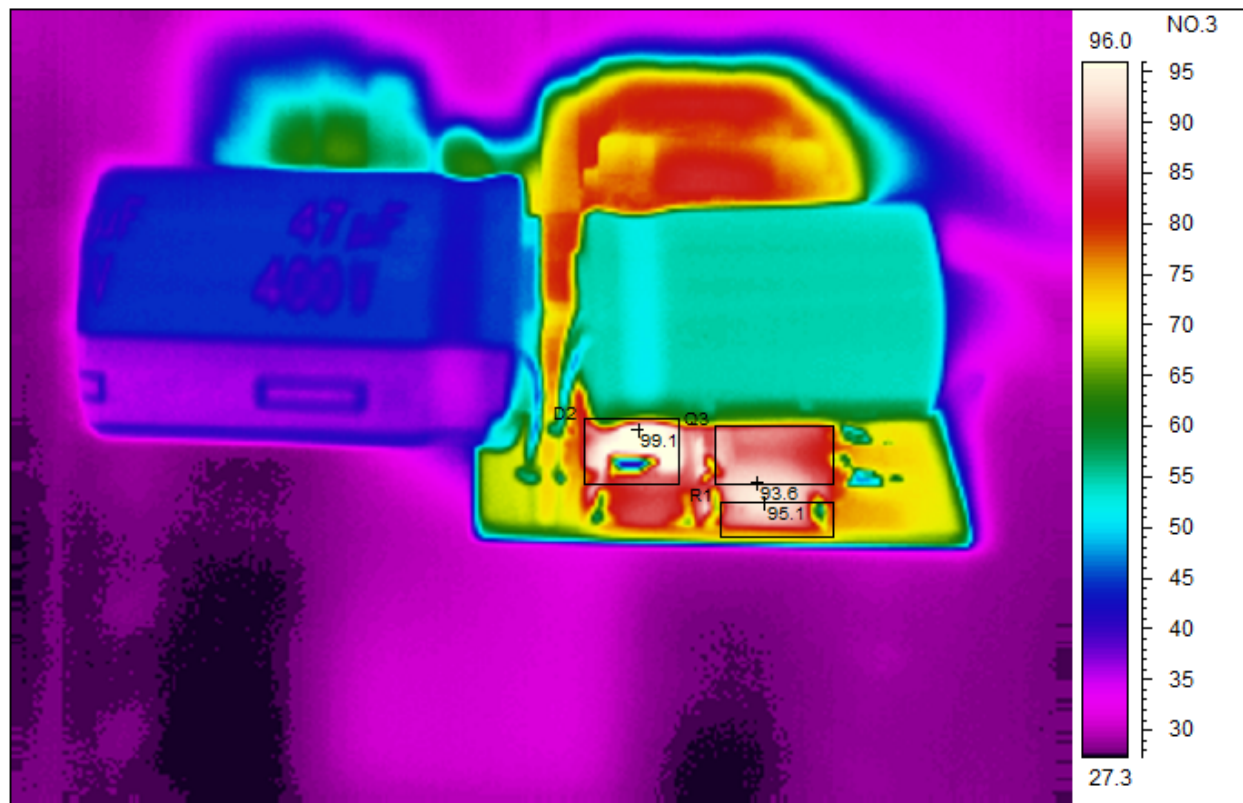


Area analysis	Value	NO.1
T1 Max	81.9°C	
D1Max	85.1°C	
L1 Max	75.4°C	

Area analysis	Value	NO.2
Q2 Max	85.3°C	
U2 Max	80.8°C	

Area analysis	Value	NO.3
D2 Max	99.1°C	
Q3 Max	93.6°C	
R1 Max	95.1°C	

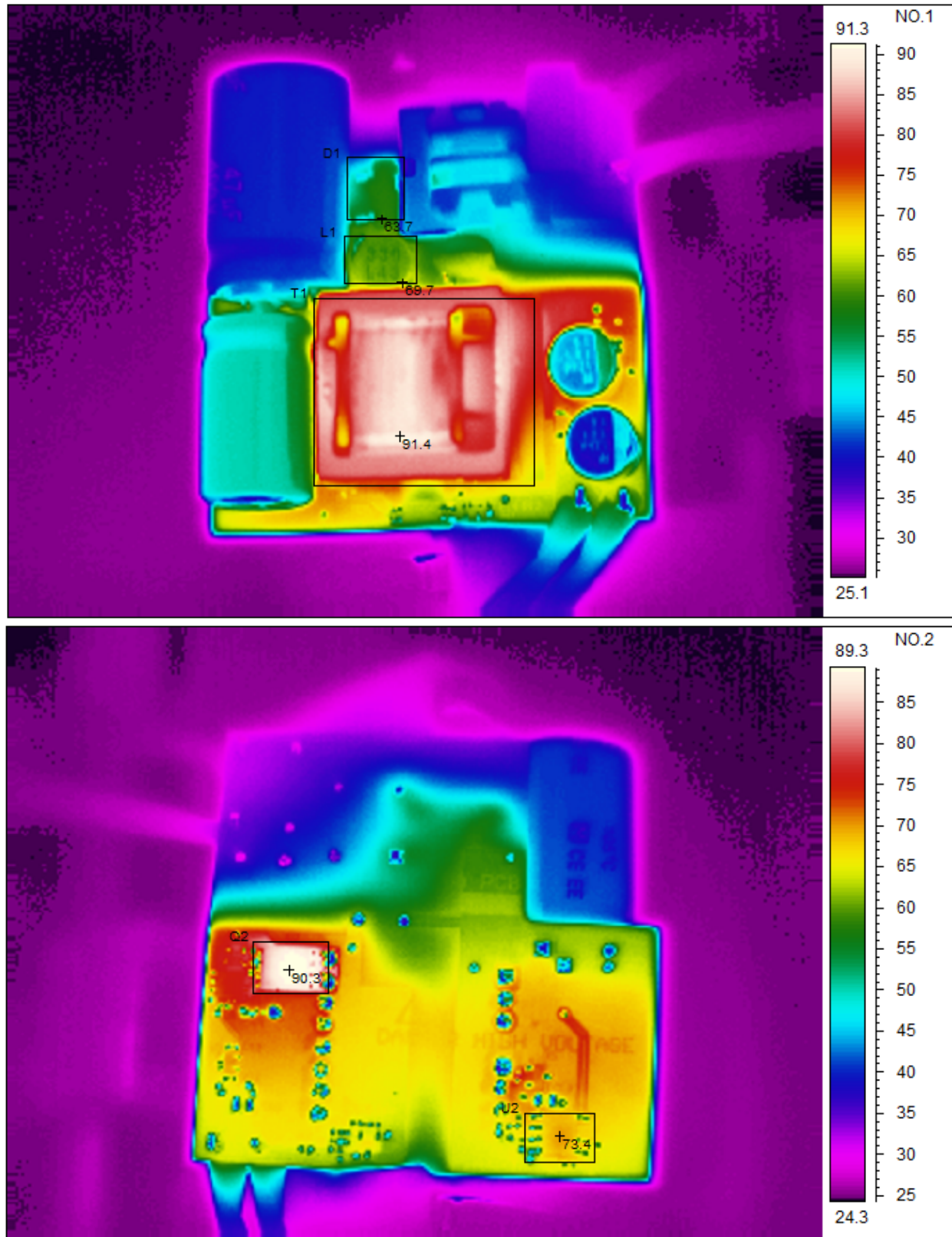5.2 230VAC/50Hz Input

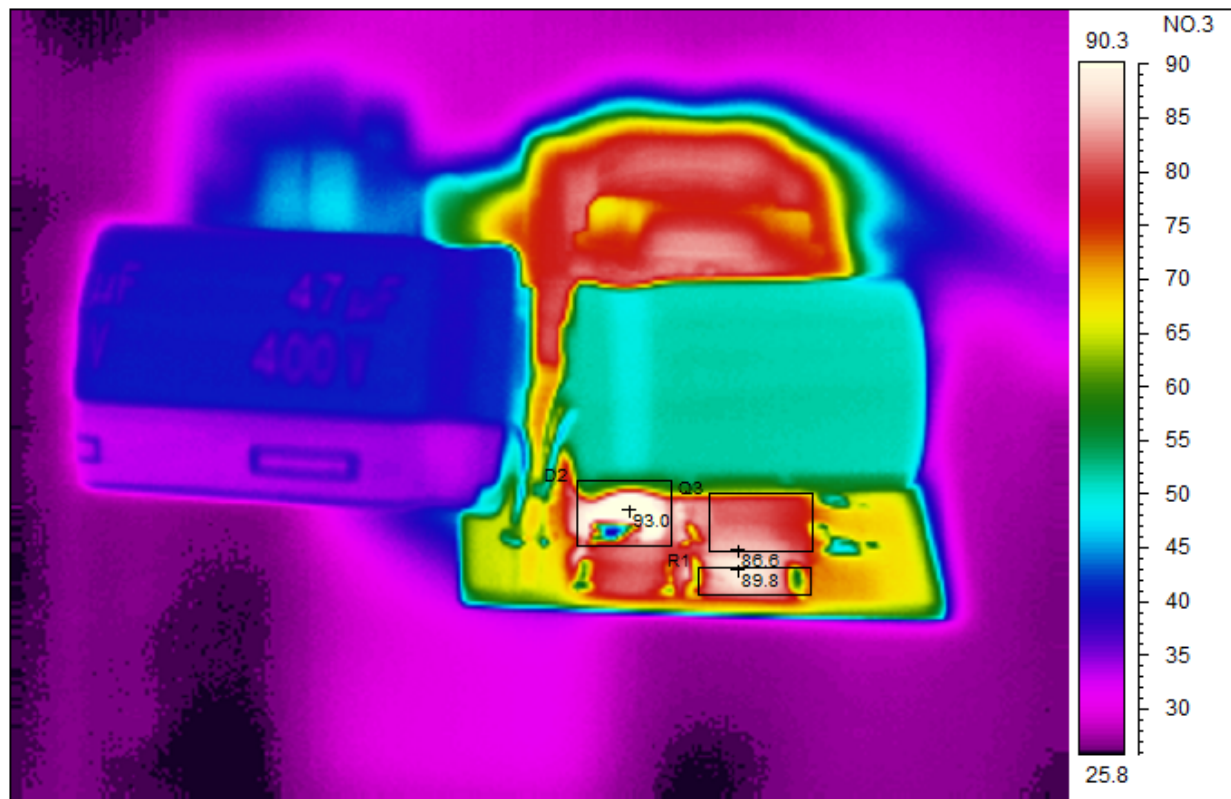

Area analysis	Value	NO.1
T1 Max	91.4°C	
D1Max	63.7°C	
L1 Max	69.7°C	


Area analysis	Value	NO.2
Q2 Max	90.3°C	
U2 Max	73.4°C	

Area analysis	Value	NO.3
D2 Max	93.0°C	
Q3 Max	86.6°C	
R1 Max	89.8°C	


6 Startup



Channel 1 shows the AC input voltage. Channel 2 shows the output voltage.

6.1 115VAC/60Hz Startup – 0A Load

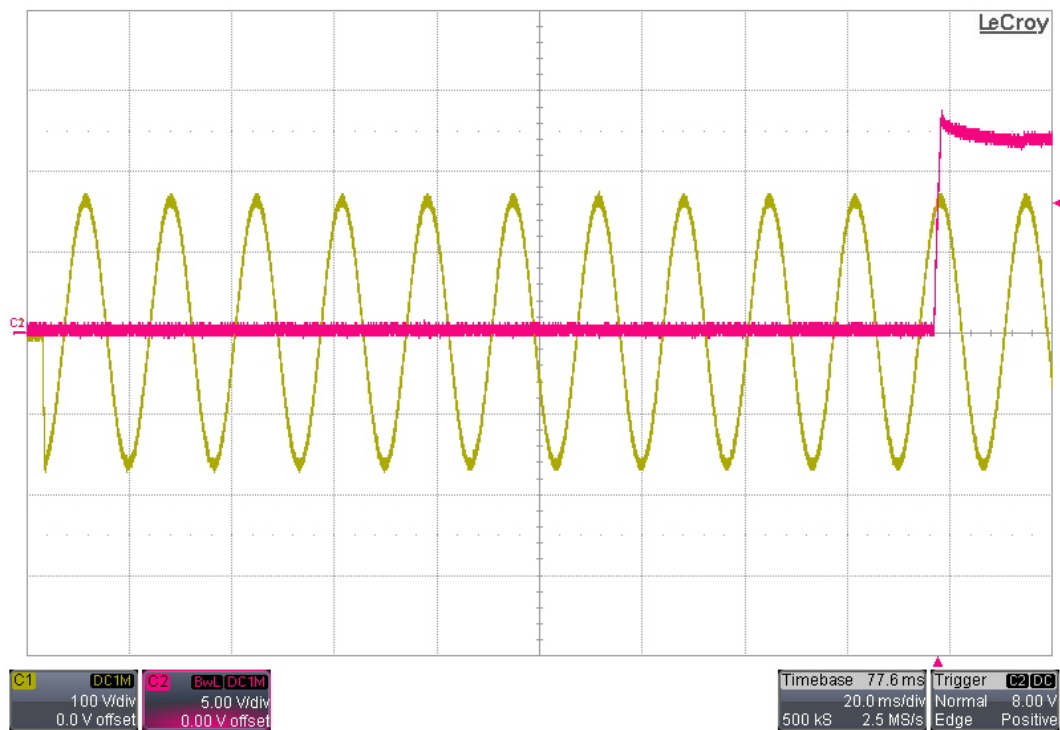

6.2 230VAC/50Hz Startup – 0A Load

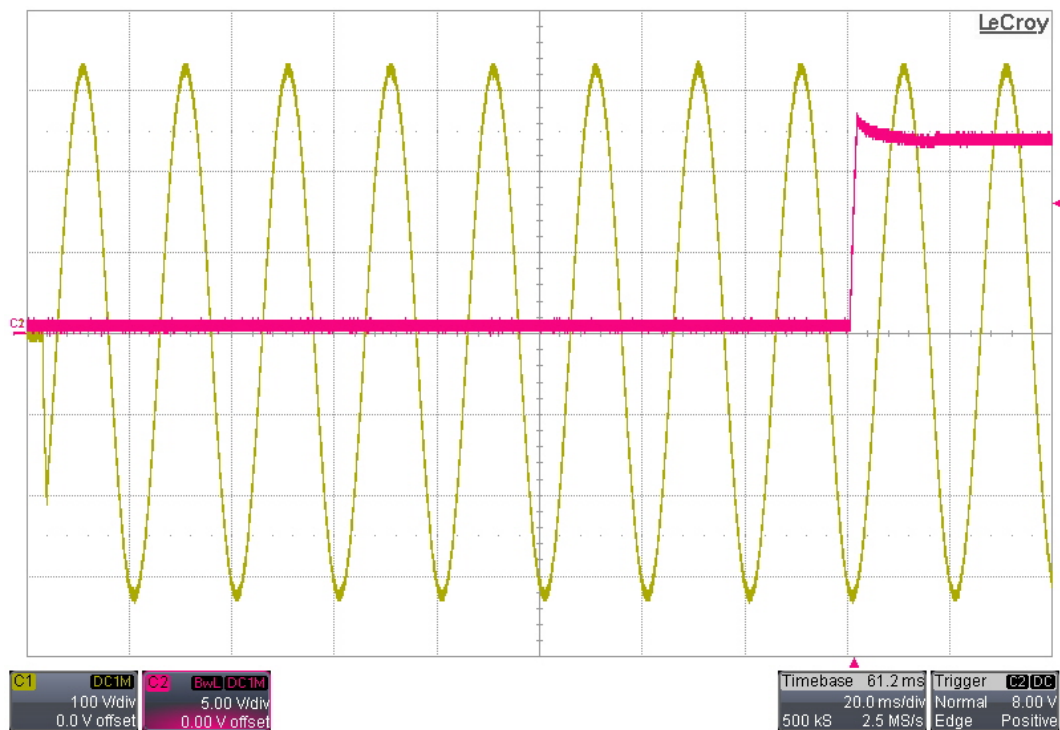


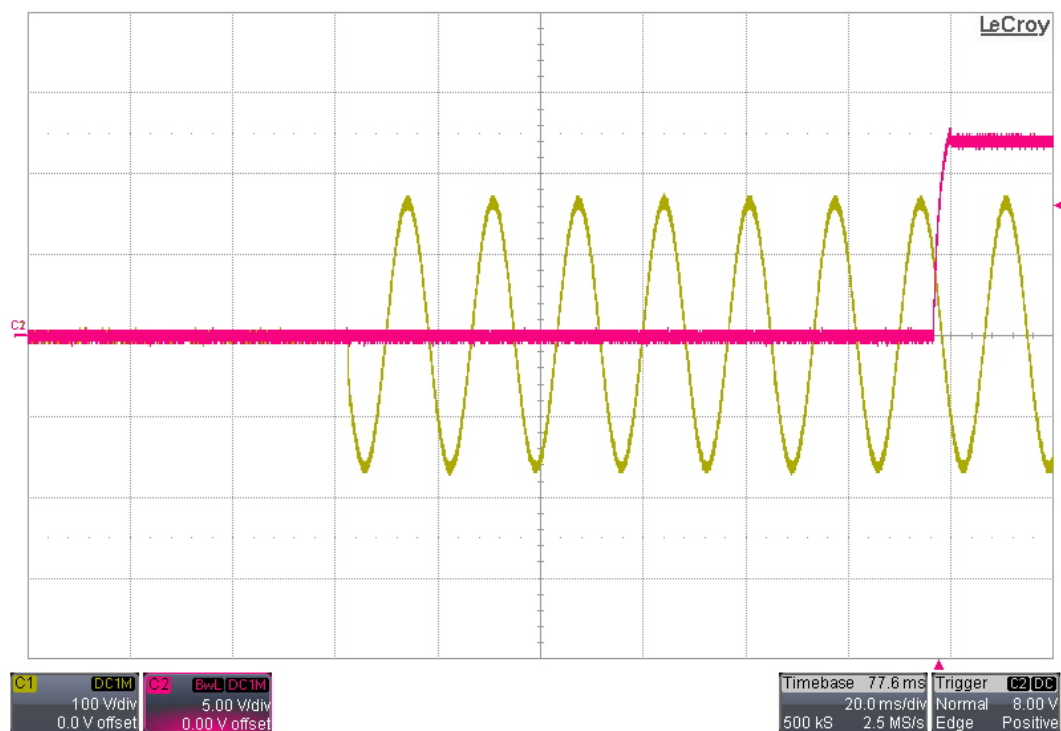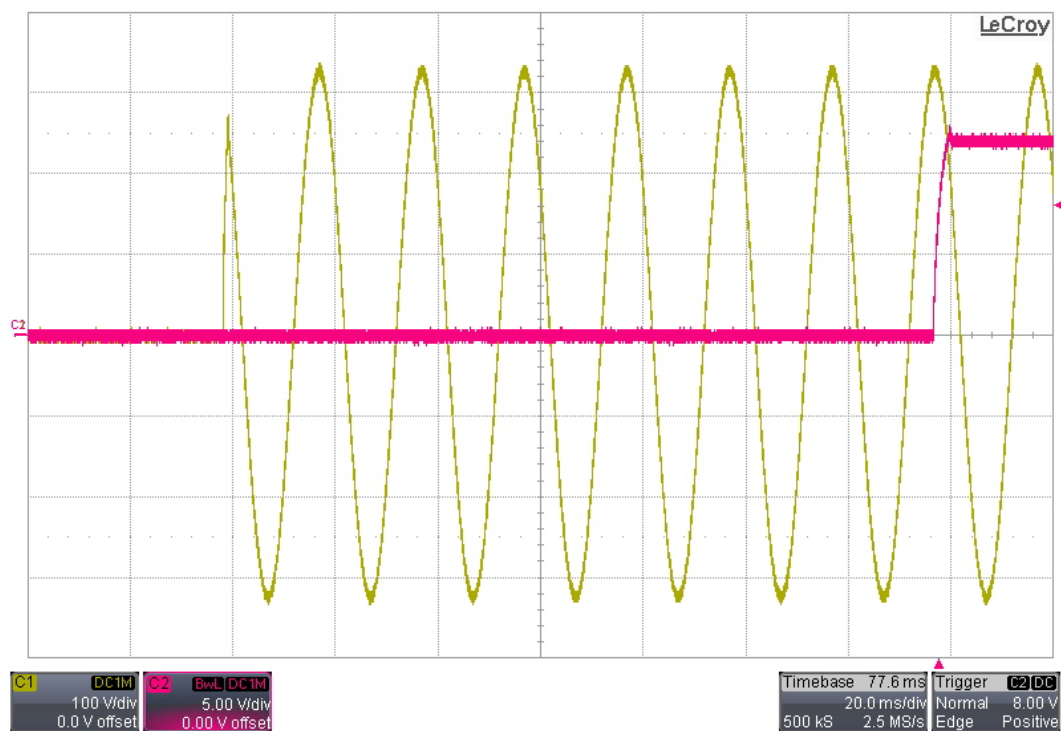6.3 115VAC/60Hz Startup – 4Ω Load**6.4 230VAC/50Hz Startup – 4Ω Load**


7 Output Ripple Voltage

The output was loaded with 3A.

7.1 115VAC/60Hz Output Ripple Voltage

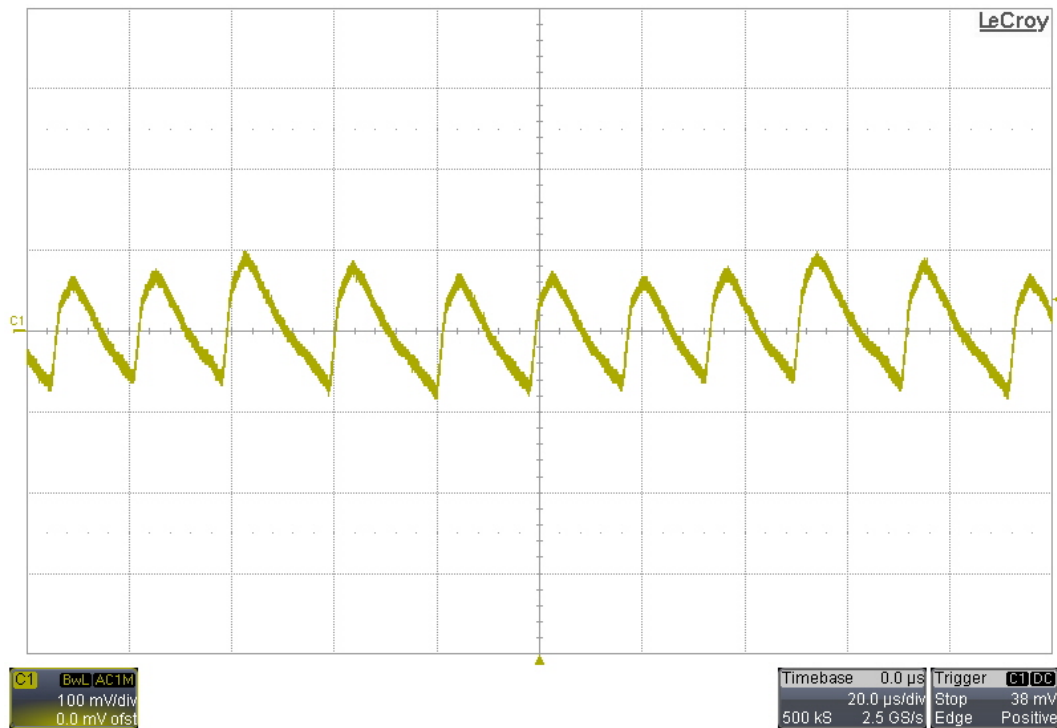


7.2 230VAC/50Hz Output Ripple Voltage

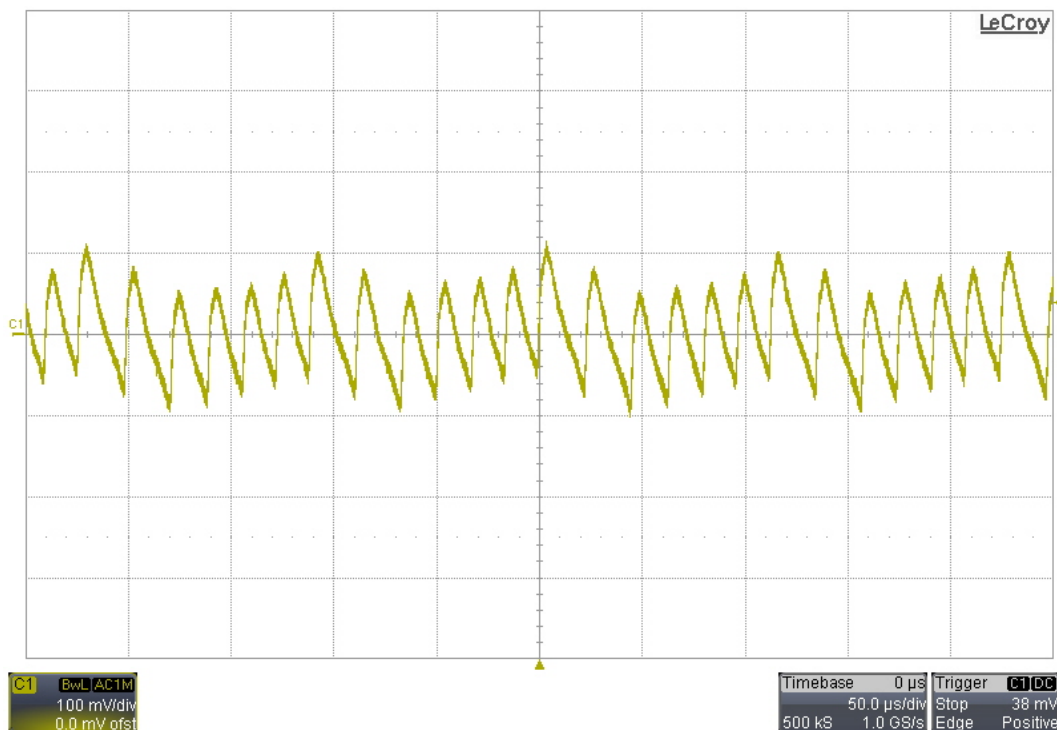


8 Frequency Response

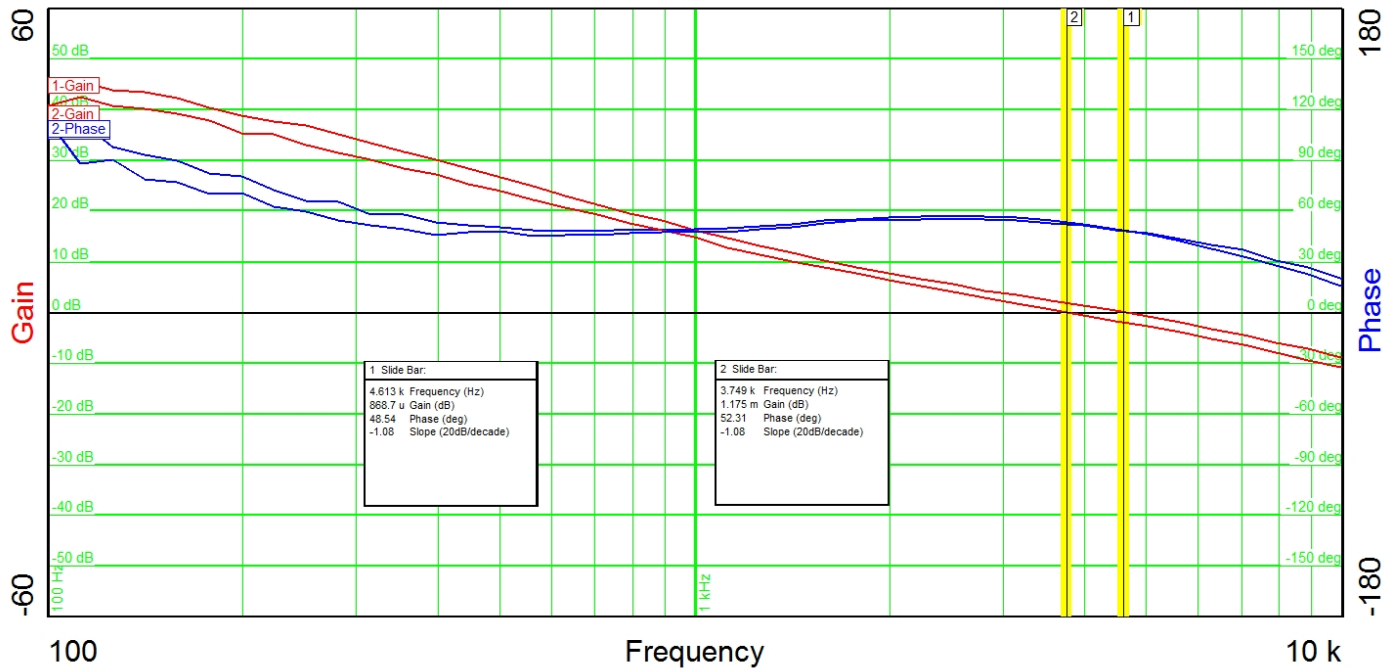The frequency response of the feedback loop measured at R9 is shown below. For the gain/phase plot #1, the input was set to 115VAC/60Hz. For the gain/phase plot #2, the input was set to 230VAC/50Hz. The output was loaded with 3A.




9 Load Transients

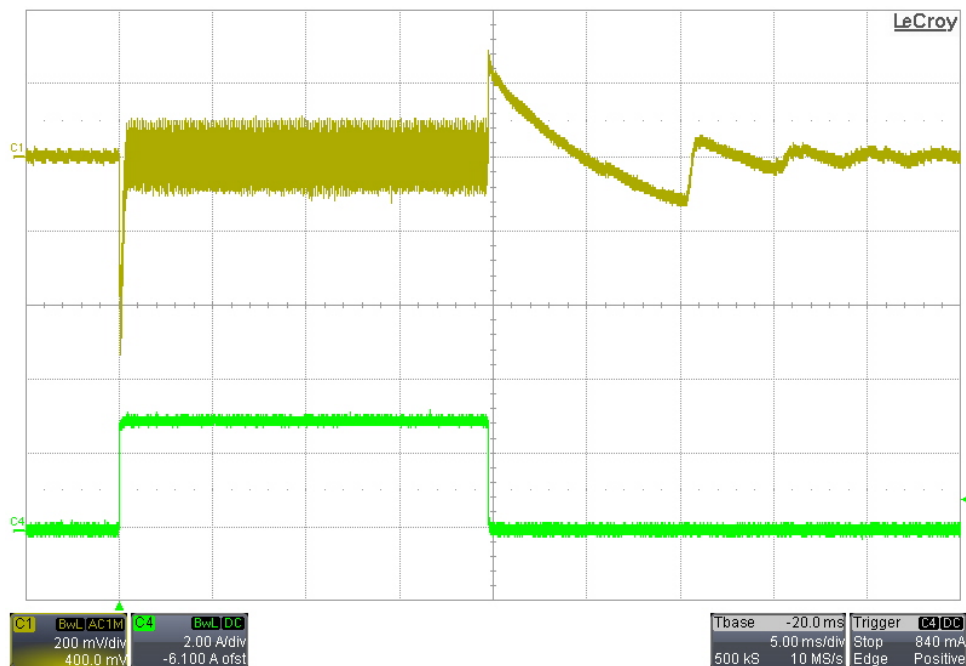9.1 0A to 3A Transient – 115VAC/60Hz Input



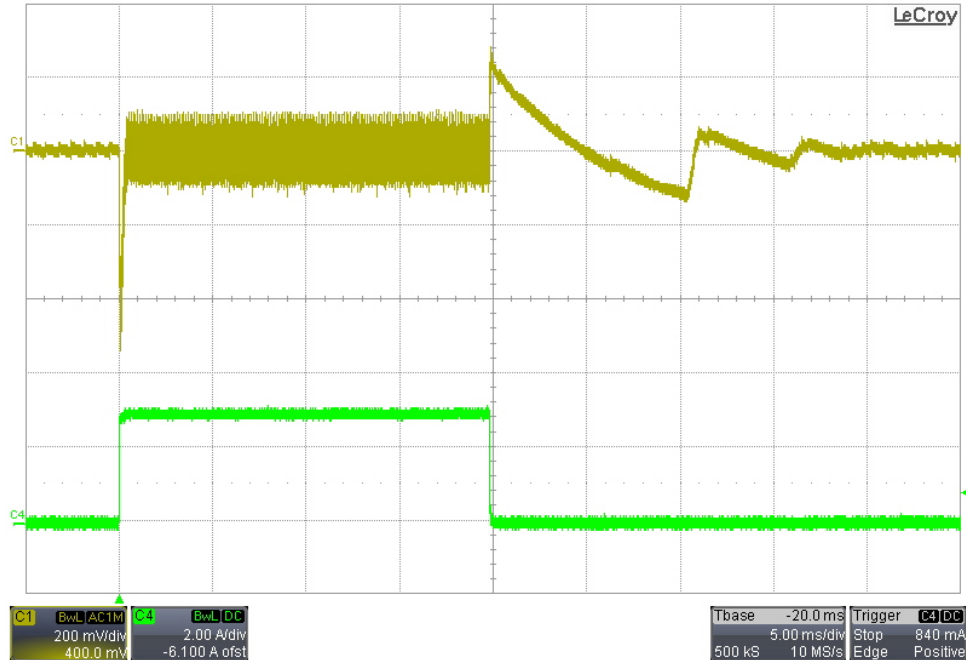9.2 0A to 2A Transient – 230VAC/50Hz Input




10 Switching Waveforms

The images below show the voltage waveforms on the switching devices within the supply. The input was 265VAC/50Hz. The output was loaded 3A.

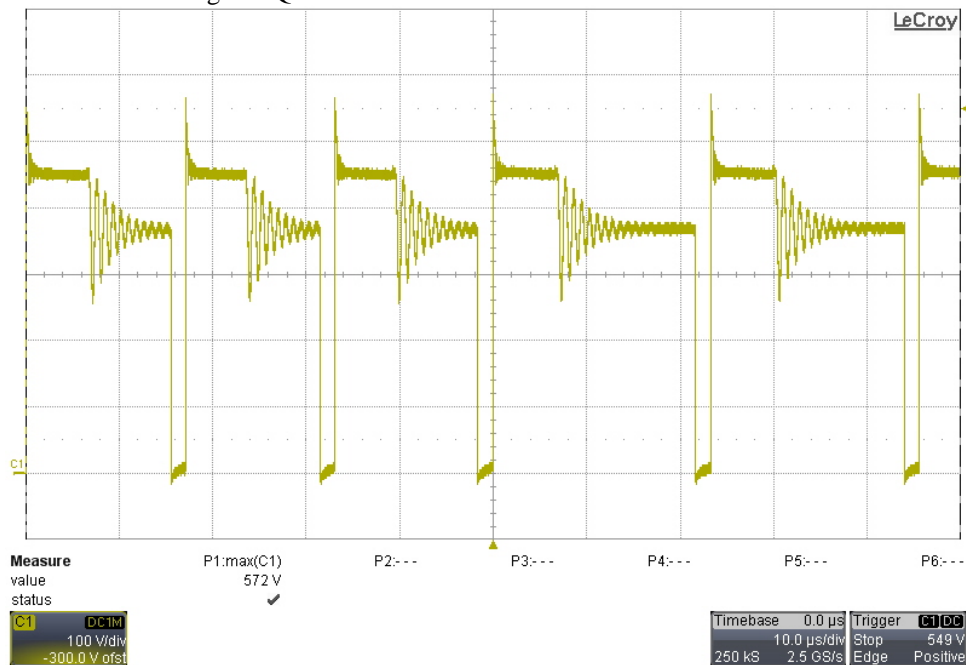
10.1 Primary Waveforms

The image below shows the drain voltage on Q3.



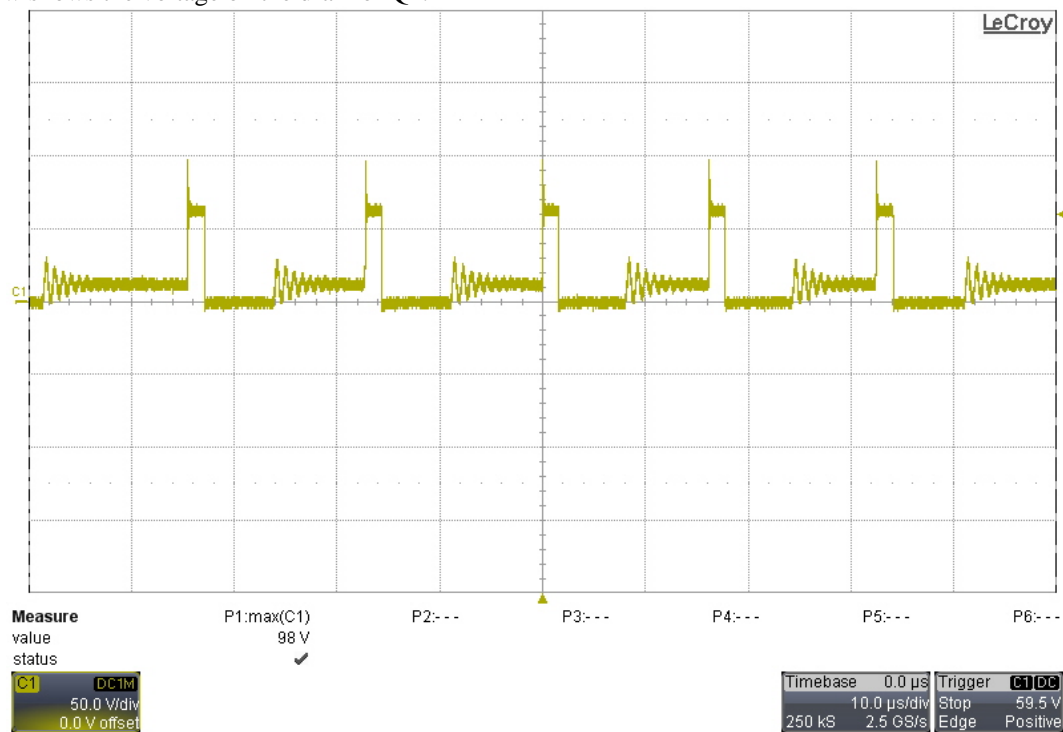10.2 Secondary Waveforms

The image below shows the voltage on the drain of Q2.



IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.