


## 1 Photo

The photographs below show the top and bottom views of the PMP12074 Rev A board, which is built on PMP11062 Rev A PCB.

### Top Side




### Bottom Side

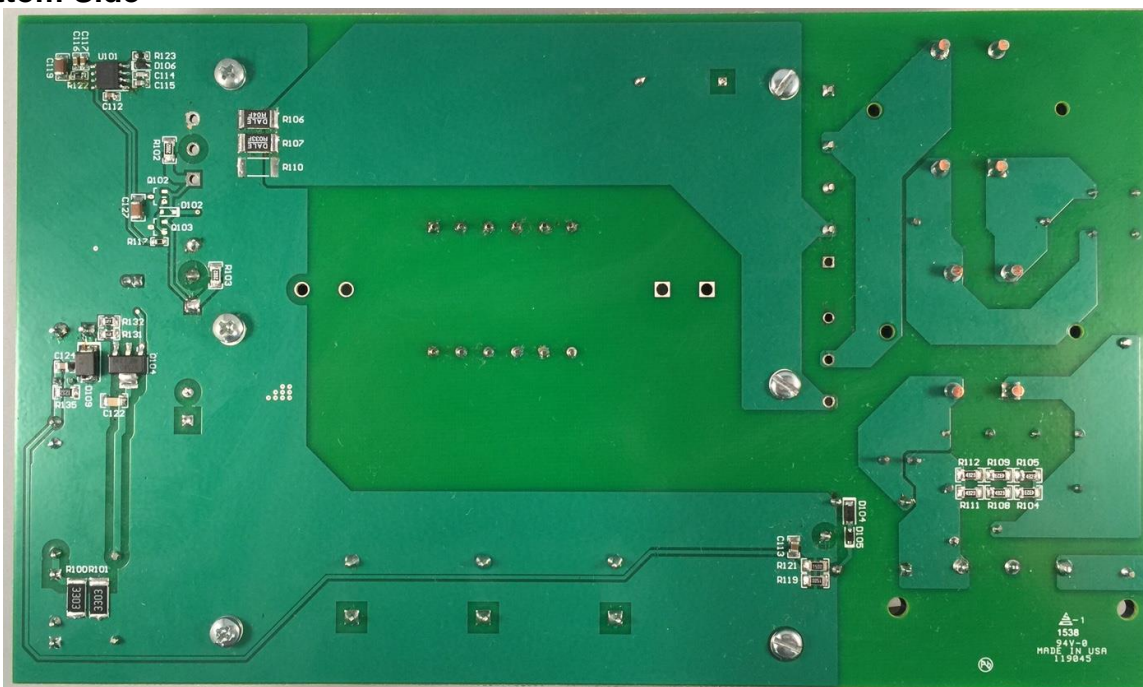


## 2 Efficiency and Power Factor

The efficiency curves of total supply are shown in the tables and graph below. Efficiency tests are performed with nature airflow.

### 2.1 Efficiency:

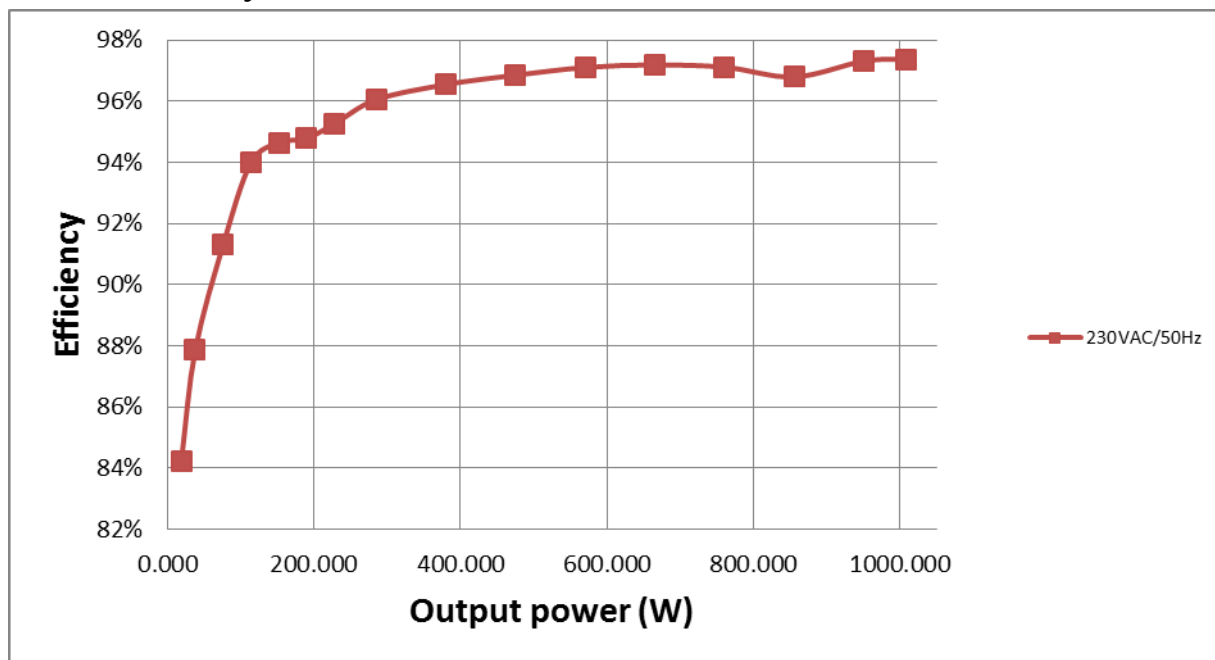

### 2.2 Power factor:

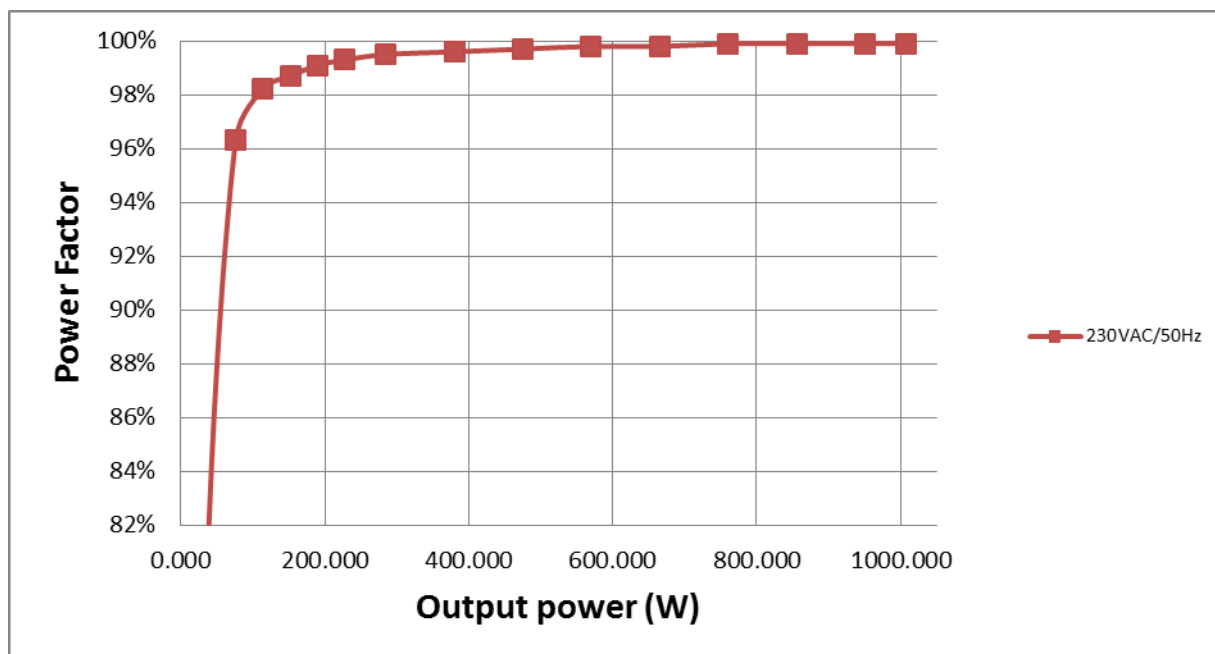


**230V<sub>AC</sub>/50Hz**

Vin,rms(V)	Iin,rms(A)	Pin(W)	P.F.	Vout(V)	Iout(A)	Pout(W)	Ploss(W)	Eff. (%)
230	4.504	1035.00	0.999	380.3	2.650	1007.795	27.2050	97.37%
230	4.254	977.00	0.999	380.3	2.500	950.750	26.2500	97.31%
230	3.850	884.00	0.999	380.3	2.250	855.675	28.3250	96.80%
230	3.410	783.20	0.999	380.3	2.000	760.600	22.6000	97.11%
230	2.981	684.60	0.998	380.2	1.750	665.350	19.2500	97.19%
230	2.559	587.30	0.998	380.2	1.500	570.300	17.0000	97.11%
230	2.139	490.70	0.997	380.2	1.250	475.250	15.4500	96.85%
230	1.718	393.70	0.996	380.1	1.000	380.100	13.6000	96.55%
230	1.297	296.80	0.995	380.1	0.750	285.075	11.7250	96.05%
230	1.048	239.40	0.993	380.1	0.600	228.060	11.3400	95.26%
230	0.880	200.50	0.991	380.1	0.500	190.050	10.4500	94.79%
230	0.708	160.64	0.987	380.1	0.400	152.040	8.6000	94.65%
230	0.537	121.32	0.982	380.1	0.300	114.030	7.2900	93.99%
230	0.376	83.27	0.963	380.1	0.200	76.020	7.2500	91.29%
230	0.231	43.25	0.814	380	0.100	38.000	5.2500	87.86%
230	0.173	22.57	0.568	380.1	0.050	19.005	3.5650	84.20%
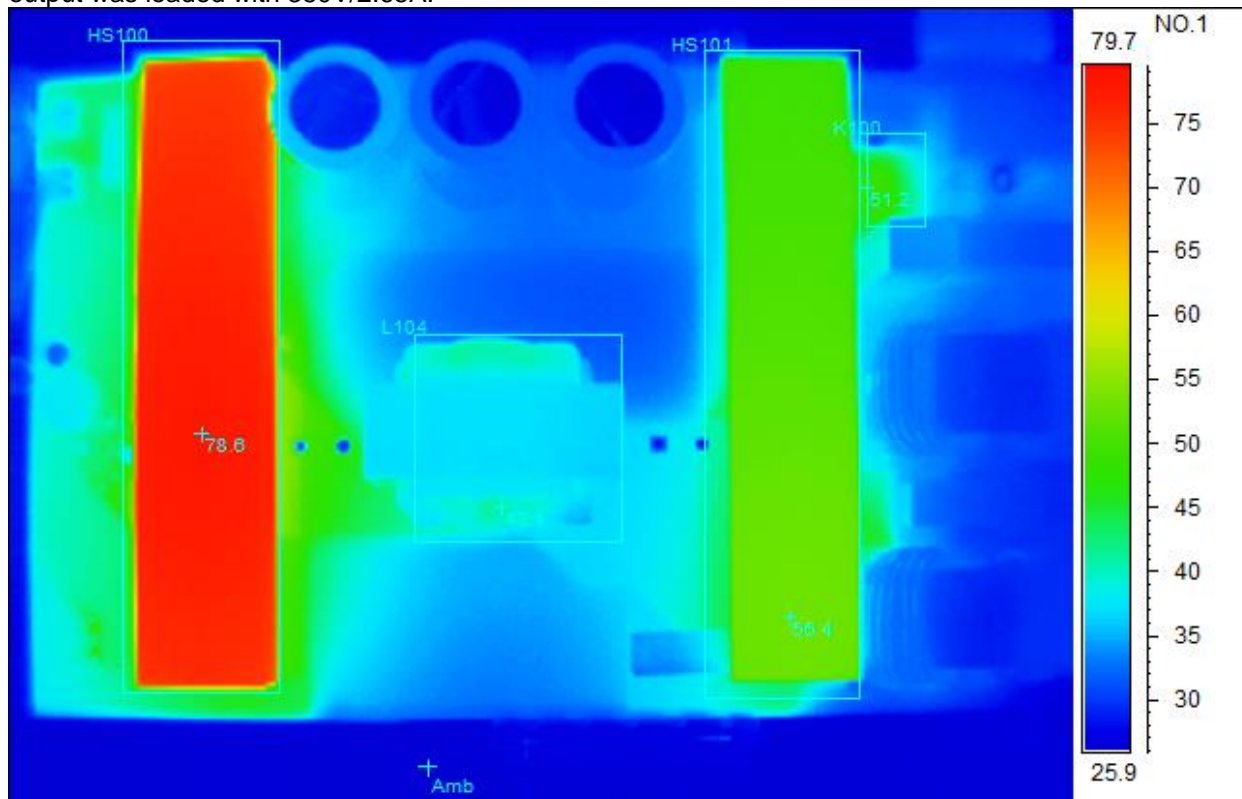
### 3 Thermal Images

The thermal images below show top views of the board. The board is placed horizontally during the test. The ambient temperature was 25°C with natural airflow. 230V<sub>AC</sub>/50Hz AC voltage is applied to input. The output was loaded with 380V/2.65A.



Spot analysis	Value
Amb Temperature	26.0°C
Area analysis	Value
K100Max	51.2°C
HS101Max	55.4°C
L104Max	43.1°C
HS100Max	78.6°C




## 4 Startup

The voltages at startup are shown in the images below.

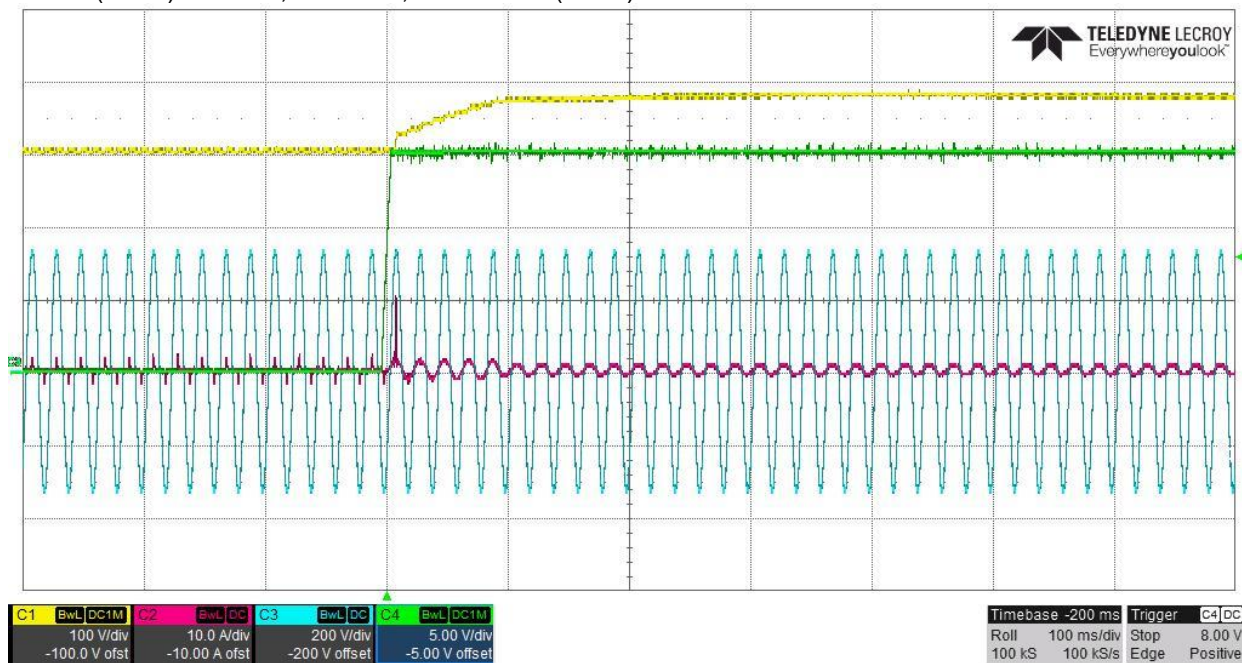
### 4.1 230V<sub>AC</sub>/50Hz – 100W full load on J100

CH1: V(C104) CH2: Iin, CH3: Vin, and CH4: V(C123).


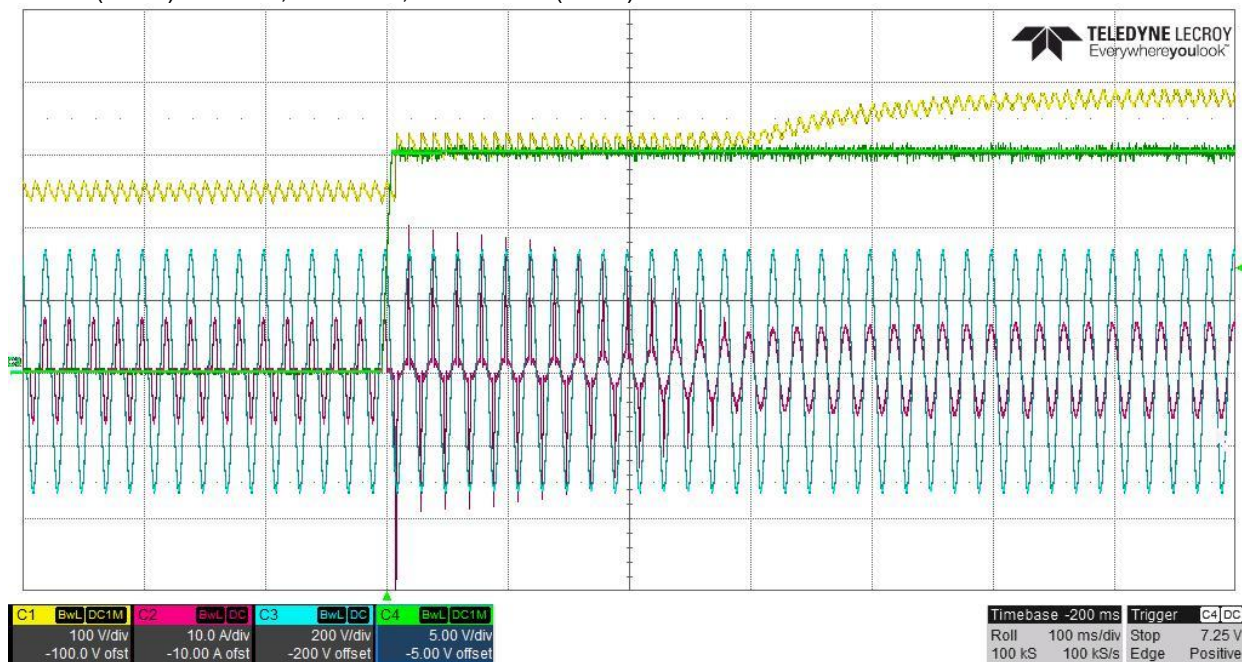
### 4.2 230V<sub>AC</sub>/50Hz – 1000W full load on J100

CH1: V(C104) CH2: Iin, CH3: Vin, and CH4: V(C123).




## 5 Turn-off

The voltages at turn-off are shown in the images below.
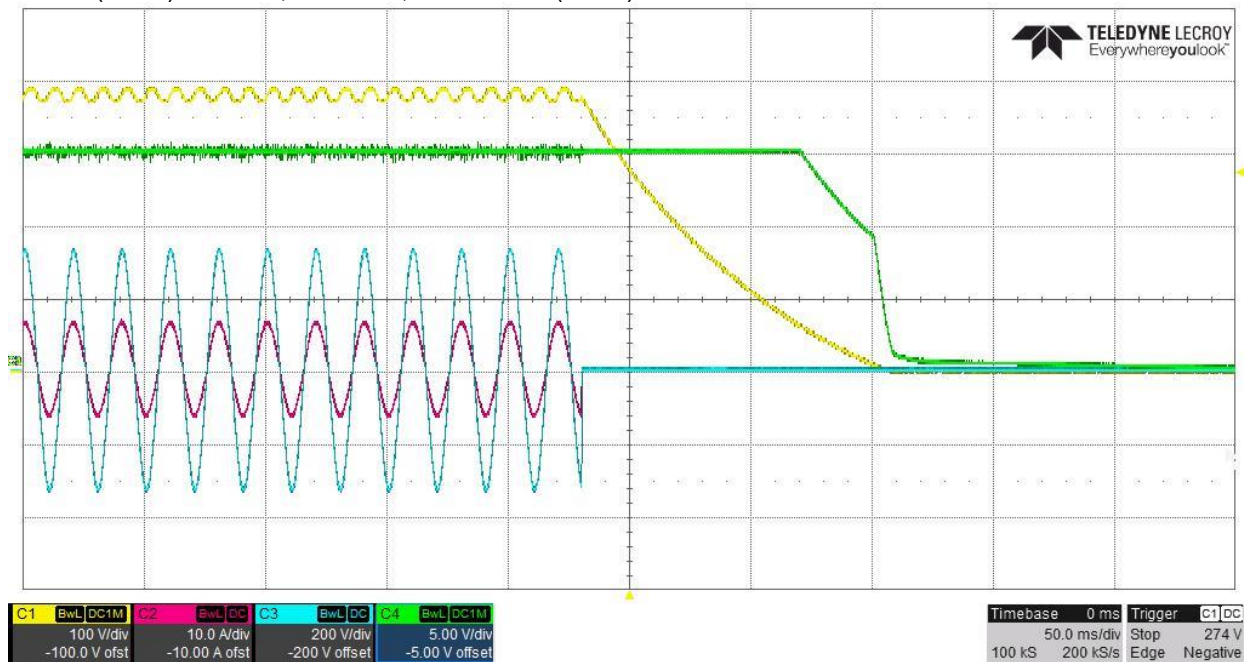
### 5.1 230V<sub>AC</sub>/50Hz – 1000W full load on J100

CH1: V(C104) CH2: I<sub>in</sub>, CH3: V<sub>in</sub>, and CH4: V(C123).




## 6 Output Ripple Voltage

The output ripple voltage (in AC level) during 1000W full load is shown in the plots below.

### 6.1 230V<sub>AC</sub>/50Hz

CH1: V(C104) CH2: Iin, and CH3: Vin.

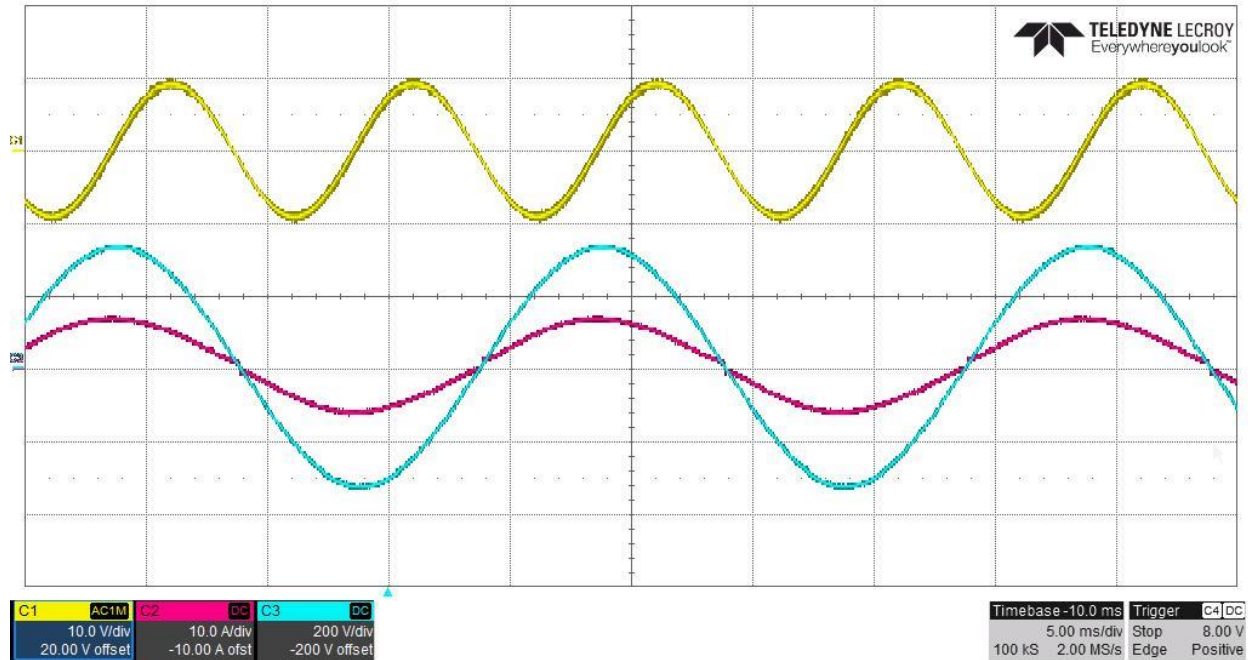


## 7 Transient Response

Transient responses are shown in the plots below.

### 7.1 230V<sub>AC</sub>/50Hz, load changes from 1.15A to 2.65A

CH1: V(C102) and CH2: Iout.

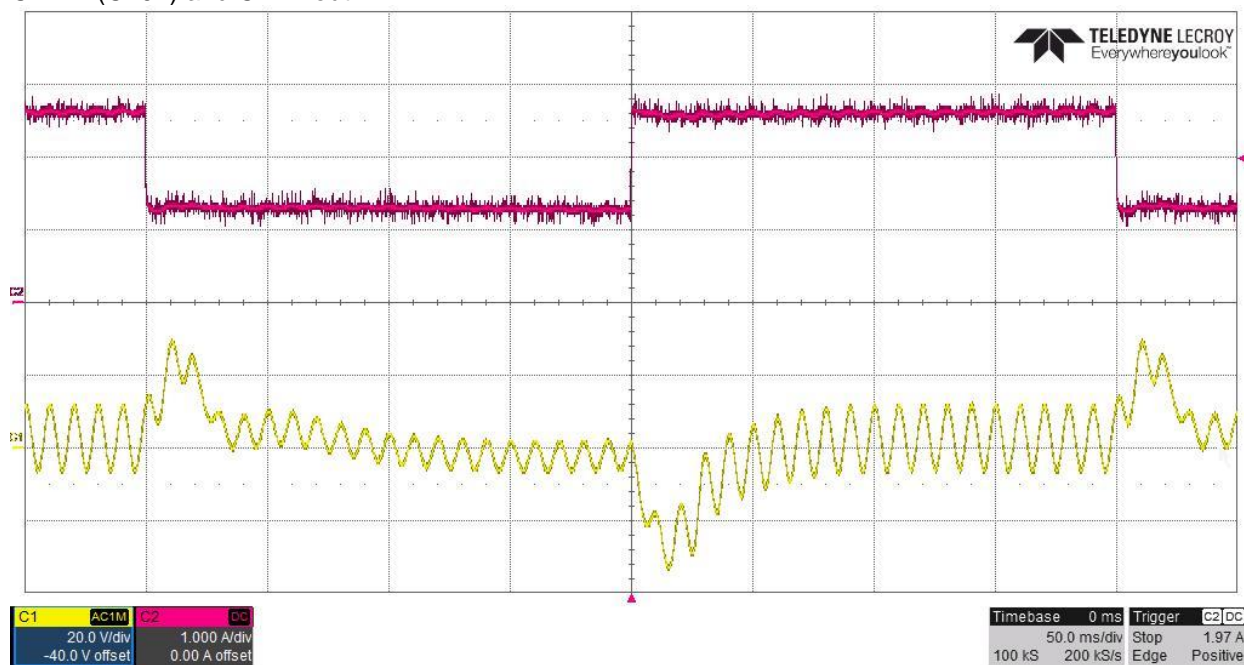




## 8 Key Waveforms



### 8.1 Input current and voltage waveforms

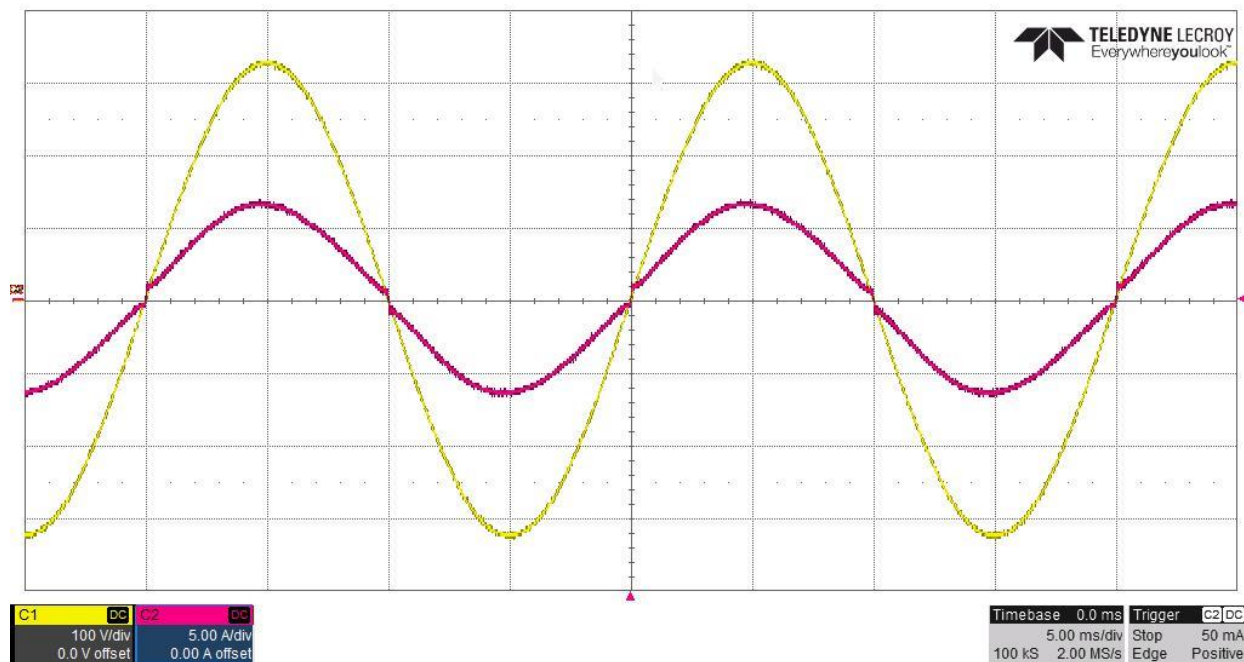
#### 8.1.1 230V<sub>AC</sub>/50Hz, 1000W.


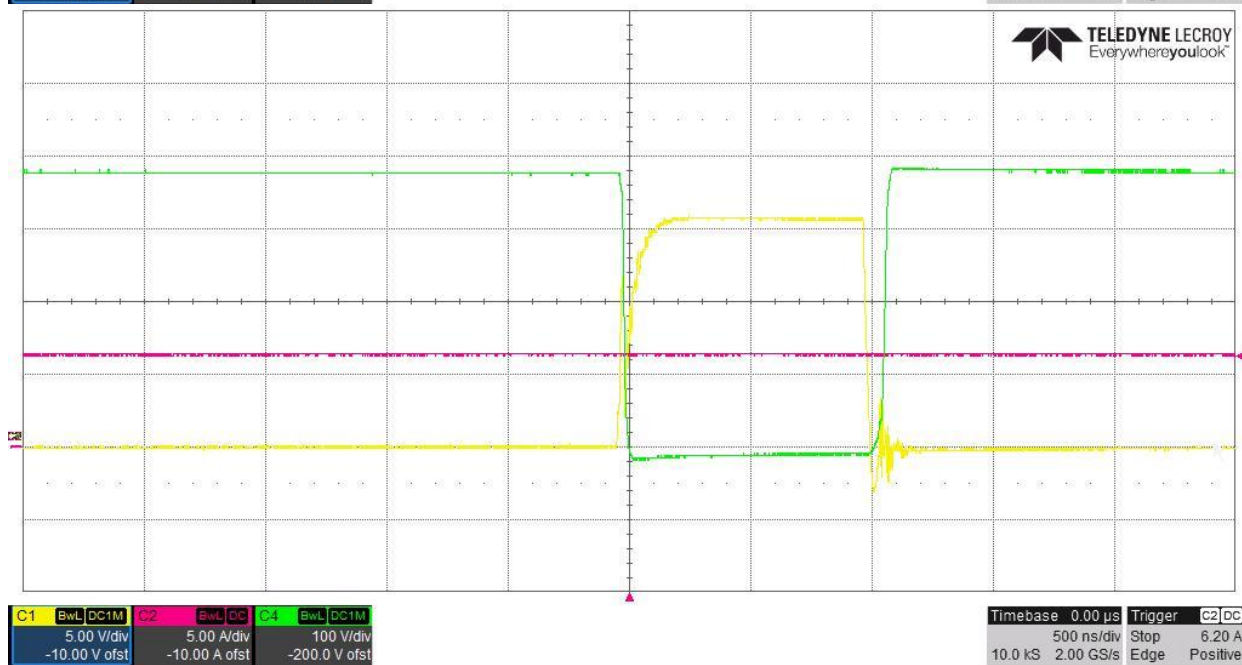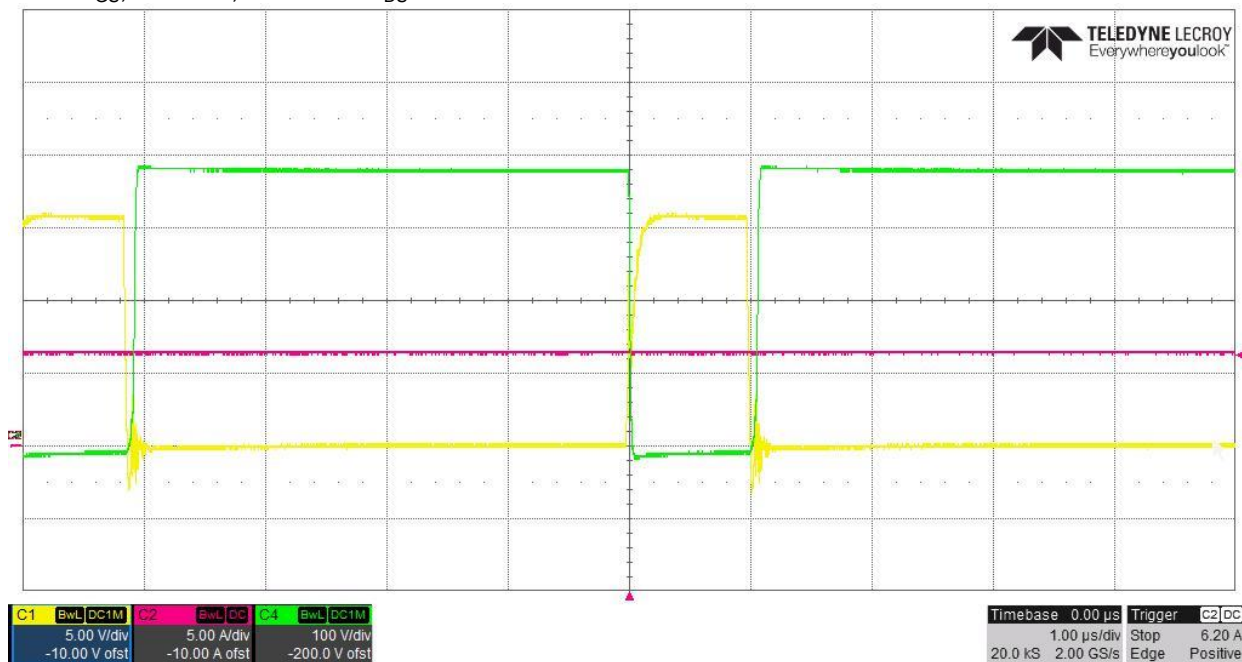
## 8.2 Q100 @ 1000W output from J100 and 230V<sub>AC</sub>/50Hz.

CH1: V<sub>GS</sub>, CH2: I<sub>in</sub>, and CH4: V<sub>DS</sub>.




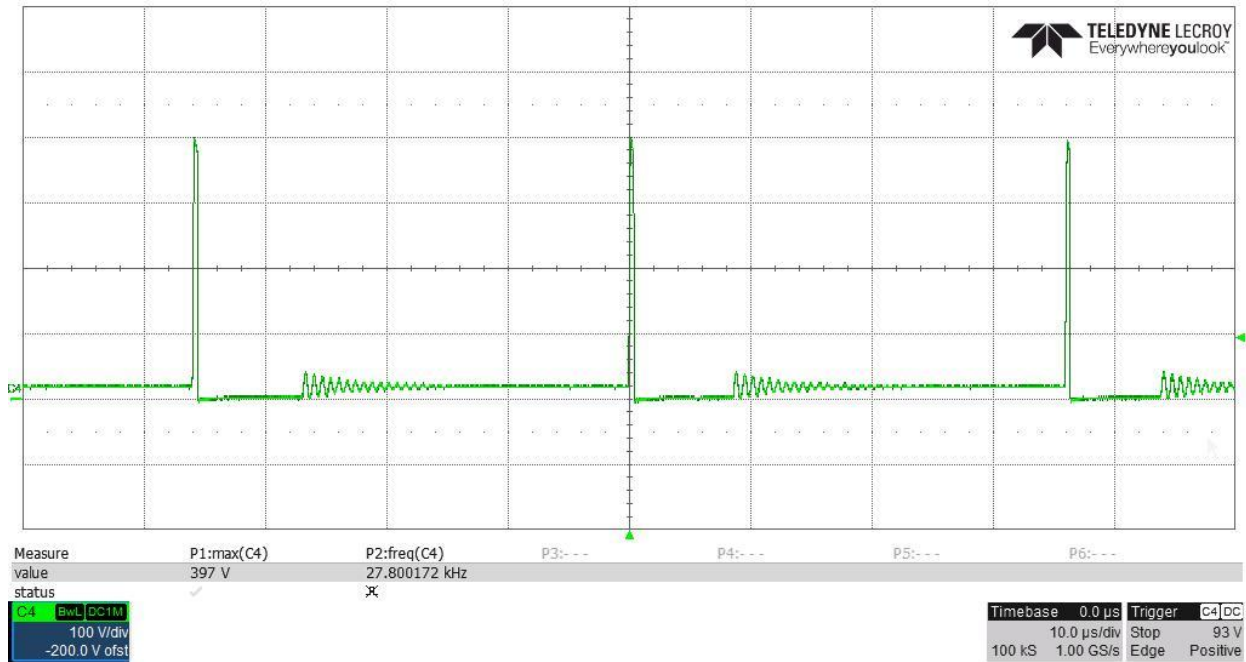**8.3 D109 @ 1000W output from J100.**


## 9 Conducted EMI:

The following curves show the **peak scan** results with **maximum hold** on PMP12074Rev A board. The board is loaded with 145Ω resistor.
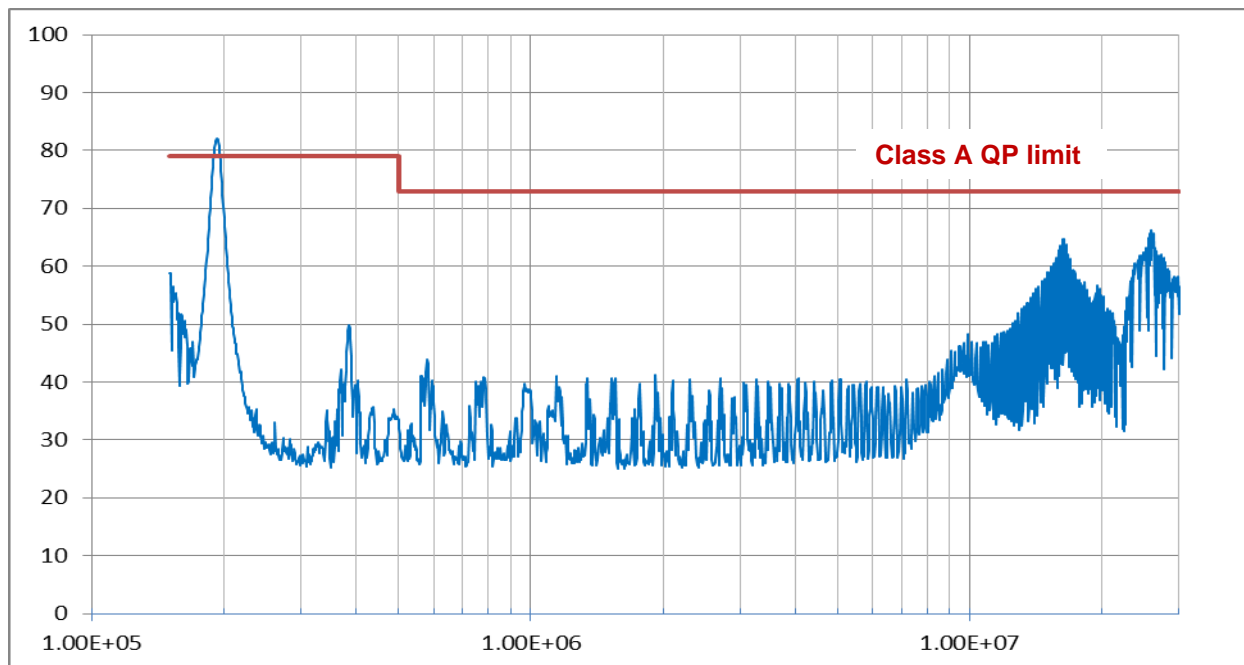
### 9.1 230V<sub>AC</sub>/50Hz, $I_{in}=4.33A$ : Line


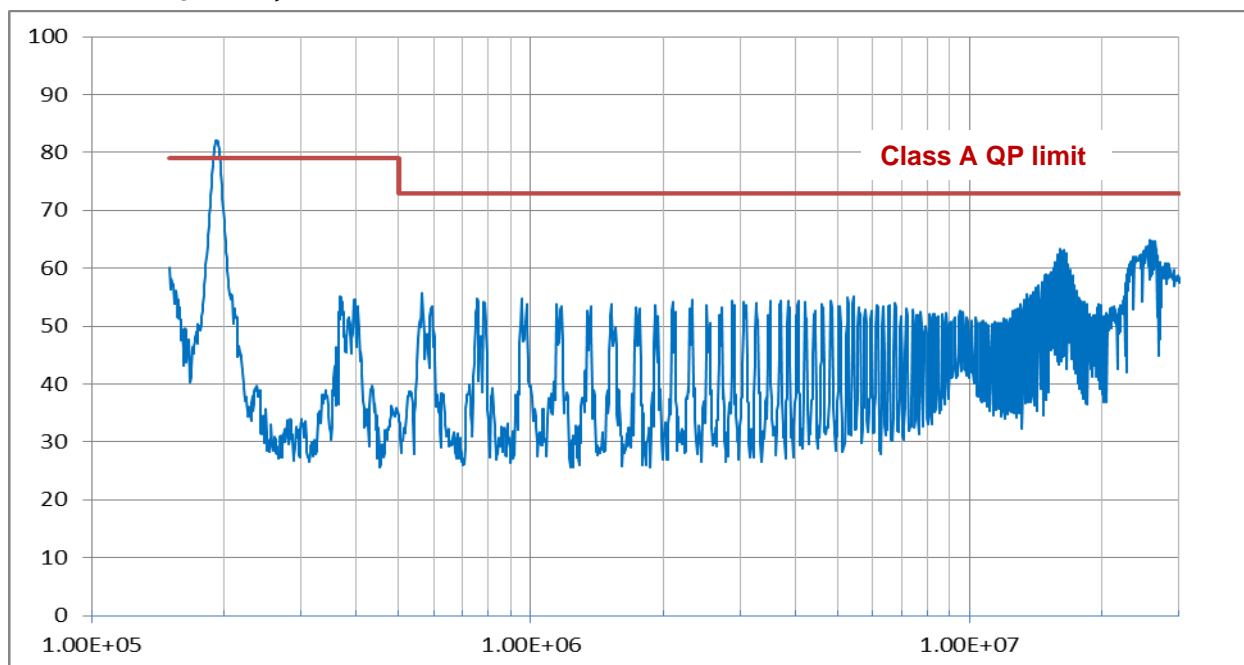
### 9.2 230V<sub>AC</sub>/50Hz, $I_{in}=4.33A$ : Neutral



## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Designer(s)") who are developing systems that incorporate TI products. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.

TI's provision of reference designs and any other technical, applications or design advice, quality characterization, reliability data or other information or services does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such reference designs or other items.

TI reserves the right to make corrections, enhancements, improvements and other changes to its reference designs and other items.

Designer understands and agrees that Designer remains responsible for using its independent analysis, evaluation and judgment in designing Designer's systems and products, and has full and exclusive responsibility to assure the safety of its products and compliance of its products (and of all TI products used in or for such Designer's products) with all applicable regulations, laws and other applicable requirements. Designer represents that, with respect to its applications, it has all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. Designer agrees that prior to using or distributing any systems that include TI products, Designer will thoroughly test such systems and the functionality of such TI products as used in such systems. Designer may not use any TI products in life-critical medical equipment unless authorized officers of the parties have executed a special contract specifically governing such use. Life-critical medical equipment is medical equipment where failure of such equipment would cause serious bodily injury or death (e.g., life support, pacemakers, defibrillators, heart pumps, neurostimulators, and implantables). Such equipment includes, without limitation, all medical devices identified by the U.S. Food and Drug Administration as Class III devices and equivalent classifications outside the U.S.

Designers are authorized to use, copy and modify any individual TI reference design only in connection with the development of end products that include the TI product(s) identified in that reference design. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of the reference design or other items described above may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS AND OTHER ITEMS DESCRIBED ABOVE ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY DESIGNERS AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS AS DESCRIBED IN A TI REFERENCE DESIGN OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

TI's standard terms of sale for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>) apply to the sale of packaged integrated circuit products. Additional terms may apply to the use or sale of other types of TI products and services.

Designer will fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of Designer's non-compliance with the terms and provisions of this Notice.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2016, Texas Instruments Incorporated